
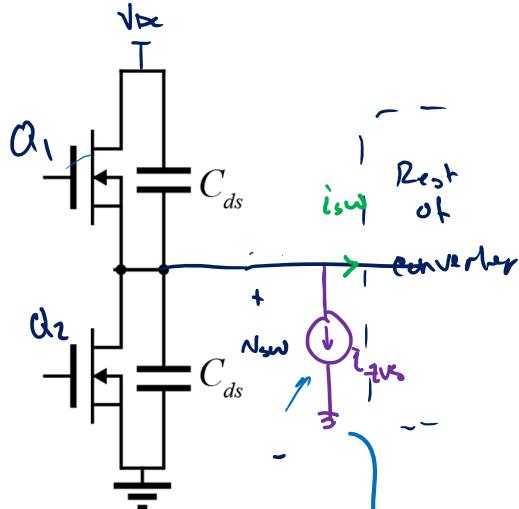





ZVS Assist Circuits

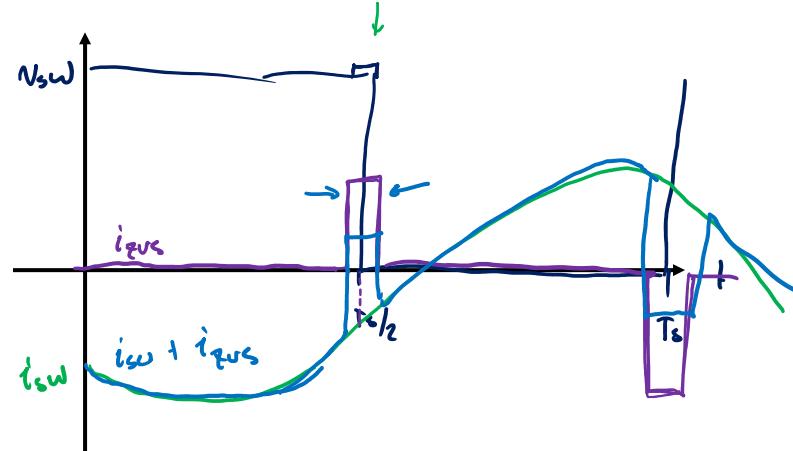

generate currents to assist w/ ZVS with minimal
- impact on main converter operation
- additional turns losses
other losses





ZVS Tank Examples

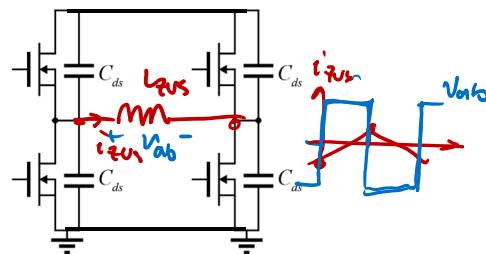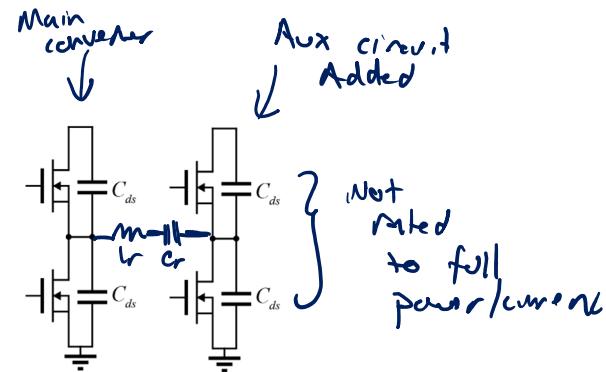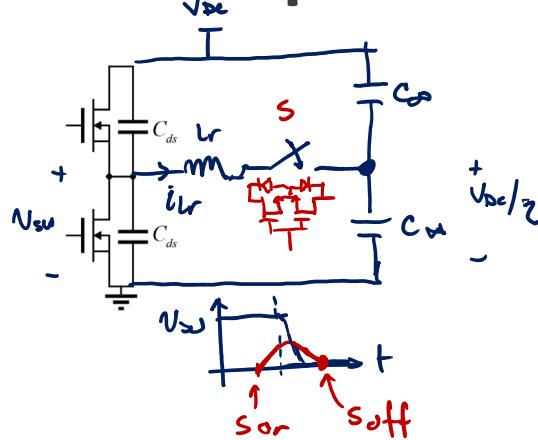


RESONANT SWITCH MODELING

Switching Losses in a Half Bridge (L7)

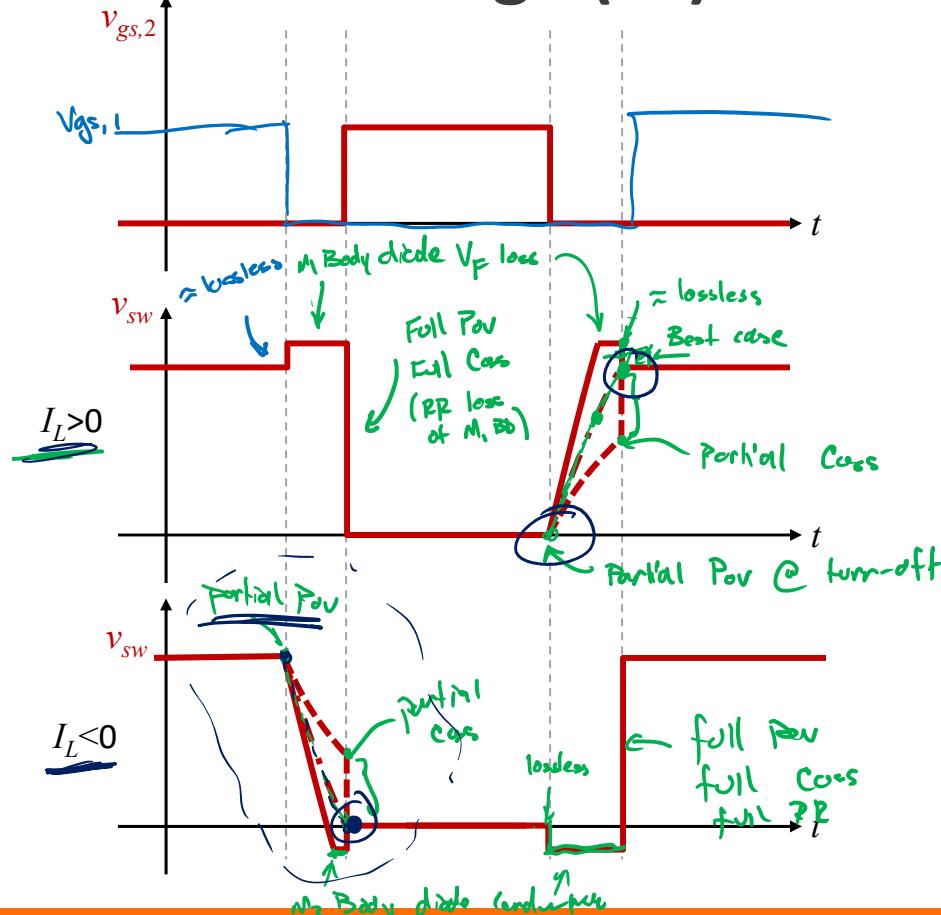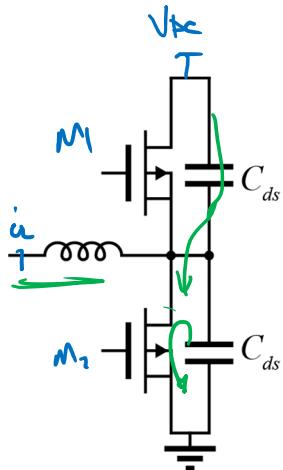

Ideal Switching Waveforms (L8)

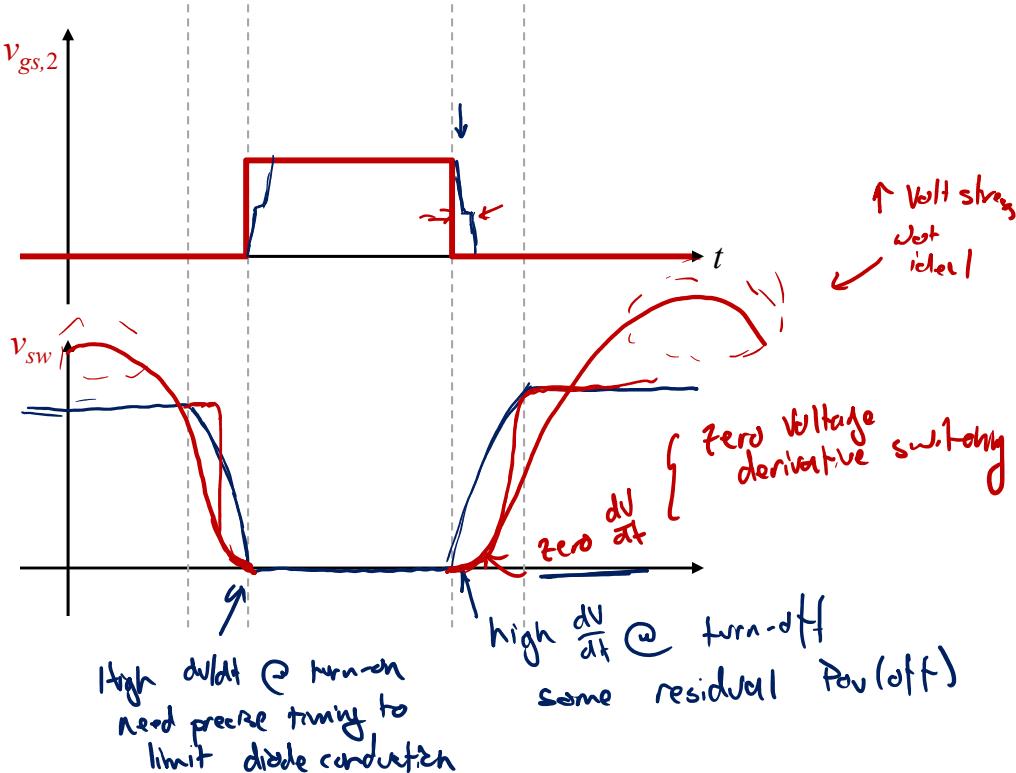

Class-E Amplifier

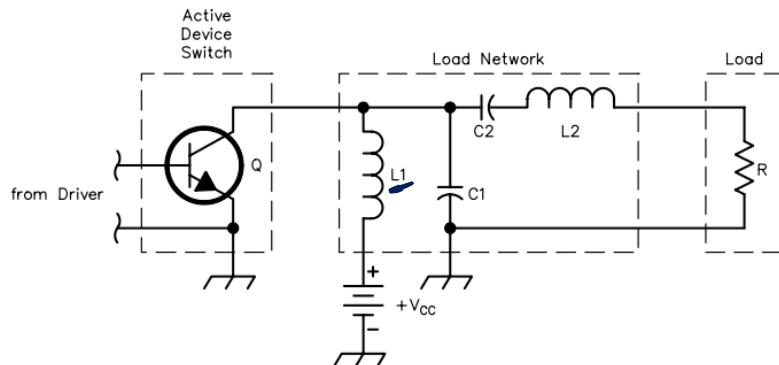


Fig 2—Schematic of a low-order Class-E amplifier.



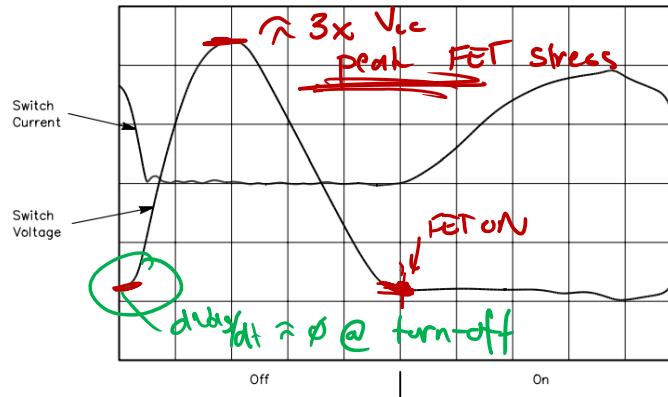
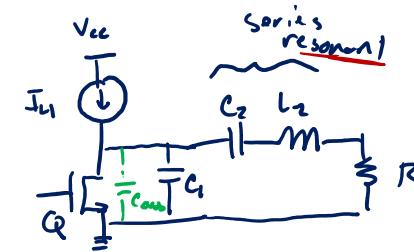
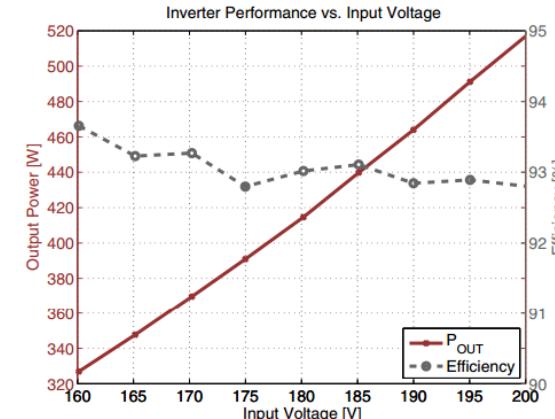


Fig 3—Actual transistor voltage and current waveforms in a low-order Class-E amplifier.

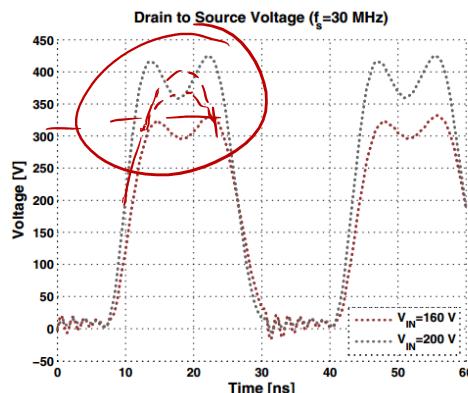

N. O. Sokal, "Class-E RF Power Amplifiers," 2001

Class Φ_2 Inverter

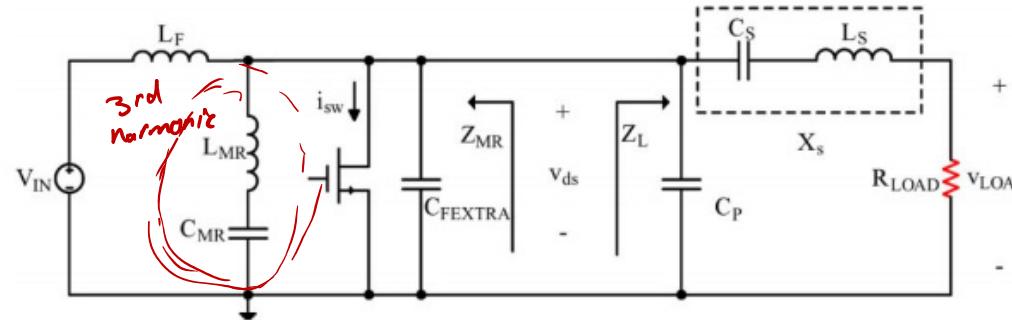

J. M. Rivas, O. Leitermann, Y. Han , A. D. Sagneri, and D. J. Perreault, " A High-Frequency Resonant Inverter Topology With Low-Voltage Stress", 2008

VHF DC-DC Converter

Φ_2 Boost Converter

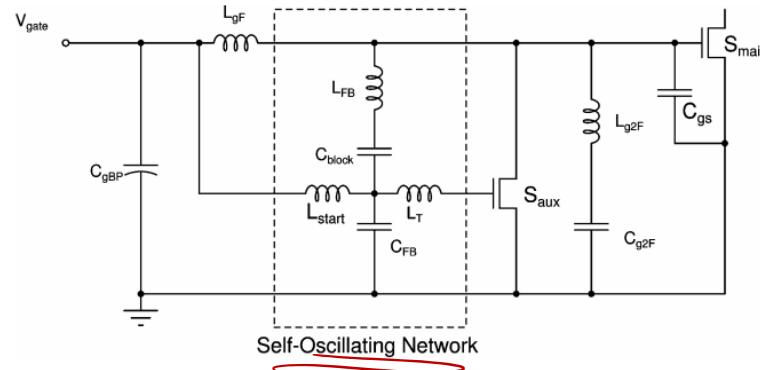
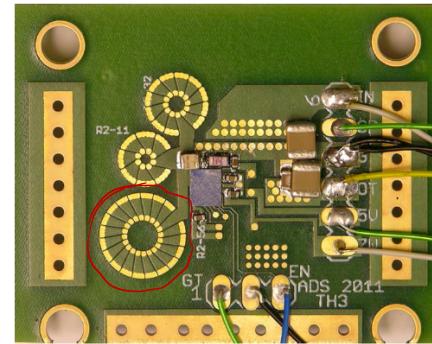
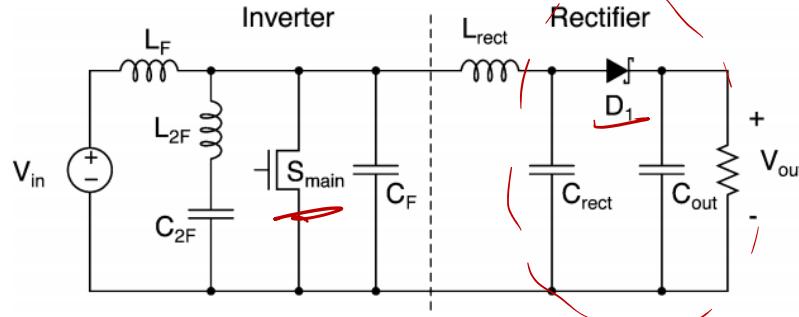


Fig. 5. Trapezoidal resonant gate drive circuit with self-oscillating network. The converter is enabled by applying the voltage V_{gate} , and disabled by setting V_{gate} to zero. This gate driver is employed in the 110-MHz converter (Fig. 9).

Chapter 20: Resonant Switch Topologies


↳ 2nd Edition
Ch 23 in 3rd Edition

- Introduction
- 20.1 The zero-current-switching quasi-resonant switch cell
 - 20.1.1 Waveforms of the half-wave ZCS quasi-resonant switch cell
 - 20.1.2 The average terminal waveforms
 - 20.1.3 The full-wave ZCS quasi-resonant switch cell
- 20.2 Resonant switch topologies
 - 20.2.1 The zero-voltage-switching quasi-resonant switch
 - 20.2.2 The zero-voltage-switching multiresonant switch
 - 20.2.3 Quasi-square-wave resonant switches
- 20.3 Ac modeling of quasi-resonant converters
- 20.4 Summary of key points

The resonant switch concept

General idea:

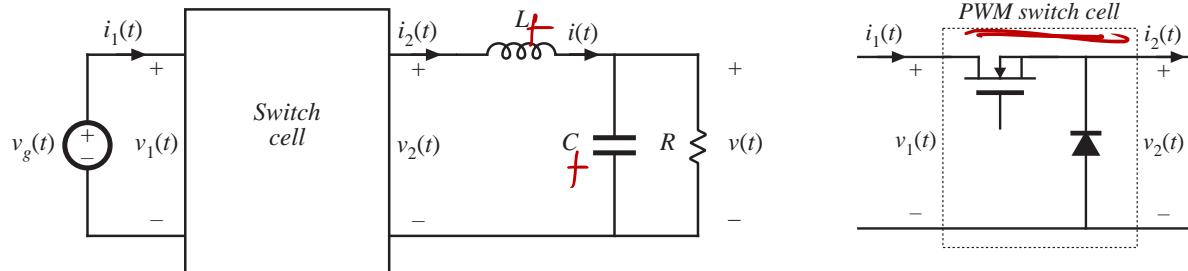
- PWM switch network is replaced by a resonant switch network
- This leads to a quasi-resonant or quasi-squarewave version of the original PWM converter




Example: realization of the switch cell in the buck converter

High Frequency Switch Network

Converter examples

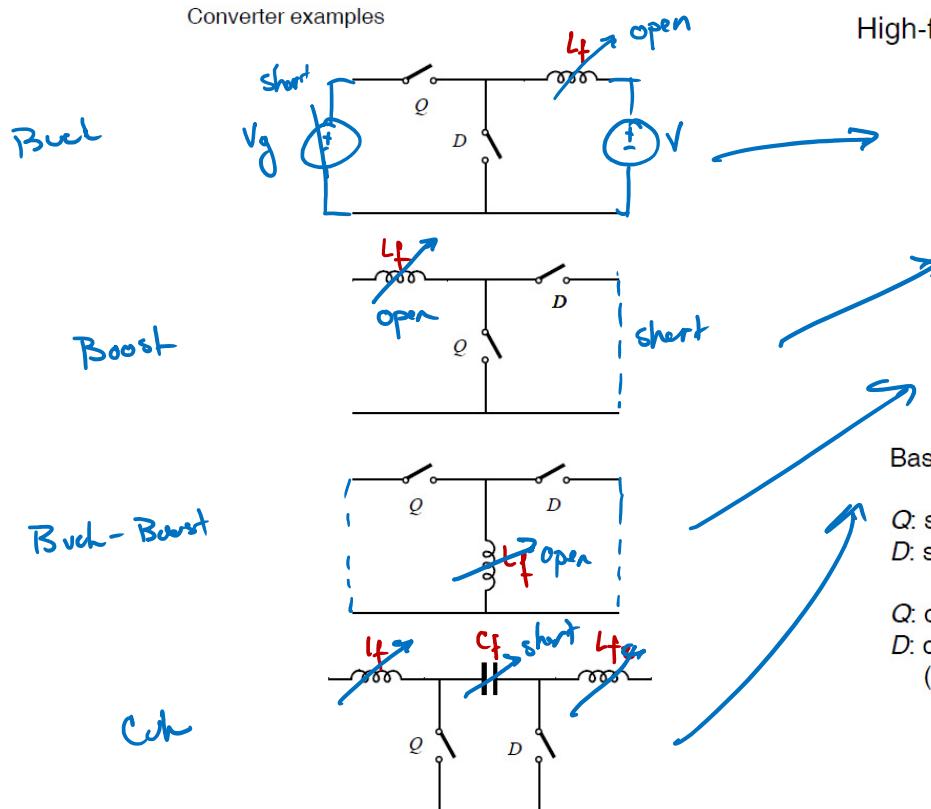

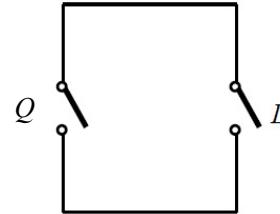High-frequency view of the switch network




Basic switch implementation options

Q : single-quadrant (transistor)
 D : single-quadrant (diode)


Q : current-bidirectional (e.g. MOSFET)
 D : current-bidirectional synchronous rectifier
(e.g. MOSFET)

ZVS-QSW: Review

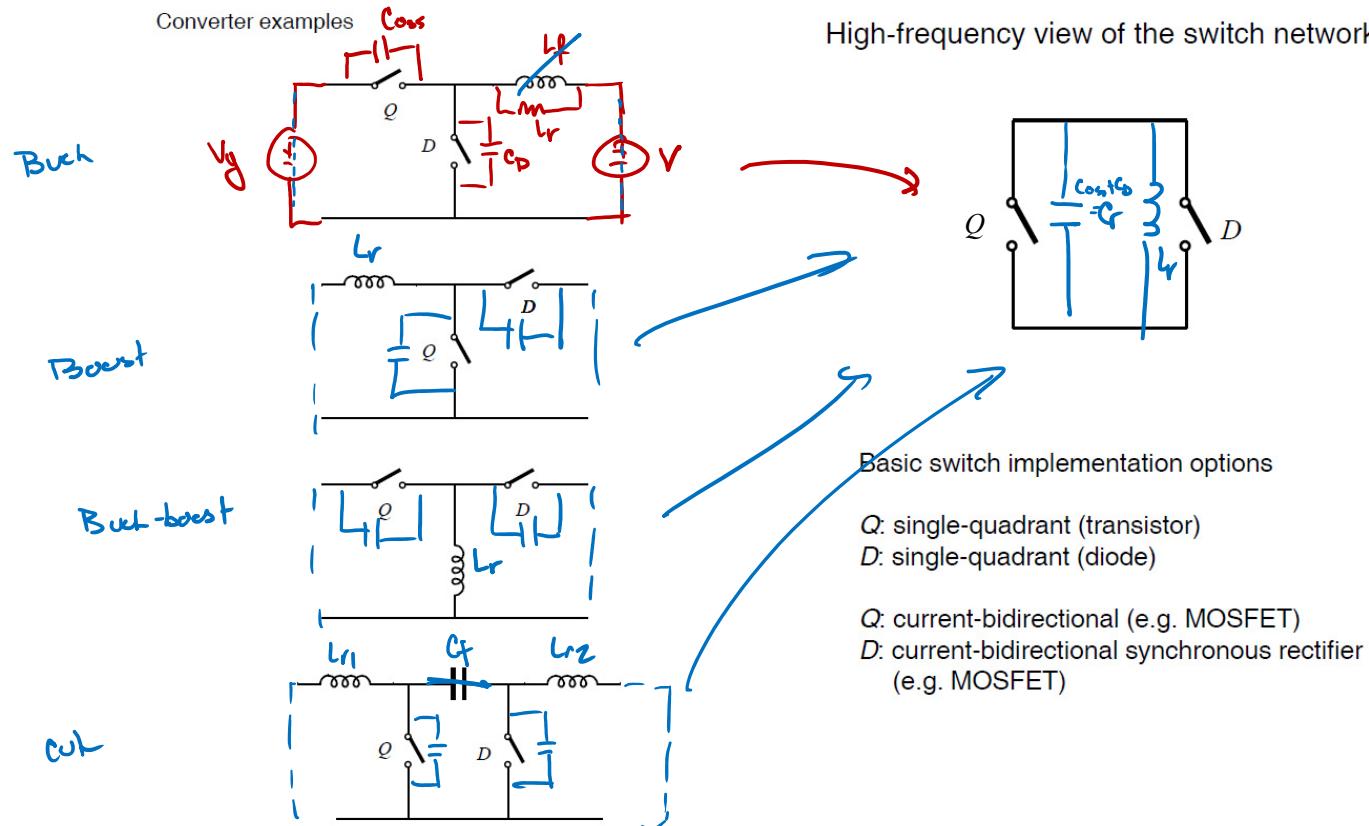


Classification of Resonant-Switch Converters



Quasi-squarewave

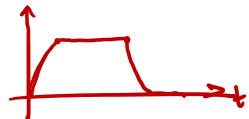



ZVS of Q
Covered previously in class

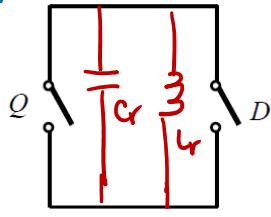

Quasi-resonant

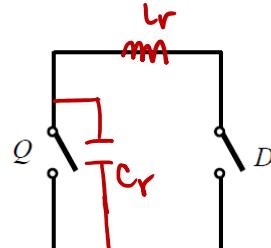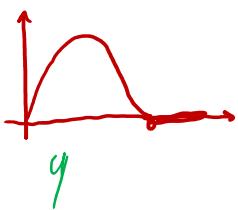

ZCS of Q

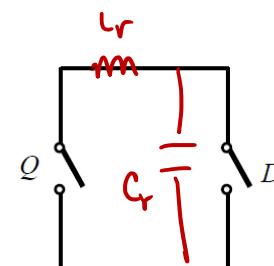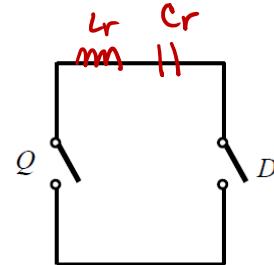

covered in
the book

ZVS-QR Buck

