
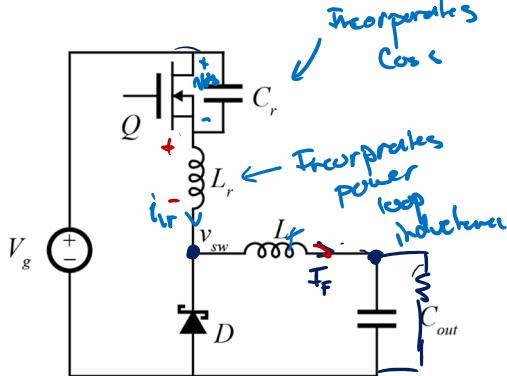


ZVS-QR Buck


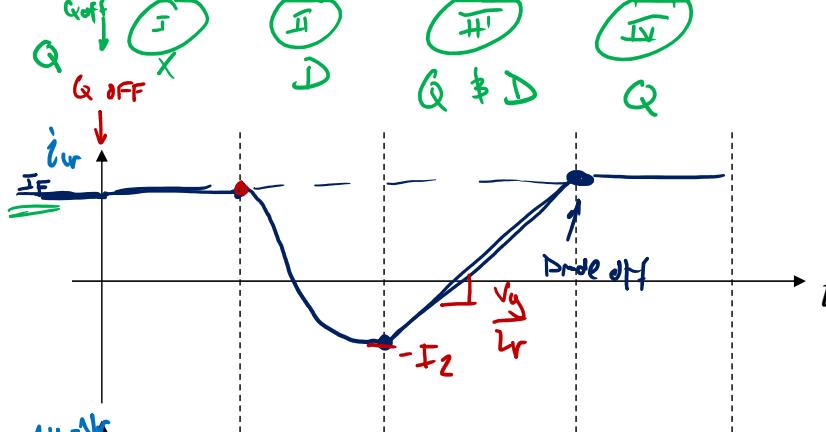


conducting:
 I: $Q \text{ ON}$
 II: $Q \text{ OFF}$
 III: $Q \text{ OFF}$
 IV: $Q \text{ OFF}$



Characteristics:

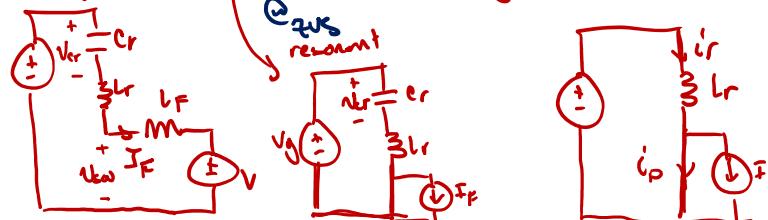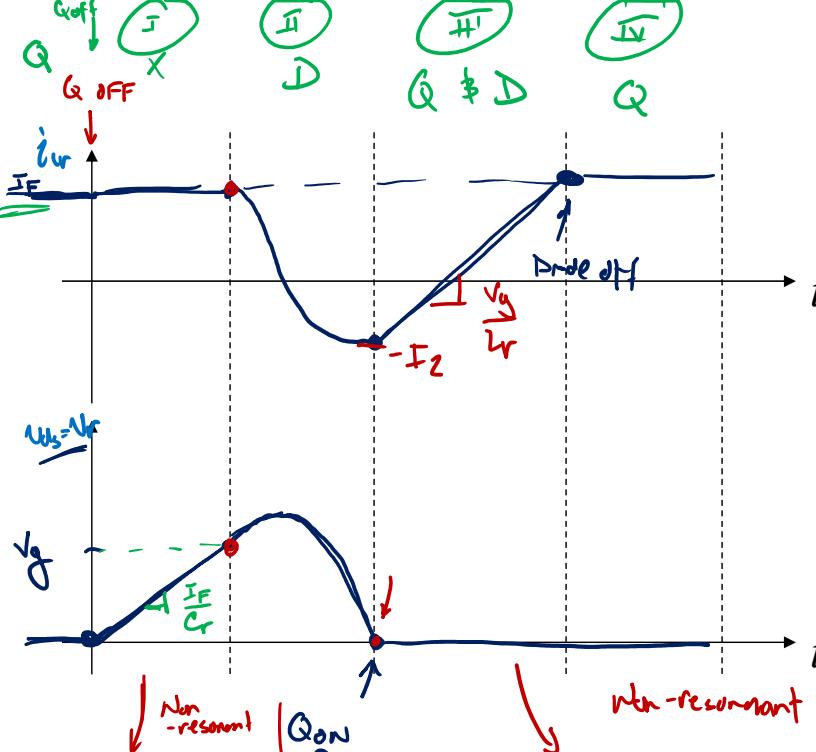- + Coss & $L_{\text{power loop}}$ are incorporated into operation
- + Peak inductor current is the peak FET current
- C_D is not part of operation
- Peak FET stresses $\downarrow V_g$



ZVS-QR State Plane

I

$$\frac{I_F}{C_r} t_1 = V_g$$

$$\theta_1 = \frac{1}{J_F}$$

II

$$J_F^2 = 1 + J_2^2$$

$$\beta = \pi + \sin^{-1}\left(\frac{1}{J_F}\right)$$

III


$$\frac{V_g}{L_r} t_3 = (I_F + I_2)$$

$$\theta_3 = J_F + J_2$$

IV

$$\theta_1 + \beta + \theta_3 + \theta_4 = \frac{2\pi}{F}$$
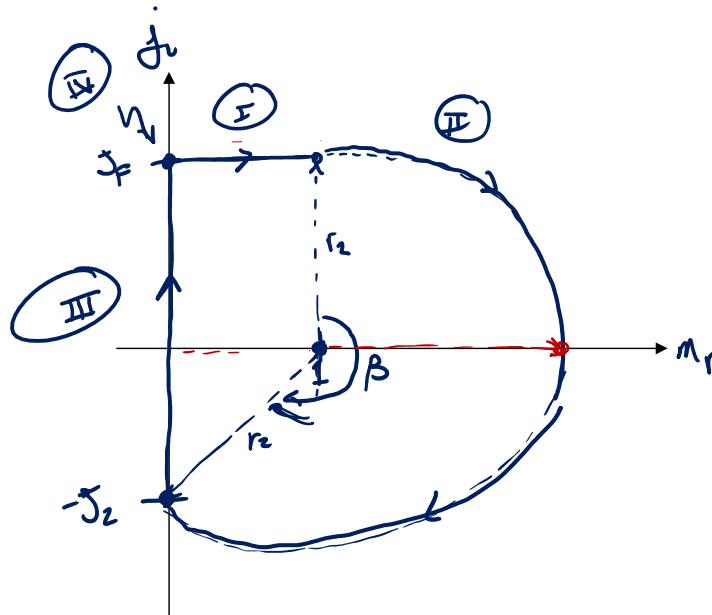
$$V_{base} = V_g \quad R_0 = \sqrt{\frac{L_r}{C_r}} \quad I_{base} = \frac{V_{base}}{R_0}$$



ZVS condition: $r_2 \geq 1$

$$J_F \neq 1$$

Averaging

Cap-Q balance on C_{out}

$$\langle i_{C_{out}} \rangle |_{T_S} = \phi \rightarrow I_L = \frac{V}{R}$$

Volt-sec balance on L_F


$$\langle N_{LF} \rangle |_{T_S} = \phi = V_g - \langle N_{cr} \rangle |_{T_S} - \cancel{\langle N_{Lr} \rangle |_{T_S}} - V$$

$$V = V_g - \frac{1}{T_S} \int_0^{T_S} N_{cr} dt$$

$$V = V_g - \frac{1}{T_S} [\lambda_1 + \lambda_2]$$

$$V = V_g - \frac{1}{T_S} \left[\frac{1}{2} t_1 V_g + V_g t_\beta + L_r (I_F + I_L) \right]$$
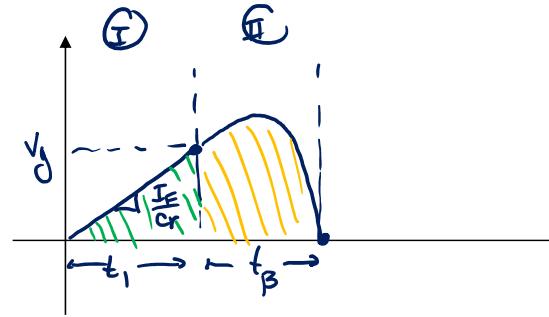
$$M = 1 - \frac{F}{2\pi} \left[\frac{1}{2} Q_1 + \beta + J_p + J_L \right]$$



$$\lambda_1 = \frac{1}{2} t_1 V_g$$

$$\lambda_2 = \int_{\text{I}}^{\text{II}} N_{cr} dt = \int_{\text{II}}^{\text{III}} (V_g - L_r \frac{di}{dt}) dt$$

$$= V_g t_\beta - L_r (-I_F - I_L)$$

$$= V_g t_\beta + L_r (I_F + I_L)$$

Complete Solution

$$M = 1 - \frac{F}{2\pi} \left[\frac{\theta_1}{2} + \beta + \gamma_2 + \gamma_F \right]$$

$$M = 1 - \frac{F}{2\pi} \left[\frac{1}{2\gamma_F} + \pi + \sin^{-1}\left(\frac{1}{\gamma_F}\right) + \sqrt{\gamma_F^2 - 1} + \gamma_F \right]$$

→ same as
 " 20.46 in 2nd Ed
 " 23.46 in 3rd Ed Fundamentals of Powr Elec

$$M = 1 - F \underline{P_{V_L}}\left(\frac{1}{\gamma_L}\right)$$

$$\rightarrow \frac{1}{\gamma_L} \leftrightarrow \gamma_L$$

$1 - F P_{V_L}(\gamma_L) = M$ of ZCS-QR Buck

This is half-wave ZVS-QR Buck




Full-wave ZVS-QR Buck



→ Requires bidirectional voltage blocking Q

ZVS bound:
 $\gamma_L \geq 1$

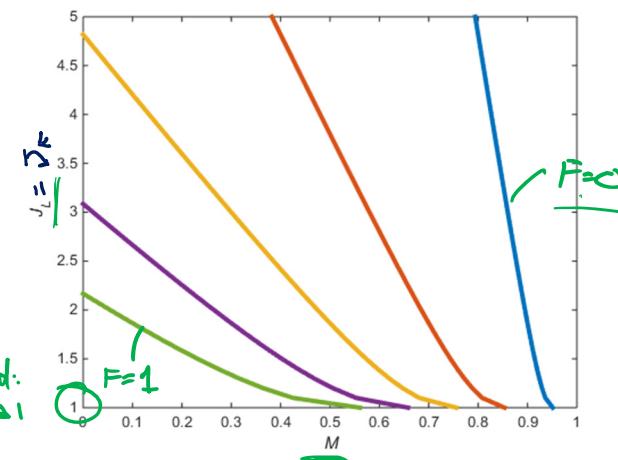

MOSFET Voltage Stresses

Peak voltage on Q:

$$N_{pk} = 1 + \beta_F$$

$$V_{pk} = V_g + \underline{\beta_F V_{base}}$$

④ Minimum ZVS power $\beta_F = 1$


$$\boxed{V_{pk} = 2V_g}$$

④ minimum ZVS power



ex If we want to keep ZVS from full power down to 20% of P_{max}

$$V_{pk} = (5+1) V_g = \underline{\underline{6V_g}}$$




Test Circuit

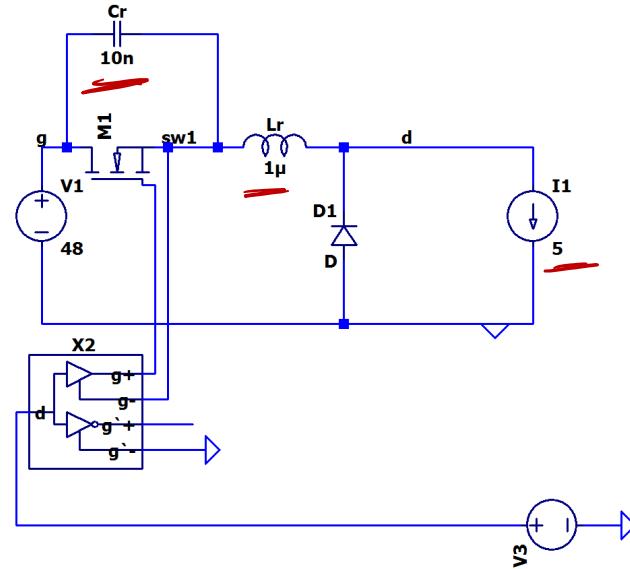

Simulation Results

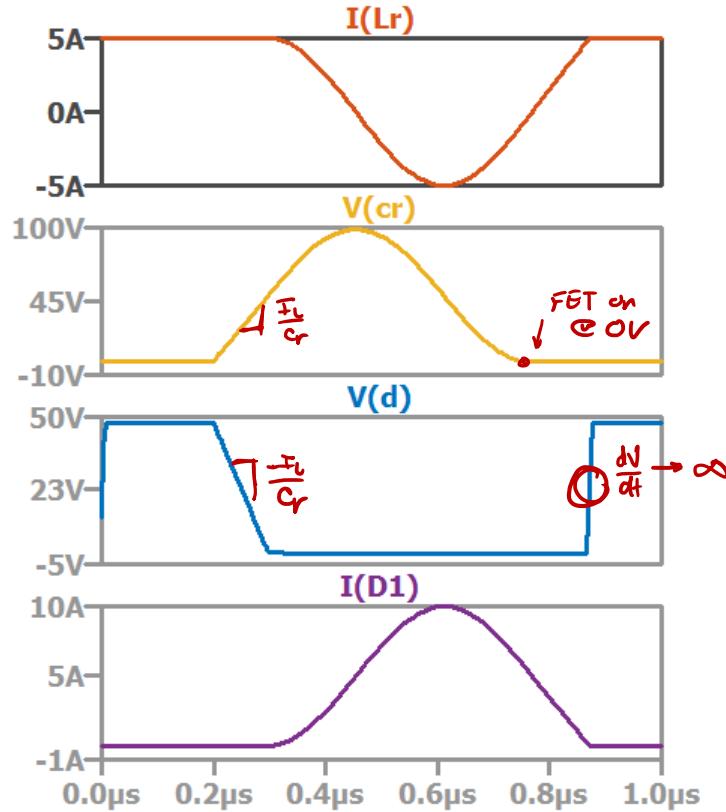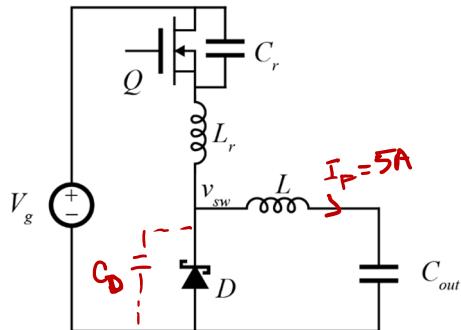

Diode Capacitance

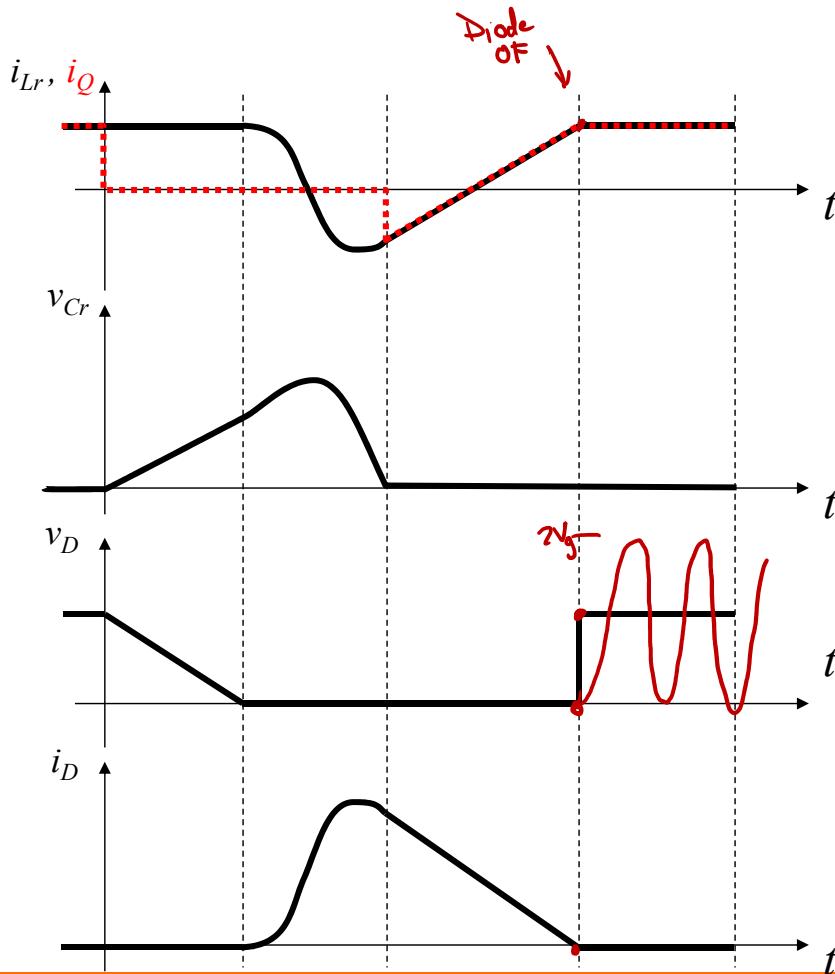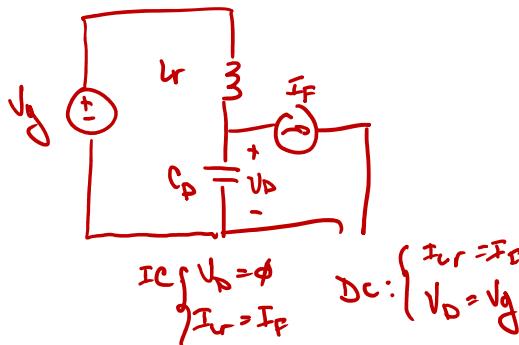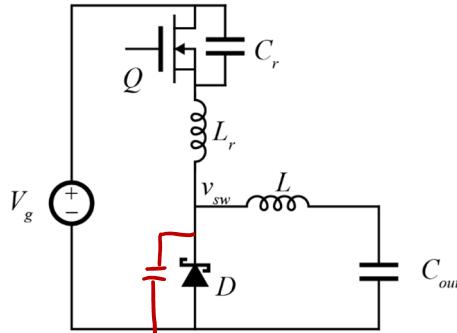

Simulation Results: Diode Capacitance

