

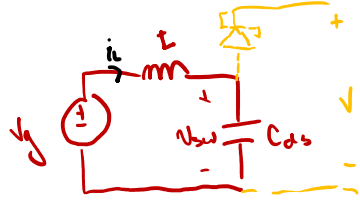


Device Capacitances

FET Turn-off

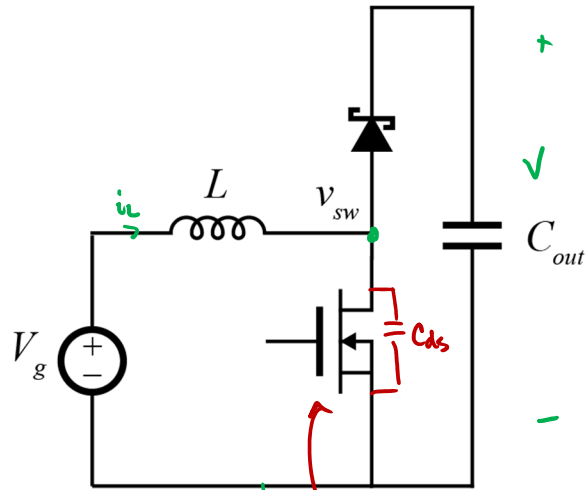

ideal
($k_{on} > \phi$)

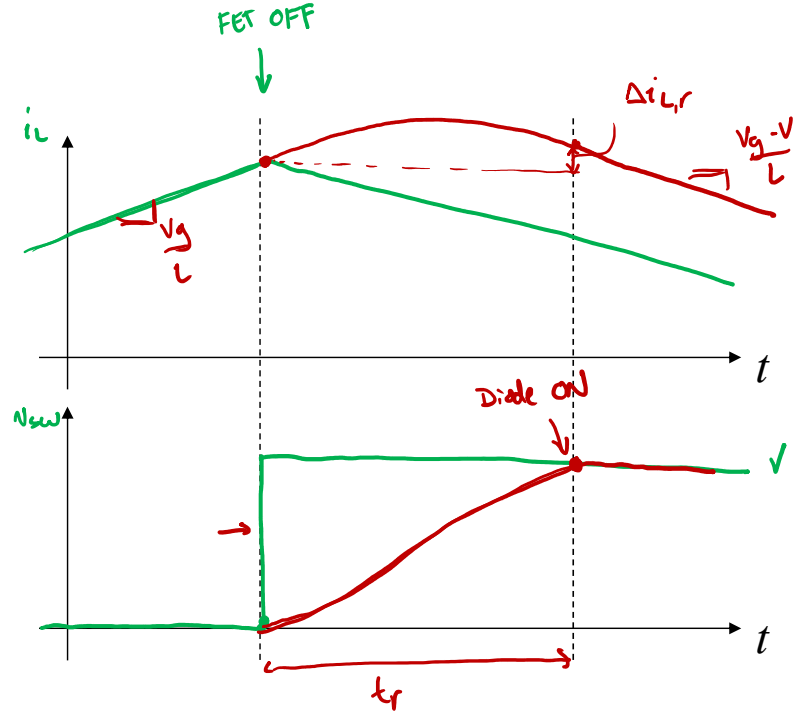



E_{loss} :
None!

461 approximations

$$t_r \approx \phi$$


$$\Delta v_{L,R} \ll I_L$$

Device Capacitances

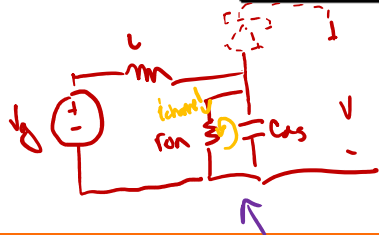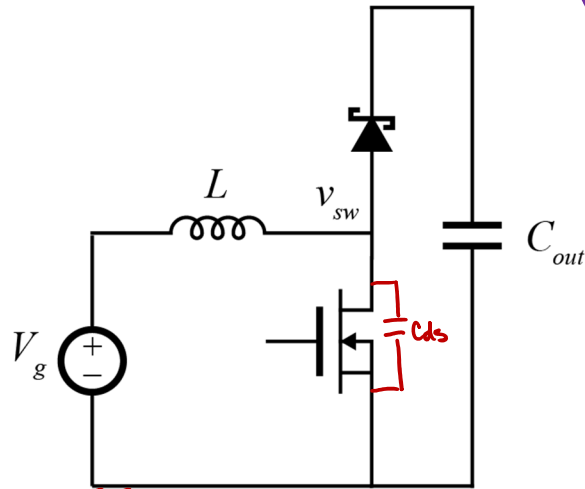


Somewhat, let's reverse i_c at this transition

FET Turn-on

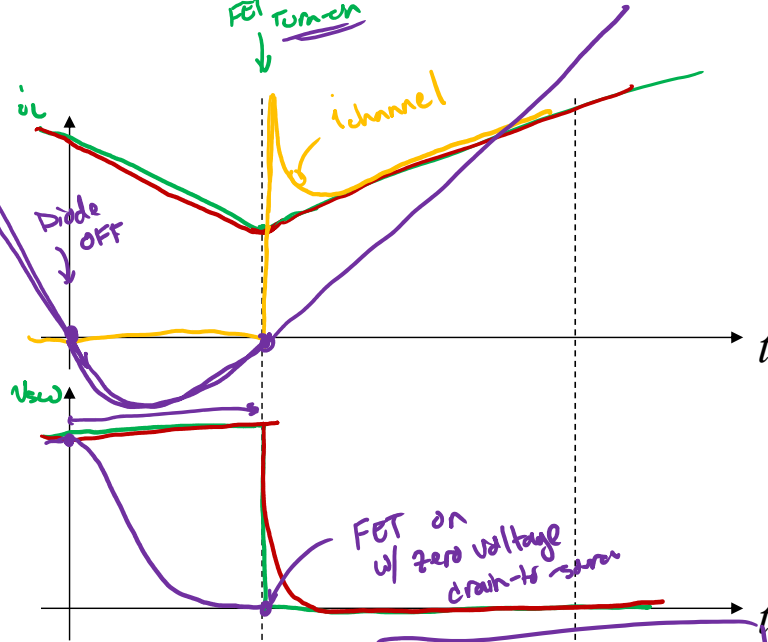

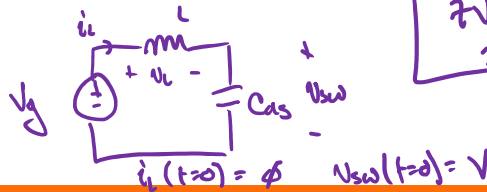
Cross: All of $\frac{1}{2} C V^2$ from turn-off



ZVS or Zero-Voltage Switching



DCM: Soft Switching

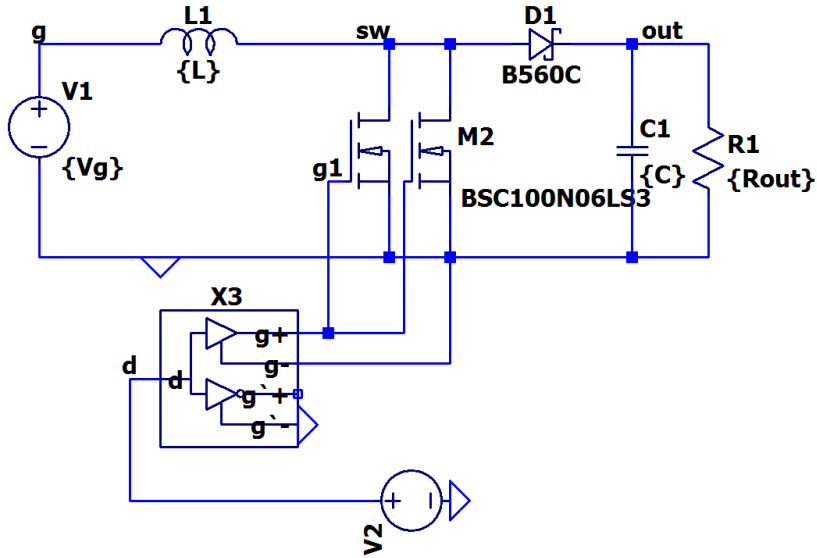


L	C_{out}	f_s	Diode	η (Sim)
22uH	22uF	202k	Si (FR)	93.9%
22uH	22uF	202k	Si Schottky	95.8%
4.6uH	22uF	202k	Si Schottky	98.2%

Drop L by
~5x


22uH

2.4% increase
in η !


DCM Simulation

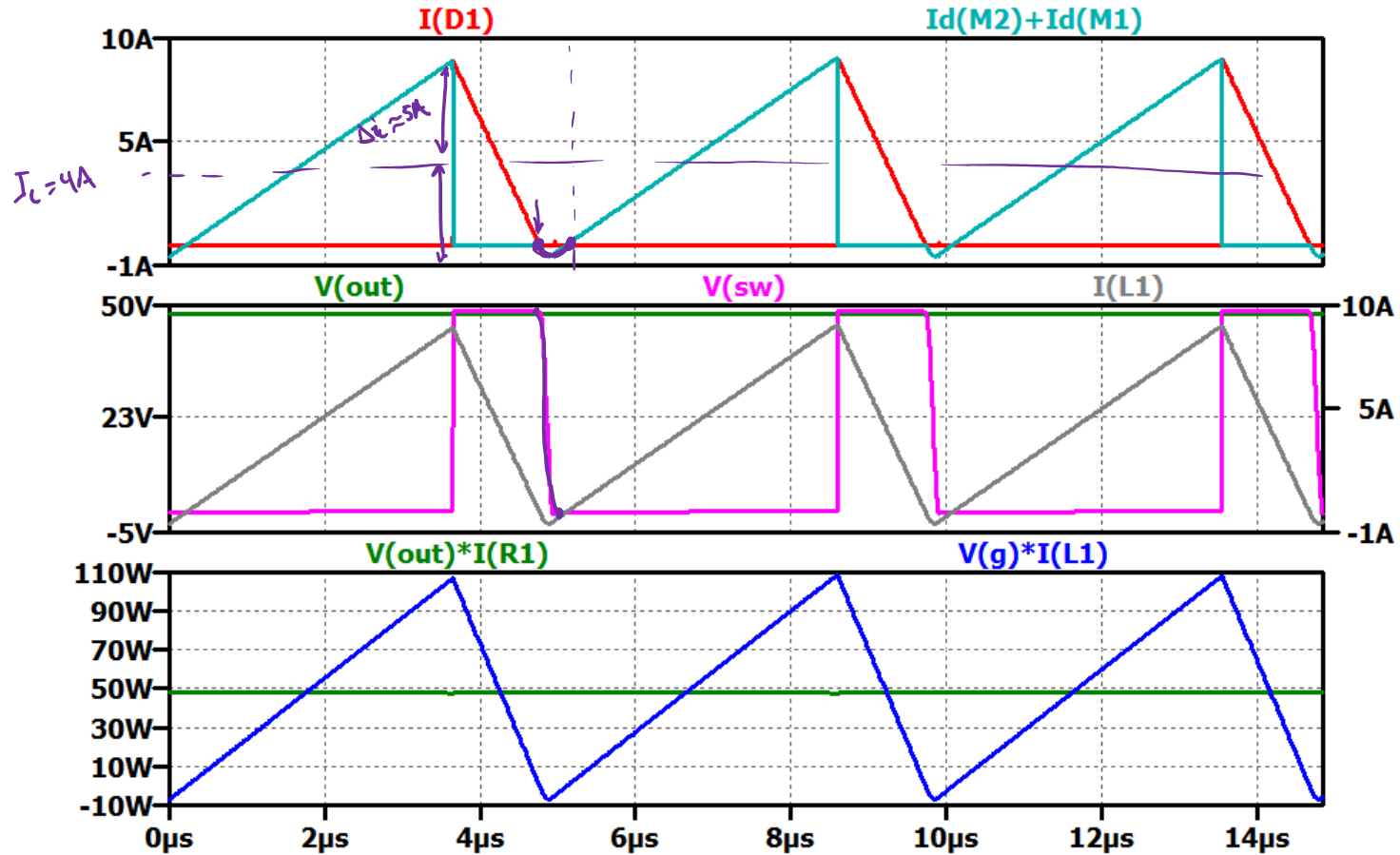


MOSFET Turn-Off

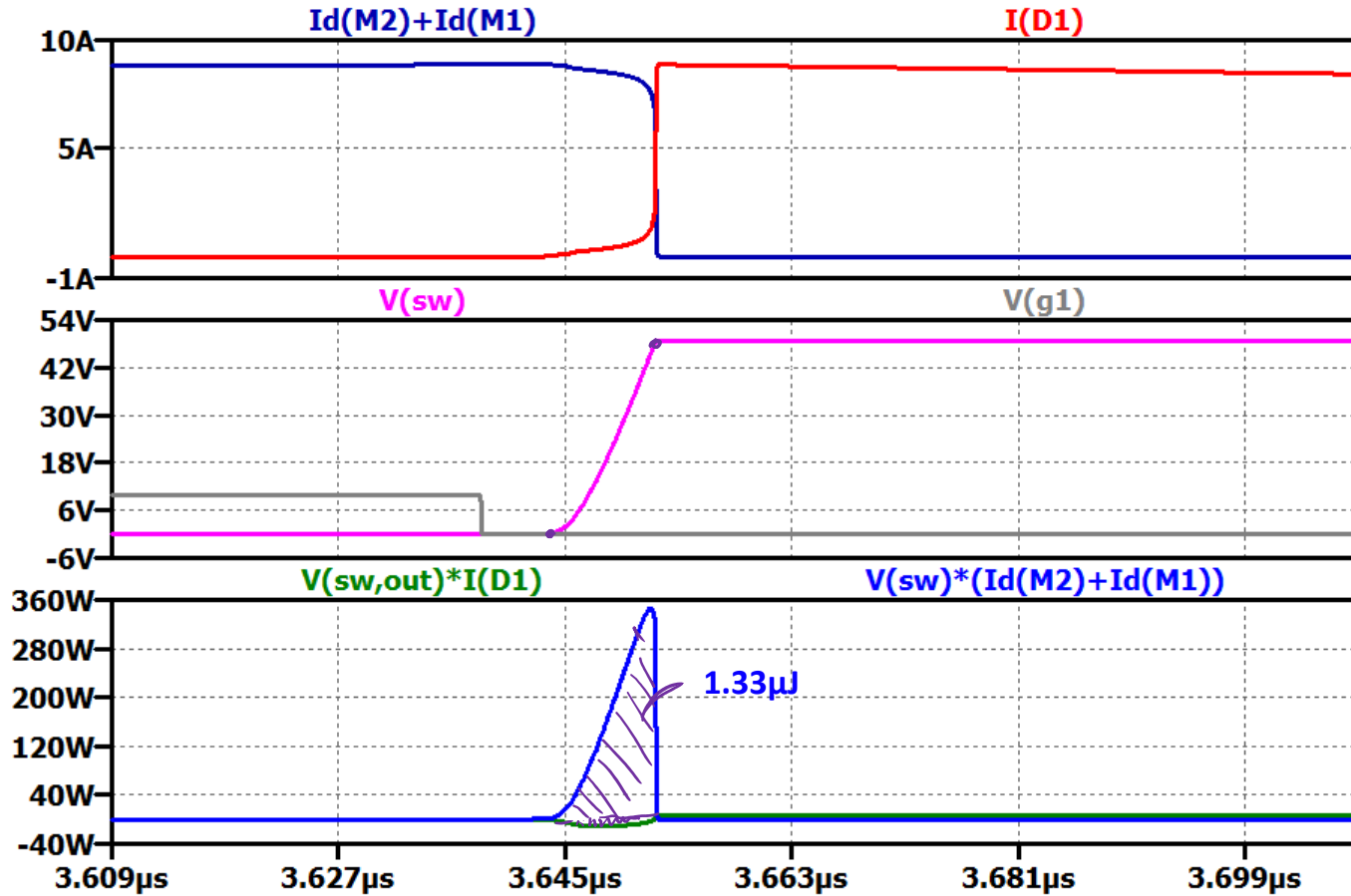

MOSFET Turn-On

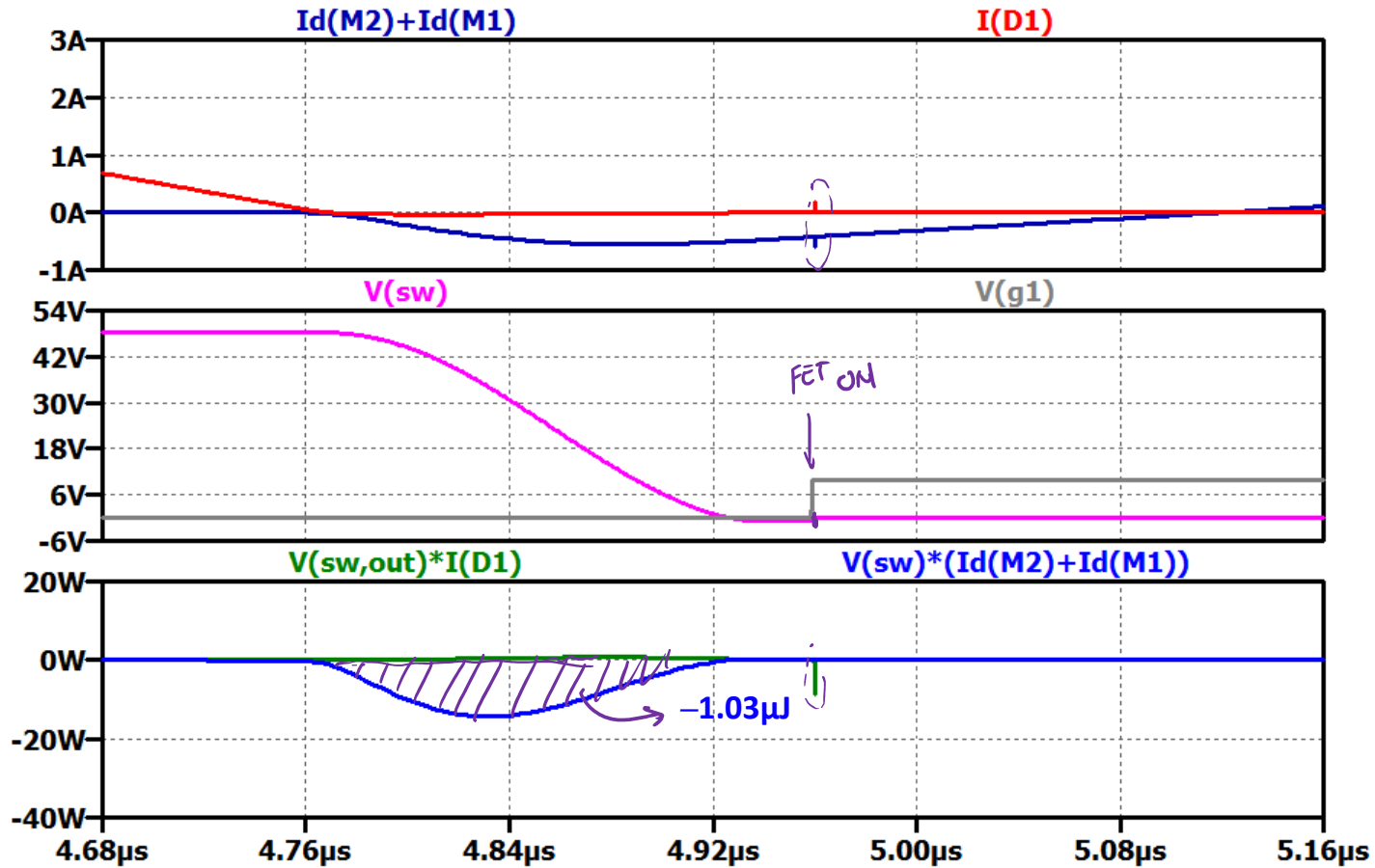


1 MHz Operation

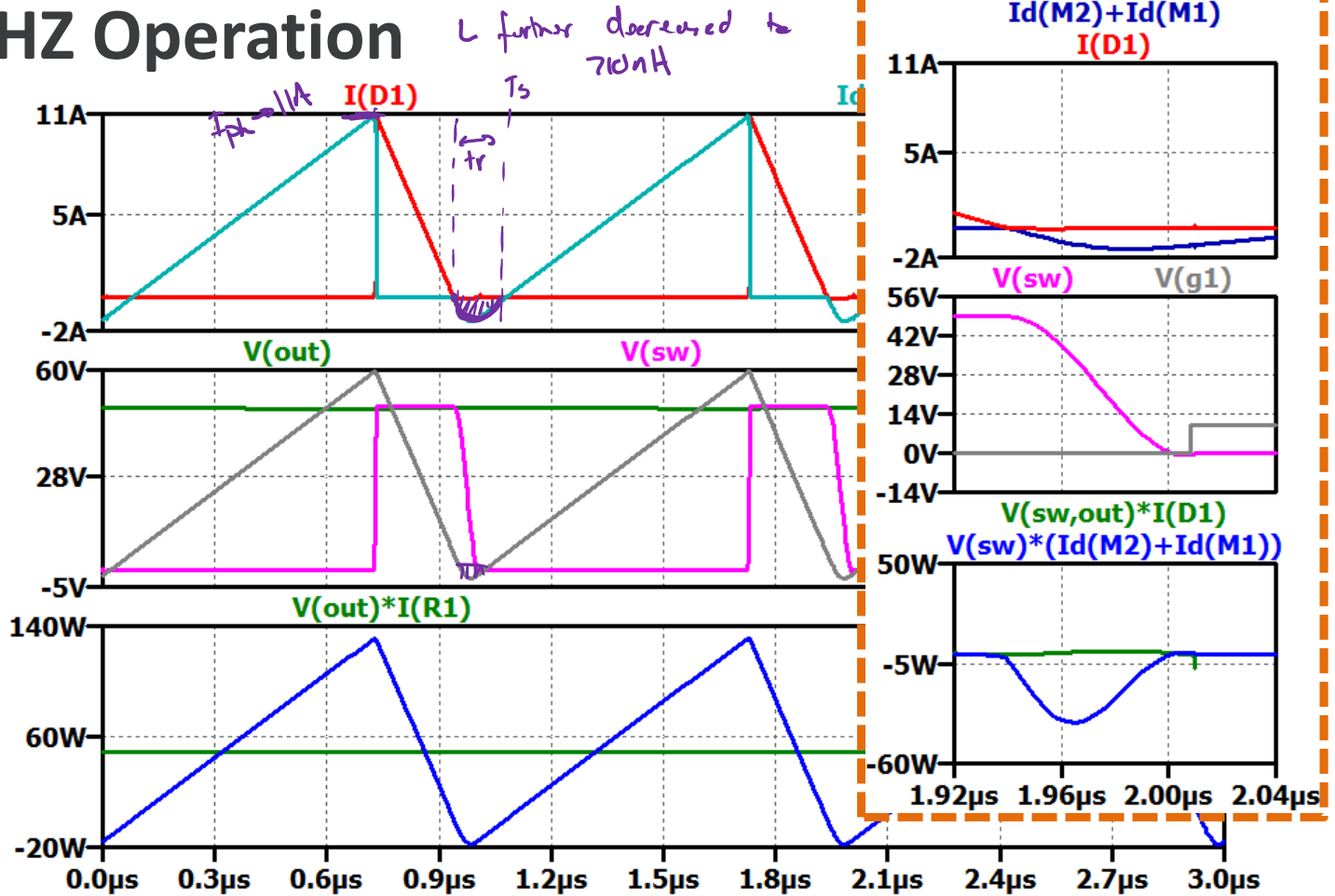


Low Power Operation

$P_{out} = 1W$

$\eta = 68\%$

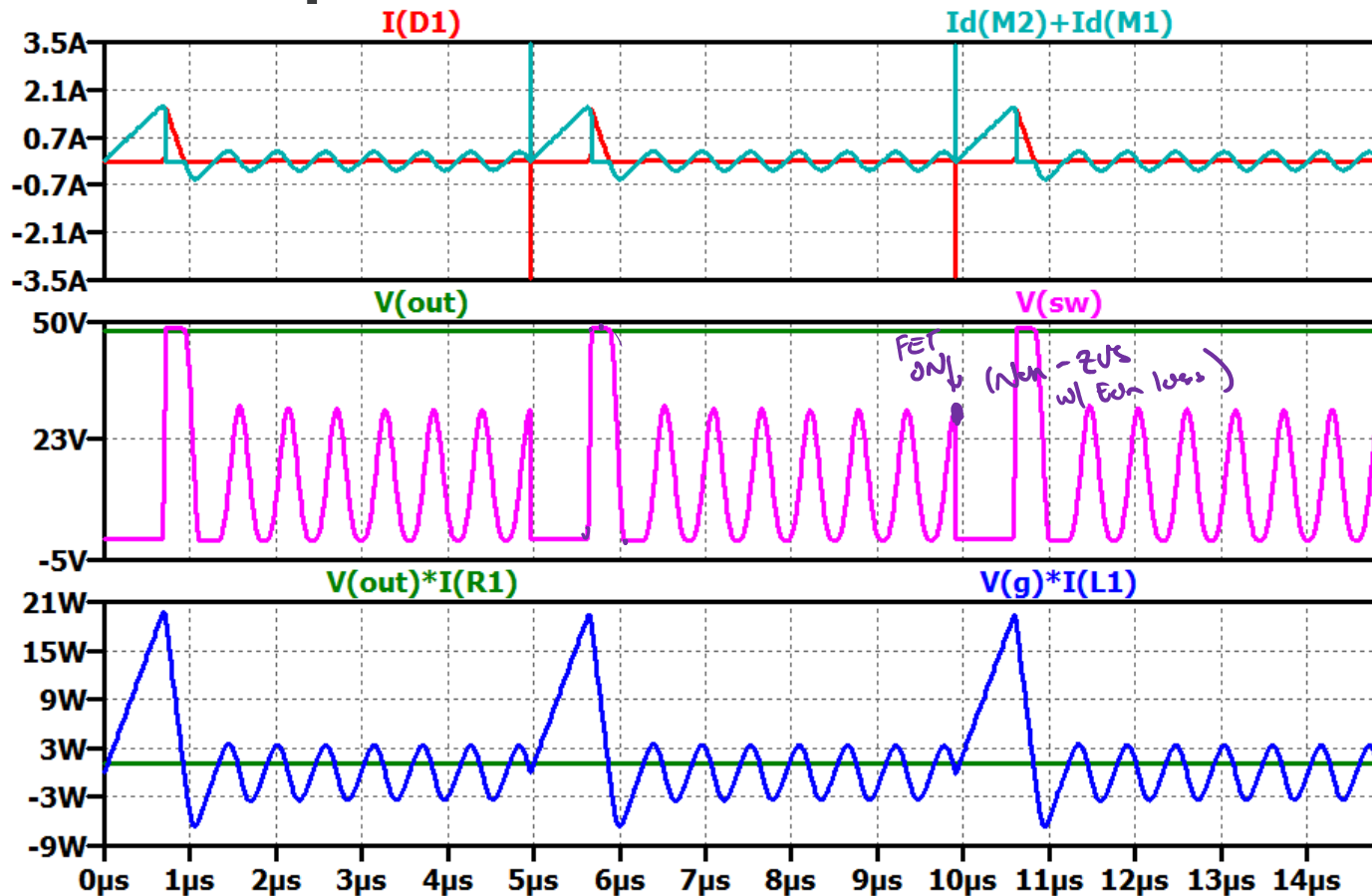


Synchronous Operation

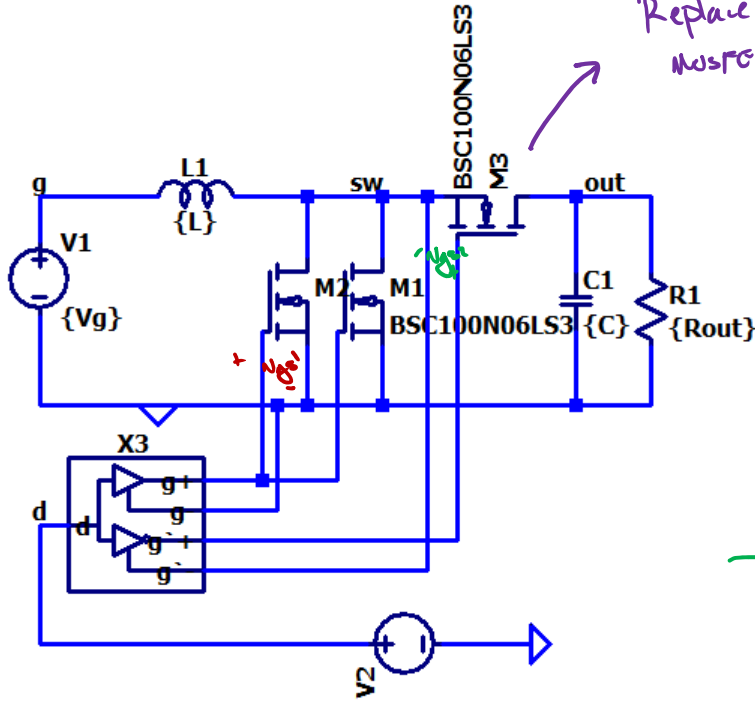

Replace diode w/ FET
 must be current-bidirectional
 + Allows control of device turn-off instant

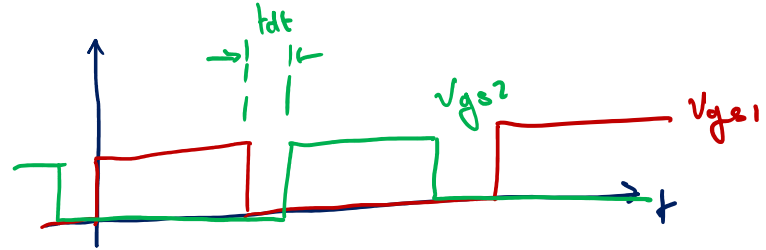
+ Replace conduction loss $V_f I$ w/ $I^2 R_{on}$
 - Need to generate two gate drive signals




Synchronous Simulation

$\eta = 98\%$

$\eta = 99.6\%$

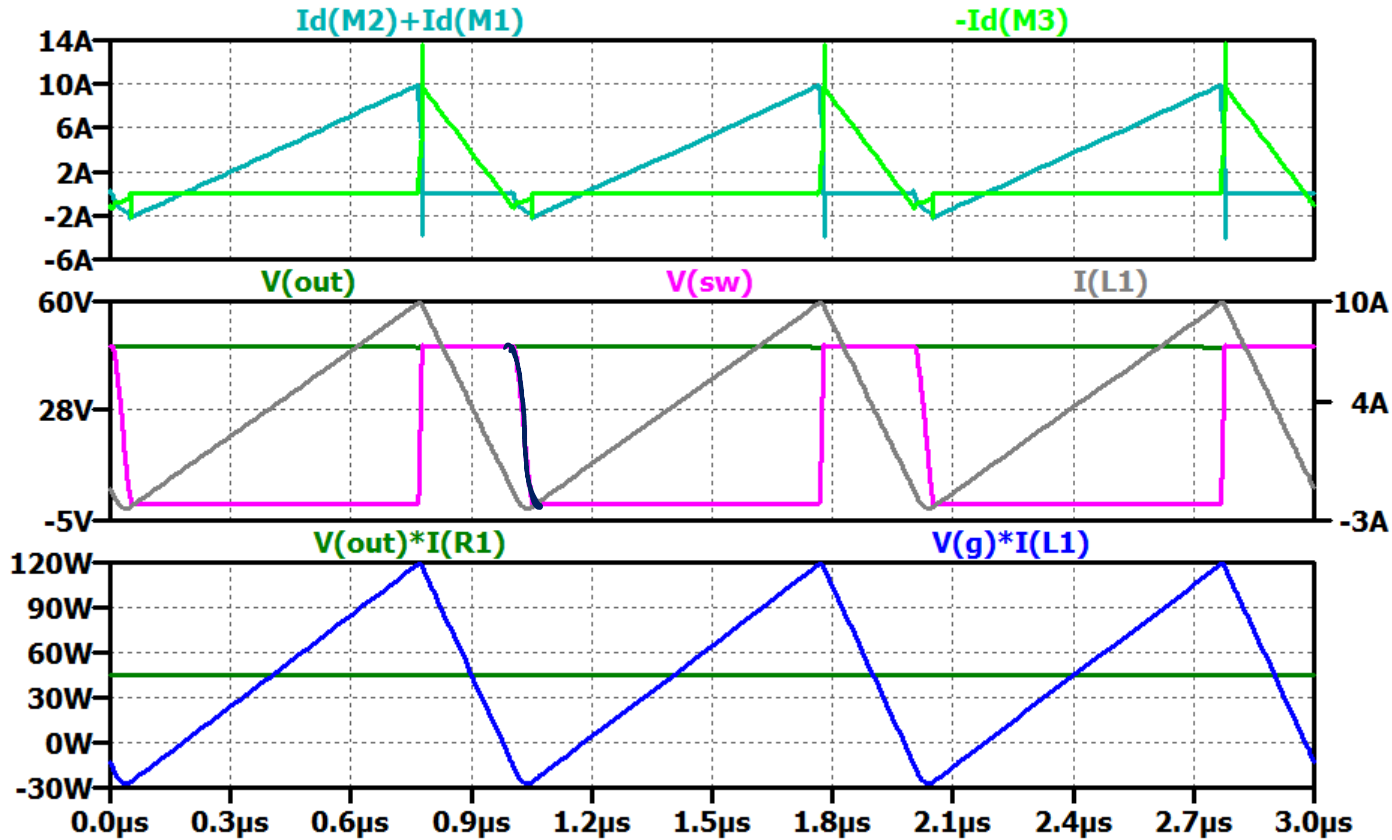


Switching Transitions

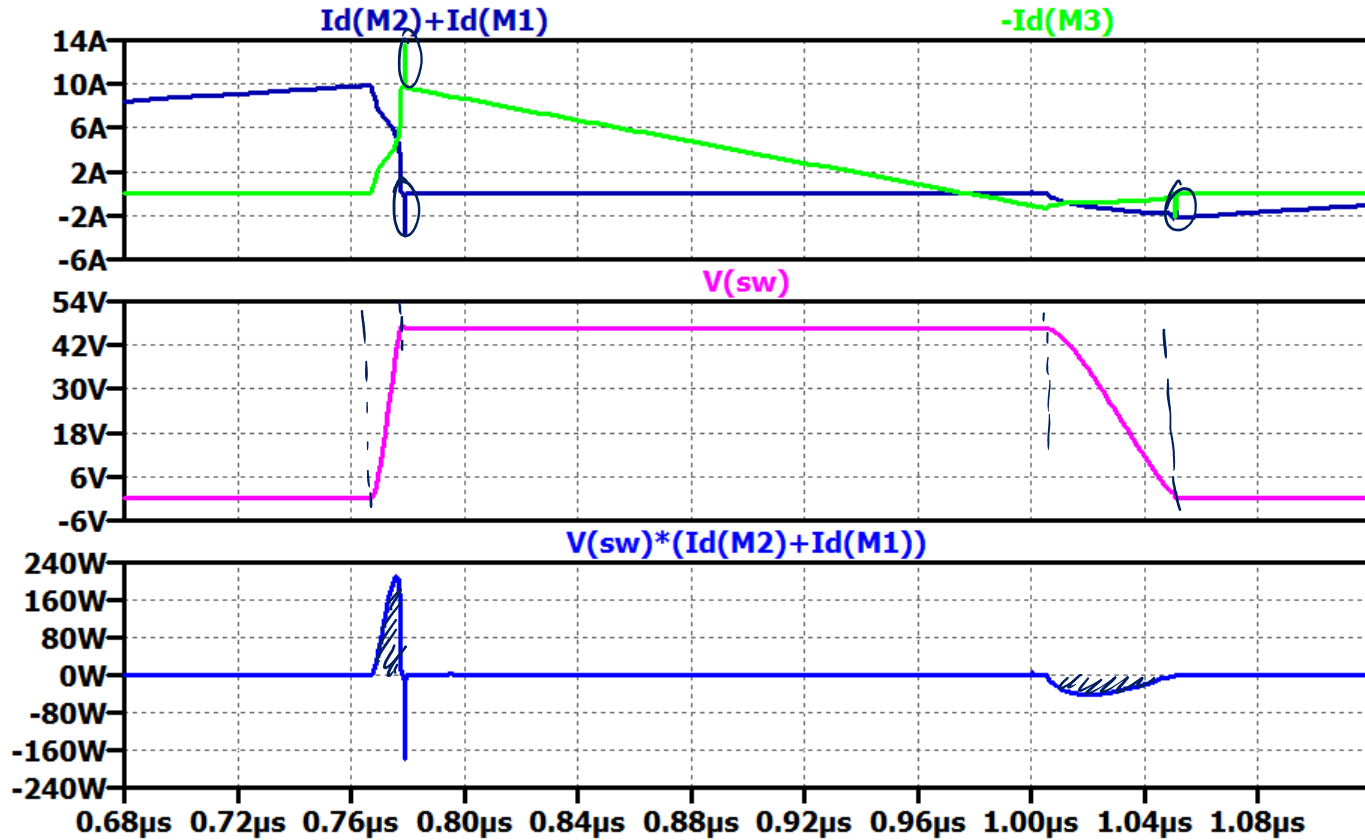


Low Power Operation $P_{out} = 1W$

$\eta = 91\%$

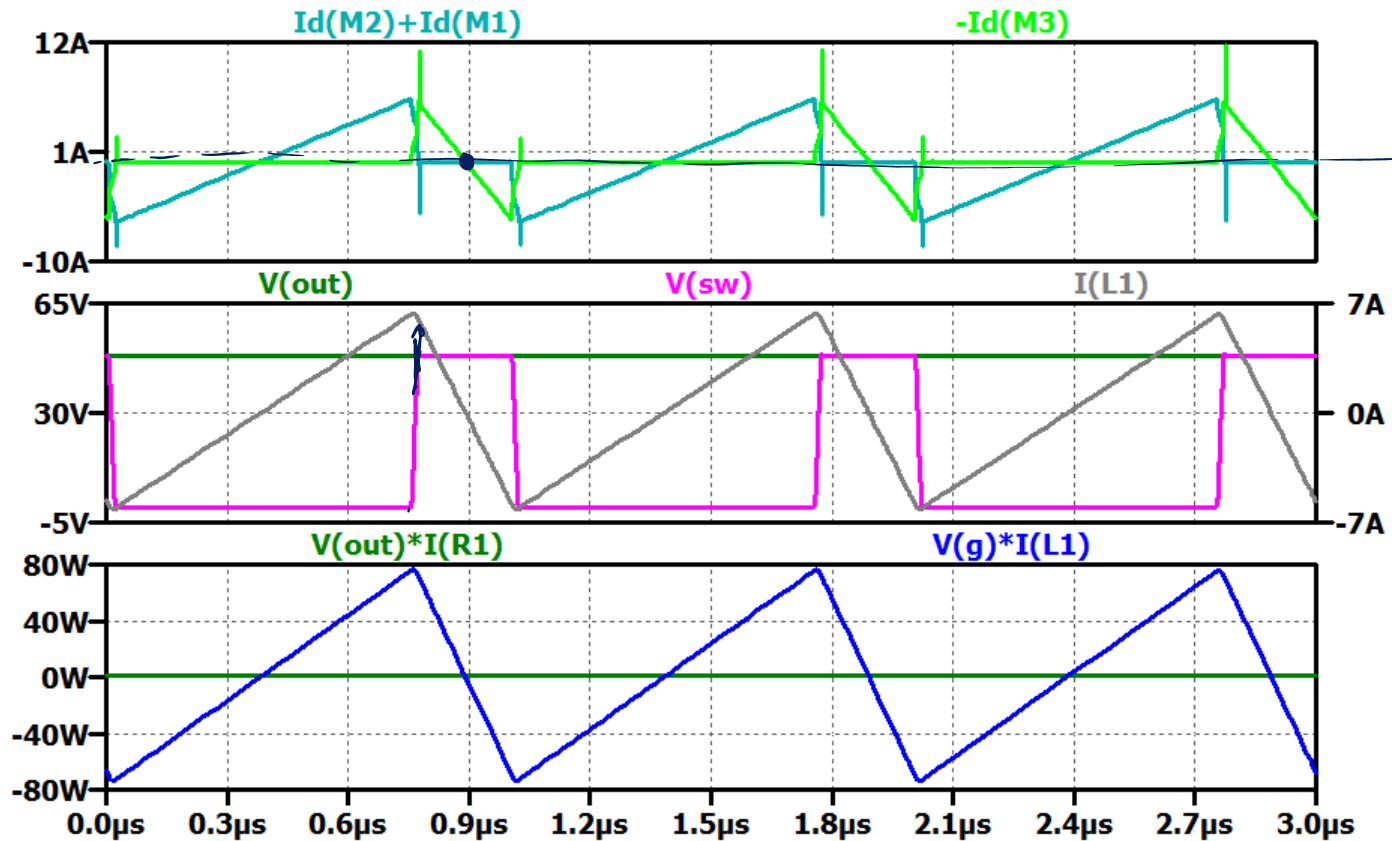

Resonant Operation

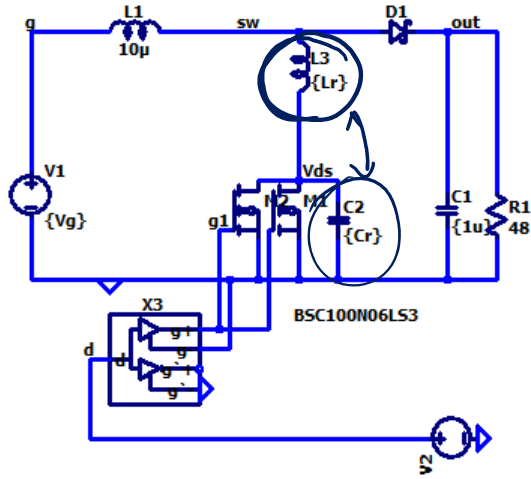

	Switching	L	C_{out}	f_s	Diode	η (Sim)
→	Hard	22uH	22uF	202k	Si (FR)	93.9%
→	Hard	22uH	22uF	202k	Si Schottky	95.8%
→	Soft	4.65uH	22uF	202k	Si Schottky	98.4%
→	Soft	710nH	4.4uF	1 MHz	Si Schottky	98.2%
→	Soft	710nH	4.4uF	1 MHz	MOSFET	99.6%
	Resonant	10uH + 2.4uH	1uF + 10nF	225 kHz	Si Schottky	98.6%
	Resonant	10uH + 2.4uH	1uF + 10nF	225 kHz	MOSFET	99.96%

} →

} →

Resonant Boost Converter

