

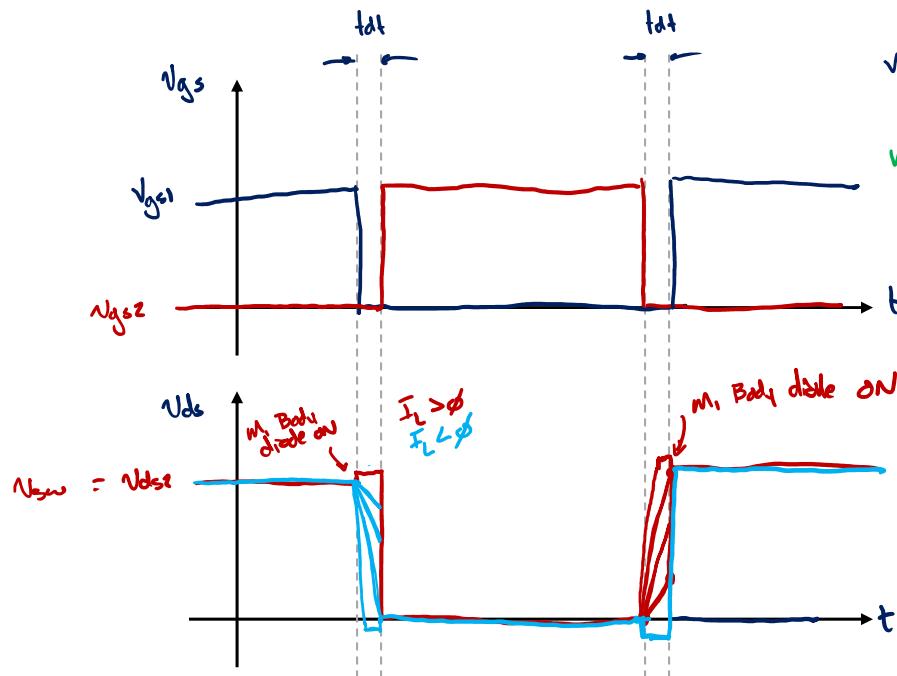


# Synchronous Switching

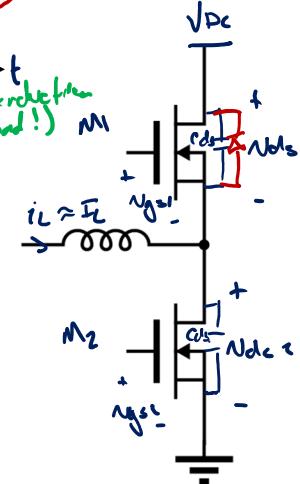

controller-specified


$t_{dt}$

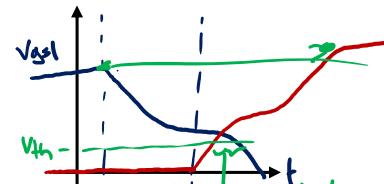


Inductively -  
clamped  
half-bridge

# MOSFET Cross Section

silicon NMOS

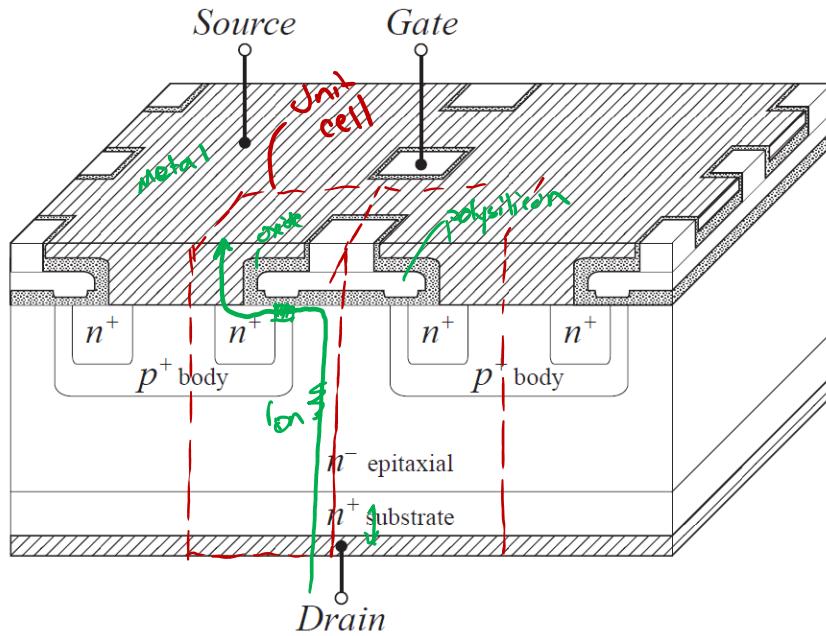

# MOSFET Depletion Capacitance

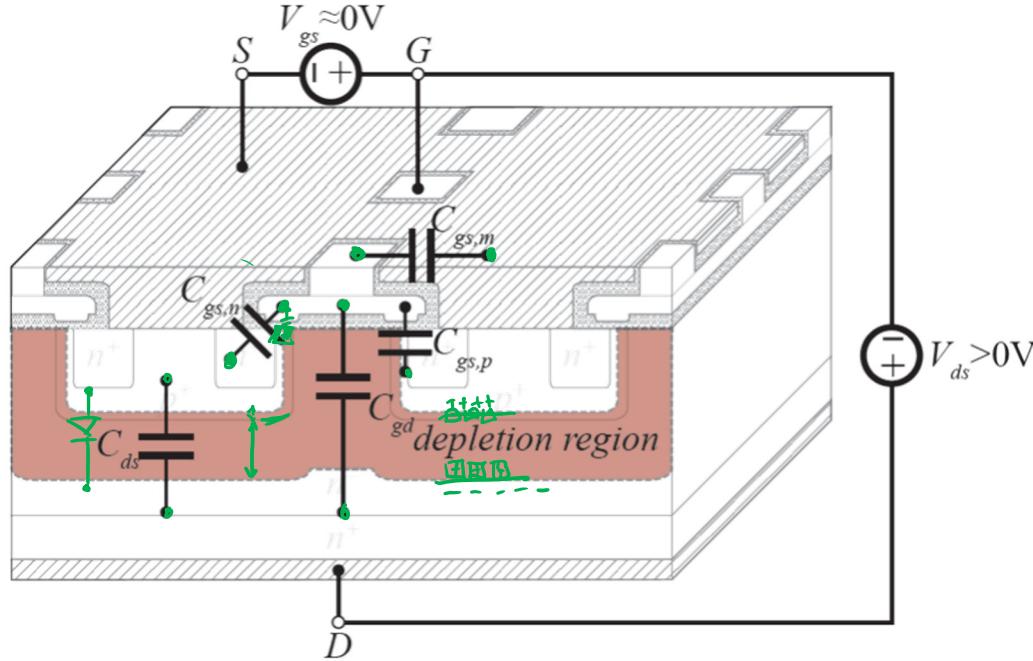

# Resistance Contributions Vs. Voltage


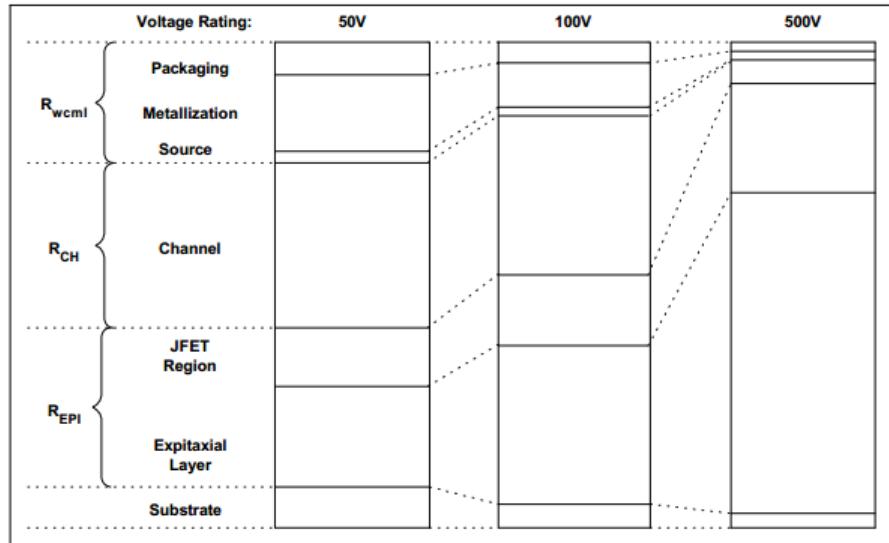


Figure 9. Relative Contributions to  $R_{DS(on)}$  With Different Voltage Ratings.



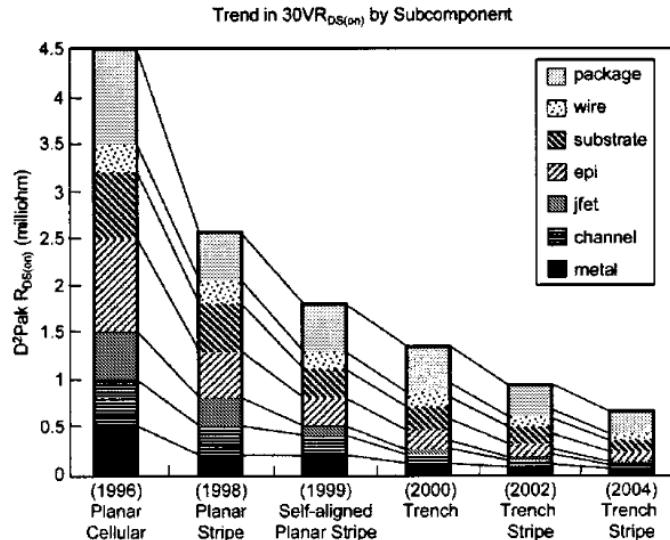


# Gate Charge

## 9 Typ. gate charge

$V_{GS} = f(Q_{gate})$ ;  $I_D = 5.2 \text{ A pulsed}$

parameter:  $V_{DD}$

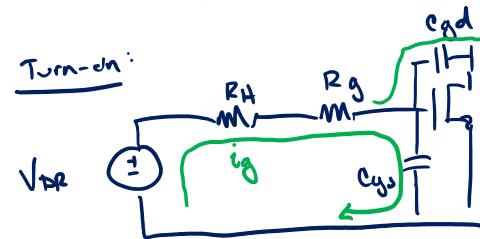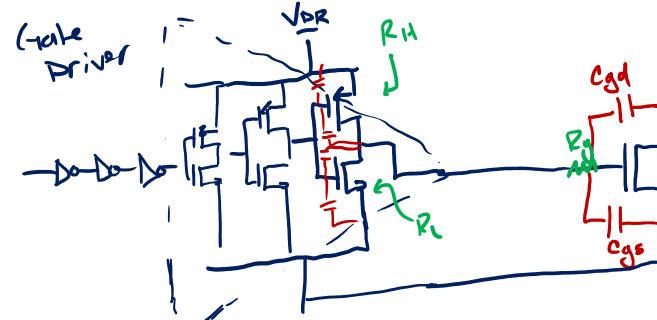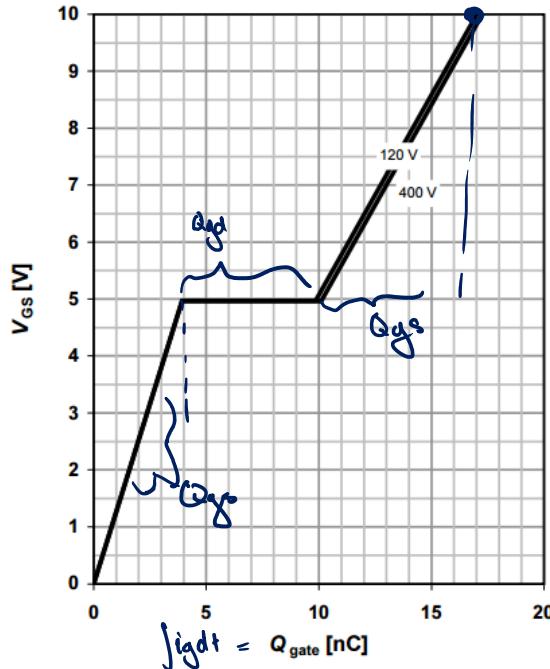

$$\begin{aligned} E_{\text{supplied}} &= \int V_{PR} i_g(t) dt \\ &= V_{PR} \int i_g(t) dt \\ &= V_{PR} Q_g \end{aligned}$$

some lost in  $R_H / R_g$   
some shared in  $C_{GS}$



all stored energy lost

$$P_g = V_{PR} Q_g f_s$$

(from  $V_{PR}$ )