



Overlap Time

9 Typ. gate charge




$V_{GS}=f(Q_{gate}); I_D=5.2\text{ A pulsed}$

parameter: V_{DD}



Gate threshold voltage	$V_{GS(th)}$	$V_{DS}=V_{GS}, I_D=0.34\text{ mA}$	2.5	3	3.5	
Gate resistance	R_G	$f=1\text{ MHz, open drain}$	-	1.8	-	Ω

  

FET Turn-On

   


Device Transconductance

  

Example Simulation

```
.ic V(g) = 0
```

```
.tran 0 50n 0 1p
```

 


```
I=IF(V(g)<10,1,0)
```




```
.model myD D(n=.01)
```

```
.model testFET VDMOS(Rg=.1 Rd=0 Rs=0 Vto=3 Kp=9 Cgdmax=0p  
+ Cgdmin=0p Cgs=0p Cjo=1.5f Is=26p Rb=0m Vds=600 Ron=385m Qg=0n)
```


Simulation Waveforms – Turn On

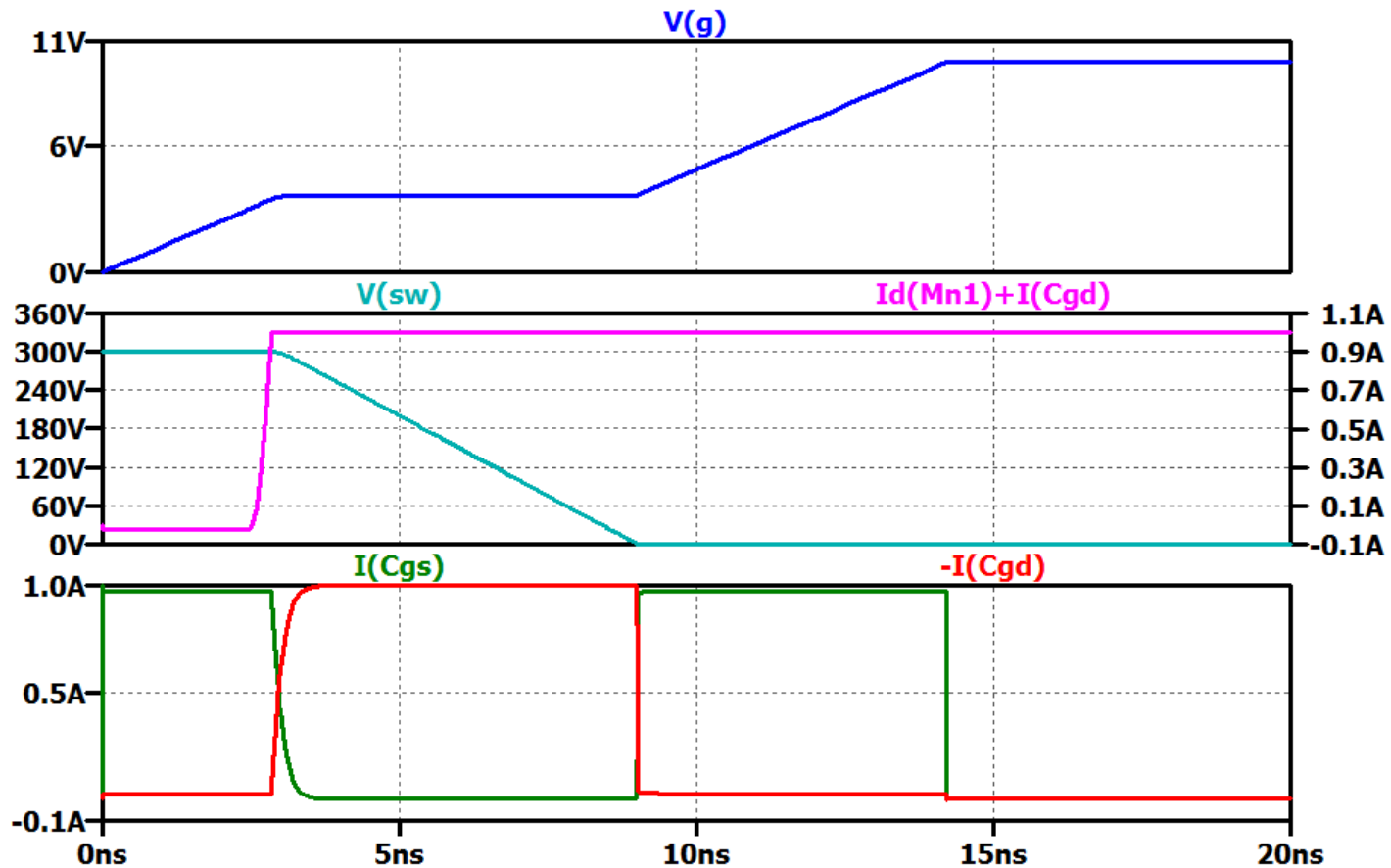


Turn-Off Transition

   

Turn-off

 


Turn-Off (Drain Dominated)

 

Gate- vs. Drain-Limited Switching

Simulation Results: C_{ds} Sweep

 

Limitations on Switching Speed

