
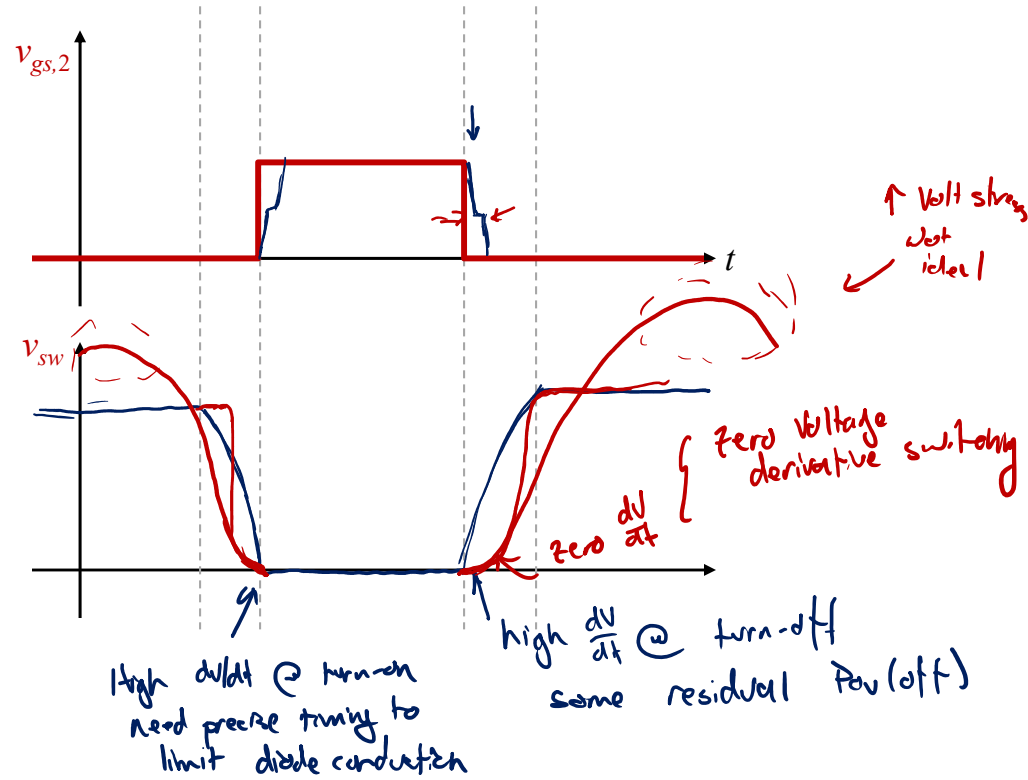



Ideal Switching Waveforms

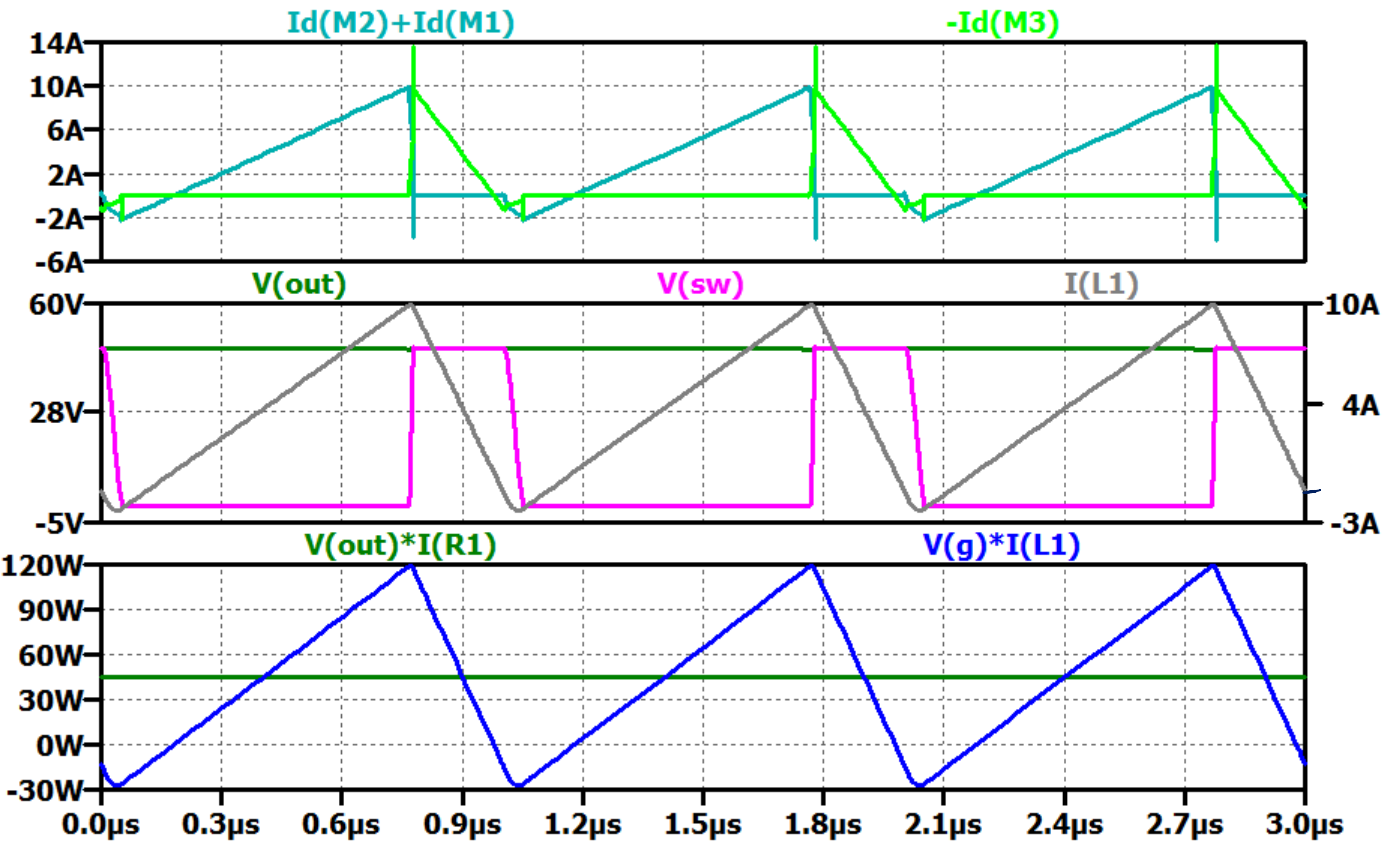

Synchronous Simulation (L3)



Synchronous Simulation (L3)

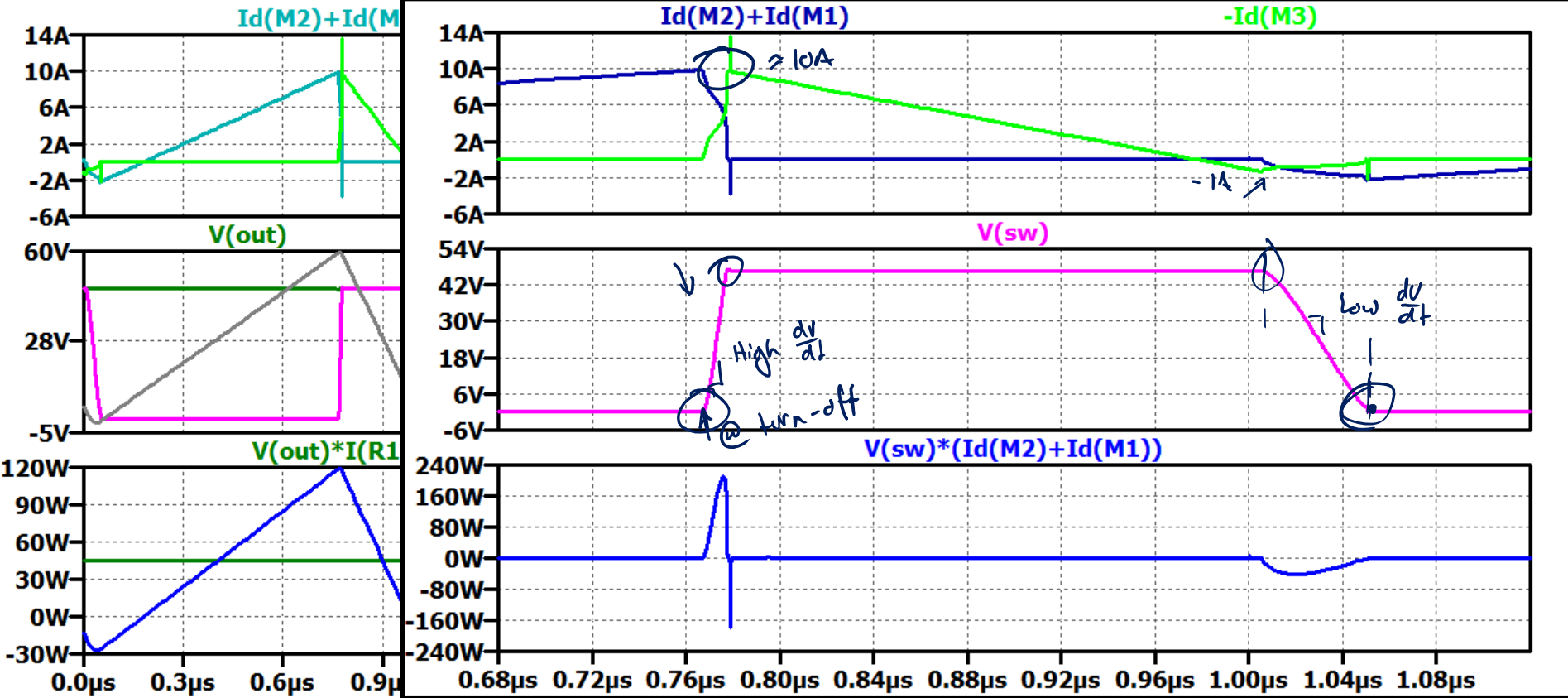

Capacitive switching loss


ANALYSIS OF NONLINEAR CAPACITANCES

Example Device $C_{oss} = C_{ds} + C_{gd} \approx C_{de}$

C_{oss} is a small-signal measurement

@ V_{DS}

$$i = C \left| \frac{dv}{dt} \right|_{v_{ds}=V_{DS}}$$

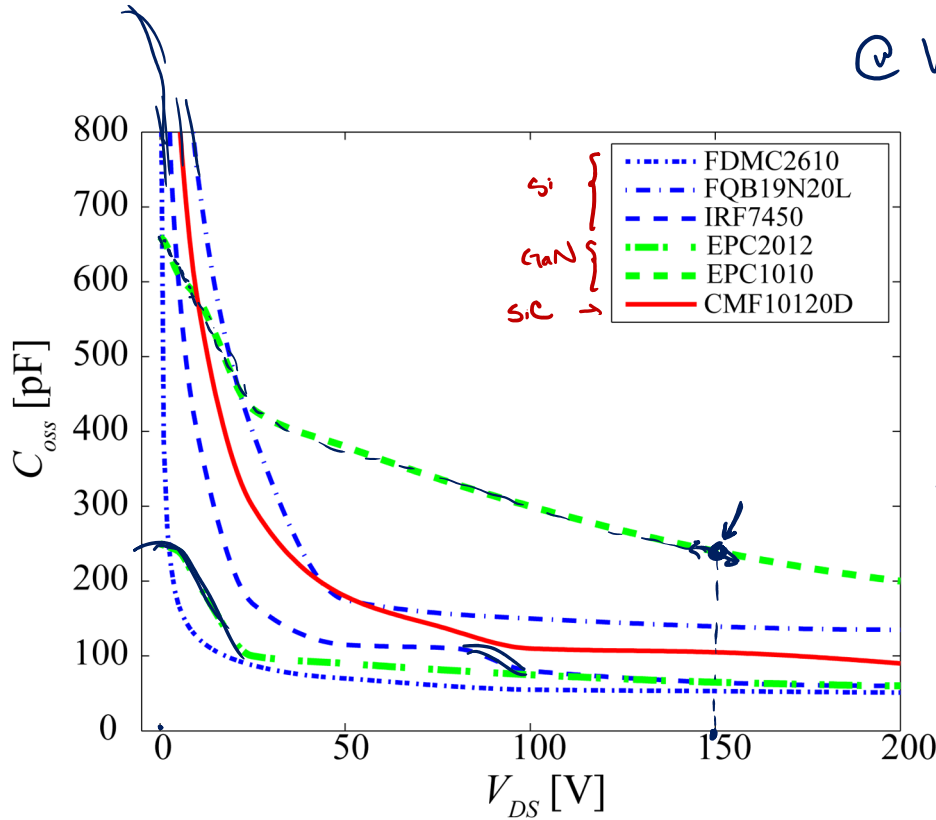

$$C_{tot} \neq C_{V_{DS}}$$

$$\Delta q = C \Delta V_{DS} \Big|_{V_{DS}}$$

Curve fit model:

$$C_{ds} = \frac{C_{j0}}{\left(1 + \frac{V_{DS}}{V_{j0}}\right)^m}$$

often $m = 1/2$

~ Empirical model


Datasheet Reported Capacitance



IPB60R385CP

13 Typ. capacitances

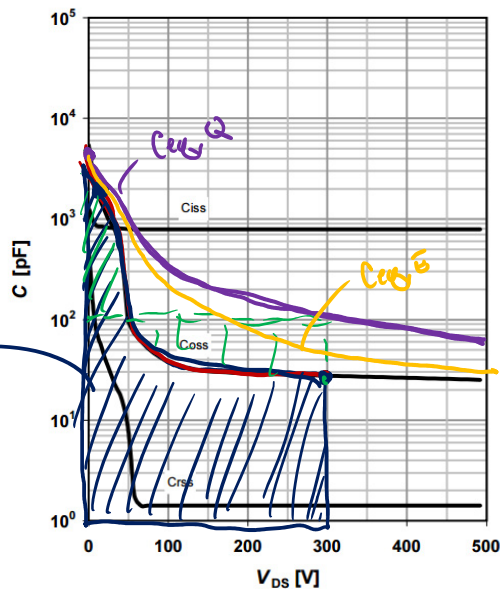
$C = f(V_{DS}); V_{GS} = 0 \text{ V}; f = 1 \text{ MHz}$



14 Typ. Coss stored energy

$E_{oss} = f(V_{DS})$

← less common for datasheets to include

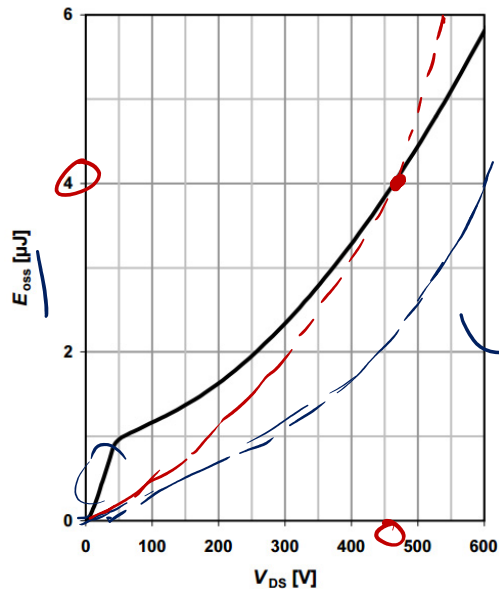

Modeling Nonlinear Capacitances



Linear

Charge @ V_{pc}

$$Q_c = \int_0^{t_f} i_c(t) dt$$

$$Q_c = \int_0^{t_f} C \frac{dv_c}{dt} dt$$

$$Q_c = \int_0^{V_{pc}} C dv_c$$

assume C constant

$$Q_c = C \int_0^{V_{pc}} (1) dv_c = \underline{\underline{C V_{pc}}}$$

$$Q_c = \int_0^{V_{pc}} C(v_c) dv_c$$

Nonlinear

cannot simplify further in nonlinear case

Energy @ V_{pc}

$$E_c = \int_0^{t_f} i_c \cdot v_c dt$$

$$E_c = \int_0^{t_f} C \frac{dv_c}{dt} v_c dt$$

$$E_c = \int_0^{V_{pc}} C v_c dv_c$$

$$E_c = C \int_0^{V_{pc}} v_c dv_c = C \frac{v_c^2}{2} \Big|_0^{V_{pc}} = \underline{\underline{\frac{1}{2} C V_{pc}^2}}$$

$$E_c = \int_0^{V_{pc}} C(v_c) v_c dv_c$$

Energy and Charge Equivalents

Linear equivalent capacitances can match a single characteristic of the full nonlinear characteristic

charge

$$Q_c = \int_0^{V_{DC}} C(v_c) dv_c = C_{eq,Q} V_{DC}$$

$$C_{eq,Q} = \frac{1}{V_{DC}} \int_0^{V_{DC}} C(v_c) dv_c$$

Linear capacitance that will have the same total charge stored at V_{DC} as the nonlinear cap

Interesting: $C_{eq,Q} = \langle C(v_c) \rangle_{V_{DC}}$
is the average capacitance on the curve


Energy

$$E_c = \int_0^{V_{DC}} C(v_c) v_c dv_c = \frac{1}{2} C_{eq,E} V_{DC}^2$$


$$C_{eq,E} = \frac{2}{V_{DC}^2} \int_0^{V_{DC}} C(v_c) v_c dv_c$$

Linear cap with same total energy at V_{DC} as nonlinear cap

C_{oss} Losses in a Half Bridge

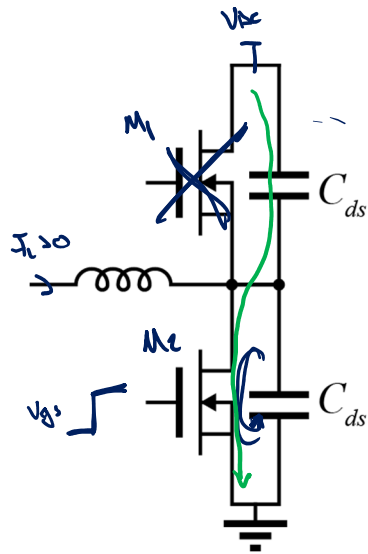


turn-on
equiv.
circuit
→

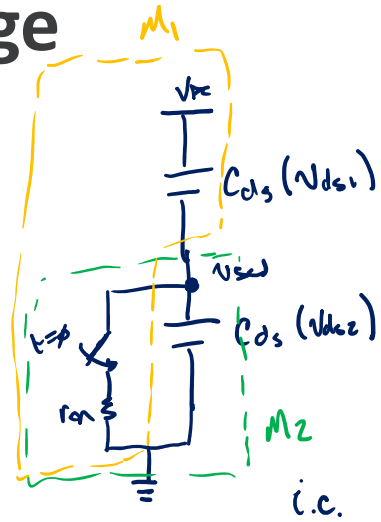

i.c. $v_{sw}(t=0) = V_{dc}$

M₂ Energy Loss

i.c. $v_c(t=0) = V_{DC}$

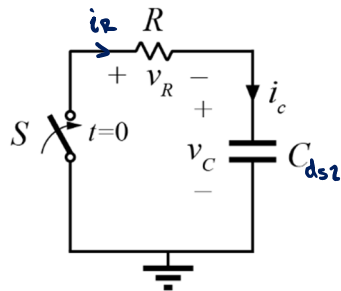

$$E_R = \int_0^{\infty} v_R \cdot i_R dt$$

$$E_R = \int_0^{\infty} (-v_{sw}) C_{ds2}(v_{sw}) \frac{dv_{sw}}{dt} dt$$

$$E_R = \int_{-V_{DC}}^0 (-v_{sw}) C_{ds2}(v_{sw}) dv_{sw} = \int_0^{V_{DC}} v_{sw} C_{ds2}(v_{sw}) dv_{sw}$$

$$E_R = E_C = \int_0^{V_{DC}} v_c C(v_c) dv_c$$

$$v_R = -v_{sw}$$

$$i_R = i_C = C_{ds2}(v_c) \frac{dv_c}{dt}$$

$$v_c = v_{sw}$$

$$C = C_{ds2}$$

By insight:

$$E_R = E_C = \frac{1}{2} C_{ds2} V_{DC}^2$$