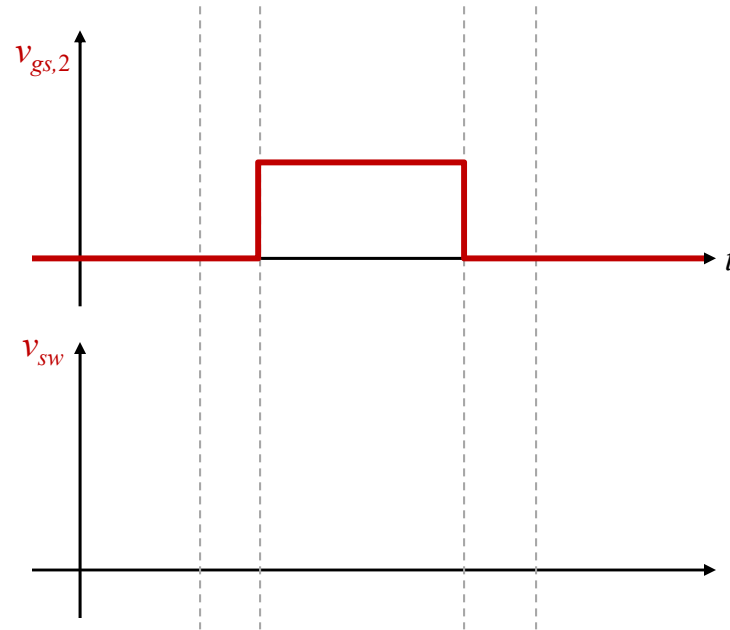



Ideal Switching Waveforms



Capacitive switching loss

ANALYSIS OF NONLINEAR CAPACITANCES

Example Device C_{oss}

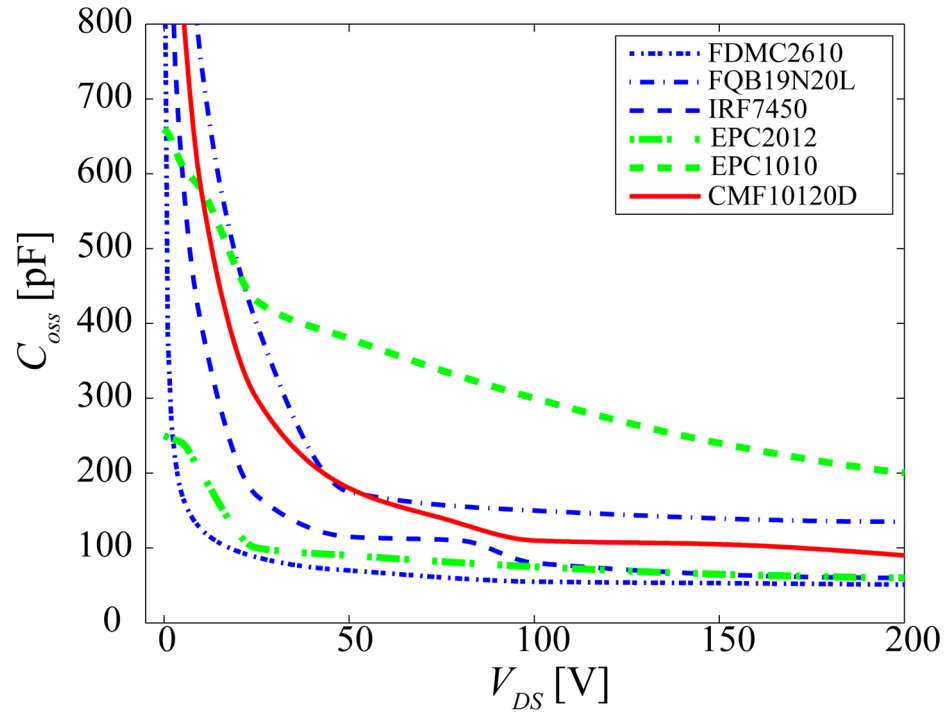


Datasheet Reported Capacitance



IPB60R385CP


13 Typ. capacitances

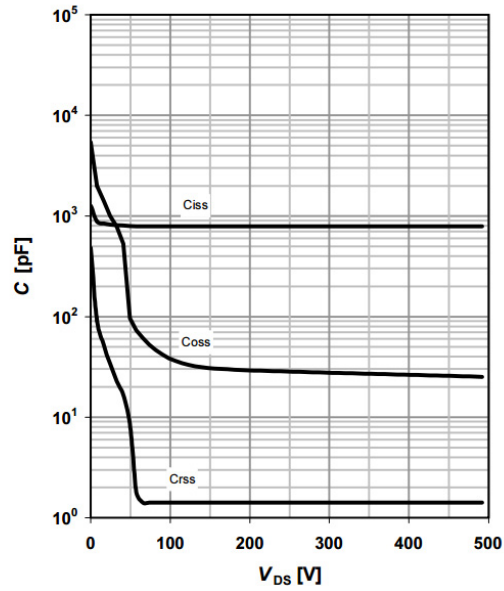$C=f(V_{DS}); V_{GS}=0\text{ V}; f=1\text{ MHz}$



14 Typ. C_{oss} stored energy


$E_{oss}=f(V_{DS})$

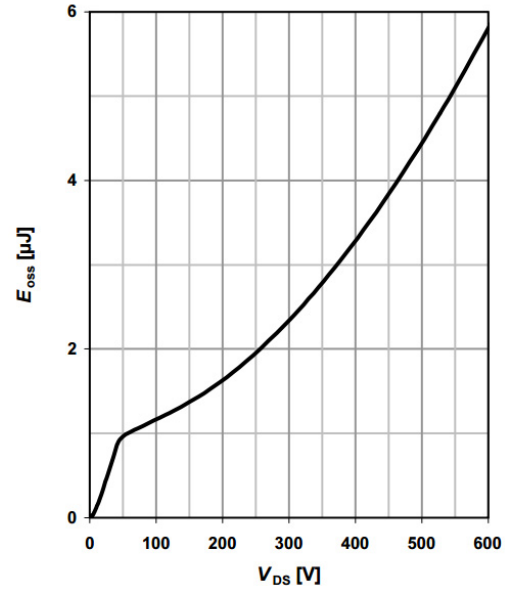


Modeling Nonlinear Capacitances

Energy and Charge Equivalents


C_{oss} Losses in a Half Bridge

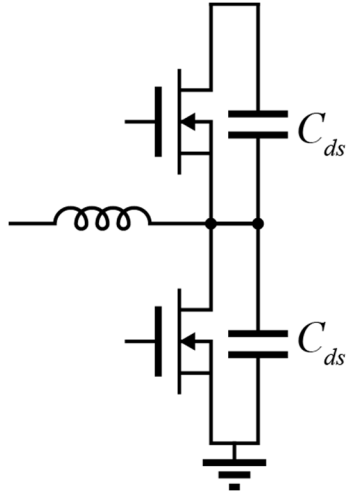

M_2 Energy Loss


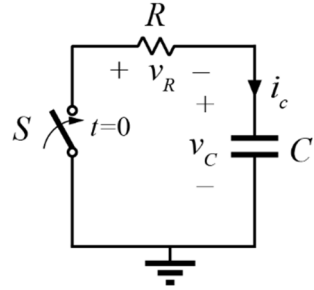


M_1 Energy Loss

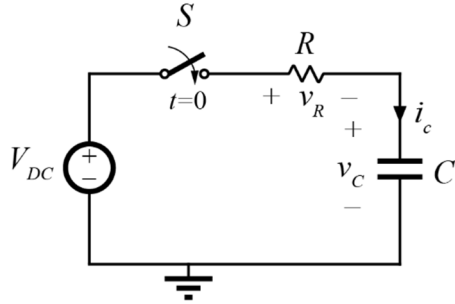

Total Half Bridge C_{oss} Loss

Energy Equivalent

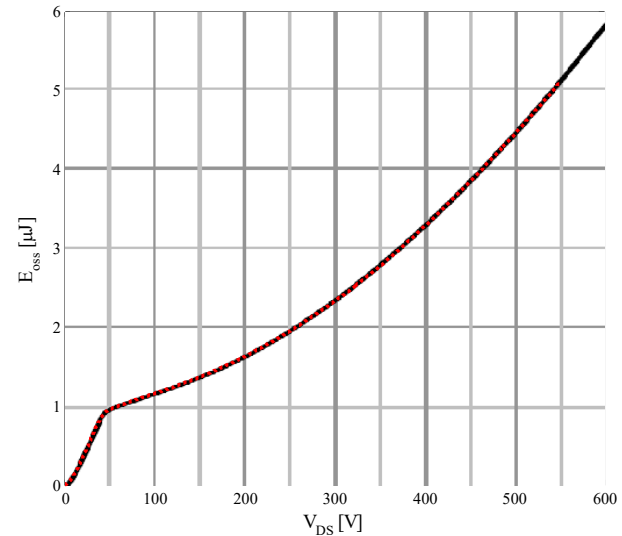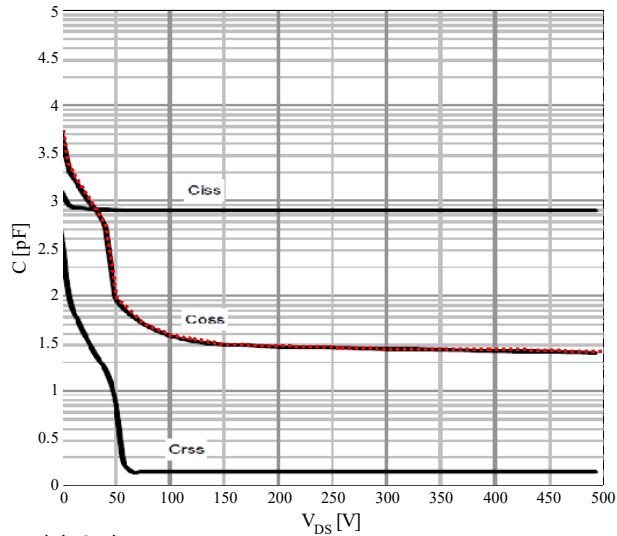

Matlab Code:

```
Vdc = 550;
```

```
Vds = [0 5 10 40 50 75 100 150 200 300 400 500 600];
```

```
Coss = [5500 2500 1900 550 95 50 38 30 29 27 27 25 24]*1e-12;
```

```
vx = 0.01:.01:Vdc;
```

```
Cx = 10.^interp1(Vdc,log10(Coss),vx,'linear');
```

```
E = cumtrapz(vx, Cx.*vx);
```

```
Ceq_e = 2*(E)./vx.^2;
```