

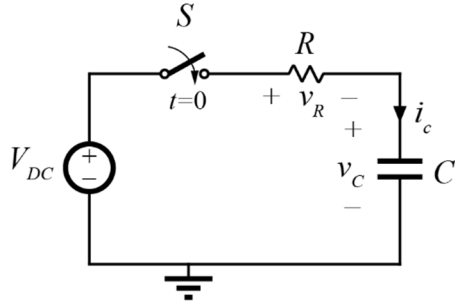


M_1 Energy Loss

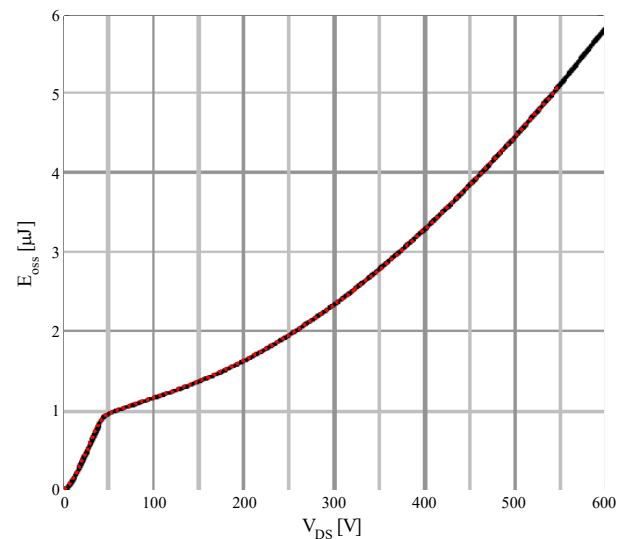

Total Half Bridge C_{oss} Loss

Energy Equivalent

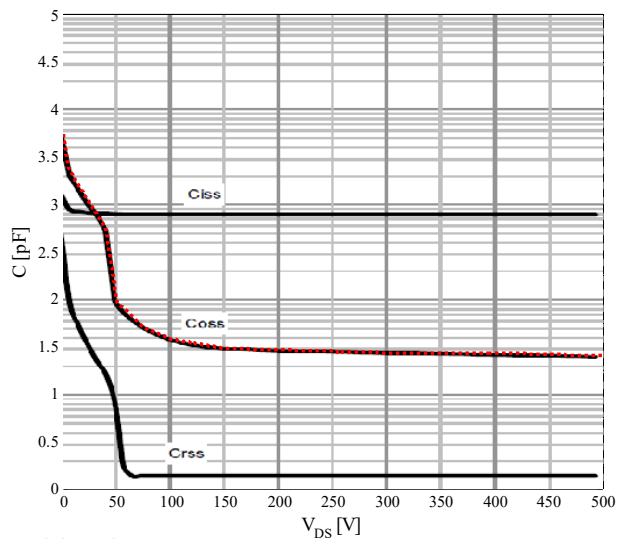

Matlab Code:

```
Vdc = 550;
```

```
Vds = [0 5 10 40 50 75 100 150 200 300 400 500 600];  
Coss = [5500 2500 1900 550 95 50 38 30 29 27 27 25 24]*1e-12;
```

```
vx = 0.01:.01:Vdc;  
Cx = 10.^interp1(Vdc,log10(Coss),vx,'linear');
```

```
E = cumtrapz(vx, Cx.*vx);  
Ceq_e = 2*(E)./vx.^2;
```

Nonlinear Capacitance Extraction

- <http://web.eecs.utk.edu/~dcostine/personal/PowerDeviceLib/DigiTest/index.html>

Datasheet Reported Capacitance


Dynamic characteristics

Input capacitance	C_{iss}	$V_{GS}=0\text{ V}, V_{DS}=100\text{ V},$ $f=1\text{ MHz}$	-	790	-	pF
Output capacitance	C_{oss}		-	38	-	
Effective output capacitance, energy related ⁶⁾	$C_{o(er)}$	$V_{GS}=0\text{ V}, V_{DS}=0\text{ V}$ to 480 V	-	36	-	
Effective output capacitance, time related ⁷⁾	$C_{o(tr)}$		-	96	-	
Turn-on delay time	$t_{d(on)}$	$V_{DD}=400\text{ V},$ $V_{GS}=10\text{ V}, I_D=5.2\text{ A},$ $R_G=3.3\ \Omega$	-	10	-	ns
Rise time	t_r		-	5	-	
Turn-off delay time	$t_{d(off)}$		-	40	-	
Fall time	t_f		-	5	-	

⁶⁾ $C_{o(er)}$ is a fixed capacitance that gives the same stored energy as C_{oss} while V_{DS} is rising from 0 to 80% V_{DSS} .

⁷⁾ $C_{o(tr)}$ is a fixed capacitance that gives the same charging time as C_{oss} while V_{DS} is rising from 0 to 80% V_{DSS} .

Example Simulation

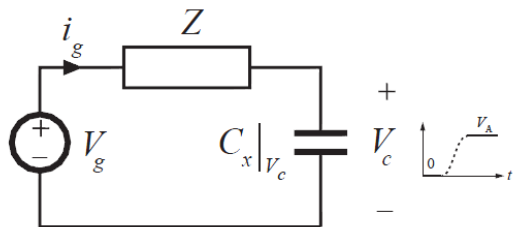


$$C_{eq,Q} = 70.5 \text{ pF},$$




$$C_{eq,E} = 56.4 \text{ pF},$$

$$C_{eq,tzvs} = 64.1 \text{ pF}$$

$$C_{eq,Z} = 84.5 \text{ pF}.$$

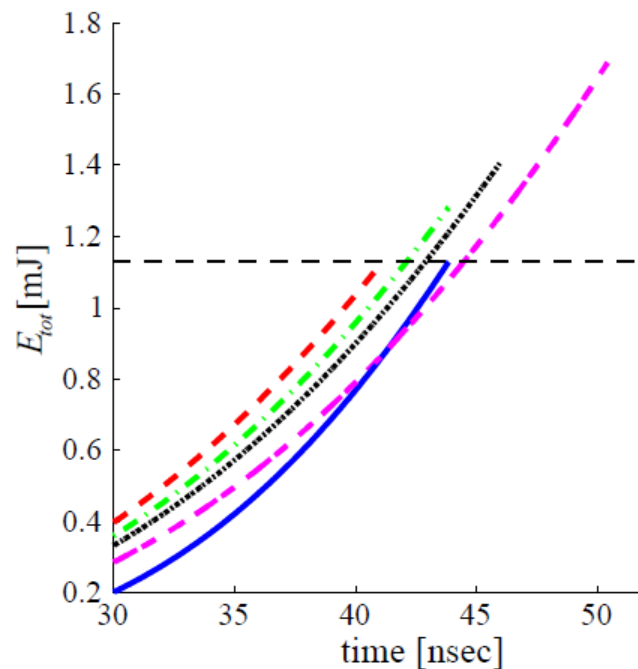



Further Simulation

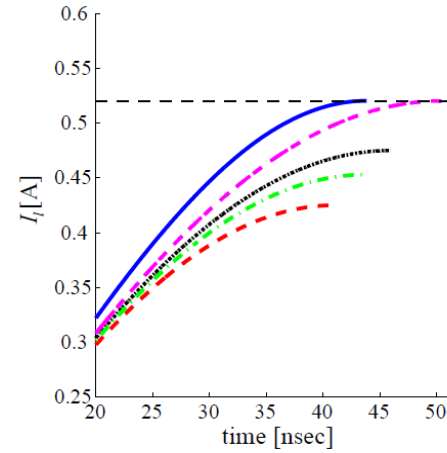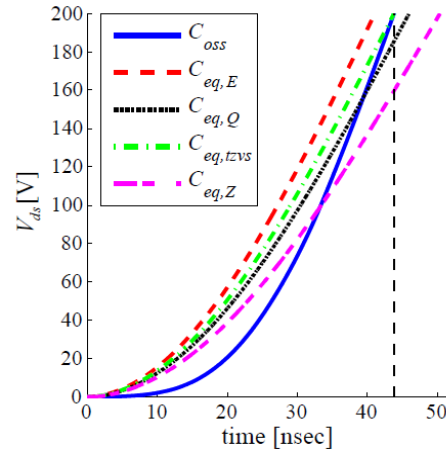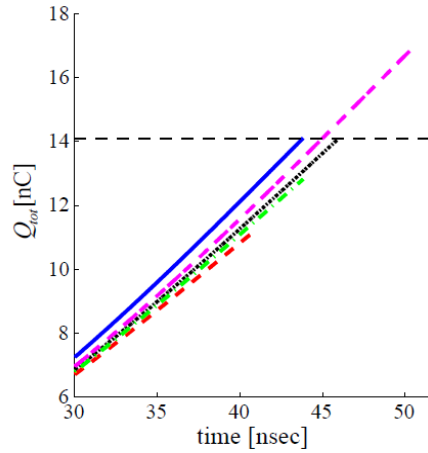


Solving resonance in power electronics

STATE PLANE ANALYSIS


Motivation

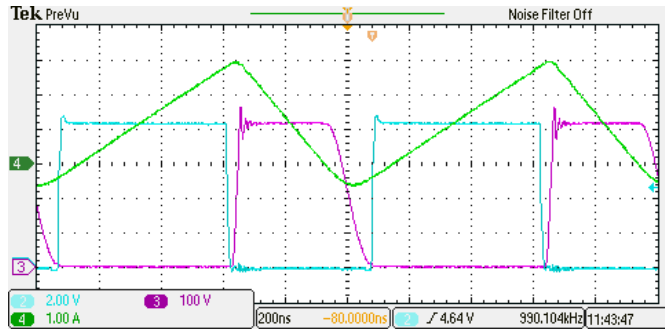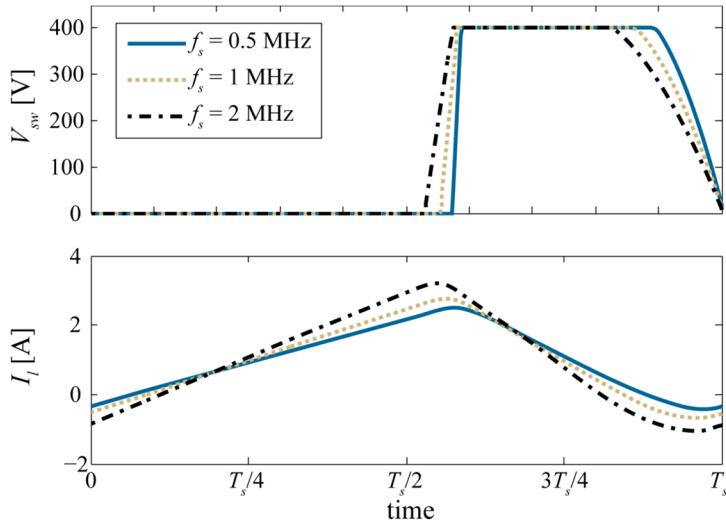

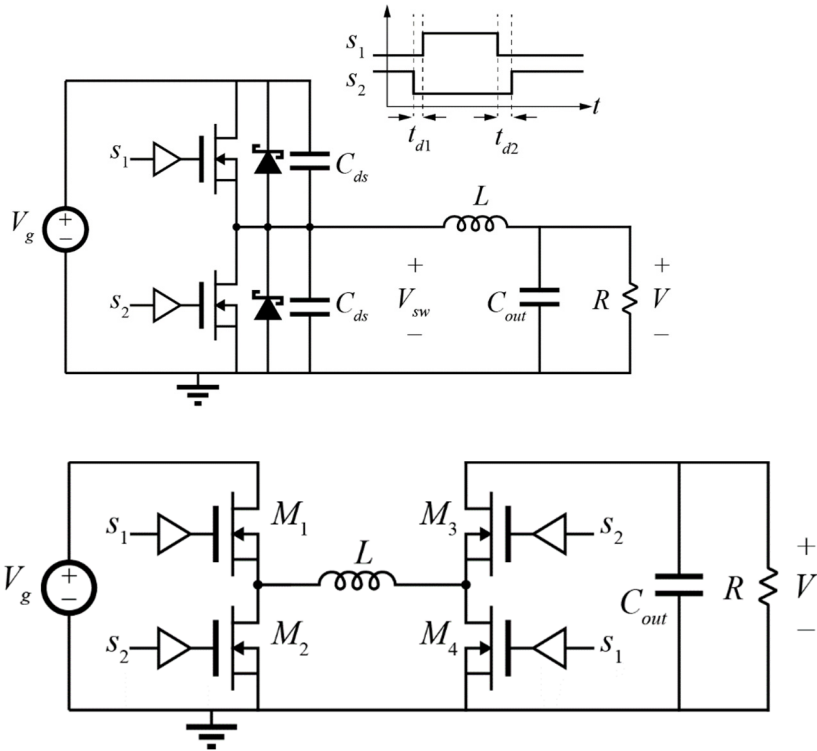Time-Domain Analysis of Switching Transitions



Resonant Circuit Solution

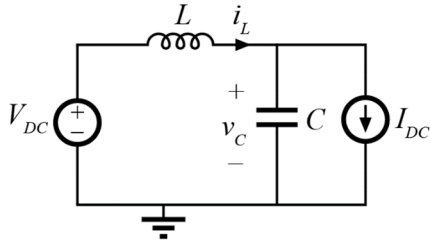

$$v_c(t) = V_{DC} + (V_0 - V_{DC}) \cos\left(\frac{t}{\sqrt{LC}}\right) + (I_0 - I_{DC}) \sqrt{\frac{L}{C}} \sin\left(\frac{t}{\sqrt{LC}}\right)$$

$$i_L(t) = I_{DC} + (I_0 - I_{DC}) \cos\left(\frac{t}{\sqrt{LC}}\right) + (V_{DC} - V_0) \sqrt{\frac{C}{L}} \sin\left(\frac{t}{\sqrt{LC}}\right)$$

Normalization and Notation

$$v_c(t) = V_{DC} + (V_0 - V_{DC}) \cos(\omega_0 t) + R_0(I_0 - I_{DC}) \sin(\omega_0 t)$$

$$i_L(t) = I_{DC} + (I_0 - I_{DC}) \cos(\omega_0 t) + \frac{1}{R_0} (V_{DC} - V_0) \sin(\omega_0 t)$$

$$v_c(t) = V_{DC} + (V_0 - V_{DC}) \cos(\omega_0 t) + R_0(I_0 - I_{DC}) \sin(\omega_0 t)$$

$$i_L(t) = I_{DC} + (I_0 - I_{DC}) \cos(\omega_0 t) + \frac{1}{R_0} (V_{DC} - V_0) \sin(\omega_0 t)$$

