

Design of a Series Resonant Converter

The SRC of Fig. 1 is designed with the following parameters. Note that $V_{out} \neq nV_g$.

- $L_l = 30\mu\text{H}$
- $C_r = 5\text{ nF}$
- $V_g = 100\text{ V}$
- $V_{out} = 150\text{ V}$
- $n = 1$
- $F = 1.1$

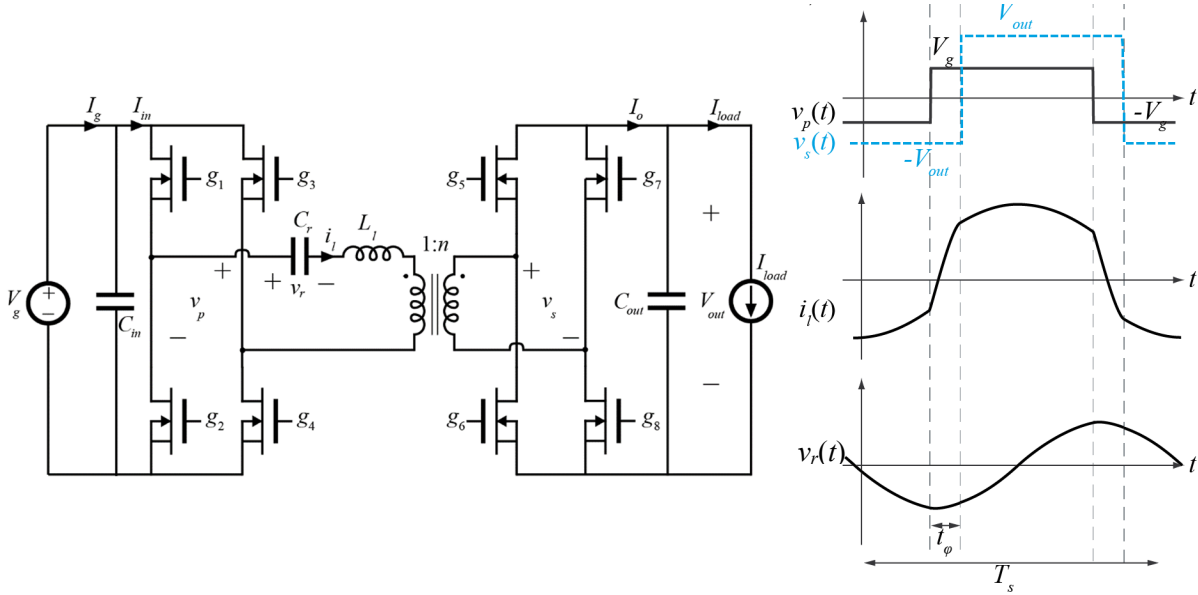


Fig. 1: Series resonant converter

At an operating point of $P_{out} = 750\text{ W}$, solve the following. Select an operating point with minimal peak currents, if multiple solutions exist for the given parameters.

- Derive a complete set of state plane equations for the SRC at this operating point.
- Sketch the m_r - j_l state plane over one complete period. Label all salient features over one half-period
- Solve the state plane Give values for f_s and t_ϕ
- Sketch the time-domain waveforms for $i_l(t)$ and $v_r(t)$. Label peak values, as well as the values at each switching instant.