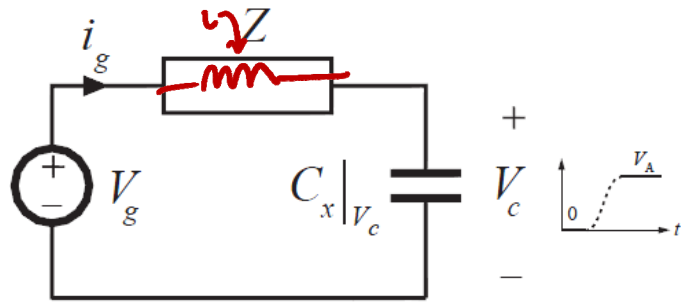


Example Simulation



$$C_{eq,Q} = 70.5 \text{ pF},$$


≈ middle

$$C_{eq,tzvs} = 64.1 \text{ pF}$$




$$C_{eq,E} = 56.4 \text{ pF},$$

smallest

$$C_{eq,Z} = 84.5 \text{ pF}.$$

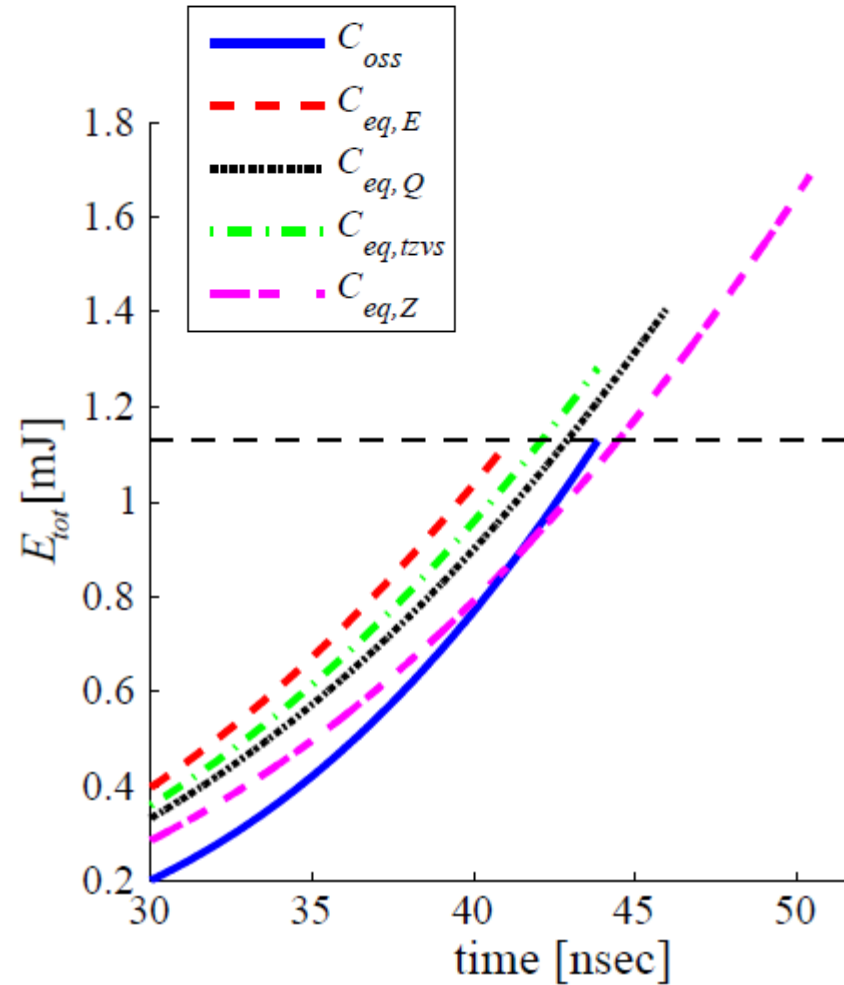


Further Simulation

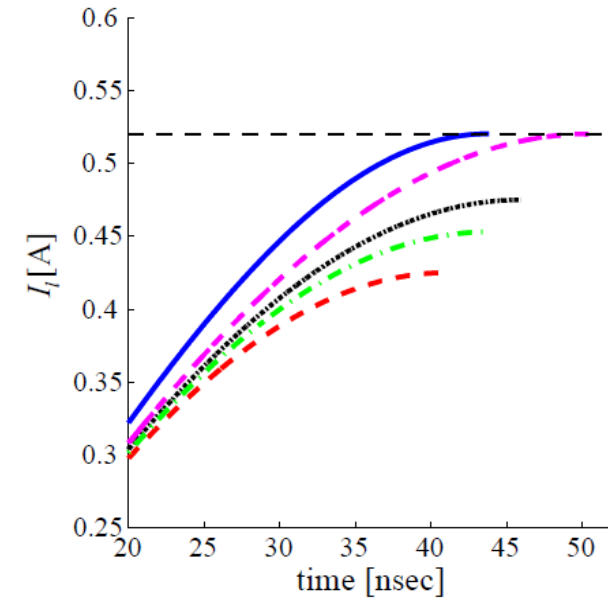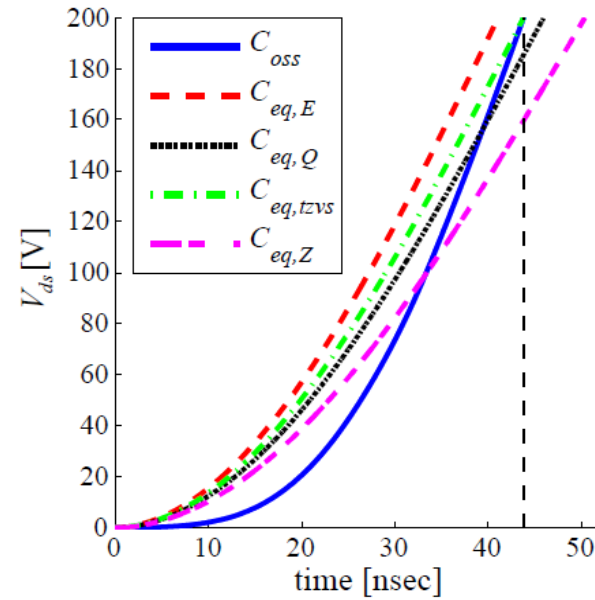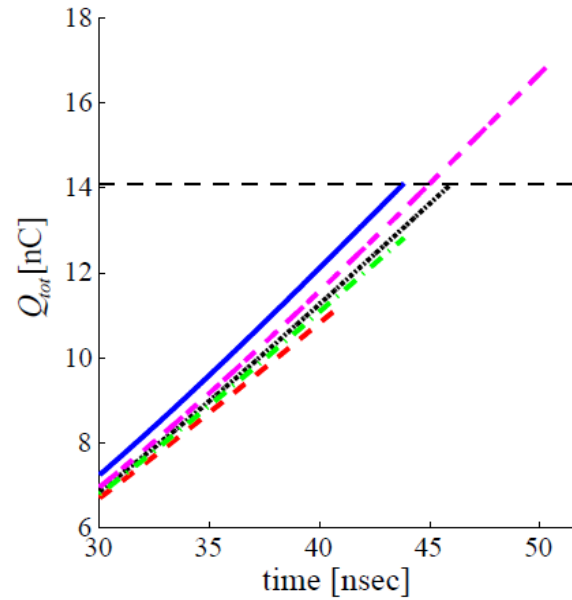


Nonlinear Cap Simulation Implementations
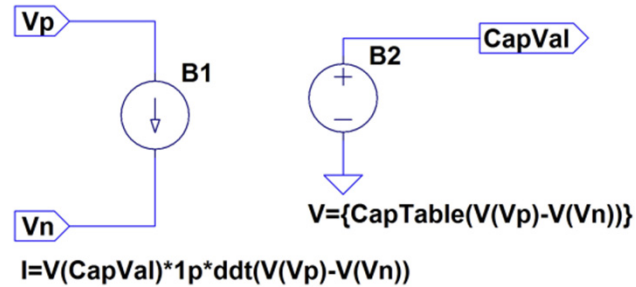
```
.func CapTable(x)= {table(x,0,850, 2.51 , 716.572, ...)}
```






(a)

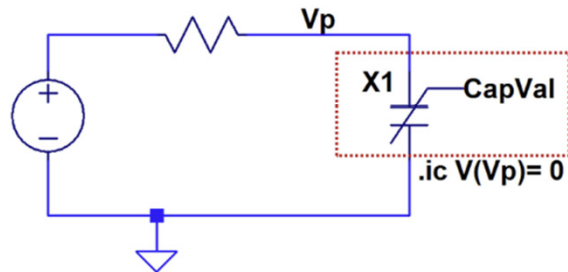


(b)

Capacitance Model: Ideal Linear tanh

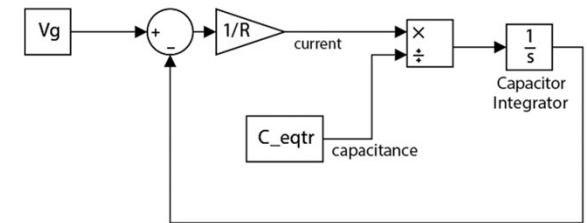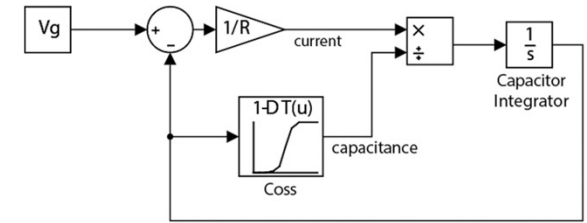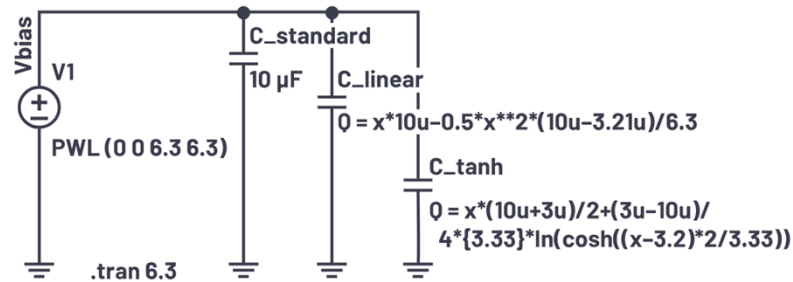

(a)


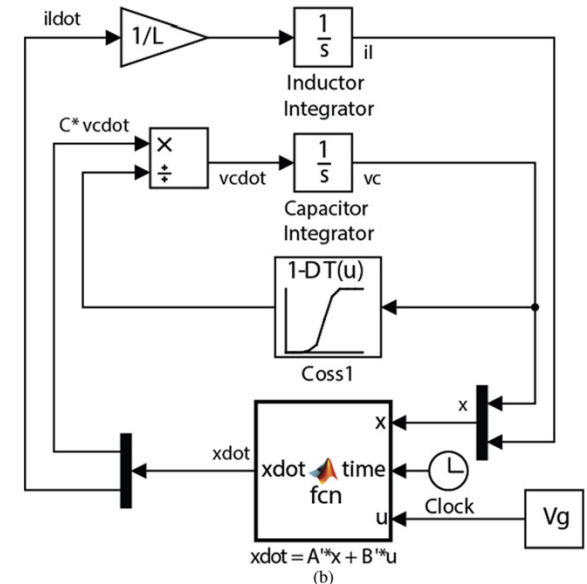


(b)

Solving resonance in power electronics



STATE PLANE ANALYSIS

Motivation

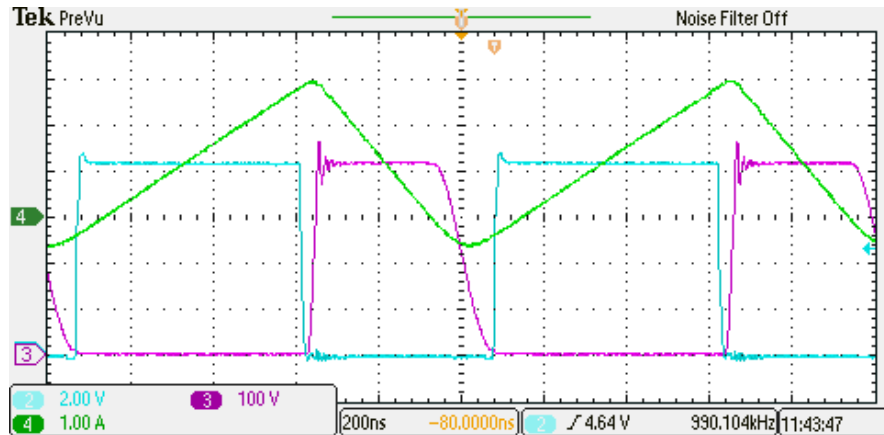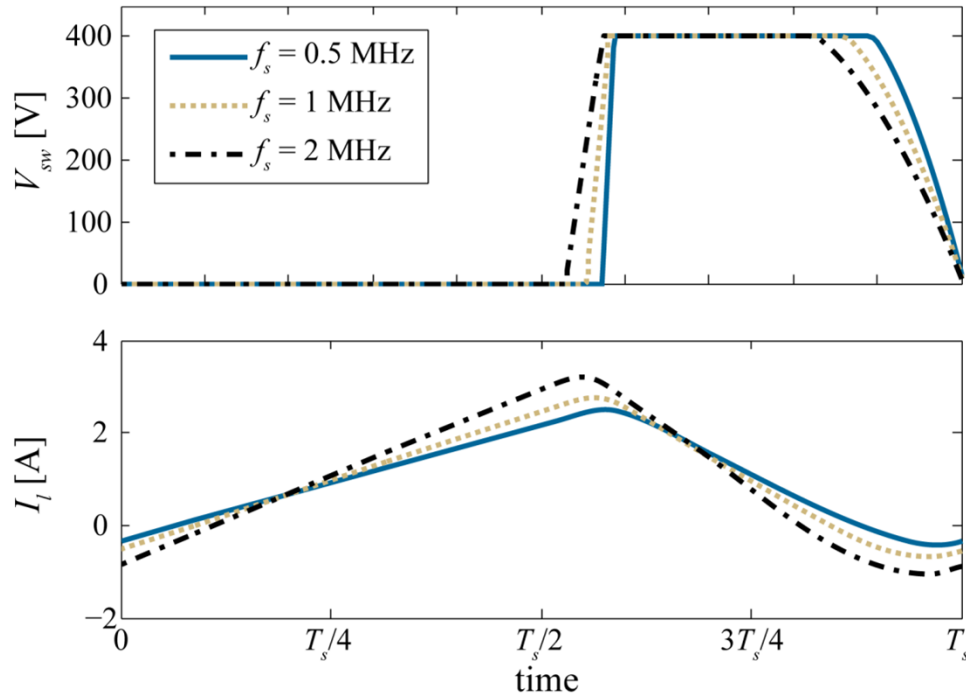


Time-Domain Analysis of Switching Transitions

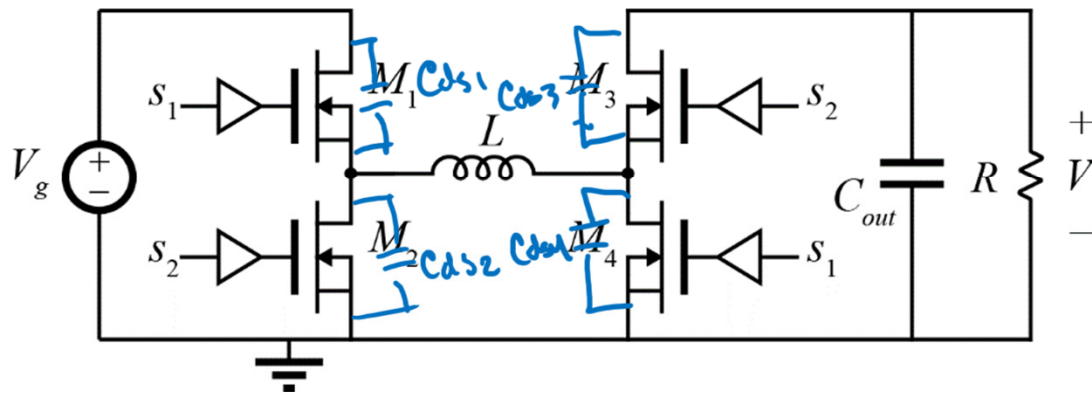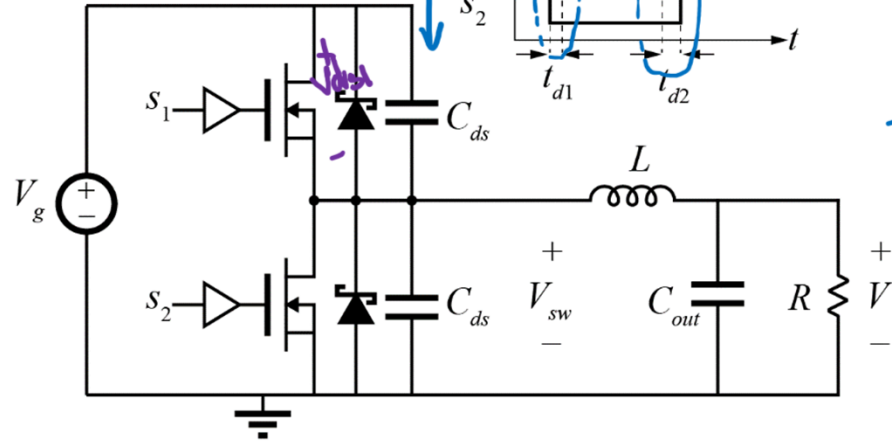
C_{ds} is approximated as linear
dead time ZVS dynamics



During t_{off}

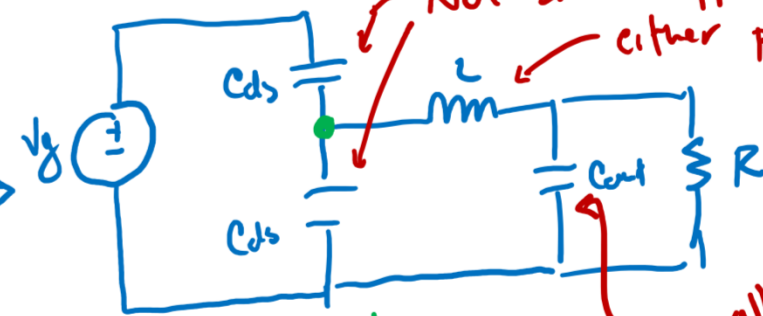


ac equivalent

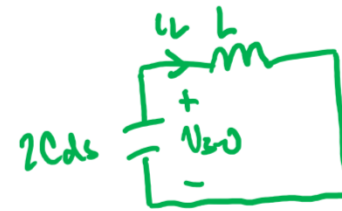


Not small-ripple
either possible
assume large resonant
behaviors matter
small ripple probably applies

During t_{off}

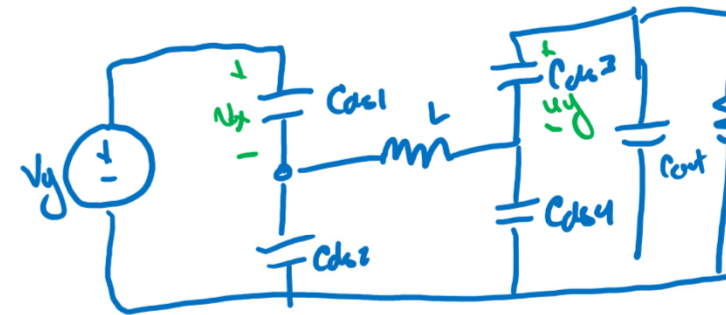


ac eqn

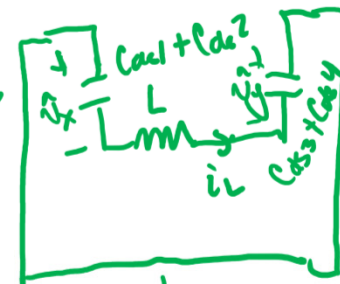

State plane: 1L & 1C & any DC sources

Resonant Circuit Solution

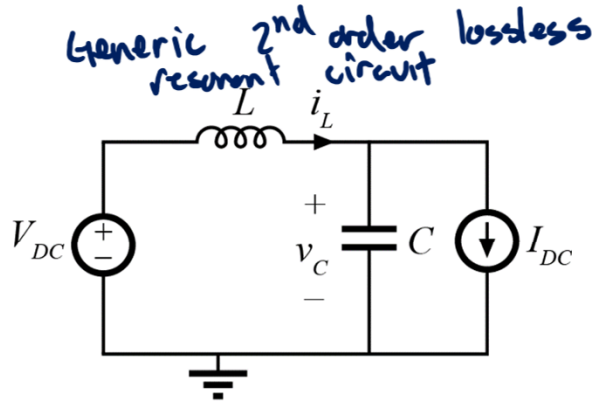

Initial conditions
@ $t=0$
 $v_C(t=0) = V_0$
 $i_L(t=0) = I_0$

$$\left. \begin{array}{l} \textcircled{1} \quad C \frac{dv_C}{dt} = i_L(t) - I_{DC} \\ \textcircled{2} \quad L \frac{di_L}{dt} = V_{DC} - v_C(t) \end{array} \right\} \begin{array}{l} V_{DC} - v_C(t) = L \frac{d}{dt} \left(C \frac{dv_C}{dt} + I_{DC} \right) \\ LC \frac{d^2 v_C}{dt^2} + v_C(t) - V_{DC} = 0 \end{array}$$

$$\begin{cases} v_{C,h}(t) = A \cos(\omega t) + B \sin(\omega t) \\ v_{C,p}(t) = V_{DC} \end{cases}$$

$$LCs^2 + 1 = 0$$

$$s = \pm j \frac{1}{\sqrt{LC}}$$

$$v_{C,h}(t) = C e^{j \frac{1}{\sqrt{LC}} t} + D e^{-j \frac{1}{\sqrt{LC}} t}$$

$$v_C(t) = V_{DC} + (V_0 - V_{DC}) \cos\left(\frac{t}{\sqrt{LC}}\right) + (I_0 - I_{DC}) \sqrt{\frac{L}{C}} \sin\left(\frac{t}{\sqrt{LC}}\right)$$

$$i_L(t) = I_{DC} + (I_0 - I_{DC}) \cos\left(\frac{t}{\sqrt{LC}}\right) + (V_{DC} - V_0) \sqrt{\frac{C}{L}} \sin\left(\frac{t}{\sqrt{LC}}\right)$$

Normalization and Notation

Notation: $2\pi f_0 = \omega_0 = \frac{1}{T_{LC}}$ $R_0 = \sqrt{\frac{L}{C}}$

$$v_c(t) = V_{DC} + (V_0 - V_{DC}) \cos(\omega_0 t) + R_0(I_0 - I_{DC}) \sin(\omega_0 t)$$

$$i_L(t) = I_{DC} + (I_0 - I_{DC}) \cos(\omega_0 t) + \frac{1}{R_0} (V_{DC} - V_0) \sin(\omega_0 t)$$

Normalization:

$$m_c(t) = \frac{v_c(t)}{V_{base}}$$

$$j_L(t) = \frac{i_L(t)}{I_{base}}$$

$$\theta_x = \omega_0 t_x$$

V_{base} is anything you want

$$I_{base} \equiv \frac{V_{base}}{R_0}$$

$$V_{base} = V_{DC}$$

$$I_{base} = \frac{V_{DC}}{R_0}$$

$$\begin{cases} v_c(t) = V_{DC} + (V_0 - V_{DC}) \cos(\omega_0 t) + R_0(I_0 - I_{DC}) \sin(\omega_0 t) \\ i_L(t) = I_{DC} + (I_0 - I_{DC}) \cos(\omega_0 t) + \frac{1}{R_0}(V_{DC} - V_0) \sin(\omega_0 t) \end{cases}$$

$$\frac{R_0}{V_{base}} (I_0 - I_{DC}) = \frac{I_0 - I_{DC}}{I_{base}}$$

$$\begin{cases} m_c(t) = \frac{v_c(t)}{V_{base}} = m_{DC} + (m_0 - m_{DC}) \cos(\theta) + \underbrace{(j_0 - j_{DC})}_{\text{green}} \sin(\theta) \\ j_c(t) = \frac{i_L(t)}{I_{base}} = j_{DC} + (j_0 - j_{DC}) \cos(\theta) + (m_{DC} - m_0) \sin(\theta) \end{cases}$$