

$$V_{base} = V_{DC}$$

$$I_{base} = \frac{V_{DC}}{R_0}$$

$$\begin{cases} v_c(t) = V_{DC} + (V_0 - V_{DC}) \cos(\omega_0 t) + R_0(I_0 - I_{DC}) \sin(\omega_0 t) \\ i_L(t) = I_{DC} + (I_0 - I_{DC}) \cos(\omega_0 t) + \frac{1}{R_0}(V_{DC} - V_0) \sin(\omega_0 t) \end{cases}$$

$$\frac{R_0}{V_{base}} (I_0 - I_{DC}) = \frac{I_0 - I_{DC}}{I_{base}}$$

$$\begin{cases} m_c(t) = \frac{v_c(t)}{V_{base}} = M_{DC} + \underbrace{(M_0 - M_{DC})}_{A} \cos(\theta) + \underbrace{(I_0 - I_{DC})}_{B} \sin(\theta) \\ j_L(t) = \frac{i_L(t)}{I_{base}} = I_{DC} + \underbrace{(I_0 - I_{DC})}_{B} \cos(\theta) + \underbrace{(M_{DC} - M_0)}_{-A} \sin(\theta) \end{cases}$$

$$A = M_0 - M_{DC}$$

$$B = I_0 - I_{DC}$$

$$\begin{cases} m_c(t) = M_{DC} + A \cos \theta + B \sin \theta \\ j_L(t) = I_{DC} + B \cos \theta + (-A) \sin \theta \end{cases}$$

Try looking at $(m_c(t) - M_{DC})^2 + (j_L(t) - I_{DC})^2 =$

$$\left(A^2 \cos^2 \theta + B^2 \sin^2 \theta + 2AB \cos \theta \sin \theta \right) + \left(B^2 \cos^2 \theta + A^2 \sin^2 \theta - 2AB \cos \theta \sin \theta \right)$$

$$= A^2 (\cos^2 \theta + \sin^2 \theta) + B^2 (\sin^2 \theta + \cos^2 \theta)$$

$$(m_c(t) - M_{DC})^2 + (j_L(t) - I_{DC})^2 = A^2 + B^2 = (M_0 - M_{DC})^2 + (I_0 - I_{DC})^2$$

Normalized Trajectory

$$(m_c(t) - m_{DC})^2 + (j_c(t) - j_{DC})^2 = (m_0 - m_{DC})^2 + (j_0 - j_{DC})^2$$

this is the equation for a circle in the $m_c - j_c$ plane

$$(x - x_0)^2 + (y - y_0)^2 = r^2$$


here

$$r = \sqrt{(m_0 - m_{DC})^2 + (j_0 - j_{DC})^2}$$


- DC op point defines center
- IC defines initial point & radius
- IC on 1st derivatives defines direction

State plane:

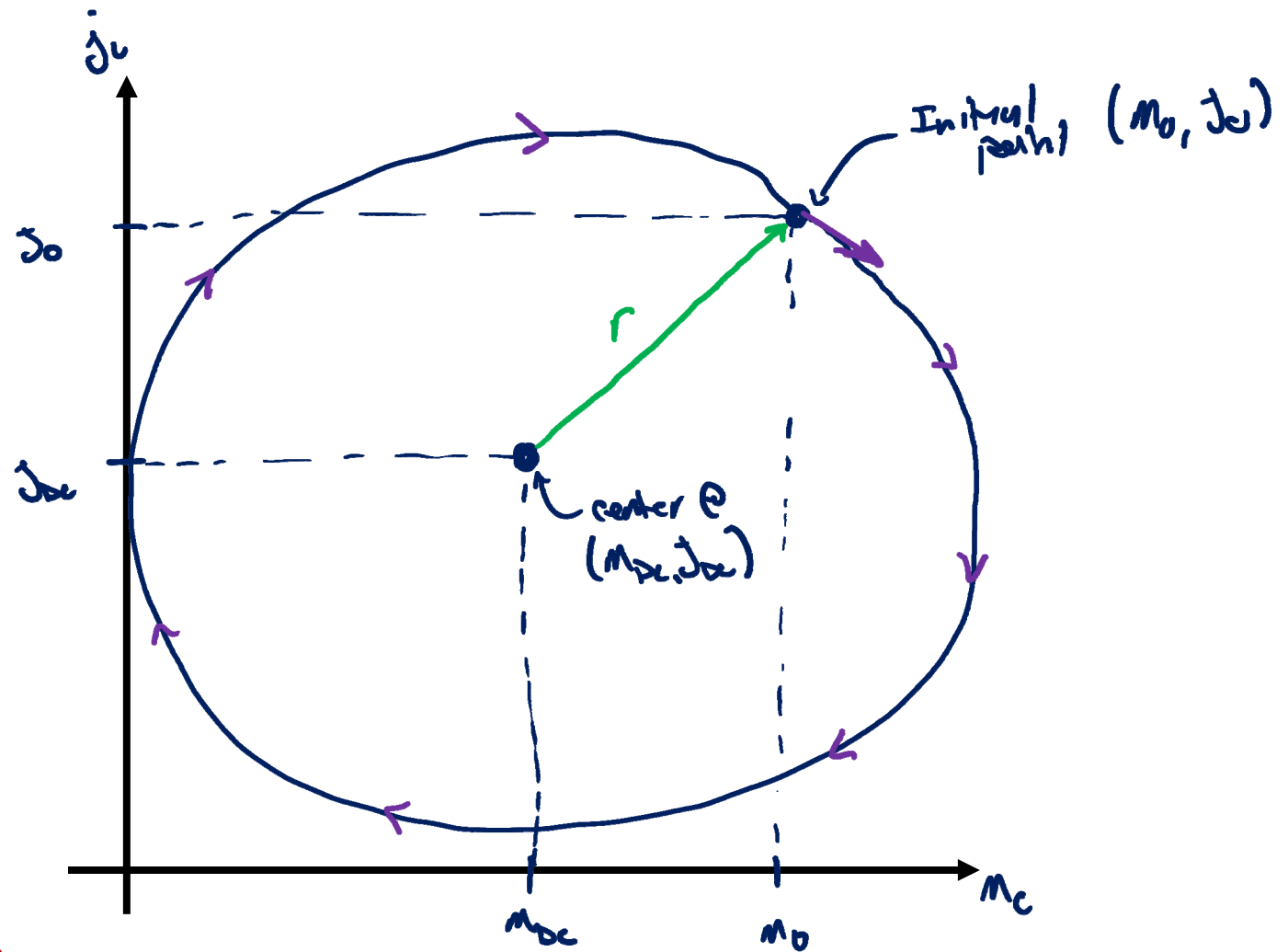for 1-L, 1-C circuits w/ DC bias
transforms diff EQ analysis to geometry



State Plane Analysis

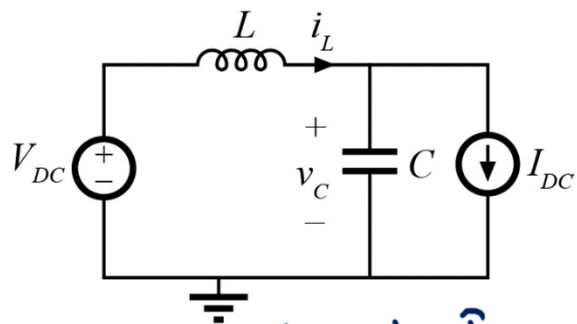


ΦI_C 's $i_L(t=0) = I_0$
 $v_C(t=0) = V_0$

DC solution is
 $v_C = V_{DC}$ & $i_L = I_{DC}$

$V_{base} = \text{anything}$
 $I_{base} = \frac{V_{base}}{R_0}$

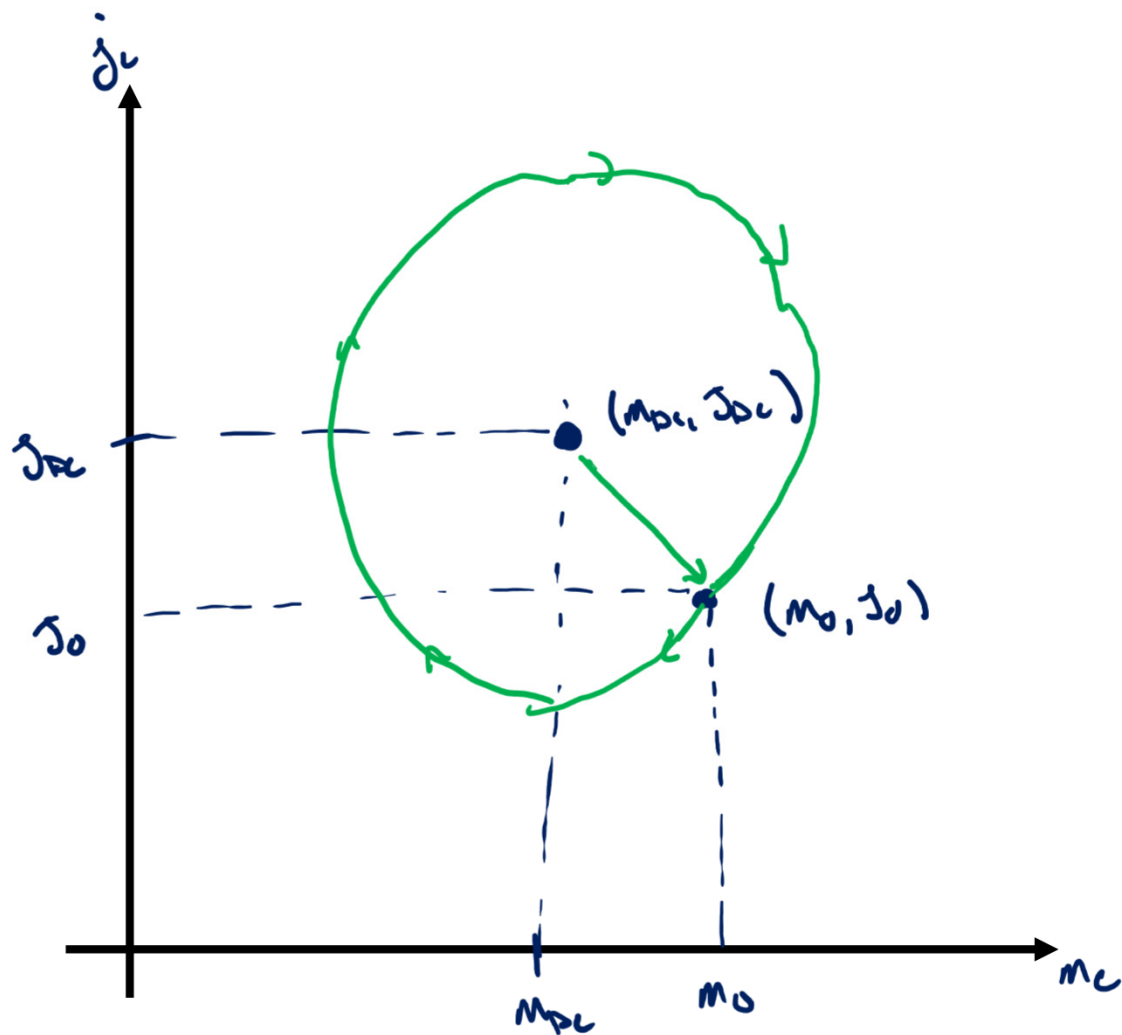Direction from IC on 1st derivative
 $m_0 > m_{DC}$, i_L initially decreasing
 $J_0 < J_{DC}$, m_C initially decreasing



[1] R. Oruganti and F. C. Lee, "Resonant Power Processors, Part I – State Plane Analysis", Industry Applications, IEEE

Tran. on, vol. 21, no. 6, nov 1985.

[2] D. P. Atherton, Nonlinear Control Engineering. London: Van Nostrand Reinhold, 1982, Ch. 2.

Example Analysis

What is t_{lph} ?

$$\begin{aligned} \mathcal{J}_{lph} &= \mathcal{J}_{pc} + r \\ &= \mathcal{J}_{pc} + \sqrt{(\mathcal{J}_0 - \mathcal{J}_{pc})^2 + (m_0 - m_{pc})^2} \\ i_{lph} &= I_{base} \cdot \mathcal{J}_{lph} = I_{pc} + \frac{V_{base}}{\omega_0} \sqrt{(\mathcal{J}_0 - \mathcal{J}_{pc})^2 + (m_0 - m_{pc})^2} \end{aligned}$$


At what time does t_{lph} occur?

$$\theta_{ph} = \omega_0 t_{ph}$$

$$\theta_{ph} = \frac{\pi}{2} + \theta_x$$

$$\theta_{ph} = \frac{\pi}{2} + \tan^{-1} \left(\frac{\mathcal{J}_{pc} - \mathcal{J}_0}{m_0 - m_{pc}} \right)$$
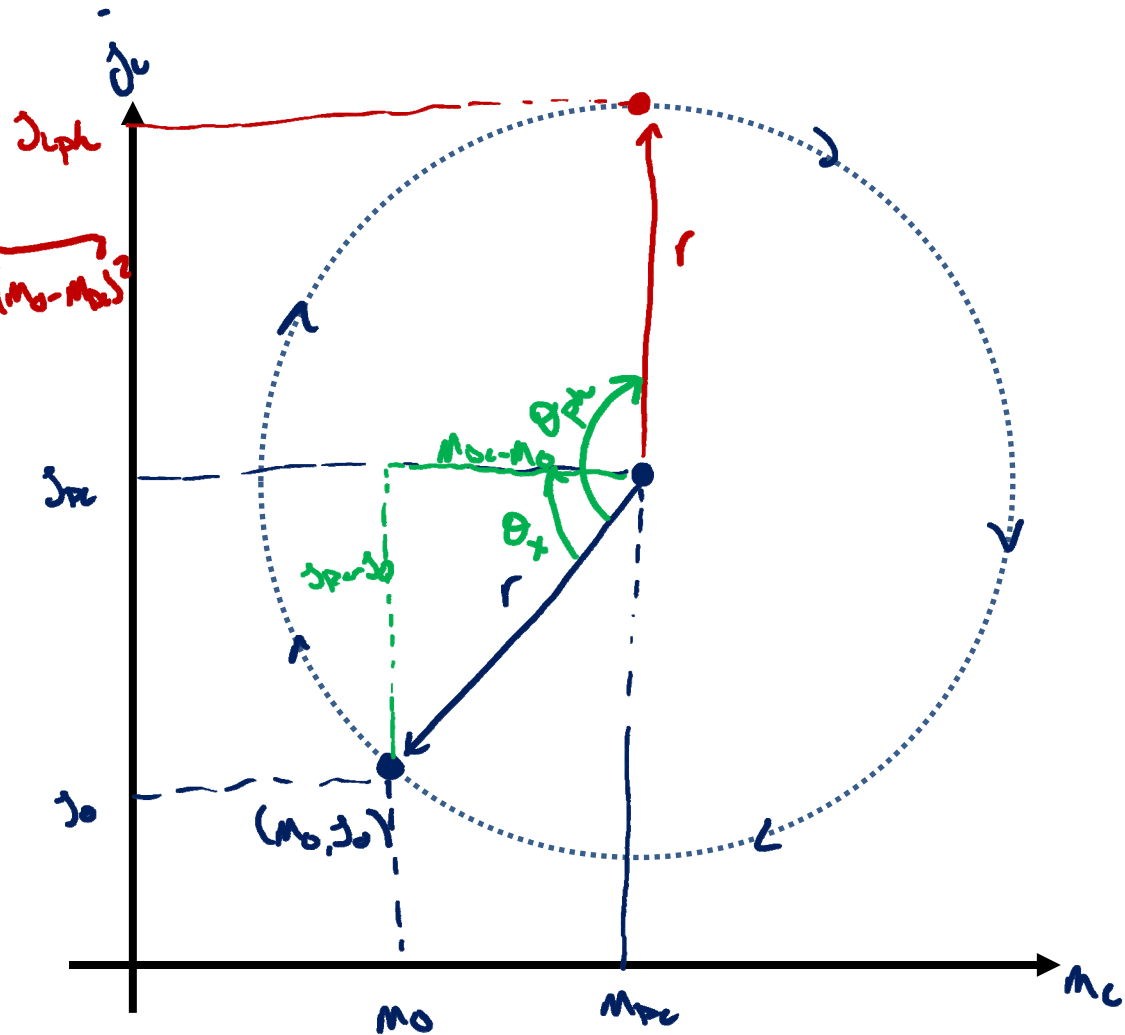
$$t_{ph} = \frac{\theta_{ph}}{\omega_0} = \frac{\pi}{2\omega_0} + \frac{1}{\omega_0} \tan^{-1} \left(\frac{\mathcal{J}_{pc} - \mathcal{J}_0}{m_0 - m_{pc}} \right)$$



State Plane Algorithm

Manipulate circuit into 1-L, 1-C & DC source equivalent
- May require some linearize & approximation

(1) Normalize

$$\begin{cases} m_c(t) = \frac{v_c(t)}{V_{base}} \\ j_c(t) = \frac{i_c(t)}{I_{base}} \\ \theta_x = \omega_0 t_x \end{cases}$$

V_{base} picked for convenience

$$I_{base} = \frac{V_{base}}{R_0}$$

$$R_0 = \sqrt{\frac{L}{C}} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

(2) plot on $m_c - j_c$ axes the normalized resonant trajectory
- center at the dc solution (m_{pc}, j_{pc})
- initial point at IC (m_0, j_0)
- initial direction from IC on 1st derivatives of $v_c(t)$ and/or $i_c(t)$

(3) solve any quantities of interest using geometry & trig

(4) Denormalize back to i, v & t

DCM Buck Converter Example ($M=1/2$)

