

$$V_{base} = V_{DC}$$


$$I_{base} = \frac{V_{DC}}{R_0}$$

$$\begin{cases} v_c(t) = V_{DC} + (V_0 - V_{DC}) \cos(\omega_0 t) + R_0(I_0 - I_{DC}) \sin(\omega_0 t) \\ i_L(t) = I_{DC} + (I_0 - I_{DC}) \cos(\omega_0 t) + \frac{1}{R_0} (V_{DC} - V_0) \sin(\omega_0 t) \end{cases}$$



$$\frac{R_0}{V_{base}} (I_0 - I_{DC}) = \frac{I_0 - I_{DC}}{I_{base}}$$

$$\begin{cases} m_c(t) = \frac{v_c(t)}{V_{base}} = m_{DC} + (m_0 - m_{DC}) \cos(\theta) + \underbrace{(j_0 - j_{DC})}_{\text{green}} \sin(\theta) \\ j_c(t) = \frac{i_c(t)}{I_{base}} = j_{DC} + (j_0 - j_{DC}) \cos(\theta) + (m_{DC} - m_0) \sin(\theta) \end{cases}$$

Normalized Trajectory

 


State Plane Analysis

 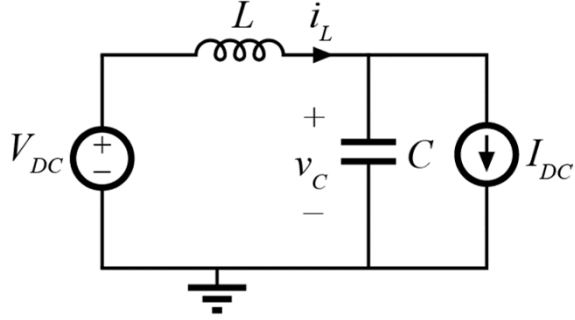


- [1] R. Oruganti and F. C. Lee, "Resonant Power Processors, Part I – State Plane Analysis", Industry Applications, IEEE Tran. on, vol. 21, no. 6, nov 1985.
- [2] D. P. Atherton, Nonlinear Control Engineering. London: Van Nostrand Reinhold, 1982, Ch. 2.

Example Analysis

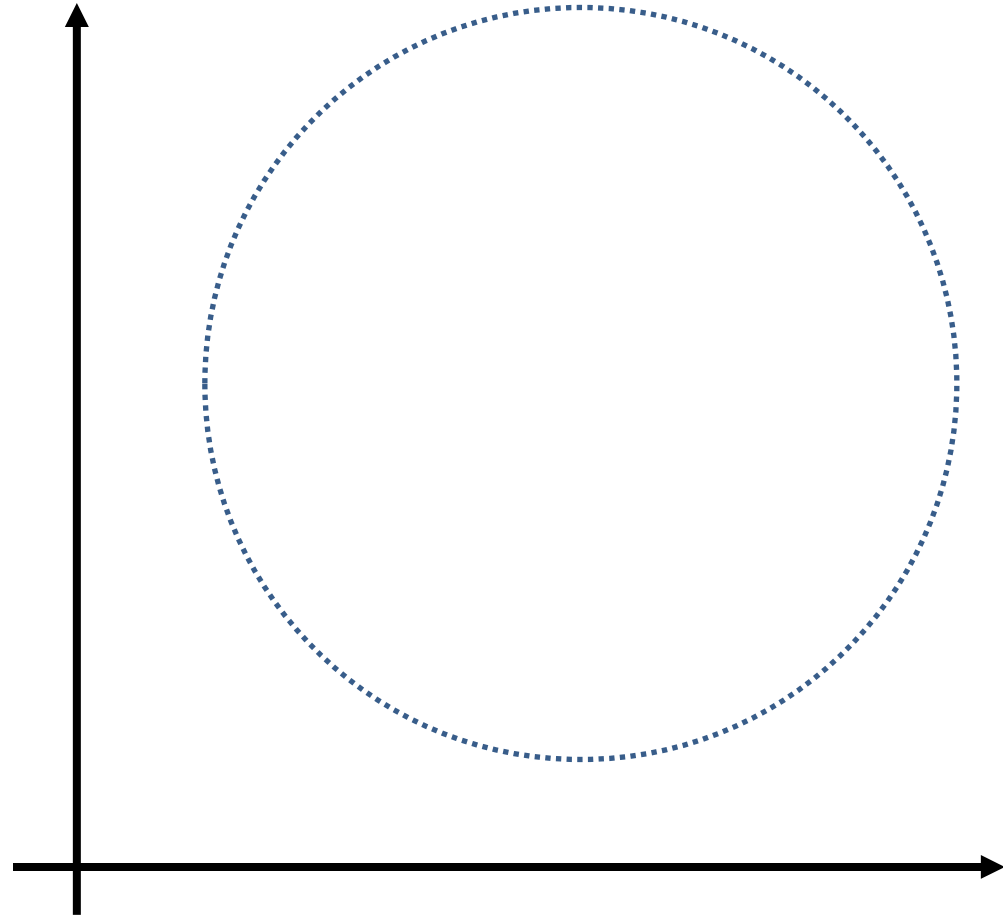

State Plane Algorithm

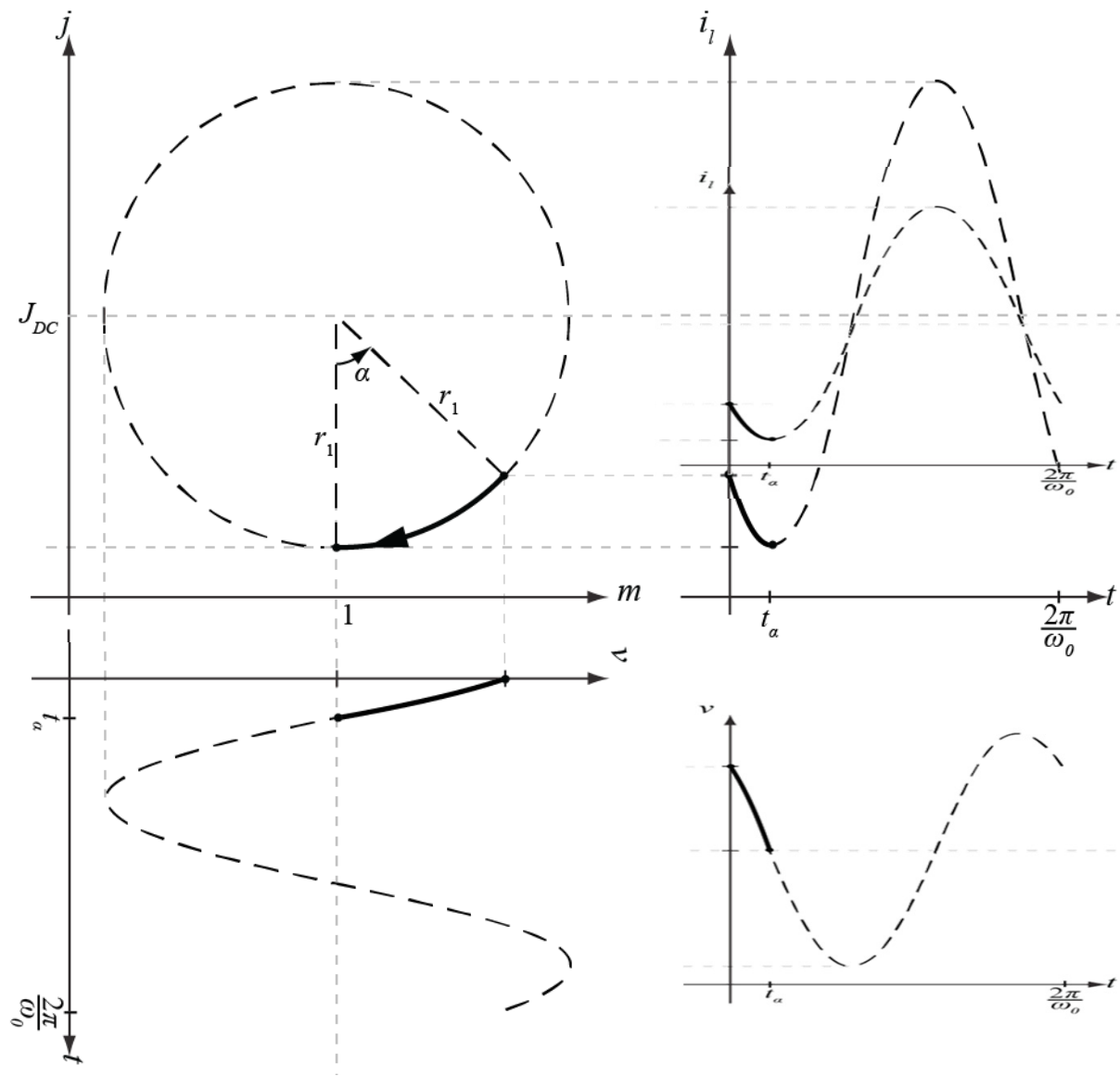

DCM Buck Converter Example ($M=1/2$)

