
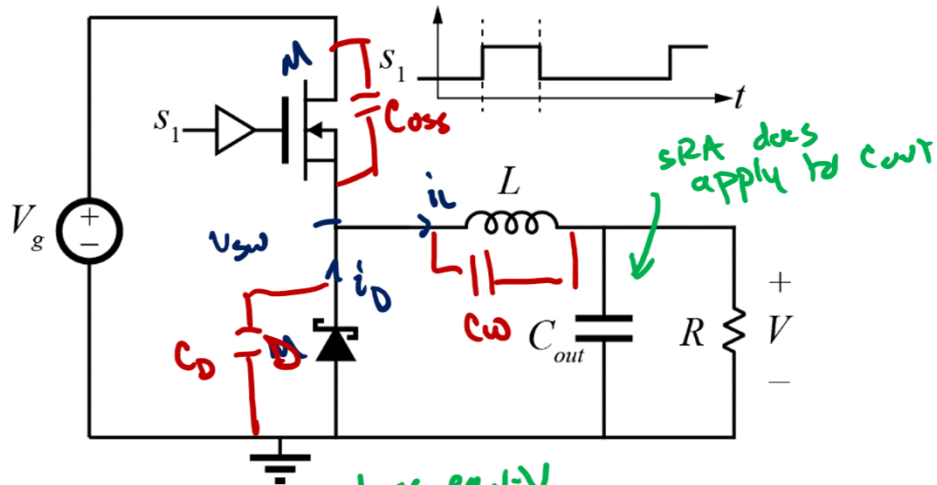


# DCM Buck Converter Example ( $M=1/2$ )

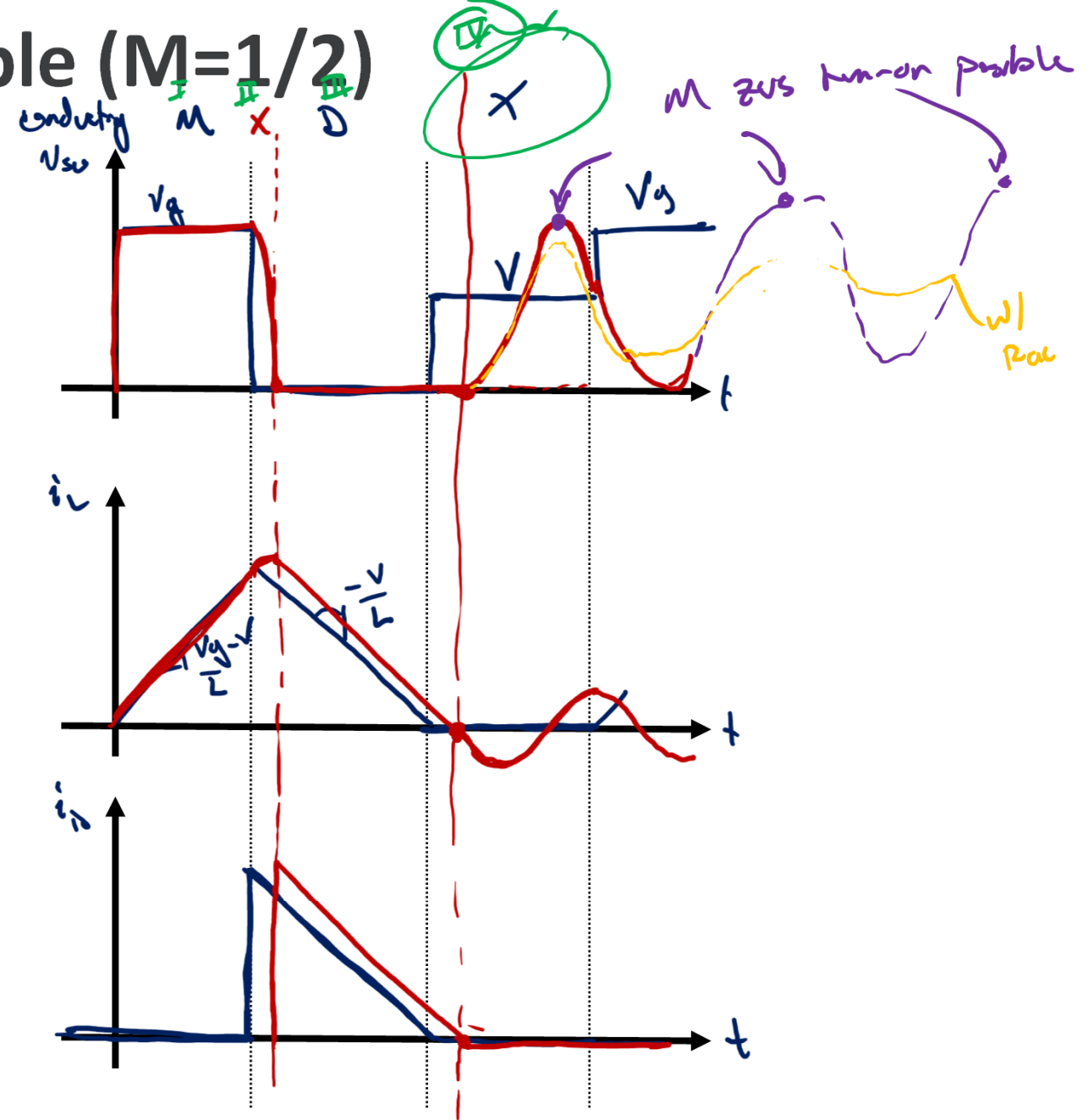

I.C. :  $i_L(t=0) = 0$   
 $v_{oss}(t=0) = 0$

DC solution:  $i_L \rightarrow 0$   
 $v_{oss} \rightarrow V$



# DCM Buck State Plane ( $M = \frac{1}{2}$ )


I.C. :  $(m_c, j_c) = (m_{dc}, j_{dc}) = (0, 0)$

D.C. solution

$$\left. \begin{array}{l} V_c \rightarrow V \\ I_c \rightarrow \phi \end{array} \right\} (m_{dc}, j_{dc})$$


$$M_{dc} = \frac{V}{V_g} = M$$

Direction :  
I.C. on 1st Derivatives


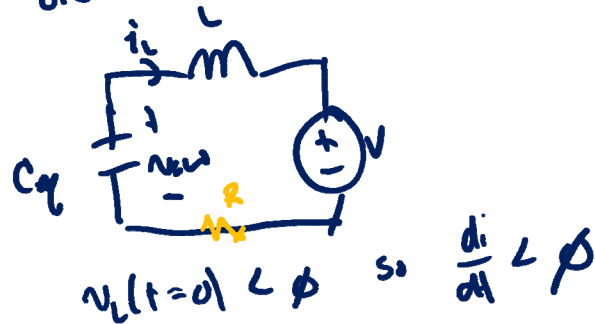


$$V_{base} = V_g$$
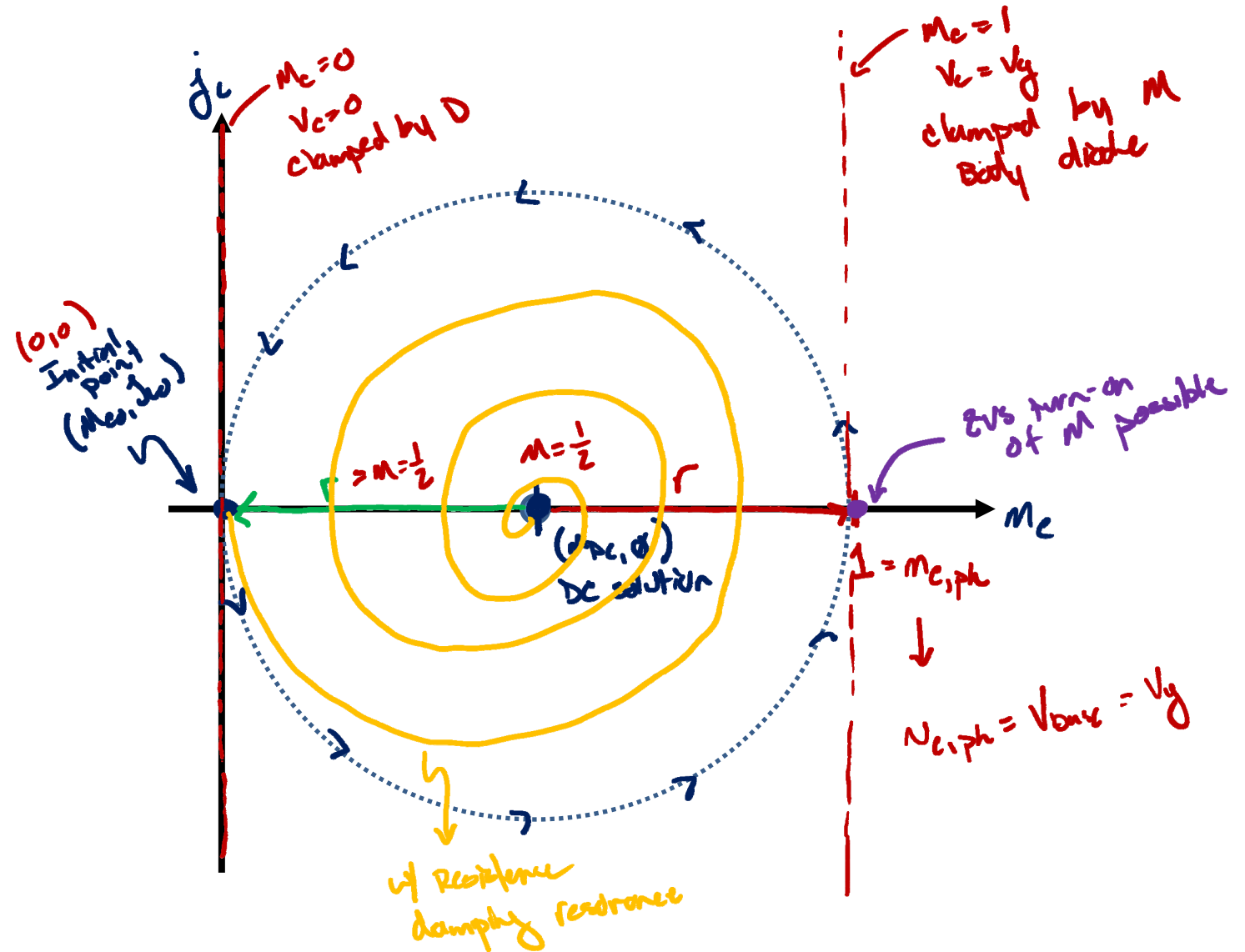
$$I_{base} = \frac{V_{base}}{R_0} = \frac{V_g}{R_0}$$




# DCM Buck M≠1/2

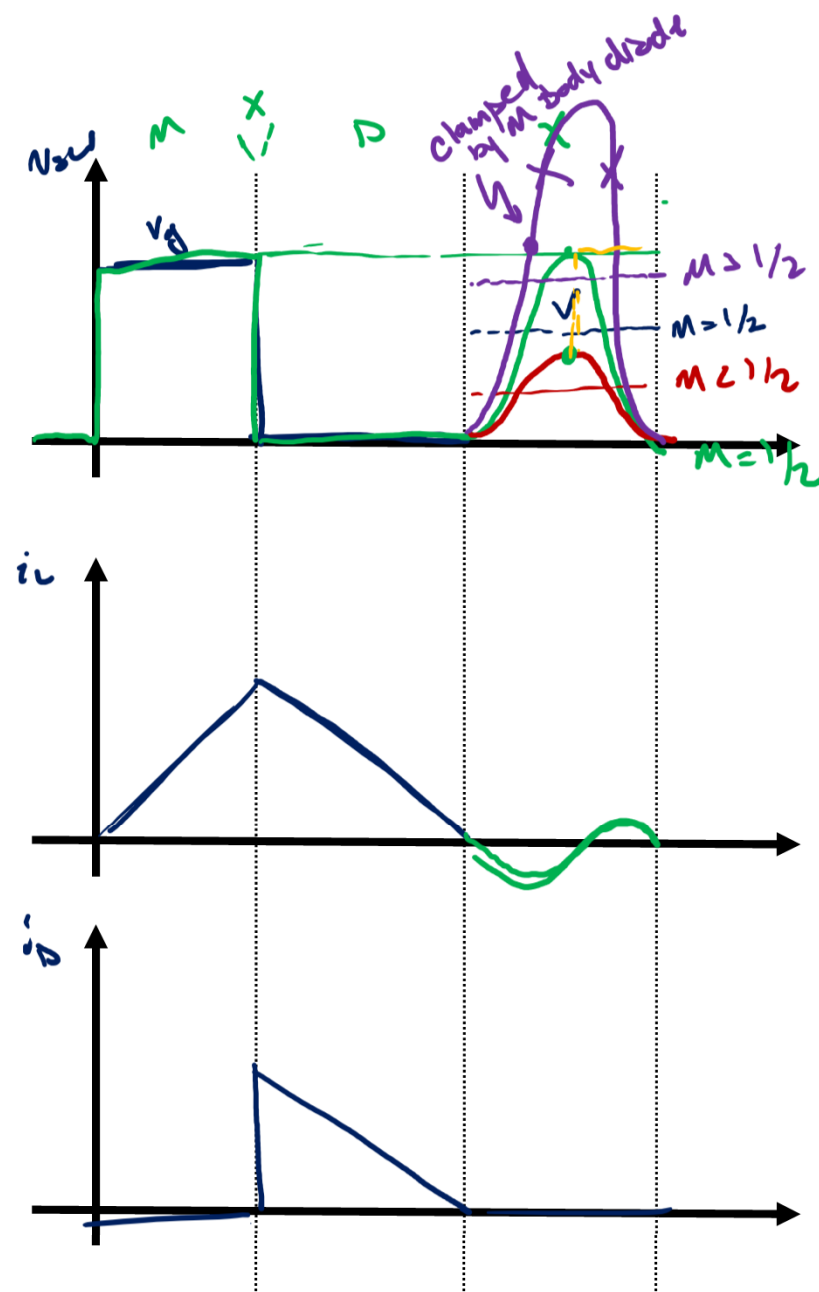
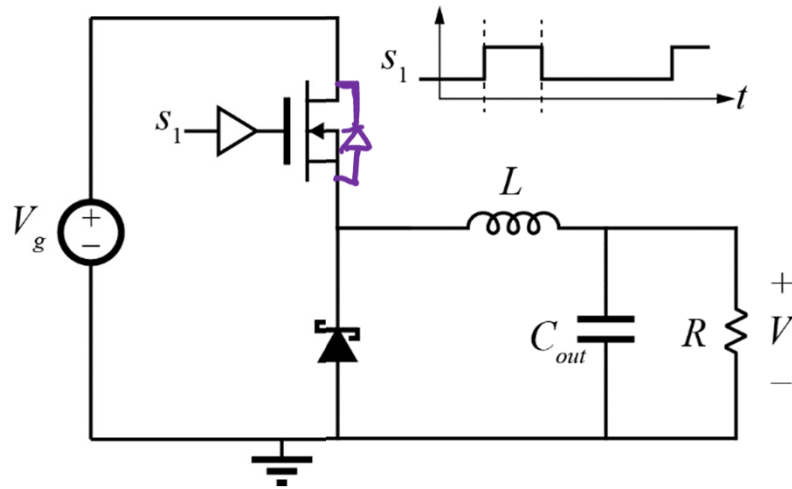

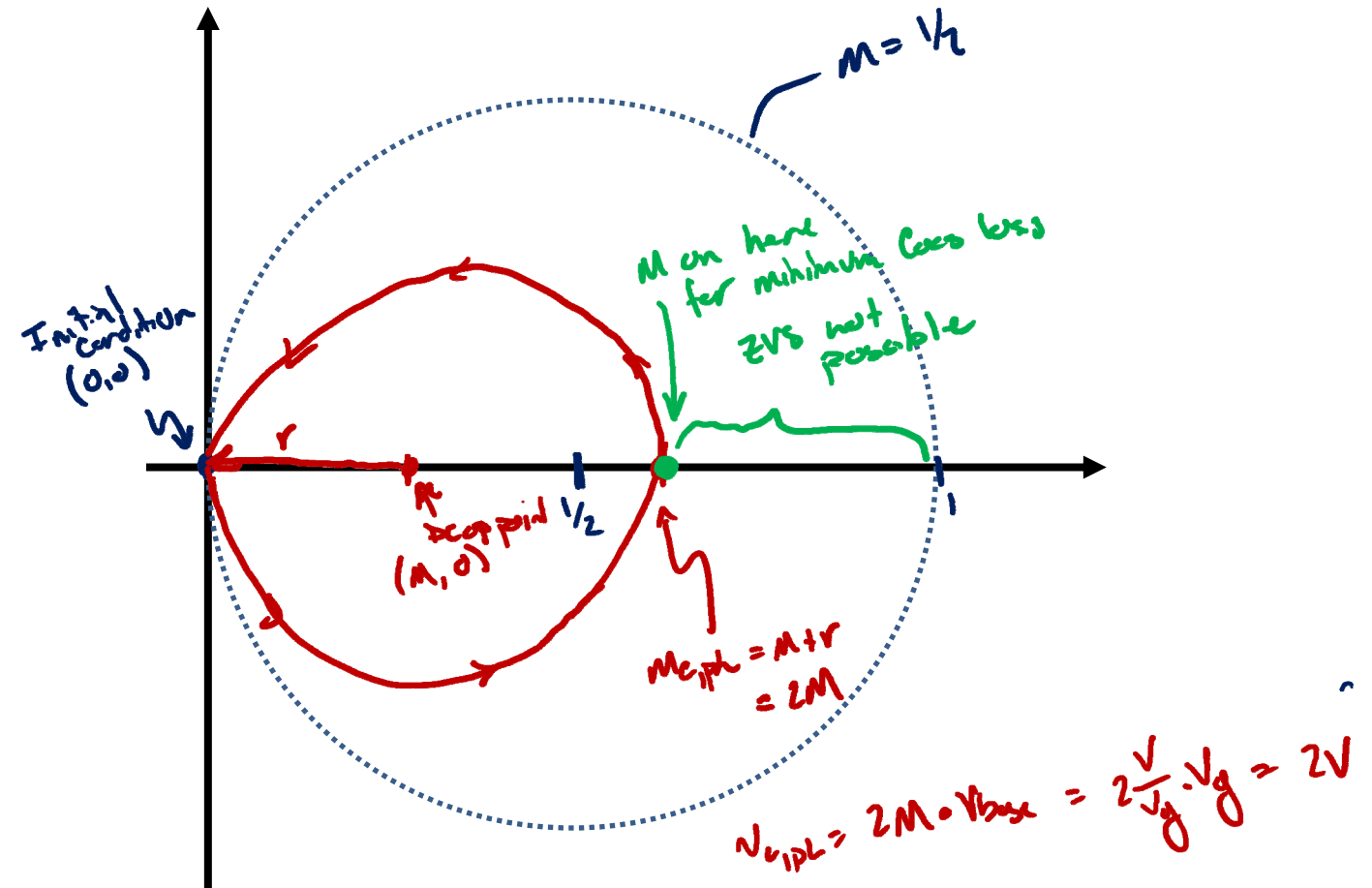
# DCM Buck State Plane ( $M < 1/2$ )

$$V_{base} = V_g, \quad I_{base} = \frac{V_g}{R_o}$$



# DCM Buck State Plane ( $M > 1/2$ )

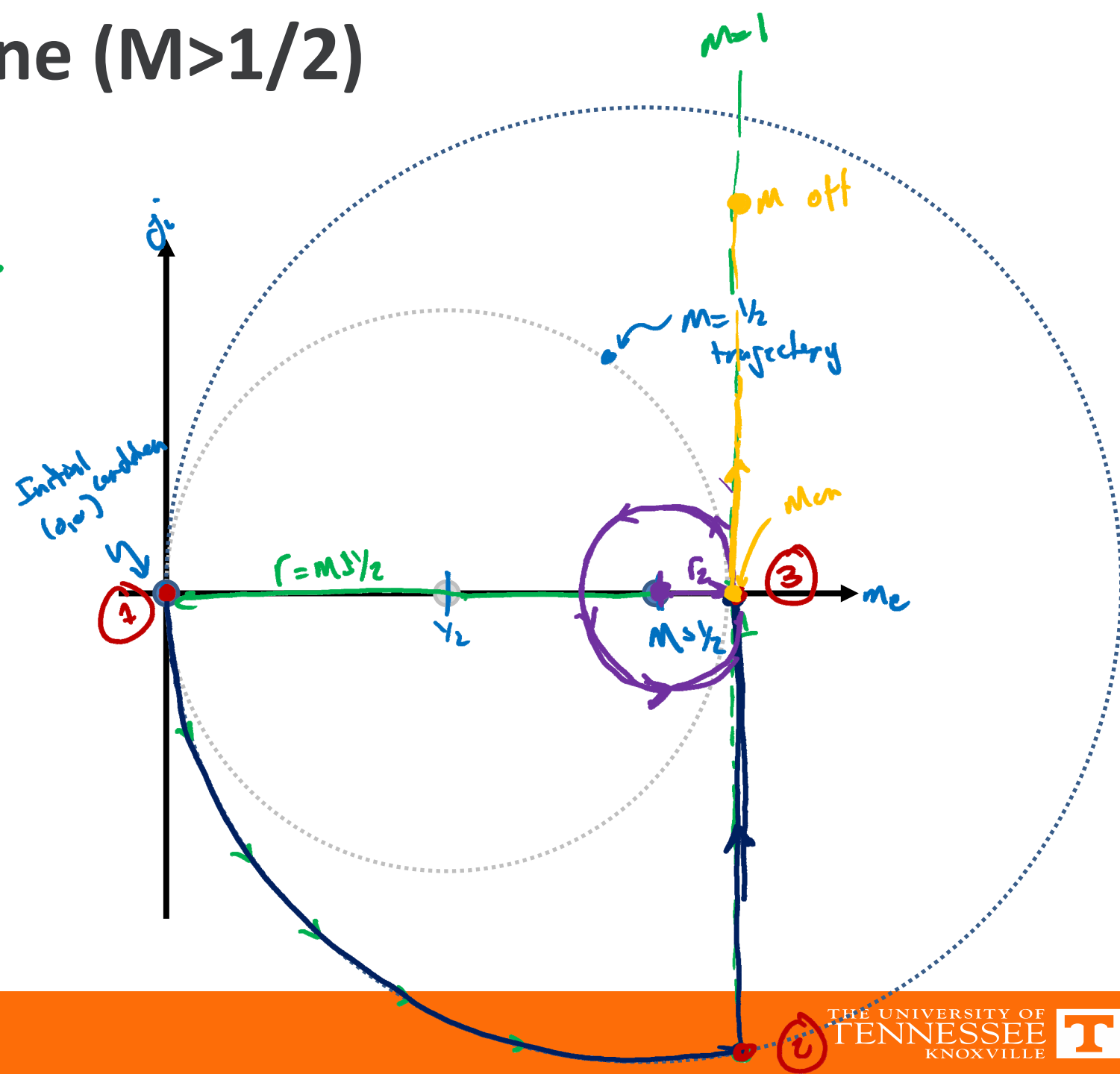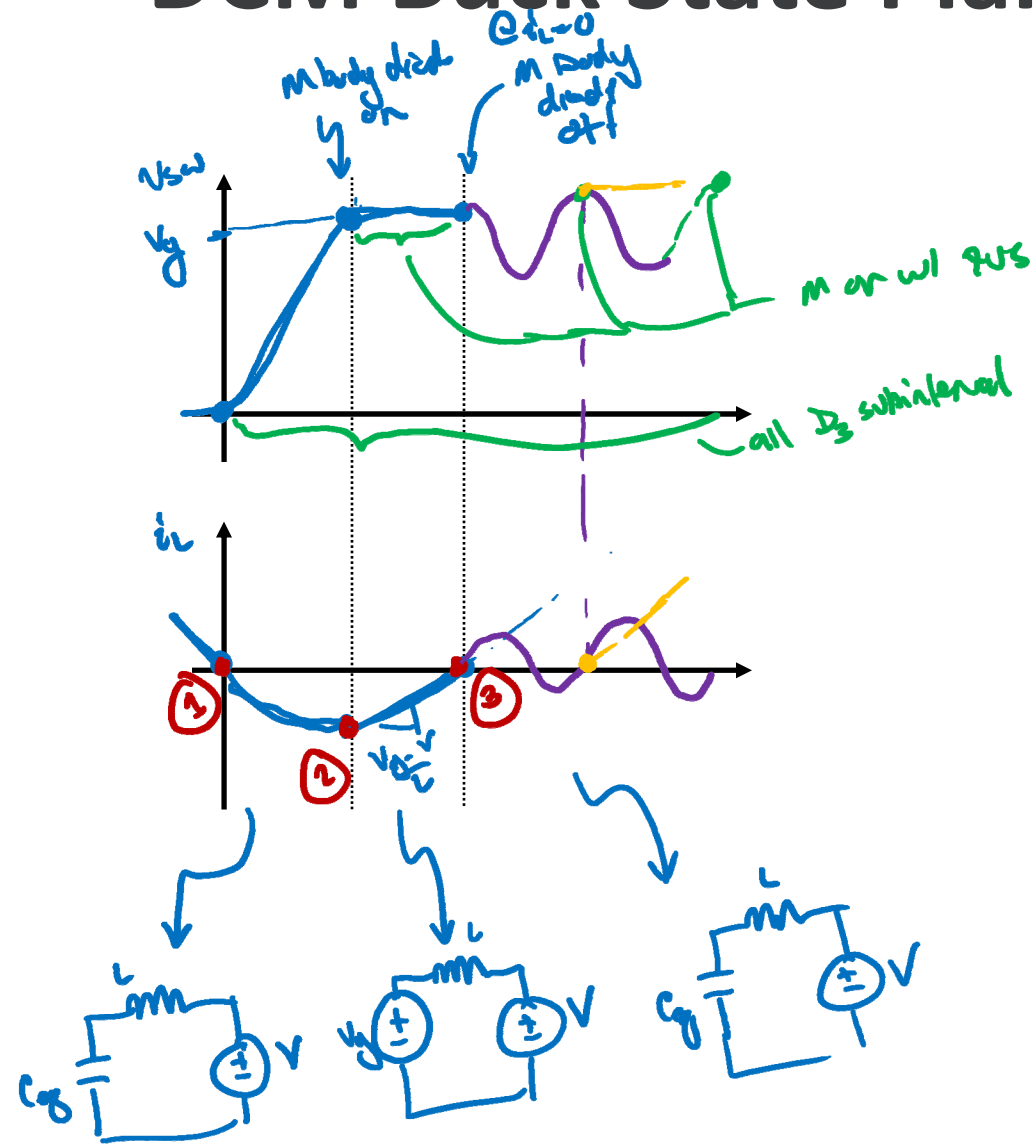

# Synchronous Buck Converter

