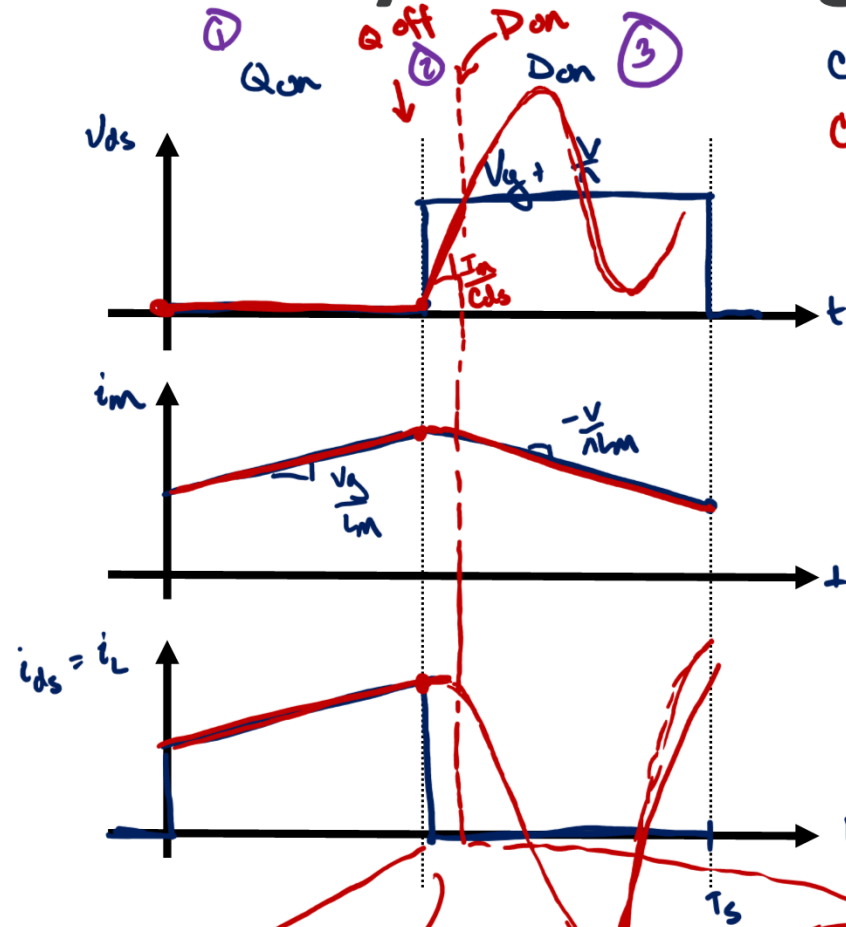





CCM Flyback: Ringing Due to L_l



$C_{ds} = \phi$ $L_l = \phi$
 $C_{ds} > \phi \neq L_l > \phi$

Assume $L_m \gg L_l$
 $\rightarrow L_m + L_l \approx L_m$

SRA applies
to $C \neq L_m$

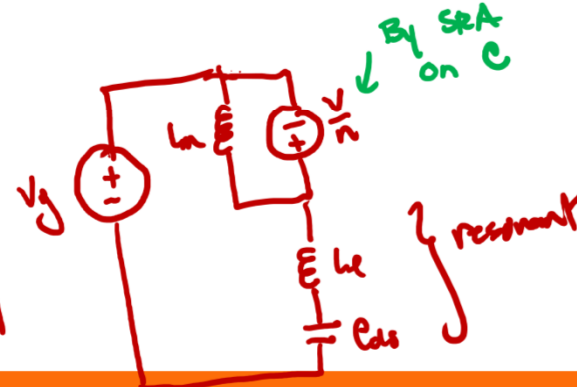
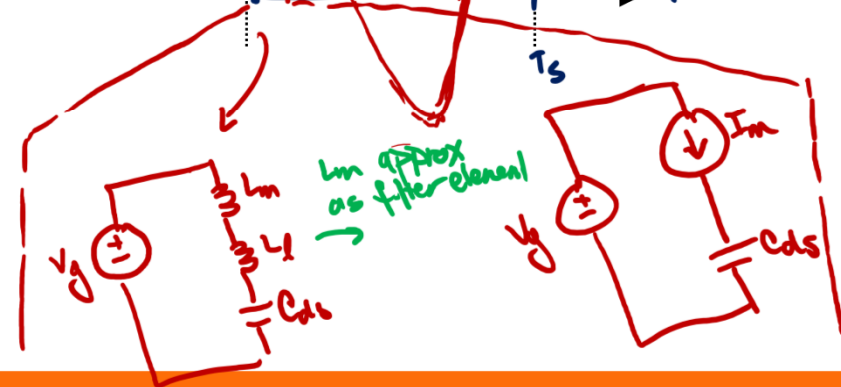
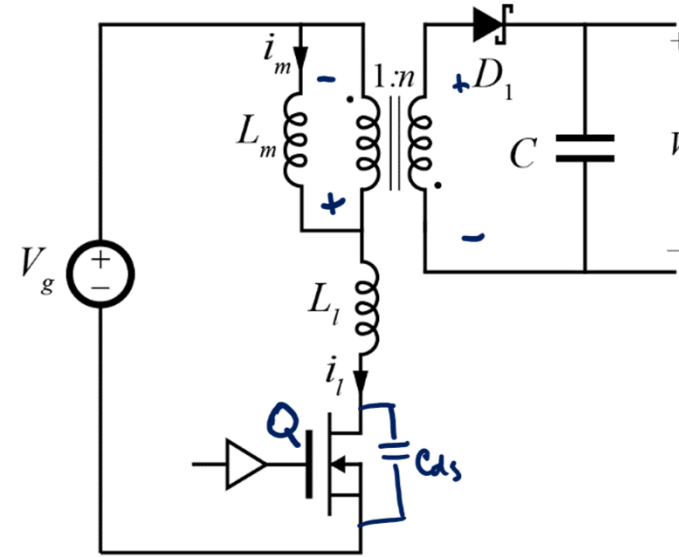


(3) DC: $v_{ds} \rightarrow V_g + \frac{V}{n}$
 $i_L \rightarrow \phi$
 IC: $i_L \rightarrow I_m$
 $v_{ds} \rightarrow V_g + \frac{V}{n}$

MOSFET Turn-off

$$V_{D_{DC}} = V_g + \frac{V}{n} \quad I_{D_{DC}} = \frac{V_{D_{DC}}}{R_D}$$
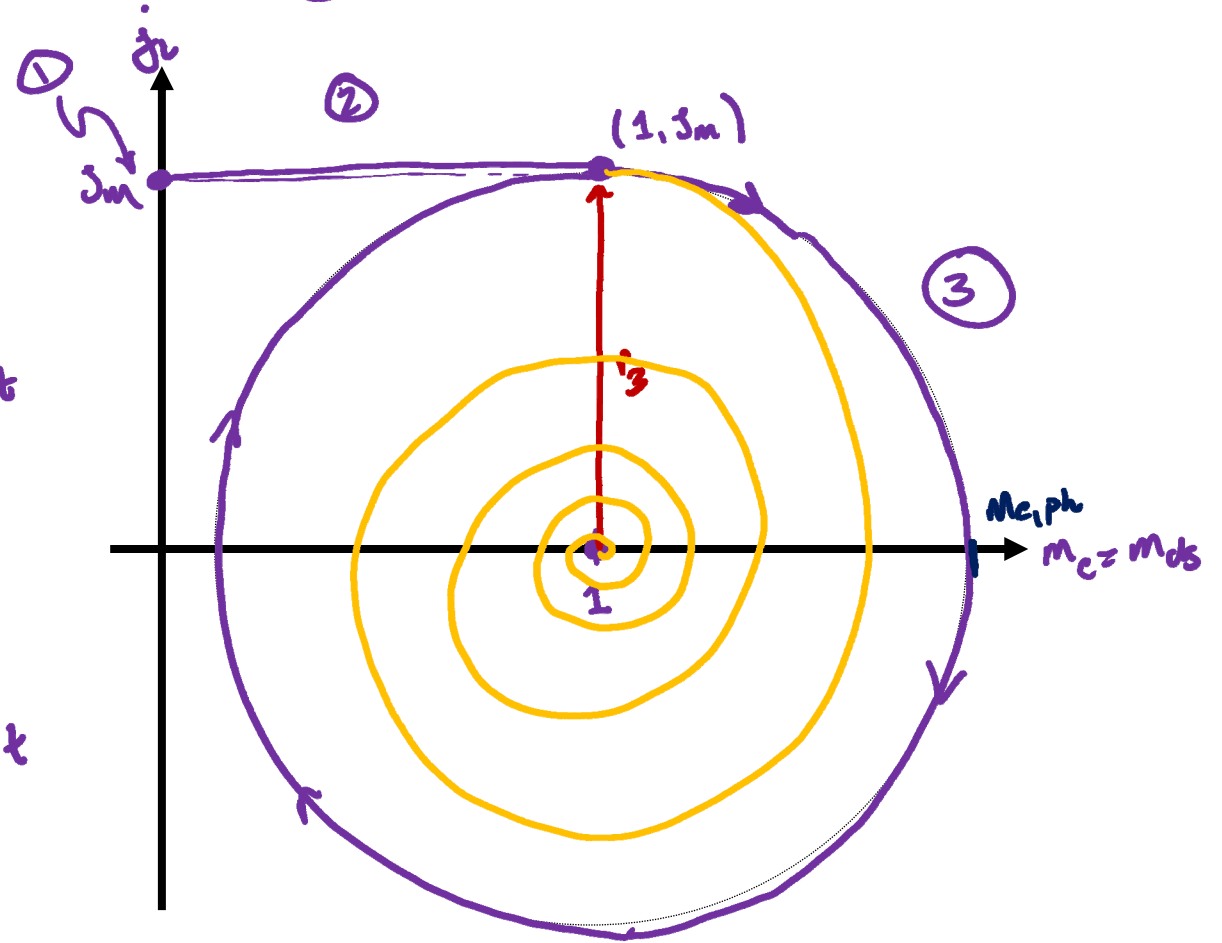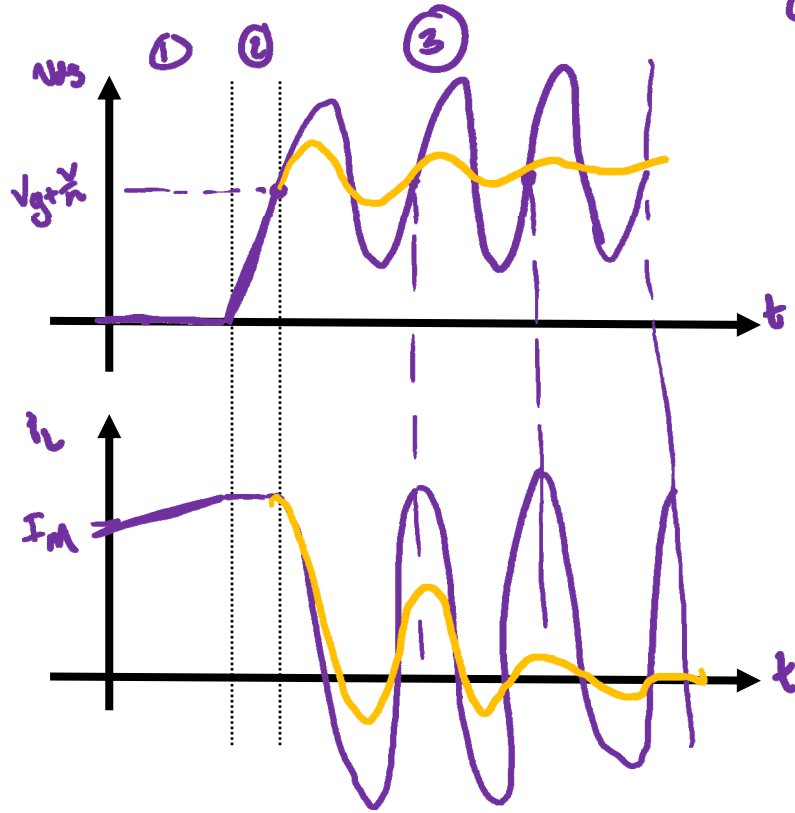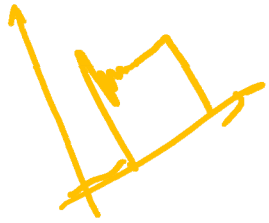
$$\textcircled{3} \text{ DC: } (1, \phi) \quad I_C: (1, I_m)$$



Leakage Voltage Stress

$$M_{os,ph} = 1 + r_3 = 1 + \Delta m$$

$$V_{ds,ph} = \underbrace{V_g + \frac{V}{n}}_{\text{Ideal}} + \underbrace{I_m R_o}_{\text{overvoltage stress}}$$

Example Design

$$V_g = 400V$$

$$V = 10V$$

$$P = 100W$$

$$f_s = 1MHz$$

$$n = \frac{1}{40}, \quad D = 0.5$$

$$C_{ds} = 100pF$$

$$L_m = 1.8mH$$

$$L_c = 35\mu H$$

(2% of L_m)

$$R_o = \sqrt{\frac{L_c}{C_{ds}}} = 600\Omega$$

$$I_m = \frac{n I_{out}}{D} = 500mA$$


$$V_{base} = V_g + \frac{V}{n} = 800V$$

$$V_{ds,ph} = 800V + (0.5) \cdot (600) = \underline{\underline{1.1kV!}}$$

↓
Huge!

Leakage Switching Loss

If all energy is damped out in ③

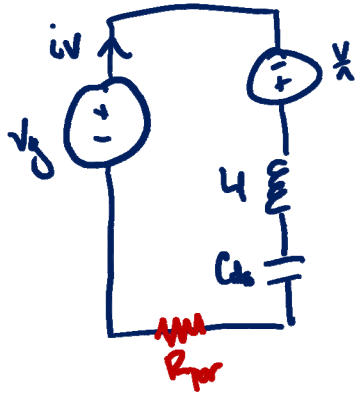

$$E_{loss} = \Delta E_l + \Delta E_c + E_v$$

$$\Delta E_l = \frac{1}{2} L_f I_m^2 - \phi$$

$$\Delta E_c = \frac{1}{2} C_{be} V_{base}^2 - \frac{1}{2} C_{be} V_{base}^2 = \phi$$

$$E_v = \int i_v \cdot (V_g + \frac{V_T}{n}) dt = (V_g + \frac{V_T}{n}) \cdot \int i_c(t) dt = \phi$$

$Q_c = \phi$ because it starts & ends @ $V_g + \frac{V_T}{n}$

$$E_{loss} = \frac{1}{2} L_f I_m^2$$


$$P_{loss} = \frac{1}{2} L_f I_m^2 f_s$$

Plug in example #'s

$$E_{loss} = 4.4 \mu J$$

$$P_{loss} = 4.4 W$$

CCM Flyback: Clamping Circuit

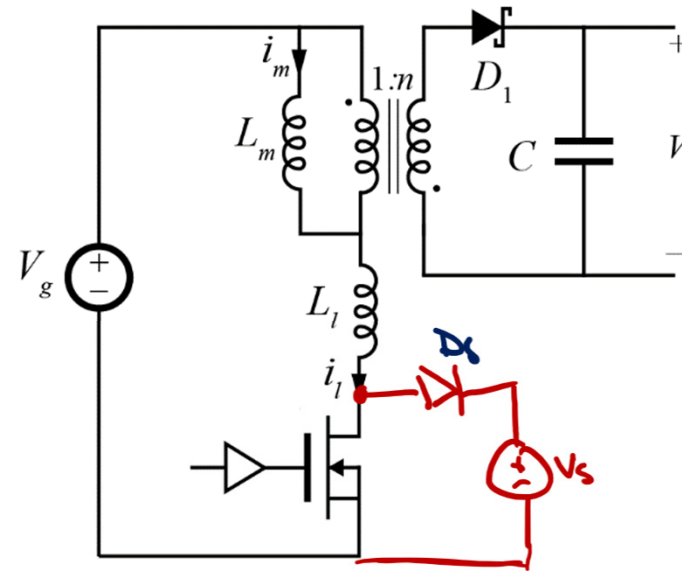

$$V_{ds, pk} > V_s > V_g + \frac{V}{n}$$

1.1 kV

Clamped State Plane

