


CCM Flyback: Ringing Due to L_1

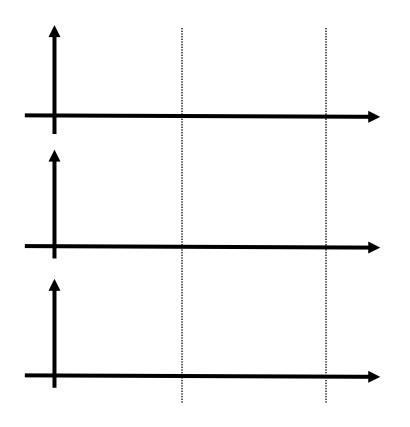

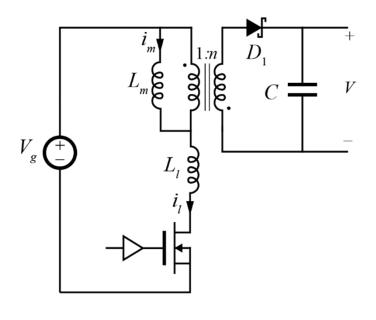


MOSFET Turn-off

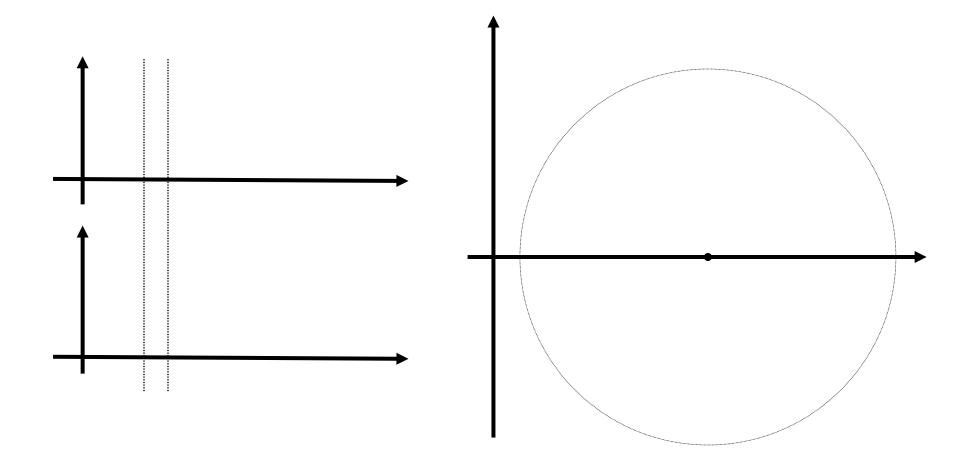

Leakage Voltage Stress

Leakage Switching Loss

CCM Flyback: Clamping Circuit

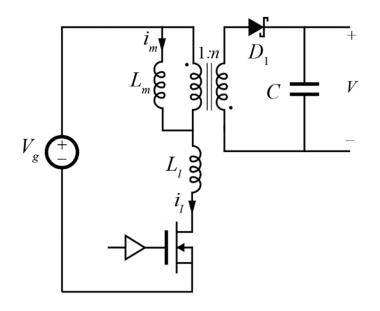

Clamped State Plane

