

Analysis: Intervals 1-3

① No equations yet

$$\frac{2\pi}{P} = \theta_1 + \theta_2 + \gamma + \theta_4 + \epsilon + \theta_6$$

② $\left(\frac{1}{J_m}\right) \frac{F_m}{Cds} t_2 = V_g + \frac{V}{n} \left(\frac{1}{F_{max} C}\right)$

$$\frac{1}{R_0 Cds} = \frac{1}{\sqrt{L_1} Cds} = \frac{1}{\sqrt{L_1} Cds} = \omega_0$$

$$J_m \frac{t_2}{Cds} = (1) R_0$$

$$J_m \theta_2 = 1$$

③

$$J_3^2 = J_m^2 = J_3^2 + (m_s - 1)^2$$

$$\gamma = \tan^{-1} \left(\frac{m_s - 1}{J_3} \right)$$

Analysis: Intervals 4-6

$$(4) \quad V_g + \frac{V}{L_L} t_4 = -(I_3 + I_4)$$

$$(1 - m_s) \frac{R_0}{L_L} t_4 = -j_3 - j_4$$

$$(1 - m_s) \theta_4 = -j_3 - j_4$$

$$(5) \quad r_s^2 = (m_s - 1)^2 + j_4^2 = 1 + j_5^2$$

$$\phi = \pi - \tan^{-1}\left(\frac{j_4}{m_s - 1}\right) - \tan^{-1}(j_5)$$

$$(6) \quad V_g + \frac{V}{L_L} t_6 = I_5 + I_m$$

$$(1) \theta_6 = j_5 + j_m$$

Analysis: Averaging

Averaging applied to all small-ripple elements
Here: L_m , C_s , C

Cap-Q balance on C_s

$$\langle i_s \rangle_{T_s} = 0 = \frac{1}{T_s} \int_0^{T_s} i_s(t) dt$$

$$\phi = \frac{1}{T_s} \int_0^{T_s} i_s(t) dt = \frac{1}{T_s} \left[\frac{I_3 - I_4}{2} t_4 \right] \rightarrow \boxed{I_3 = I_4}$$

$$\boxed{I_3 = I_4}$$

Volt-sec balance on L_m

$$\langle v_{Lm} \rangle = 0 = \frac{1}{T_s} \int_0^{T_s} v_{Lm}(t) dt$$


$$\phi = \frac{1}{T_s} \left[V_g t_1 + V_g t_2 - \left(\frac{V_g + \frac{V}{n}}{2} \right) t_2 + \left(\frac{-V}{n} \right) (t_3 + t_4 + t_5 + t_6) \right]$$

$$\phi = V_g \left(t_1 + \frac{t_2}{2} \right) + \left(\frac{-V}{n} \right) \left(\frac{t_2}{2} + t_3 + t_4 + t_5 + t_6 \right)$$

$$\boxed{\frac{V}{V_g} = n \frac{t_1 + \frac{t_2}{2}}{\frac{t_2}{2} + t_3 + t_4 + t_5 + t_6}}$$

~ if flyback approx $\rightarrow \frac{V}{V_g} = n \frac{D}{1-D}$ as in 481

Continuity

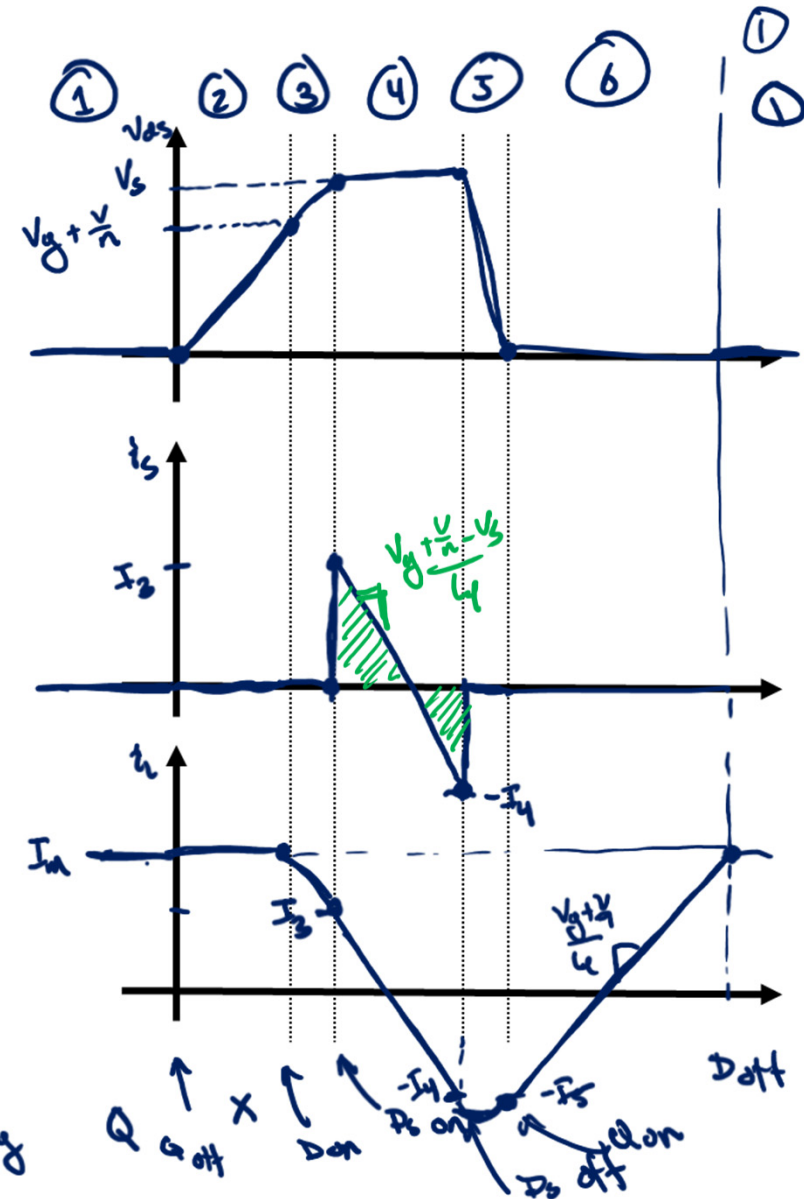

Average Output Current

Cap-Q balance on C:

$$\langle i_c \rangle_{T_s} = 0 = \frac{1}{T_s} \int_0^{T_s} \left(i_D(t) - \frac{V}{R} \right) dt$$

$$T_s \frac{V}{R} = \int_0^{T_s} i_D(t) dt$$

$$n I_{out} = \frac{1}{T_s} \int_0^{T_s} n i_D(t) dt = \int_0^{T_s} (I_m - i_L(t)) dt$$

$$= \underbrace{\frac{1}{T_s} \int_0^{t_1} (I_m - i_L(t)) dt}_{g_1} + \underbrace{\frac{1}{T_s} \int_{t_1}^{T_s} (I_m - i_L(t)) dt}_{g_2}$$

① → ⑥


$$g_1 = 0 \quad g_2 = 0$$

$$g_3 = I_m t_3 - C_{ds} \left(\cancel{V_s} - V_g - \frac{V}{2} \right)$$

$$g_4 = I_m t_4 - \frac{I_3 - I_4}{2} t_4$$

$$g_5 = I_m t_5 - C_{ds} \left(-V_s \right)$$
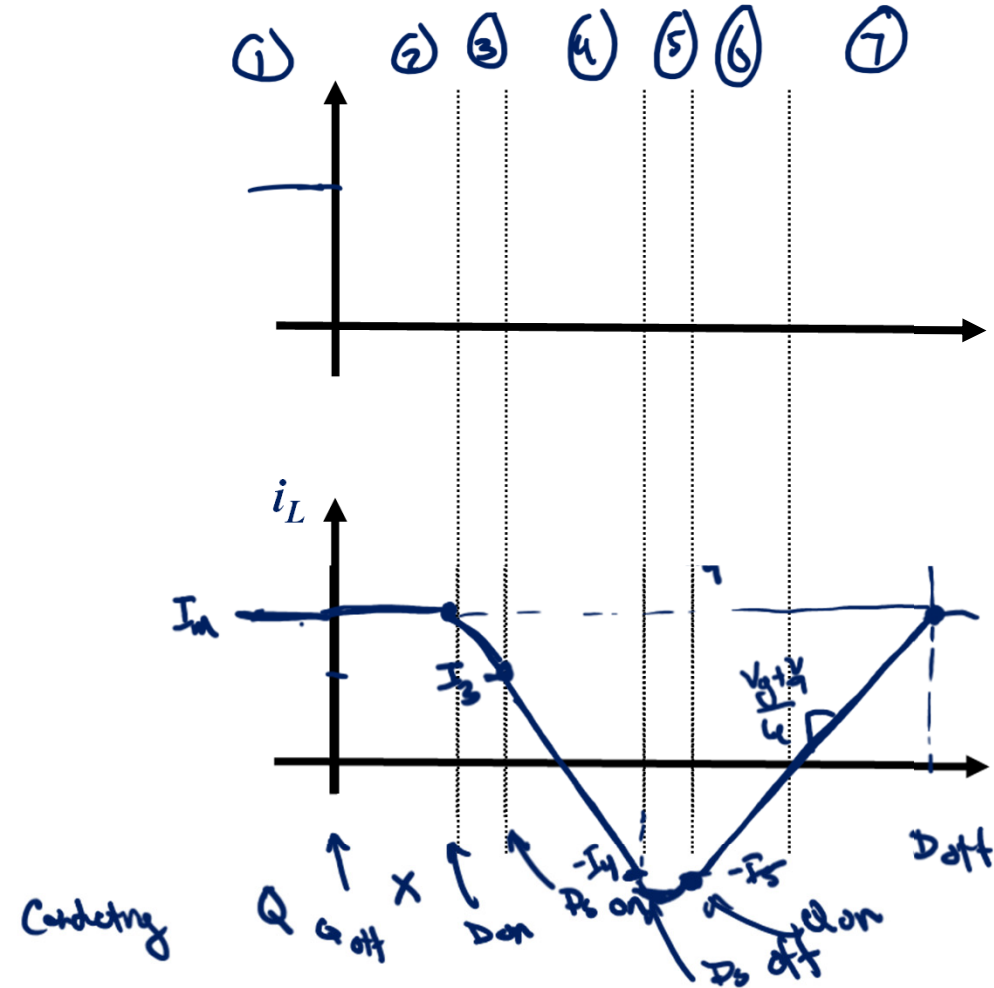
$$g_6 = I_m t_6 - \frac{I_m - I_5}{2} t_6$$



$$n I_{out} = \frac{1}{T_0} [g_3 + g_4 + g_5 + g_6]$$

$$= \frac{1}{T_0} \left[I_m t_3 + C_{ds} (V_g + \frac{V}{n}) + I_m t_4 - \frac{I_3 - I_4}{2} t_4 + I_m t_5 + I_m t_6 - \frac{I_m - I_5}{2} t_6 \right]$$

$$\stackrel{\perp}{I_{base}} = \frac{1}{T_0} \left[I_m (t_3 + t_4 + t_5 + \frac{t_6}{2}) + C_{ds} (V_g + \frac{V}{n}) - \frac{I_3 - I_4}{2} t_4 + \frac{I_5}{2} t_6 \right] \frac{1}{I_{base}} \frac{\omega_0}{\omega_0}$$

$$n S_{out} = \frac{1}{\omega_0 T_0} \left[S_m (\gamma + \theta_4 + \epsilon + \frac{\theta_6}{2}) + R_0 C_{ds} (1) - \frac{J_3 - J_4}{2} (\theta_4) + \frac{J_5}{2} (\theta_6) \right]$$

$$n S_{out} = \frac{F}{2\pi} \left[S_m (\gamma + \theta_4 + \epsilon + \frac{\theta_6}{2}) + 1 - \cancel{\frac{J_3 - J_4}{2} \theta_4} + \frac{J_5}{2} \theta_6 \right]$$