
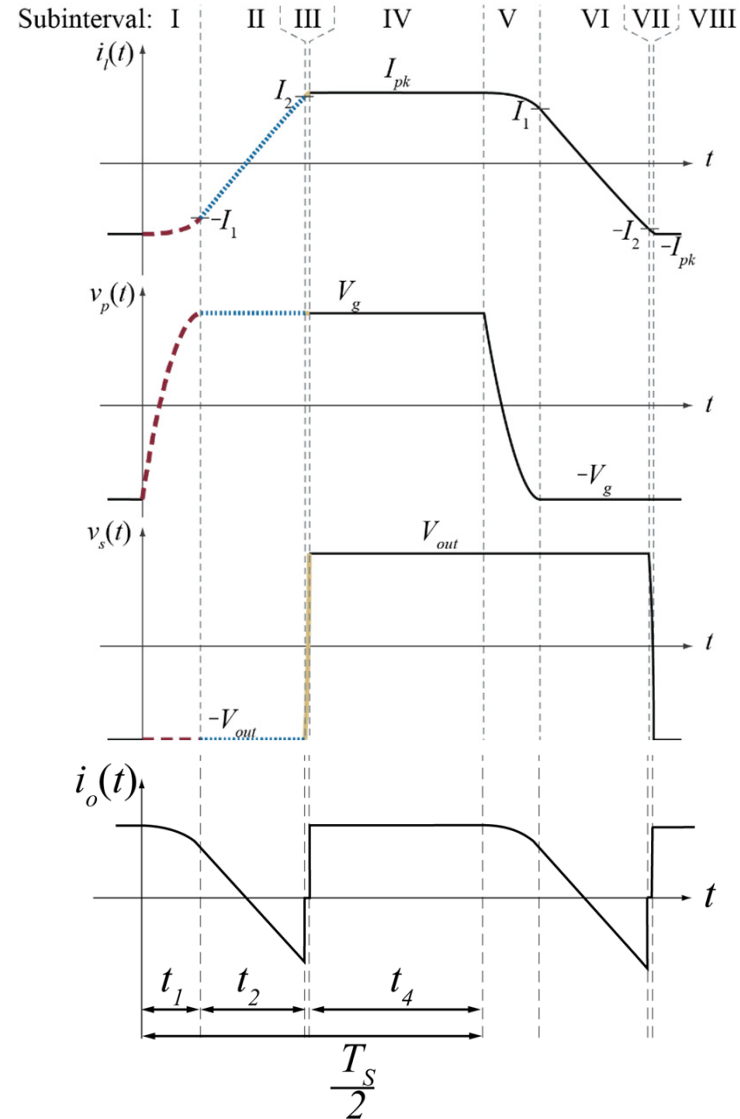


State Plane Analysis of DAB Converter

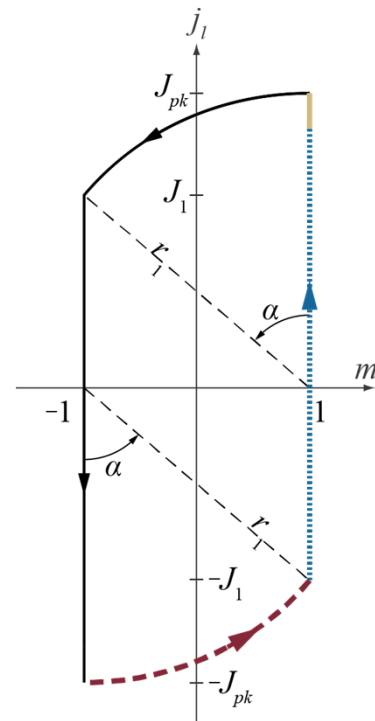


Primary



$$I_{base} = V_g \sqrt{\frac{C_p}{L_l}}$$

Secondary

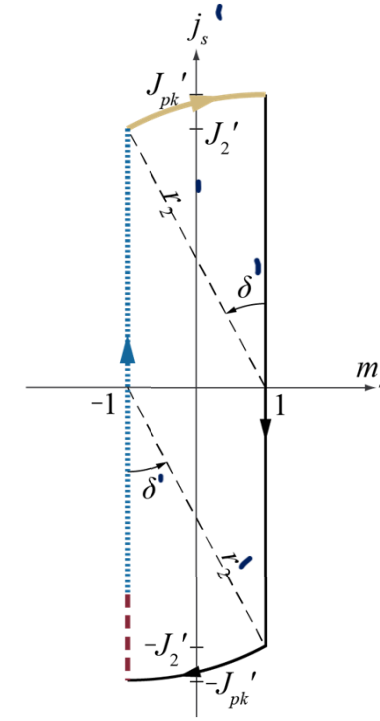

$$I_{base}' = V_g \sqrt{\frac{C_s}{n_t^2 L_l}}$$

State Plane Solution

(I) $r_1^2 = J_{pk}^2 = J_1^2 + 4$

$$\alpha = \tan^{-1} \left(\frac{2}{J_1} \right)$$

(II) $V_g + \frac{V}{n} t_2 = I_2 + I_1$

Here $M=n$, $\frac{V}{n} = V_g$

$$2 \frac{R_0}{L_1} t_2 = J_2 + J_1 = 2\theta_2$$

(III) $r_2'^2 = (J_{pk}')^2 = (J_2')^2 + 4$

$$\delta' = \tan^{-1} \left(\frac{2}{J_2'} \right)$$

$$\frac{\delta'}{\omega_0'} = t_\delta = \frac{\delta}{\omega_0}$$

$$\delta = \frac{\omega_0}{\omega_0'} \delta'$$


(IV) → Nothing from waveforms

$$\frac{T_3}{2} = t_2 + t_2 + t_\delta + t_4$$

$$\frac{\pi}{F} = \alpha + \theta_2 + \delta + \theta_4$$


$$V_{base} = V_g$$

Primary

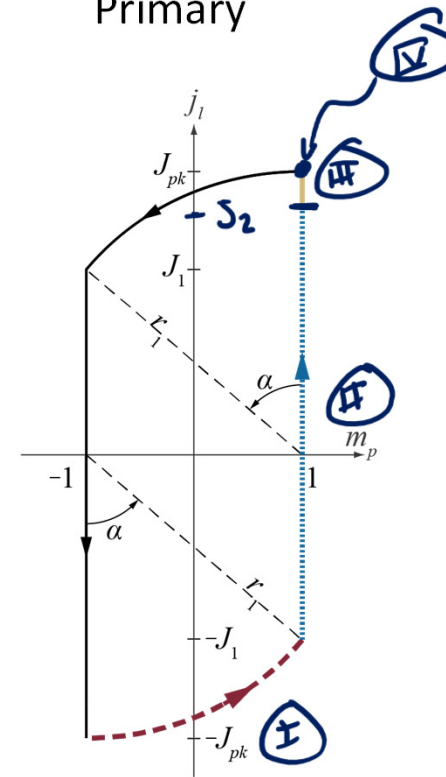

$$I_{base} = V_g \sqrt{\frac{C_p}{L_1}}$$

Secondary

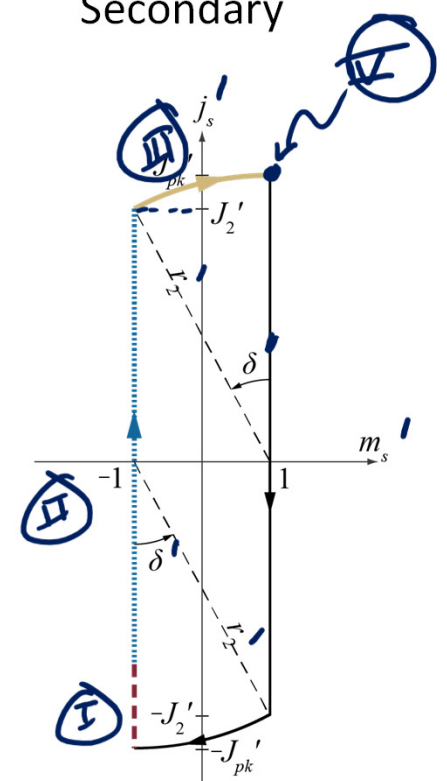

$$I_{base}' = V_g \sqrt{\frac{C_s}{n_t^2 L_1}}$$

Averaging Step (fix)

Small Ripple Approx on C_{out}

$$\frac{V}{R} = I_{out} = \frac{1}{T_s} \int_0^{T_s} i_{out}(t) dt$$


$$\eta \langle i_{out} \rangle = \frac{2}{T_s} \int_0^{T_{shz}} \eta i_{out}(t) dt$$

$$= \frac{2}{T_s} [g_1 + g_2 + \cancel{g_3} + g_4]$$



$$g_1 = C_p (2V_g)$$

$$g_2 = \frac{I_2 - I_1}{2} t_2$$

$$g_4 = I_{ph} t_4$$

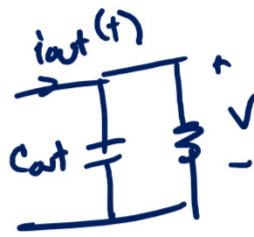
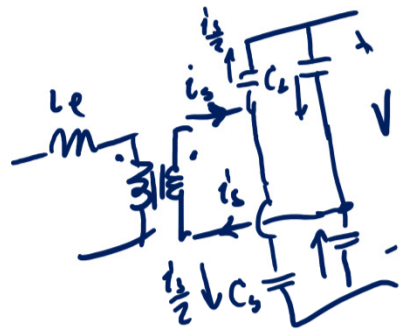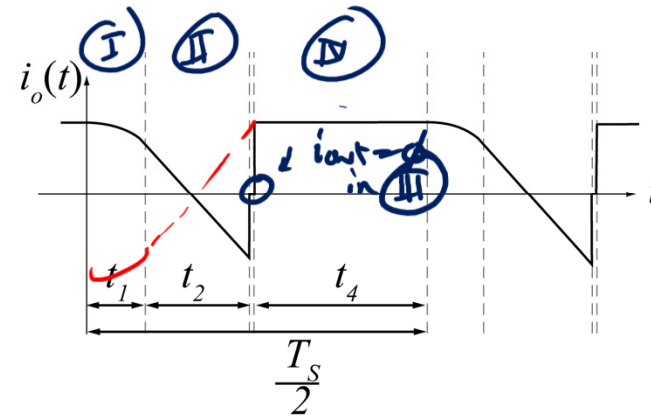
$$\eta i_{out}(t) = \begin{cases} -i_L(t), & \text{I, II} \\ +i_L(t), & \text{IV} \\ \emptyset, & \text{III} \end{cases}$$




$$\left. \begin{aligned} \eta \langle i_{out} \rangle &= \frac{2}{T_s} \left[2V_g C_p + \frac{I_2 - I_1}{2} t_2 + I_{ph} t_4 \right] \\ J = \eta J_{out} &= \frac{2}{T_s} \left[2C_p R_o + \frac{J_2 - J_1}{2} t_2 + J_{ph} t_4 \right] \quad \left(\frac{w_o}{w_i} \right) \end{aligned} \right\}$$

$$J = \eta J_{out} = \frac{F}{\pi} \left[2 + - (J_2 - J_1) \frac{\theta_2}{2} + J_{ph} \theta_4 \right]$$

Output Plane

$$J = \frac{n \langle i_{out} \rangle}{I_{base}} = \frac{F}{\pi} \left[2 + \frac{1}{4} (J_1^2 - J_2^2) + J_p \left(\frac{\pi}{F} - \alpha - \cancel{\beta} - \delta \right) \right]$$


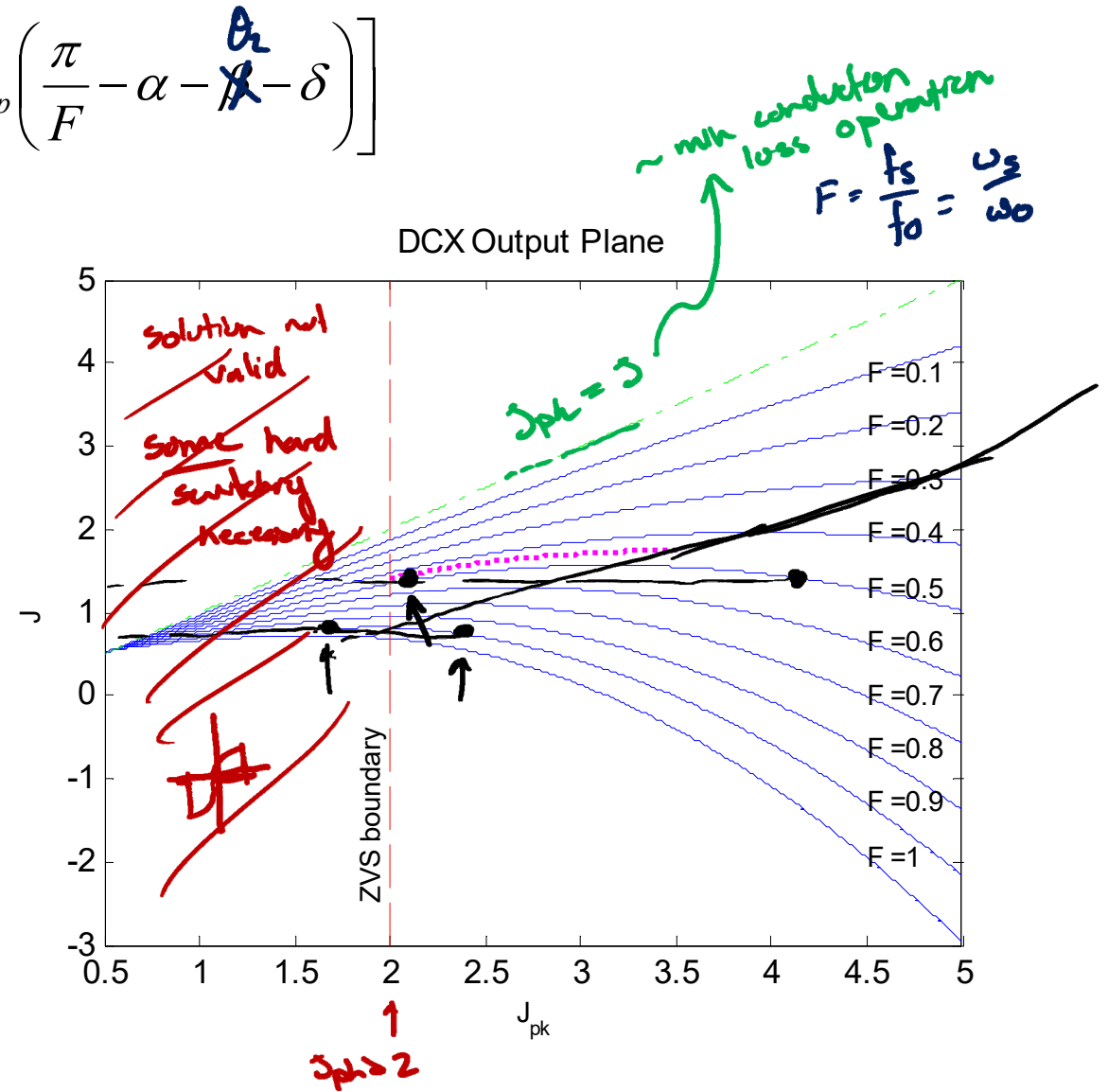
usually operate with
 $(t_{on} + t_2 + t_g) \leq \frac{T_s}{4}$



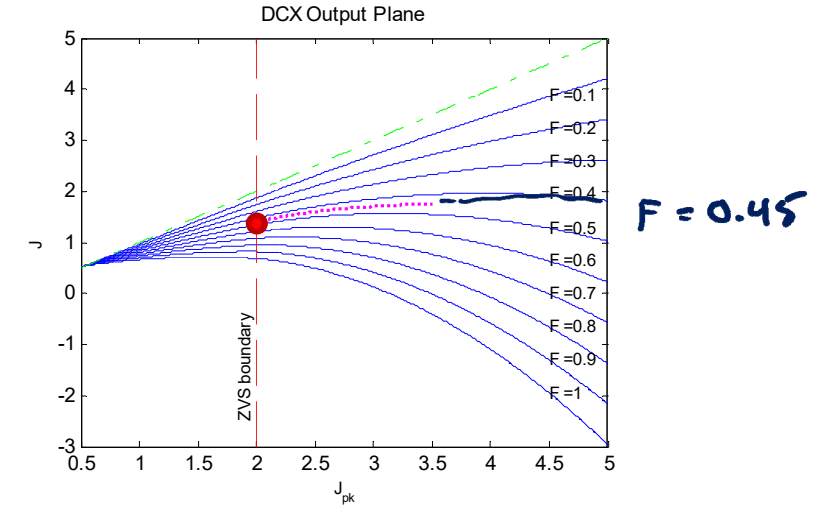
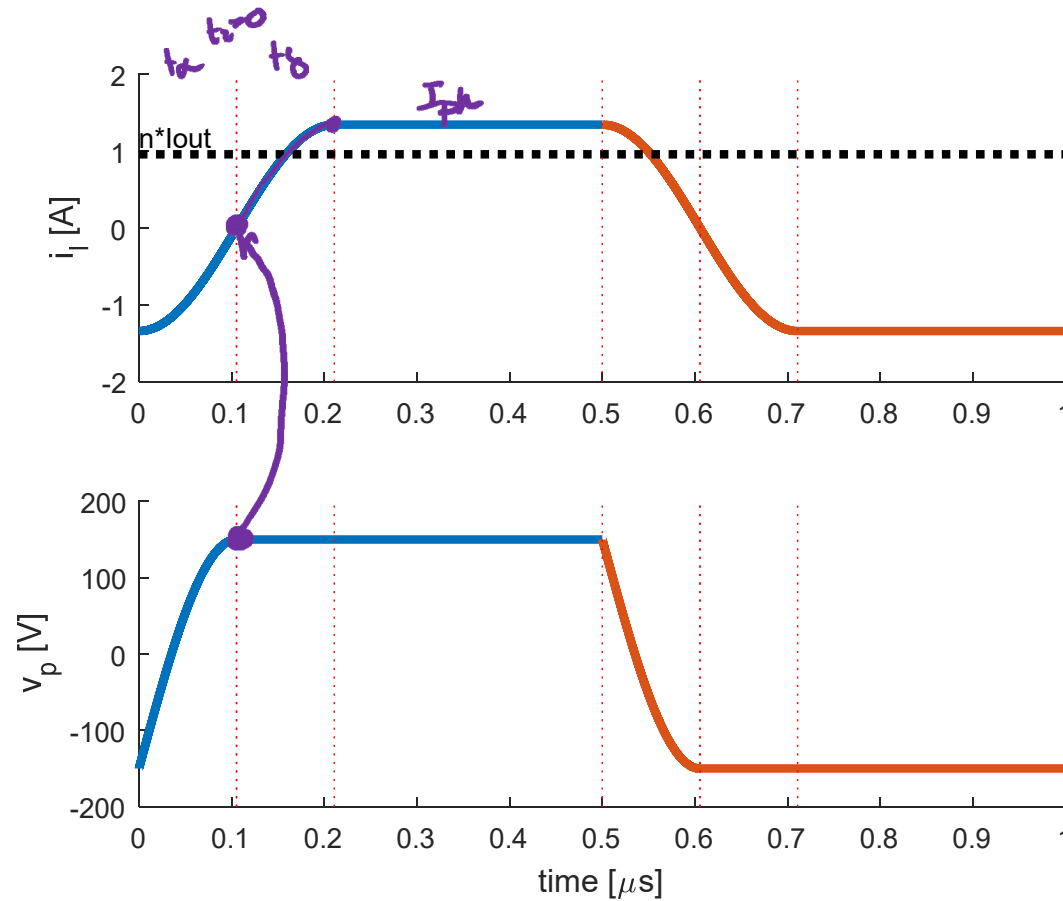
Example Waveforms

$$f_0 = 1\text{MHz} \quad V_g = 150\text{V} \quad V = 12\text{V}$$



$$L = 15\text{nH} \quad C_p = 300\text{pF} \quad C_s = \frac{C_p}{n^2}$$





Example Waveforms

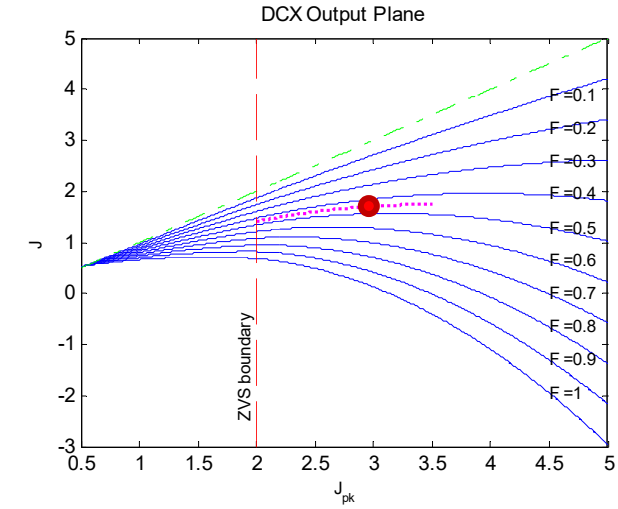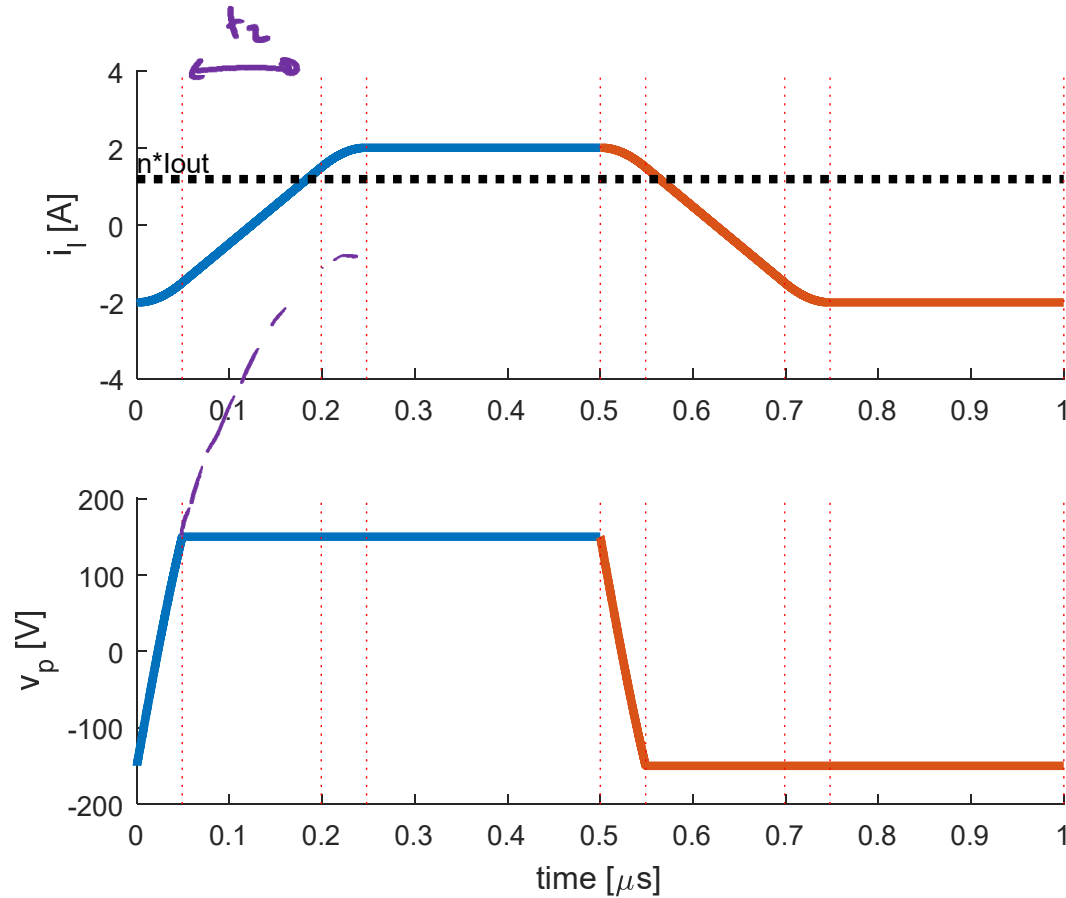



Example Waveforms

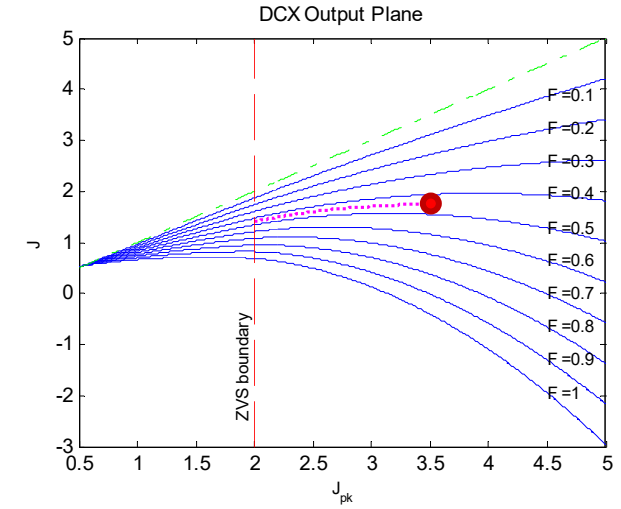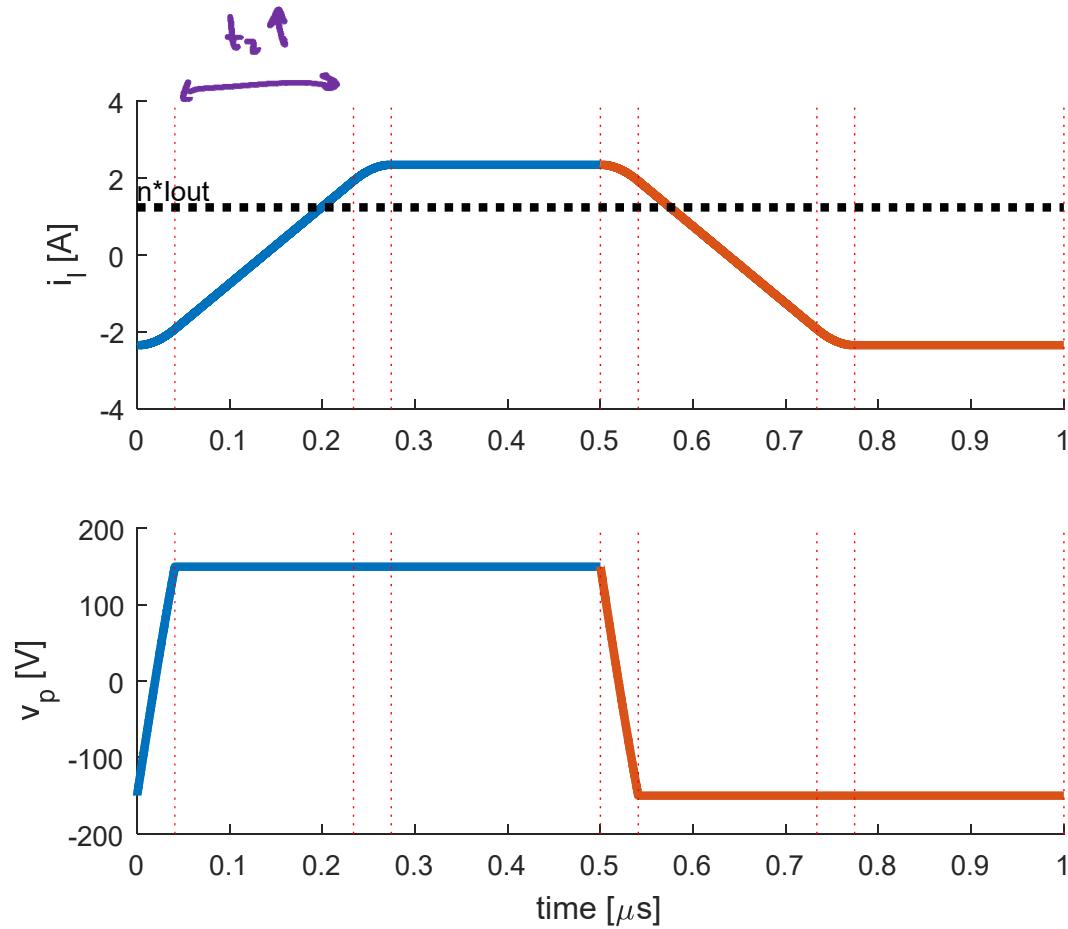


Example Waveforms

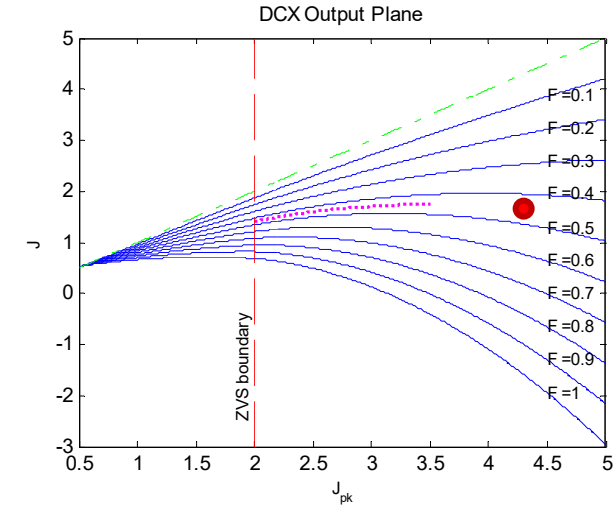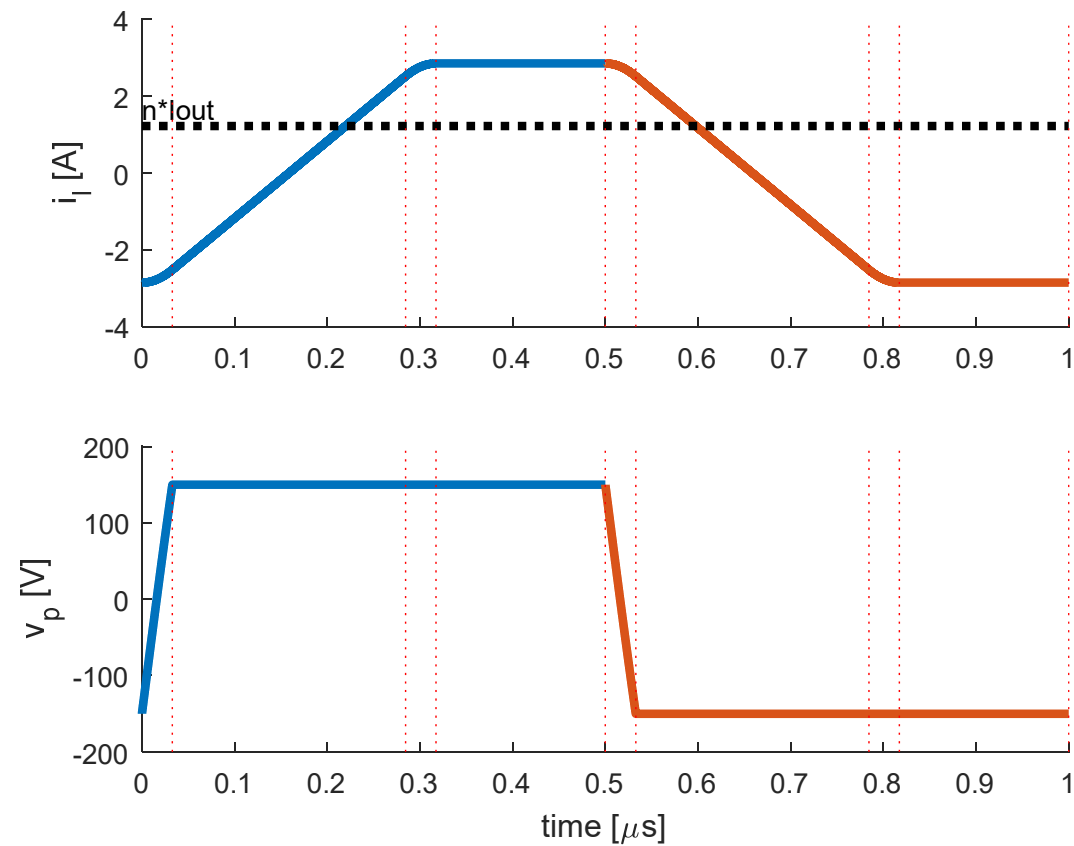


Example Waveforms

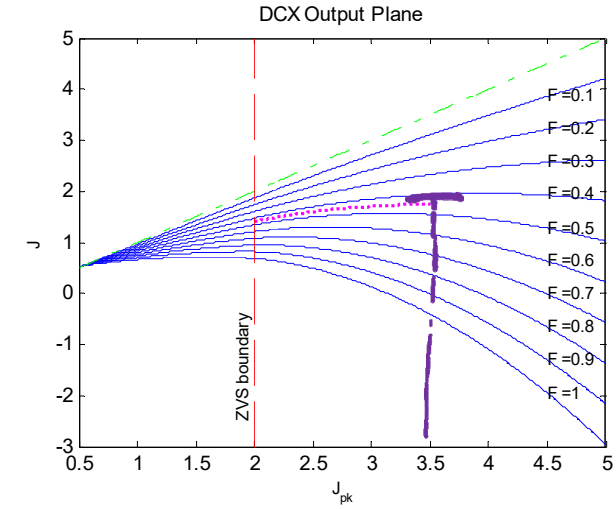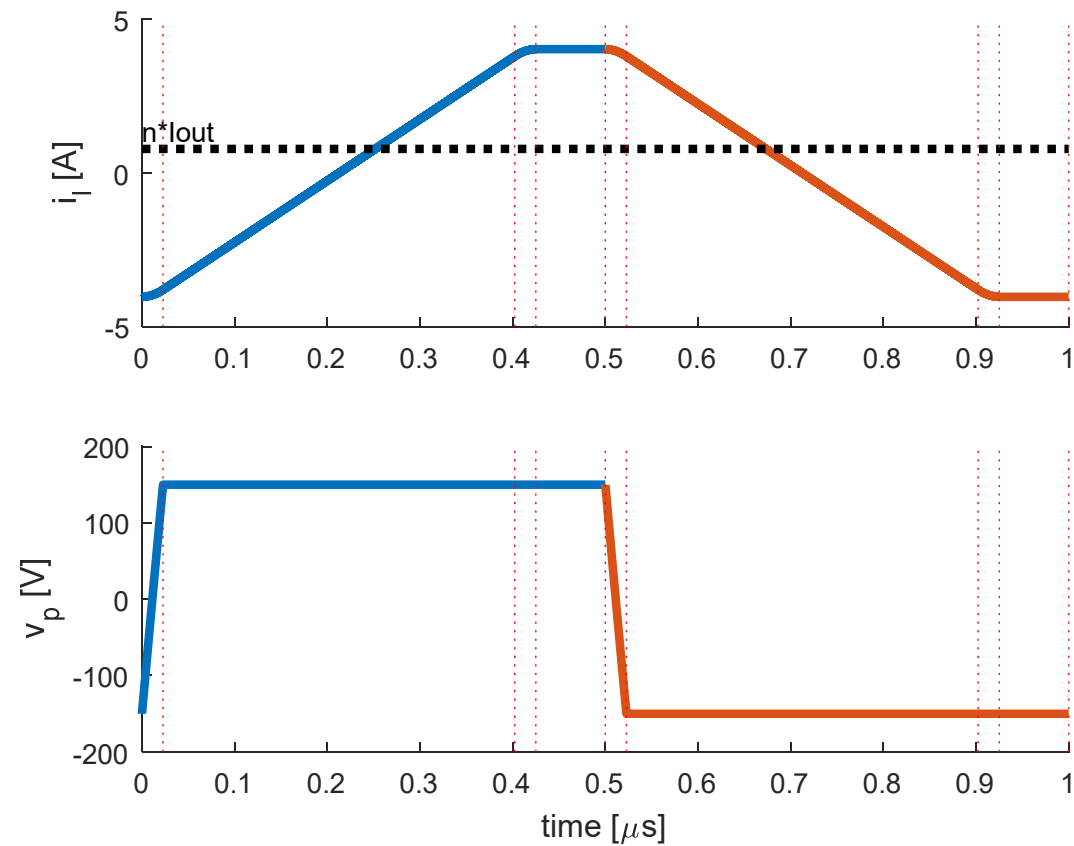


Output Current Vs. Inductance

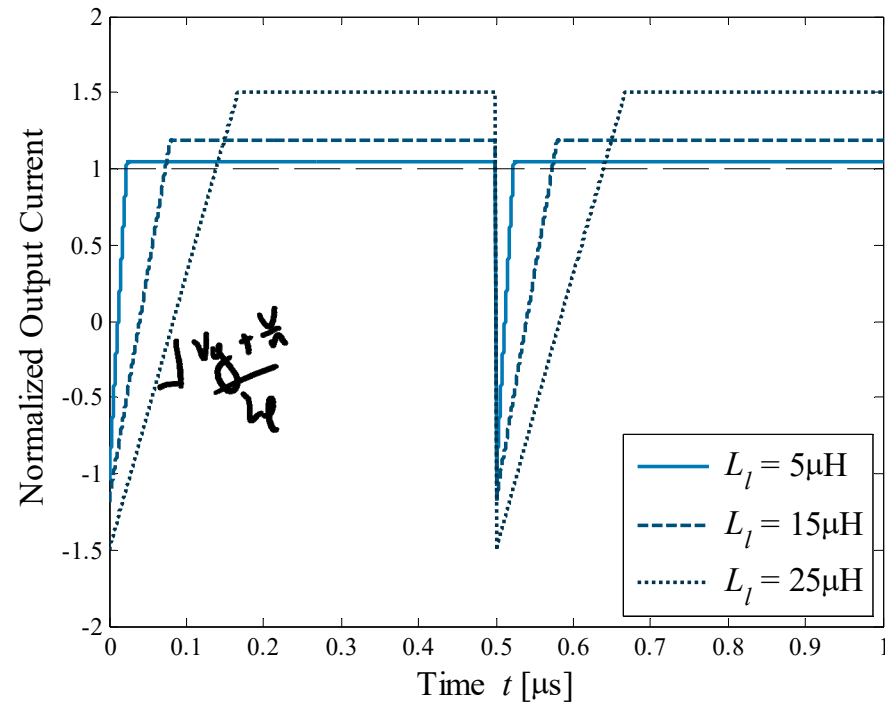

Output Current Vs. Inductance

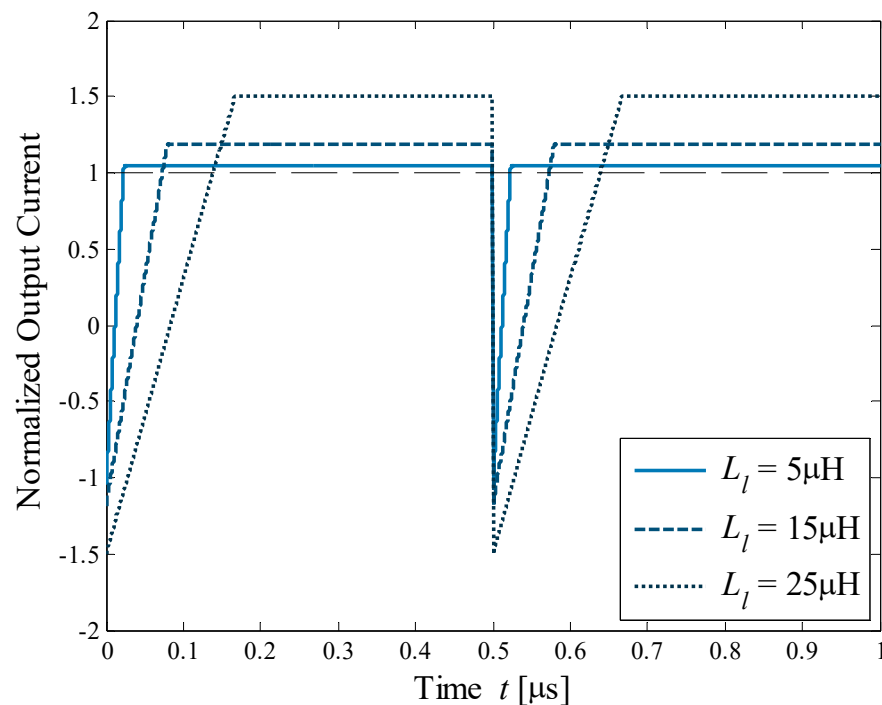

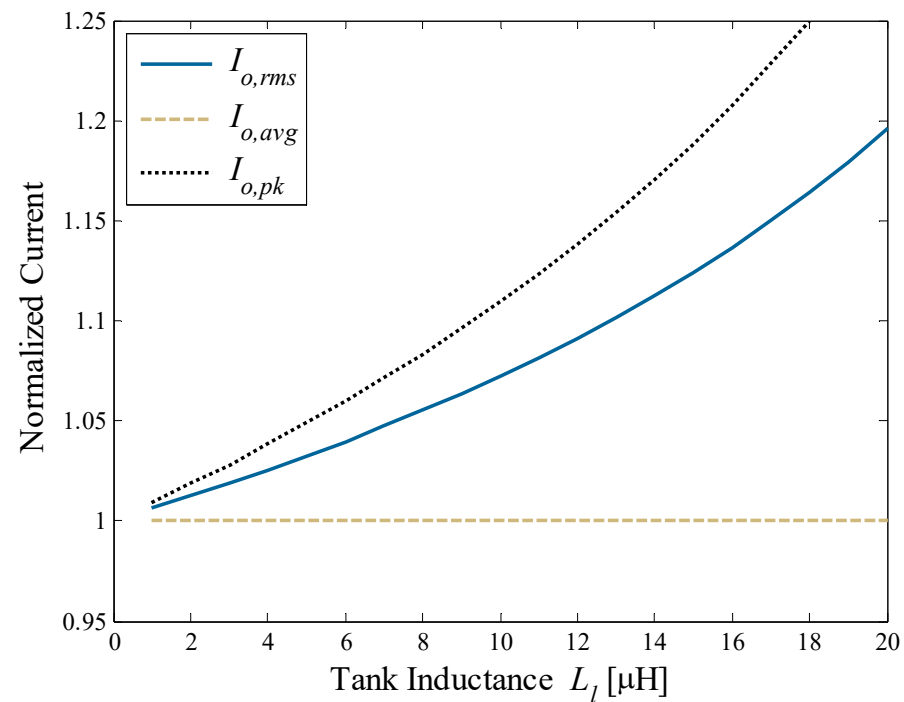$L_l \rightarrow$ small for conduction loss
 $\rightarrow$ small for max peak power




small L_l will require high resolution phase shift modulation





Constraints on Inductance

Smaller L_p means we lose ZVS
at higher powers

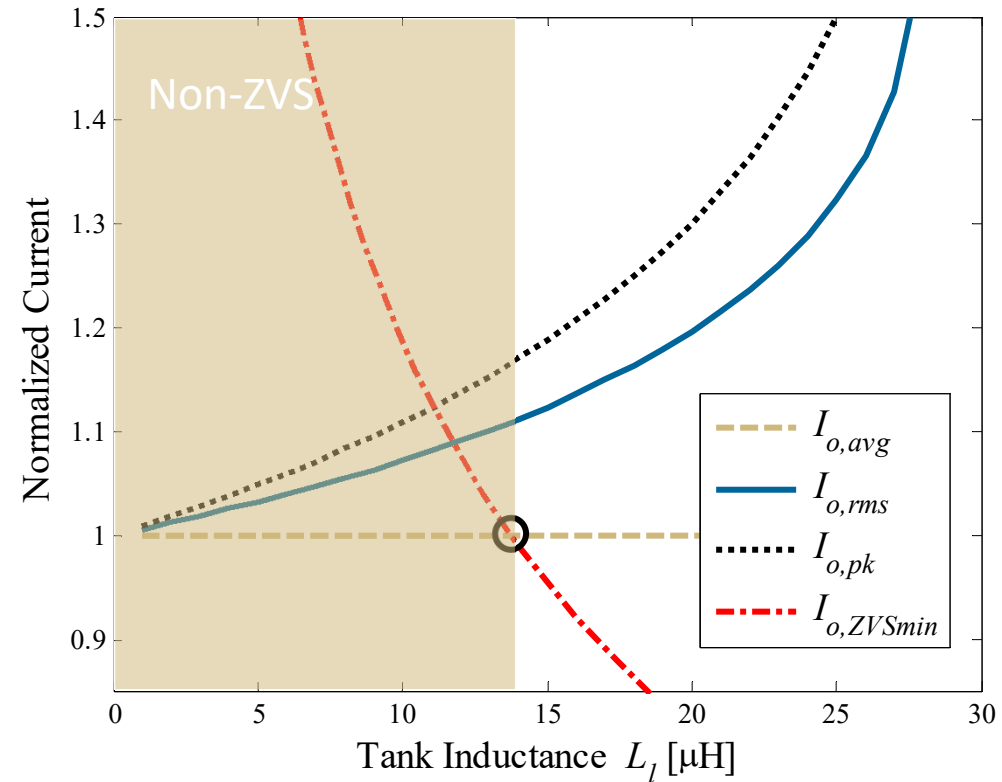Cannot keep ZVS to zero power
in this mode of operation
(Phase shift modulation)
§ (M=n)



DAB: Experimental Results

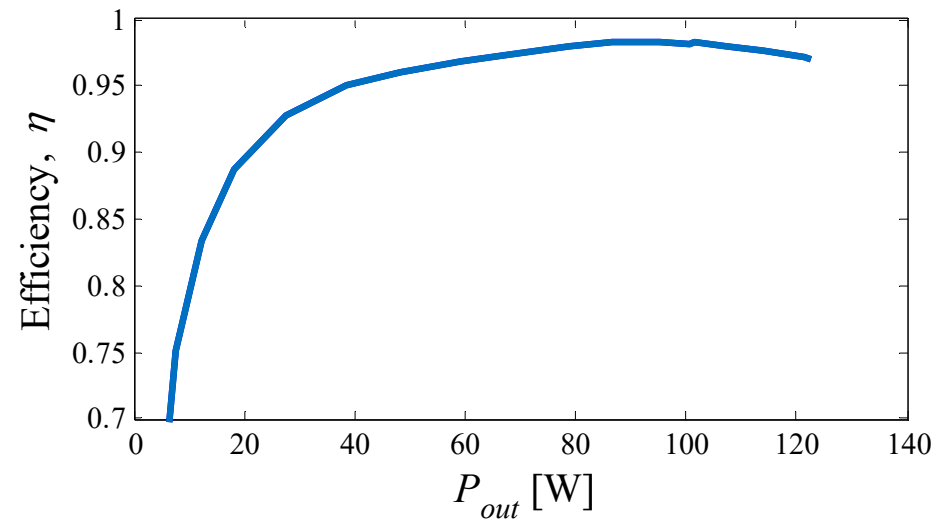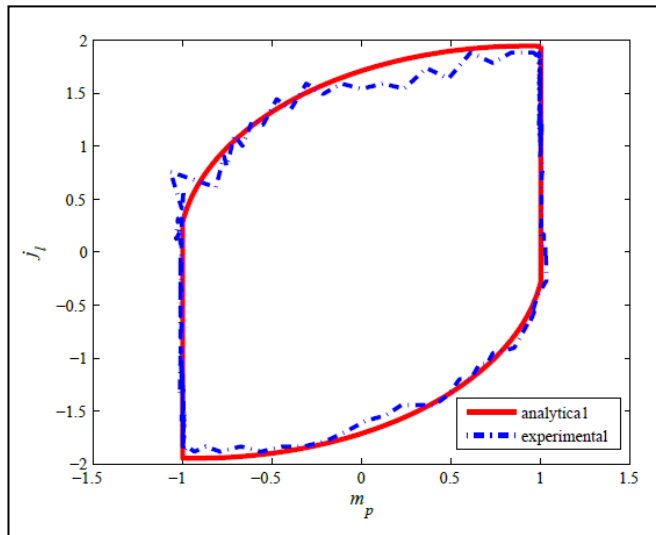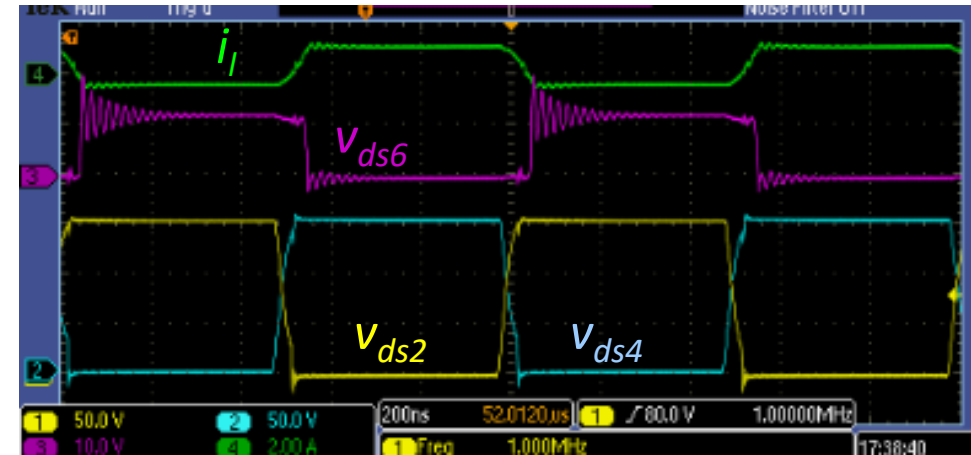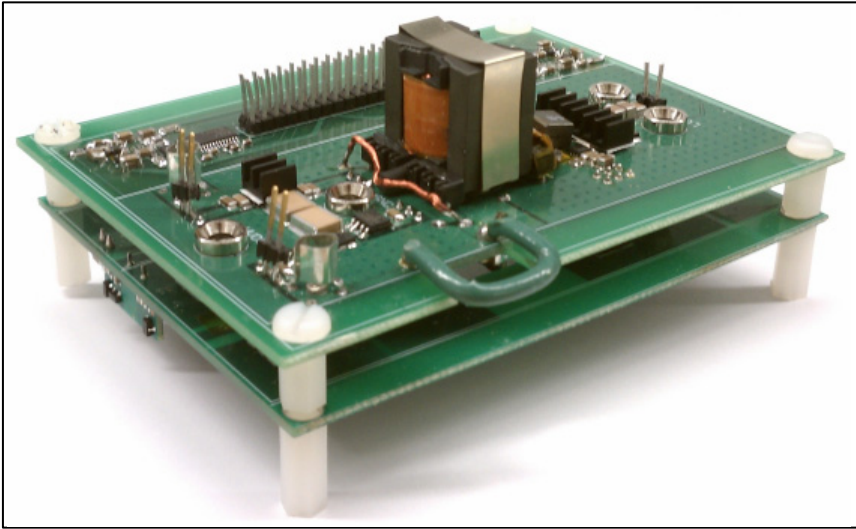

Operation with $V \neq nV_g$

