
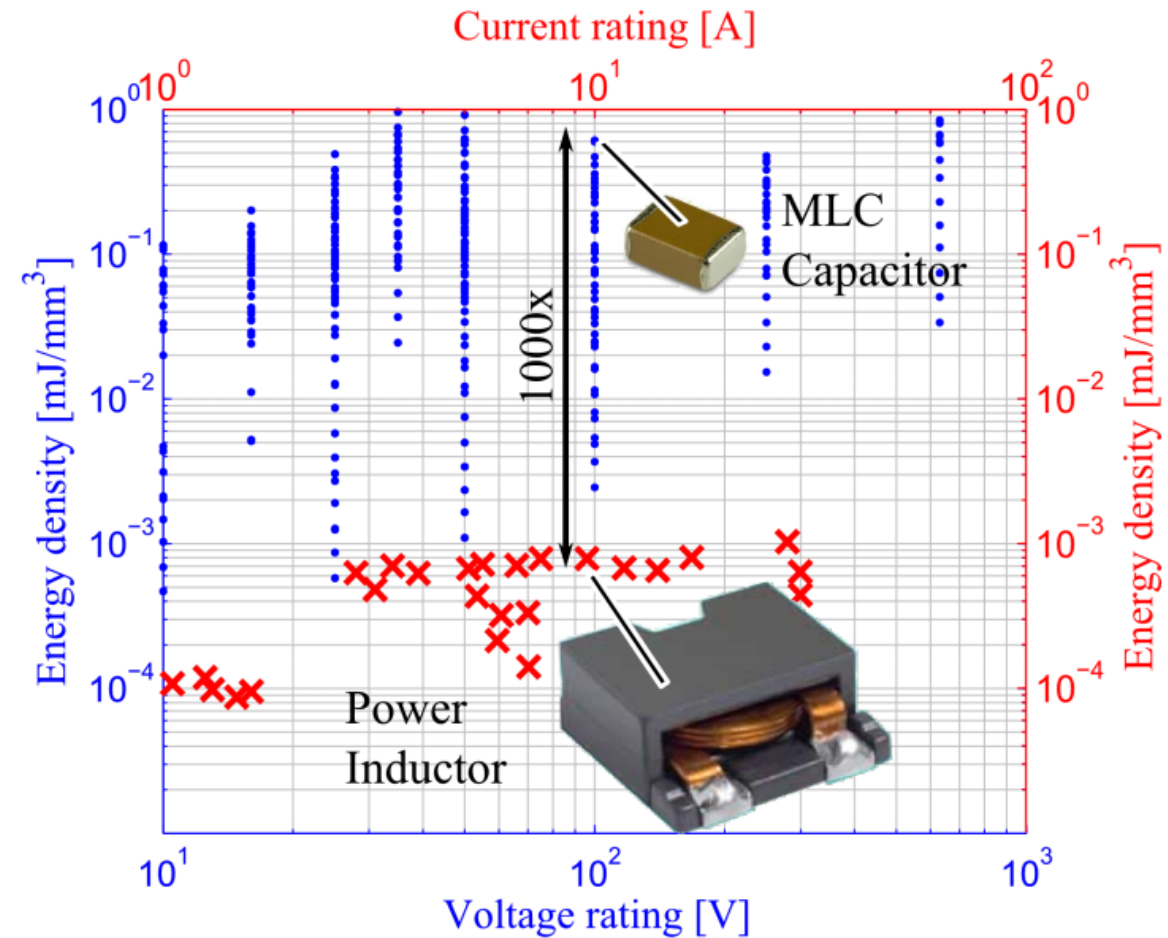


Switched Capacitor Converters

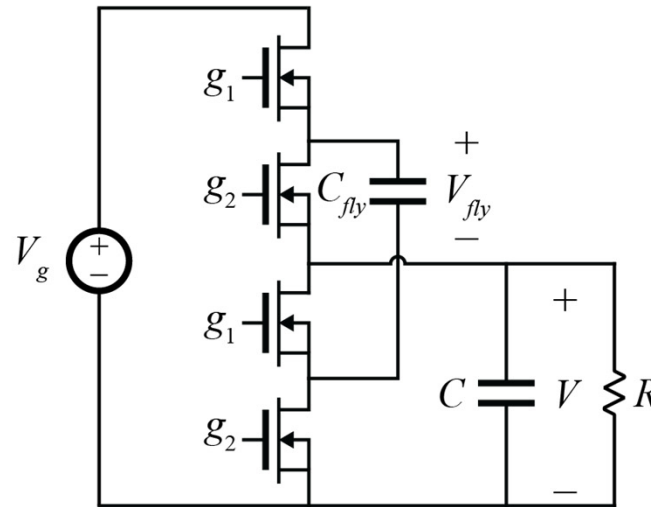

A 2:1 SC Converter



Simplified analysis

$V \approx \text{constant}$ ←

$V_{fly} \approx \text{constant}$


Assume all subinterval times are much longer than any R-C time constants w/ parasitic resistances

in ① $V + V_{fly} = V_g$

in ② $V_{fly} = V$

$$2V = V_g$$

$$\boxed{\frac{V}{V_g} = \frac{1}{2}}$$

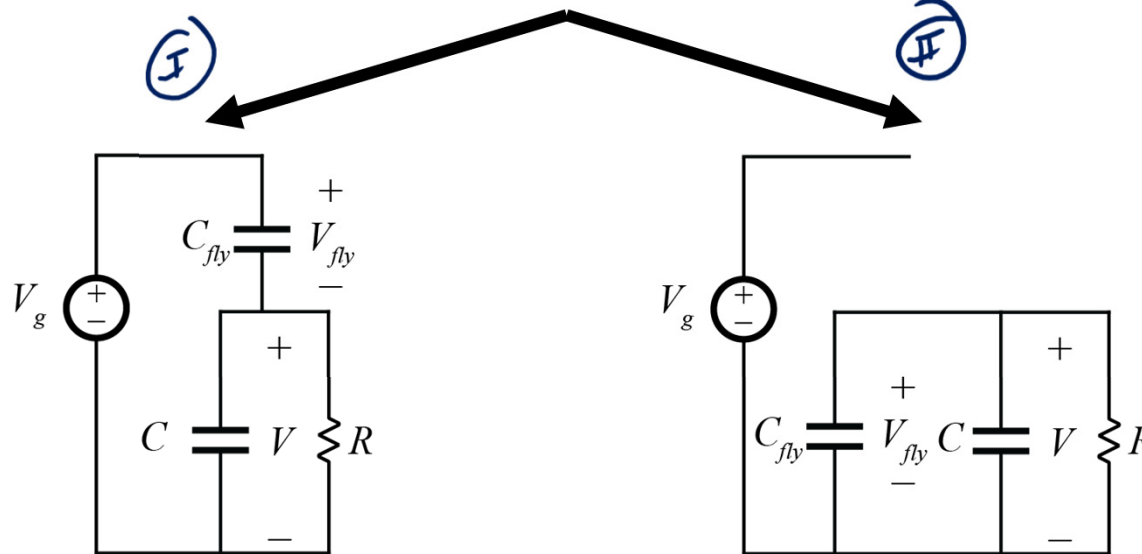


SC Converters


- Fixed conversion ratio
 - Continuous regulation impossible¹ (except linear)
 - Not lossless, even with ideal elements
 - Can be very small, fully integrated
 - Discrete caps can be smaller than inductors for comparable energy storage
 - Integrated caps are much better than on-chip inductors
 - **Resonant** versions can reduce loss
 - **Hybrid** versions can allow regulation
- } add some inductance

¹D. Wolaver, "Fundamental study of dc to dc conversion systems," dissertation, 1969

Capacitor Charging: Voltage Source

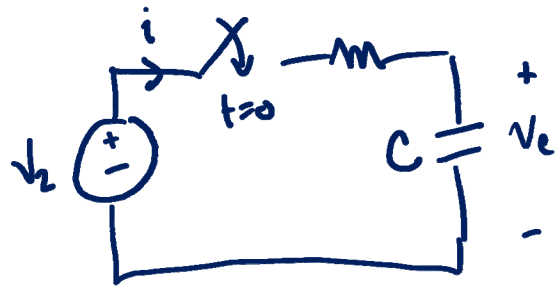

$$V_c(t \rightarrow \infty) = V_1$$

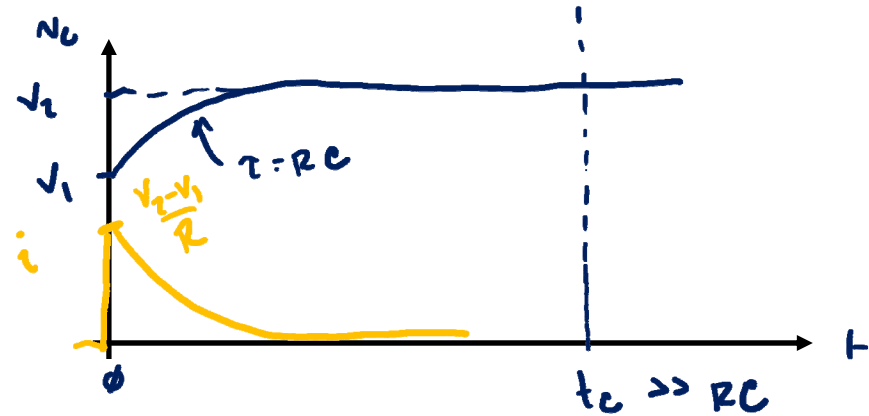

After $t_c \gg RC$

$$\Delta E_c = \frac{1}{2} C V_2^2 - \frac{1}{2} C V_1^2$$

$$\Delta E_c = \frac{1}{2} C (V_2^2 - V_1^2)$$

$$E_v = \int_0^{t_c} i \cdot V_2 dt = V_2 Q_c = V_2 C (V_2 - V_1) = E_v$$

$$E_{loss} = E_v - \Delta E_c = V_2 C (V_2 - V_1) - \frac{1}{2} C (V_2^2 - V_1^2)$$

$$= C V_2^2 - C V_2 V_1 - \frac{1}{2} C V_2^2 + \frac{1}{2} C V_1^2$$

$$= \frac{1}{2} C V_2^2 - C V_2 V_1 + \frac{1}{2} C V_1^2$$

$$= \frac{1}{2} C (V_2 - V_1)^2 = E_{loss} = \frac{1}{2} C (\Delta V_c)^2$$

$$\eta_c = \frac{\Delta E_c}{E_v} = \frac{\frac{1}{2} C (v_2^2 - v_1^2)}{v_2 C (v_2 - v_1)}$$

$$= \frac{\frac{1}{2} C v_2^2 - \frac{1}{2} C (v_2 - \Delta v_c)^2}{v_2 C \Delta v_c} =$$

$$= 1 - \frac{\cancel{\frac{1}{2} C \Delta v_c^2}}{\cancel{v_2 C \Delta v_c}}$$

$$\boxed{\eta_c = 1 - \frac{\Delta v_c}{2v_2}}$$

$$\Delta v_c = (v_2 - v_1)$$


$$v_1 = v_2 - \Delta v_c$$

$$\frac{\cancel{\frac{1}{2} C v_2^2} - \cancel{\frac{1}{2} C v_2^2} + C v_2 \Delta v_c - \frac{1}{2} C \Delta v_c^2}{v_2 C \Delta v_c}$$

if $\Delta v_c \ll v_2$, $\eta_c \rightarrow 1$

- No dependence on R
other than $t_e \gg RC$


Capacitor Charging: Current Source

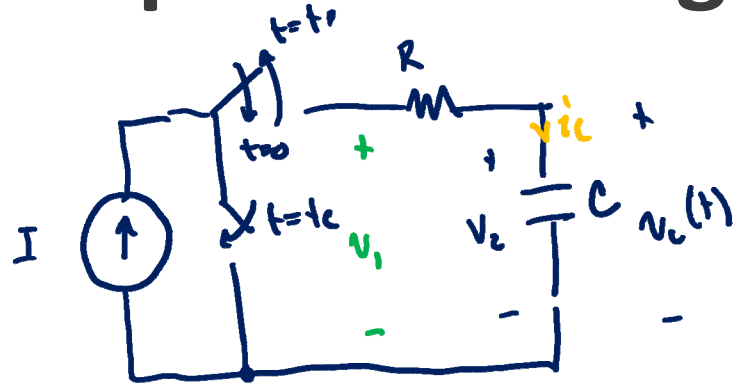

$$v_c(t \rightarrow \infty) = V_1$$

$$\frac{I}{C} t_c = V_2 - V_1$$

$$I = \frac{C(V_2 - V_1)}{t_c}$$

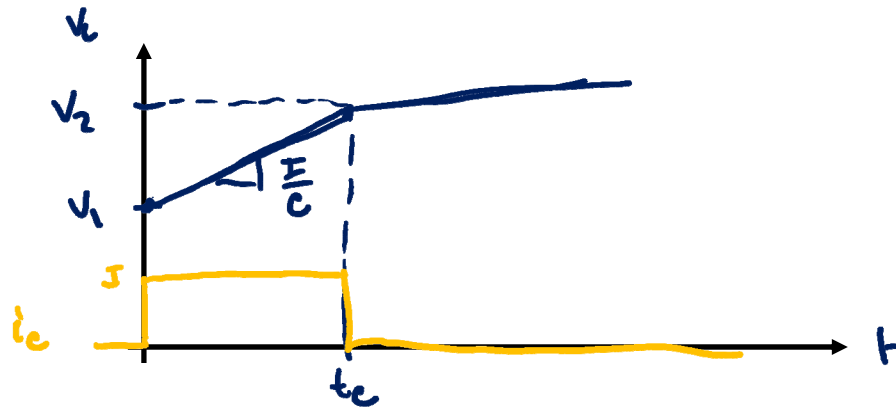

$$\Delta E_C = \frac{1}{2} C (V_2^2 - V_1^2)$$

$$E_I = \int_0^{t_c} I v_1 dt = I \int_0^{t_c} (v_c + IR) dt = \underbrace{\frac{1}{2} C (V_2^2 - V_1^2)}_{\Delta E_C} + \underbrace{I^2 R t_c}_{E_R}$$

$$= \frac{1}{2} C (V_2^2 - V_1^2) + \frac{C^2 (V_2 - V_1)^2}{t_c^2} R t_c$$

$$= \frac{1}{2} C (V_2^2 - V_1^2) + \frac{1}{2} C (V_2 - V_1)^2 \frac{2RC}{t_c}$$


scale factor
relative to
source charging

Voltage source
I - source

$$E_{krs} = \frac{1}{2} C (V_2 - V_1)^2$$
$$E_{krs} = \frac{1}{2} C (V_2 - V_1)^2 \frac{2RC}{t_c}$$

if $t_c \gg 2RC$ current source charging has known loss
if $t_c \not\gg 2RC$, unknown $\rightarrow$ voltage source charging expressions were developed for $t_c \gg RC$

Capacitor Charging: Resonant

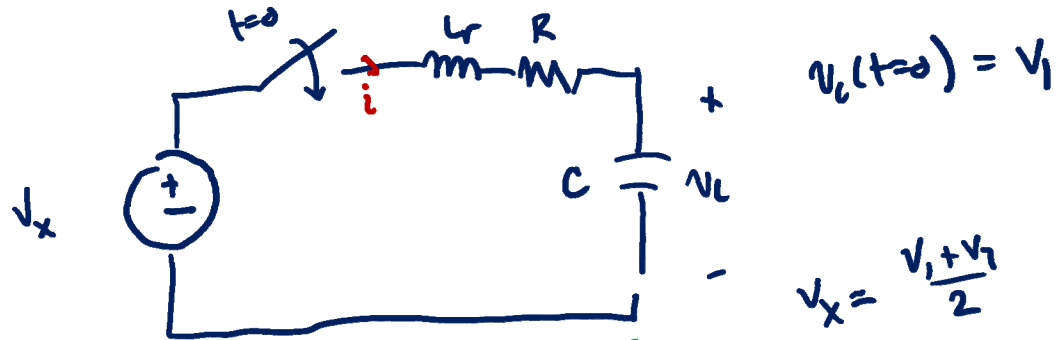


state plane: apply high- η approx
 solve waveforms w/ $R = \phi$ then calculate losses

$$\Delta E_C = \frac{1}{2} C (V_2^2 - V_1^2)$$


$$\begin{aligned}
 \bar{P}_{\text{loss}} = P_R &= I_{\text{rms}}^2 R t_c = \frac{I_{\text{ph}}^2}{2} R t_c \\
 &= \frac{1}{R_0^2} \frac{R}{2} t_c \frac{(V_2 - V_1)^2}{4} = \frac{1}{R_0^2} \frac{\pi}{\omega_0} \frac{R}{2} \frac{(V_2 - V_1)^2}{4}
 \end{aligned}$$

$$\boxed{\bar{P}_{\text{loss}} = \frac{\pi R}{4 R_0} \frac{1}{2} C (V_2 - V_1)^2}$$

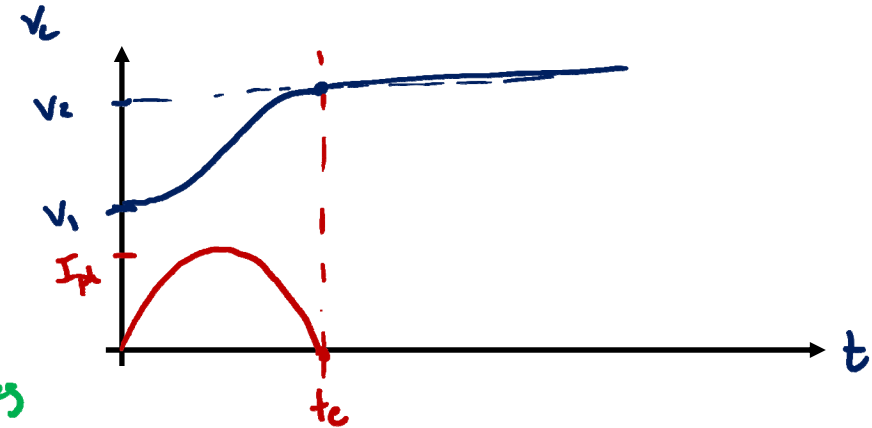if $\frac{R}{R_0} = \frac{1}{Q}$ is small, higher η then v-src charging



state plane:

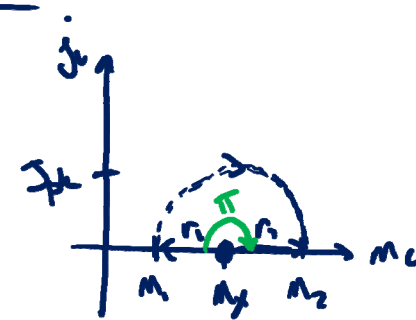

$$\begin{aligned}
 S_{\text{ph}} = r_1 &= M_x - M_1 = M_2 - M_x \\
 &= \frac{M_2 - M_1}{2}
 \end{aligned}$$

$$I_{\text{ph}} = S_{\text{ph}} \frac{V_{\text{base}}}{R_0}$$

$$I_{\text{ph}} = \frac{1}{R_0} \frac{V_2 - V_1}{2}$$

$$R_0 \omega_0 = \sqrt{\frac{L}{C}} \frac{1}{\sqrt{L/C}} = \frac{1}{C} \quad t_c = \frac{\pi}{\omega_0}$$