

## **Switched Capacitor Converters**

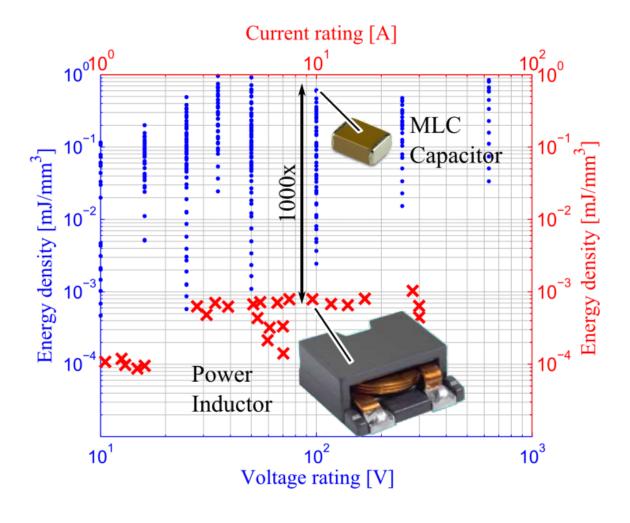

### A 2:1 SC Converter

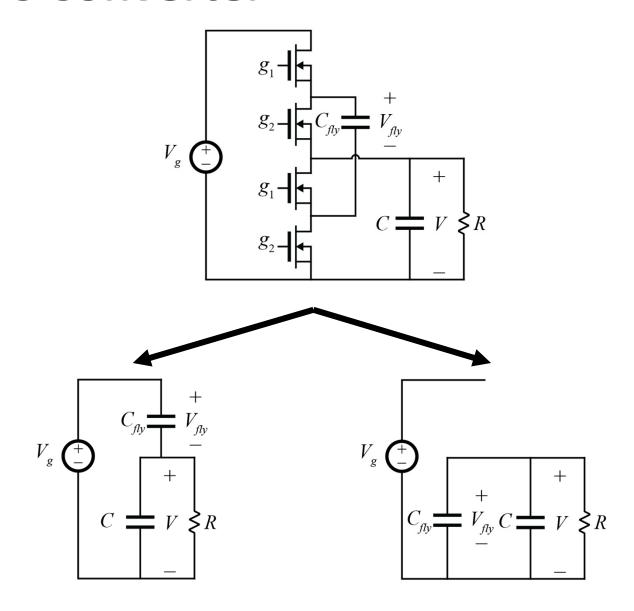

#### **SC Converters**

- Fixed conversion ratio
  - Continuous regulation impossible<sup>1</sup> (except linear)
- Not lossless, even with ideal elements
- Can be very small, fully integrated

- Resonant versions can reduce loss
- Hybrid versions can allow regulation

## **Capacitor Charging: Voltage Source**



# **Capacitor Charging: Current Source**



# **Capacitor Charging: Resonant**



# **Capacitor Charging: Cap-Cap**

