

$$E_{\text{loss}} = \frac{\pi}{4} \frac{R}{R_0} \frac{1}{2} C (V_2 - V_1)^2$$

$\frac{R}{R_0} \rightarrow$  High Q resonance will be more efficient than V-src charging

$$\frac{1}{R_0} = \omega_0 C, \quad \omega_0 = \frac{\pi}{t_c}$$


$$E_{\text{loss}} = \frac{\pi^2}{4} \frac{RC}{t_c} \frac{1}{2} C (V_2 - V_1)^2$$

$\hookrightarrow$  if  $t_c \gg RC$ , less loss than V-src charging  
if  $t_c \not\gg RC$ , V-src charging equations don't apply

Also may violate high- $Q$  approx  
in resonant charging


$$\frac{\pi^2}{4} \approx 2.5$$

# Capacitor Charging: Cap-Cap

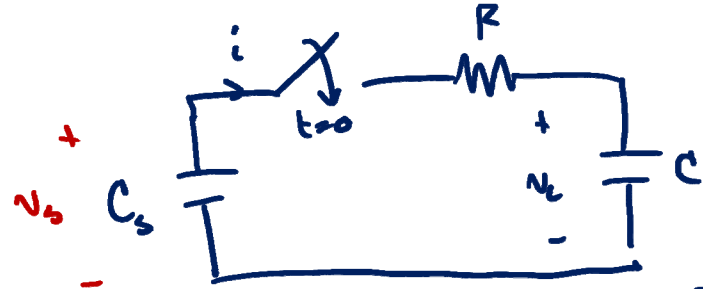

$$v_s(t=0) = V_3$$

$$v_c(t \rightarrow \infty) = V_1$$

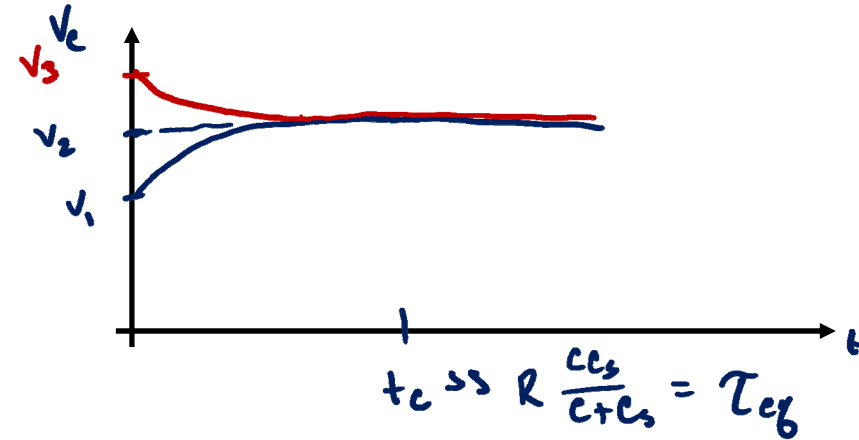

$$\text{since } |i_s| = |i_c| = |i| = Q_s = Q_c = Q$$

$$V_3 C_s + V_1 C = V_2 (C_s + C)$$

$$V_3 = \frac{V_2 (C_s + C) - V_1 C}{C_s} = \frac{C}{C_s} (V_2 - V_1) + V_2$$

$$\Delta E_c = \frac{1}{2} C (V_2^2 - V_1^2)$$

$$\Delta E_s = \frac{1}{2} C_s (V_3^2 - V_2^2) = \frac{1}{2} C_s \left[ \left( \frac{C}{C_s} \right)^2 (V_2 - V_1)^2 + \cancel{V_2^2} + 2 \frac{C}{C_s} V_2 (V_2 - V_1) - \cancel{V_1^2} \right]$$

$$= \frac{1}{2} C \left[ \left( \frac{C}{C_s} \right) (V_2 - V_1)^2 + 2 V_2 (V_2 - V_1) \right]$$

$$E_{\text{loss}} = \Delta E_s - \Delta E_c = \frac{1}{2} C \left[ \left( \frac{C}{C_s} \right) (V_2 - V_1)^2 + 2 V_2 (V_2 - V_1) - \underbrace{V_2^2 - 2 V_2 V_1 + V_1^2}_{V_2^2 - 2 V_2 V_1 + V_1^2 = (V_2 - V_1)^2} \right] = \boxed{\frac{1}{2} C \left( \frac{C}{C_s} + 1 \right) (V_2 - V_1)^2 = E_{\text{loss}}}$$

$$\underbrace{\frac{1}{2}C(V_2-V_1)^2}_{\text{same as V-src charging}} \underbrace{\left(1 + \frac{C}{C_s}\right)}_{\text{if } C_s \gg C, \text{ same as V-src charging}}$$

same as V-src  
charging

if  $C_s \gg C$ , same as V-src charging

if  $C_s \not\gg C$ , higher loss than V-src charging

if  $C = C_s \rightarrow 2\times$  loss of V-src charging

# Comparison of Capacitor Charging

for C charging from  $V_1$  to  $V_2$  in time  $t_c$

Voltage Source

$$\frac{P_{loss}}{\frac{1}{2} C (V_2 - V_1)^2}$$

Assumptions

$$t_c \gg RC = \tau$$

Current Source

$$\frac{1}{2} C (V_2 - V_1)^2 \frac{2RC}{t_c}$$

X

Resonant

$$\frac{1}{2} C (V_2 - V_1)^2 \frac{\pi^2 RC}{4t}$$

High-Q resonance so state plane solution applies  $R_0 \gg R$

or

$$\frac{1}{2} C (V_2 - V_1)^2 \frac{R}{R_0} \frac{\pi}{4}$$





Cap - Cap

$$\frac{1}{2} C (V_2 - V_1)^2 \left( \frac{C}{C_s} + 1 \right)$$

$$t_c \gg R \left( \frac{CC_s}{C + C_s} \right) = \tau_{eq}$$
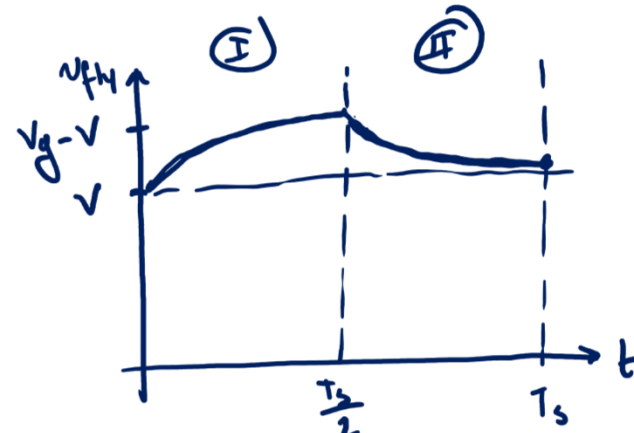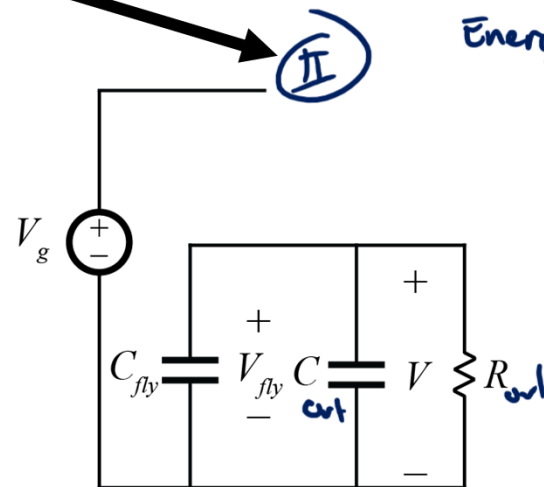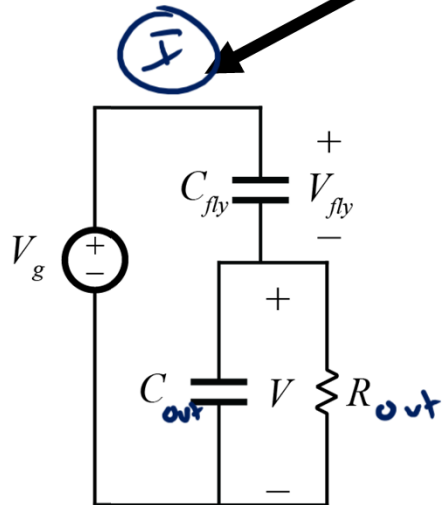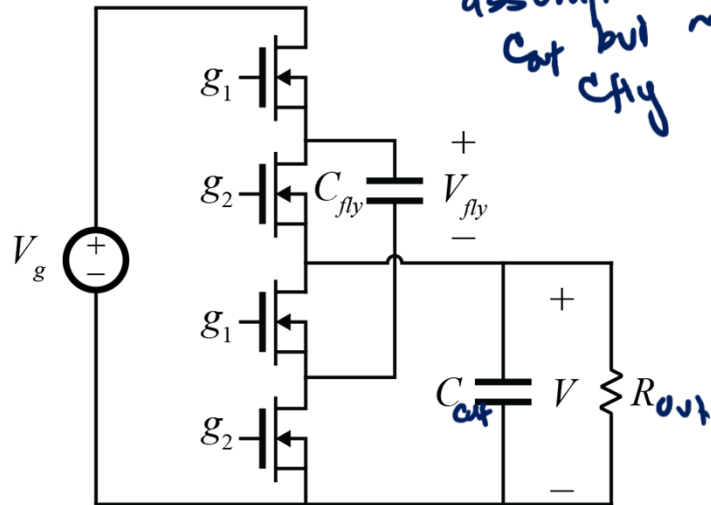
# 2:1 SC Revisited

still apply  
small-ripple  
assumption  
on  
 $C_{out}$  but  
not  
 $C_{fly}$



Operating with  $t_c \gg RC_{th}$ ,  $t_c = \frac{T_s}{2} \gg RC_{th}$

$R \rightarrow$  resistance in charging path

$$R = 2 \times r_{on} + ESR_c + R_{par}$$

Energy loss =

$$\begin{cases} \text{①} & \frac{1}{2} C_{th} (V_g - V - V)^2 \\ \text{②} & \frac{1}{2} C_{th} (V_g - V - V)^2 \end{cases}$$

$$E_{loss} = C_{th} (V_g - 2V)^2$$


$$P_{loss} = C_{fly} (V_g - 2V)^2 f_s$$

$$P_{in} = V_g C_{fly} (V_g - 2V) f_s$$

# Equivalent Circuit Model

$$P_{loss} = C_{th} (V_g - 2V)^2 f_s$$

$$P_{in} = V_g C_{th} (V_g - 2V) f_s$$

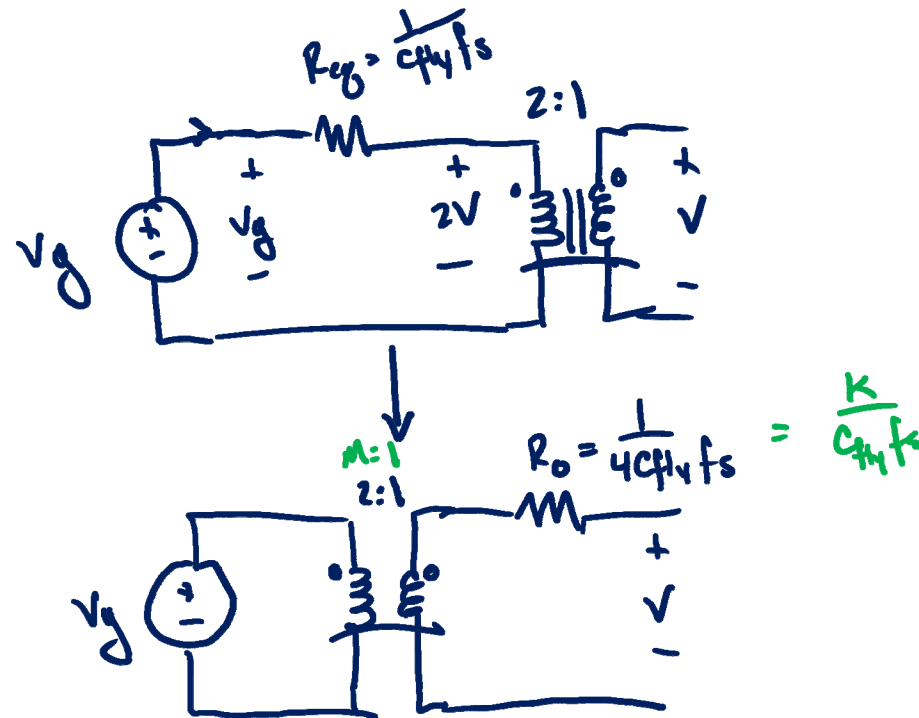

- No regulation possible except losses
- For high  $\eta$ , want small  $R_o$   
 $\rightarrow \uparrow C_{th} \text{ \& \& } \uparrow f_s$
- For  $t_c \gg R C_{th}$
- as long as above is true,  
 $R > 2r_{on} + 0.5 R_c + R_{par}$   
 doesn't affect  $\eta$