
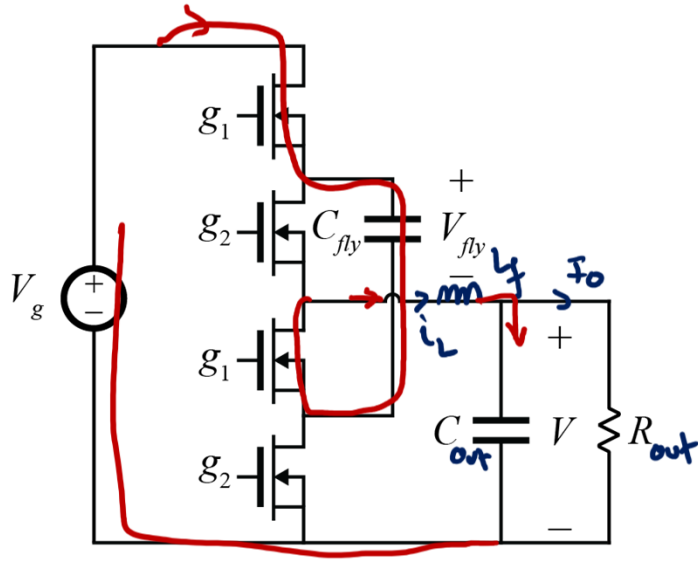


2:1 – Current Loaded

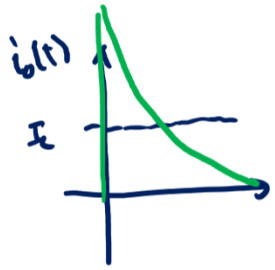

- 2:1 SC converter with current load
- 3-level buck converter
- Flying capacitor multilevel (FMC) buck converter

$L_f \rightarrow$ large, filter inductor, $i_L \approx I_L$

from previous results

$$E_{loss} = \begin{cases} \textcircled{I} & \frac{1}{2} C_{fly} (V_2 - V_1)^2 \frac{2RC_{fly}}{t_c} \\ \textcircled{II} & \frac{1}{2} C_{fly} (V_2 - V_1)^2 \frac{2RC_{fly}}{t_c} \end{cases}$$

$R = 2 \times r_{on} + ESR_{C_{fly}} + R_L + R_{par} + ESR_{C_{out}}$

$t_c = \frac{T_s}{2}$

$$E_{loss} = \underbrace{C_{fly}^2 (V_2 - V_1)^2}_{C_{fly} \Delta V_L = \Delta Q_{fly} = I_L \frac{T_s}{2}} \frac{4R}{T_s}$$

$$C_{fly} (V_2 - V_1) = C_{fly} \Delta V_L = \Delta Q_{fly} = I_L \frac{T_s}{2}$$



$$E_{loss} = \left(I_L \frac{T_s}{2} \right)^2 \frac{4R}{T_s}$$

$$= I_L^2 R T_s$$

$$\boxed{P_{loss} = I_L^2 R}$$

$$I_L = I_o$$

2:1 – Resonant Implementation

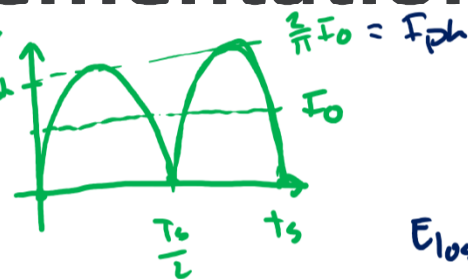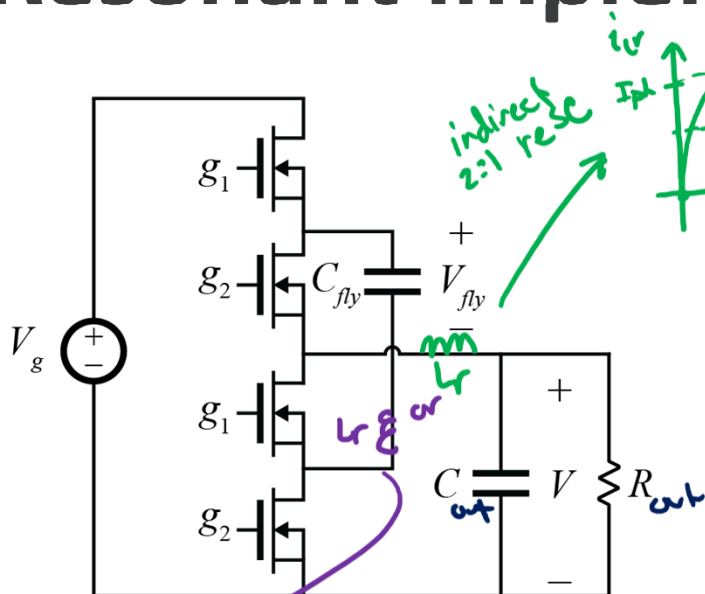

$$E_{loss} = C_{fly} (V_2 - V_1)^2 \frac{\pi^2 R_{eff}}{4 t_e}, \quad t_e = \frac{T_s}{2}$$


$$C_{fly} (V_2 - V_1) = \Delta Q_{fly} = I_0 \frac{T_s}{2}$$

$$P_{loss} = E_{loss} f_s = \left(I_0 \frac{T_s}{2} \right)^2 \frac{\pi^2 R}{4 \frac{T_s}{2}}$$


$$P_{loss} = \left(I_0 \frac{1}{T_s} \frac{\pi}{2} \right)^2 R$$

$$P_{loss} = I_{L,rms}^2 R$$
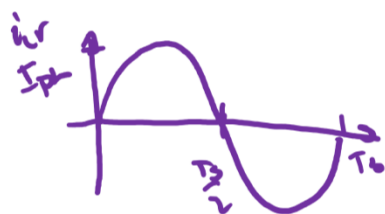
$$R = Z_{ron} + R_l + t_s R_{eff} + \dots$$




Slow and Fast Switching Limits

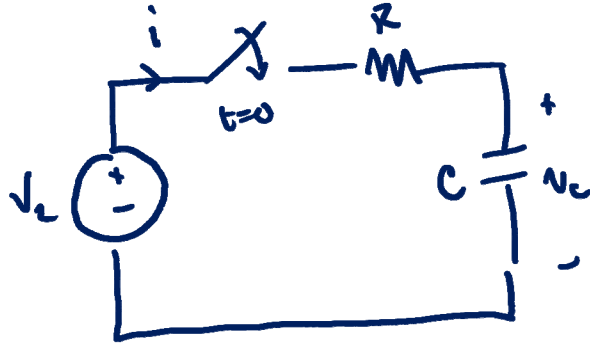

$$V_c(t=0) = V_1$$

$$V_c(t) = V_1 + (V_2 - V_1) \left(1 - e^{-\frac{t}{RC}}\right)$$

t_c/τ	$\frac{\Delta V_c}{V_2 - V_1}$
∞	100%
3	95%
1	63%
$1/2$	39%
$1/10$	9.5%

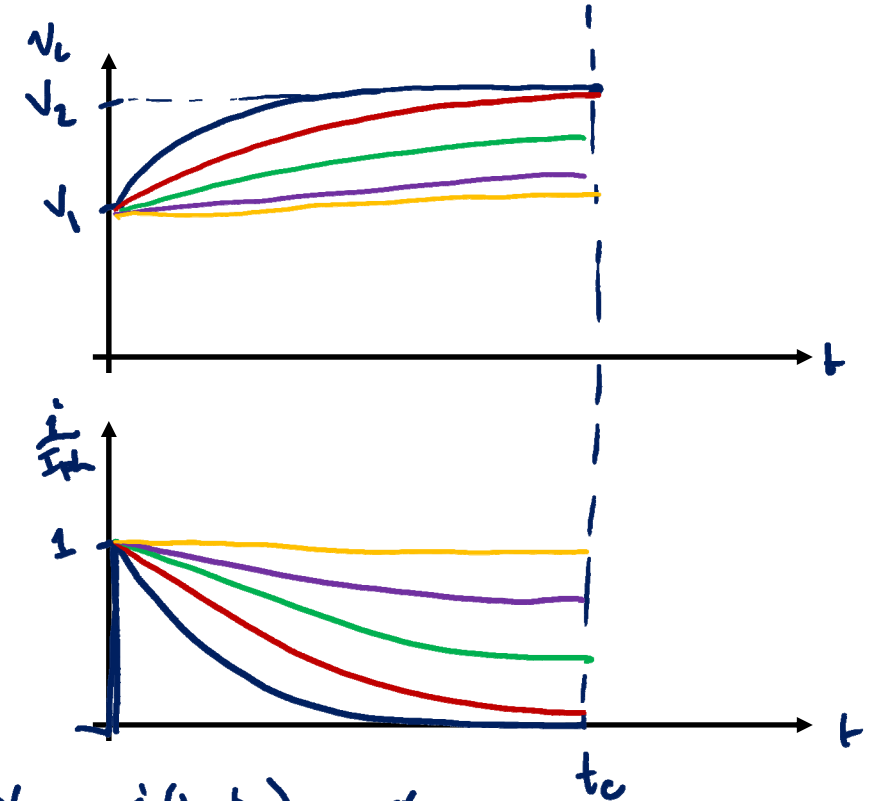

$$I_{pk} = \frac{V_2 - V_1}{R}$$

if $t_c \gg \tau \rightarrow V_c(t=t_c) = V_2$ $i(t=t_c) \rightarrow 0$
slow switching limit (SSL)


if $t_c \ll \tau \rightarrow V_c(t=t_c) < V_2$ $i(t=t_c) > 0$
Fast switching limit (FSL)

2:1 SC – FSL Model

in FSL, $t_c \ll \tau = RC$


$$\begin{aligned}
 P_{out} &= \frac{1}{T_s} \int_0^{T_s} V \cdot i_o(t) dt \\
 &= V \cdot \frac{1}{T_s} \left[\overset{\textcircled{I}}{\frac{V_g - \cancel{V_{th}} - V}{R} \frac{T_s}{2}} + \overset{\textcircled{II}}{\frac{\cancel{V_{th}} - V}{R} \frac{T_s}{2}} \right] \\
 &= V \cdot \frac{1}{T_s} \left[\frac{V_g - 2V}{R} \frac{T_s}{2} \right]
 \end{aligned}$$
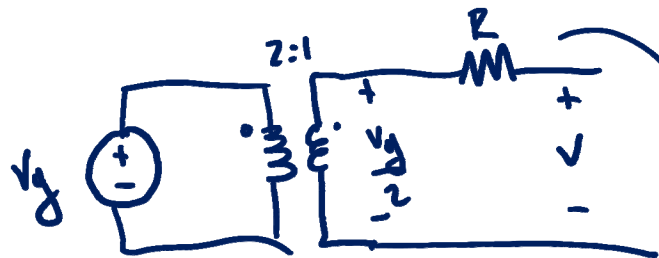
$$P_{out} = V \cdot \frac{\frac{V_g}{2} - V}{R}$$




$$R = 2 \times r_{on} + ESR_c + \dots$$
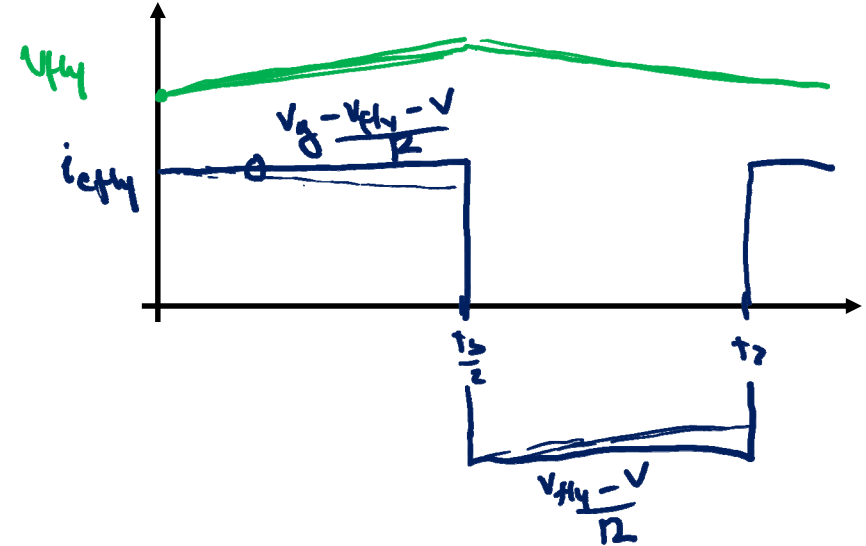
$$R = \begin{cases} \frac{1}{4Cf_{sw}} & \text{SSL } (t_c \gg \tau) \\ Z_{ron} + ESR_c + R_{par} & \text{FSL } (t_c \ll \tau) \end{cases}$$



SC Output Resistance

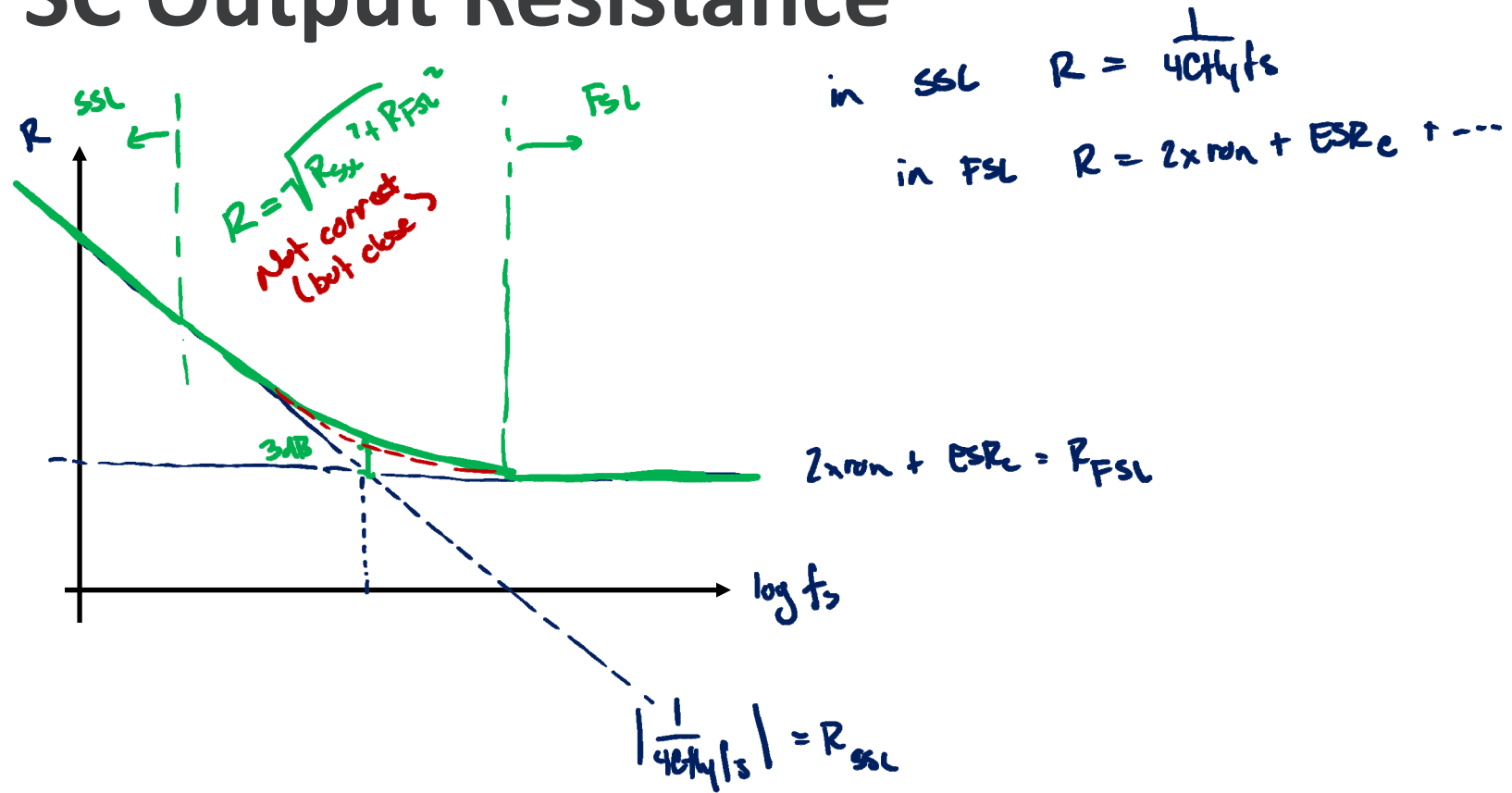

$$R = \frac{1}{4Cf_s}$$

$$RCf_s = \tau = \frac{T_s}{4} = \frac{t_c}{2}$$