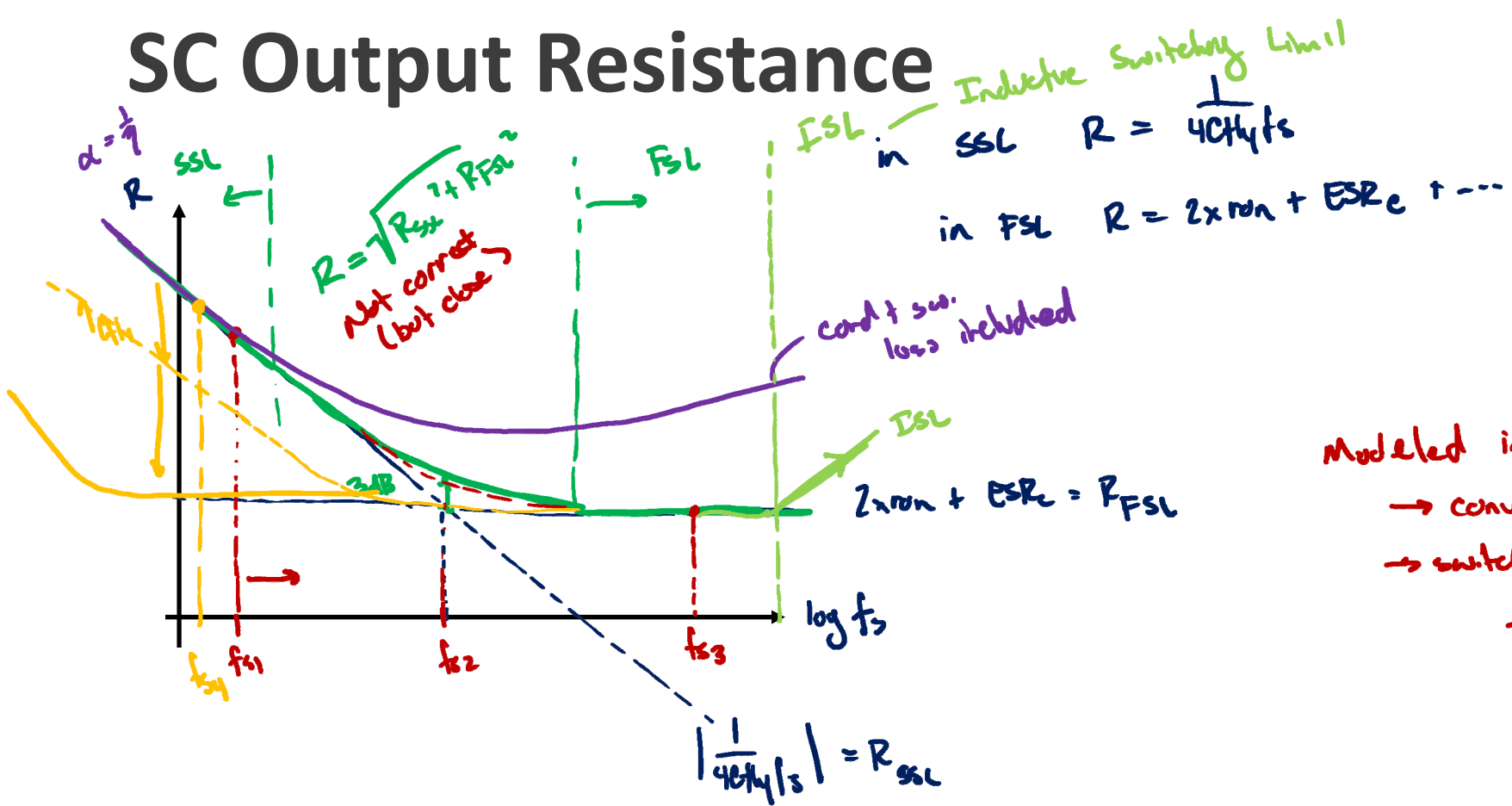


SC Output Resistance




Modeled in this is 'charge sharing' losses

- converter conduction losses
- switching losses not included
- No overlap loss (per previous analysis)
- No clamped inductive switching
- Cross losses of all FETs


$$R = \frac{1}{4Cf_s}$$

$$RCf_s = \tau = \frac{T_s}{4} = \frac{t_c}{2}$$

SC Converter Topologies (step-up)


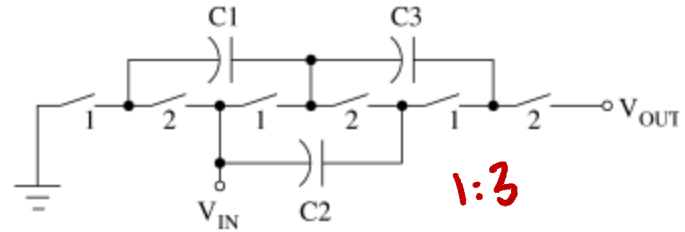


a) Ladder

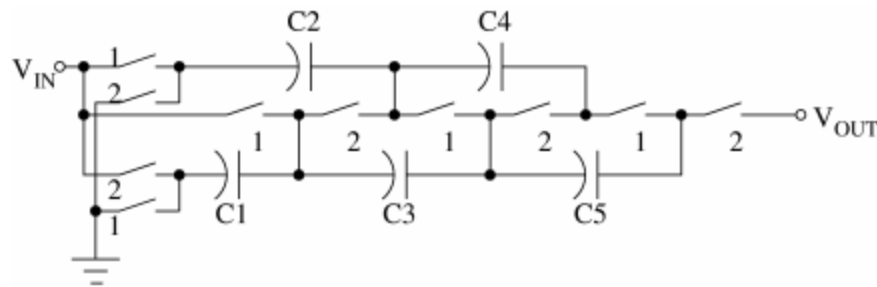


c) Fibonacci

b) Dickson Charge Pump

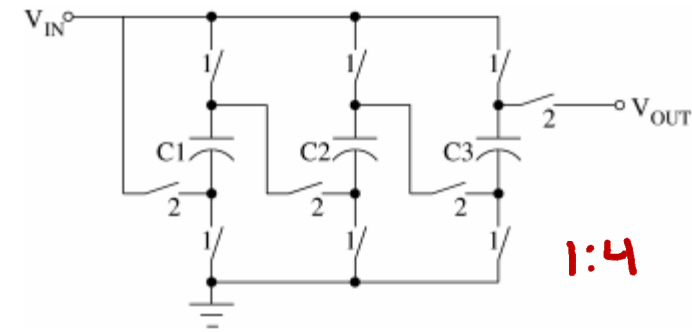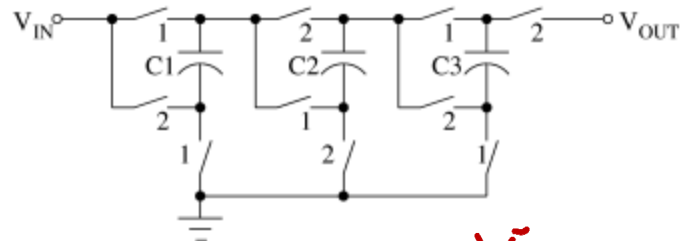

d) Series-Parallel

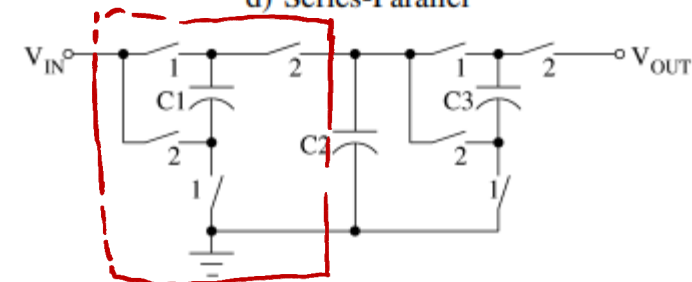


e) Doubler

Dickson Converter (step-down)

C_5 in series between V_g & V_{out}

in(I)

in(II)

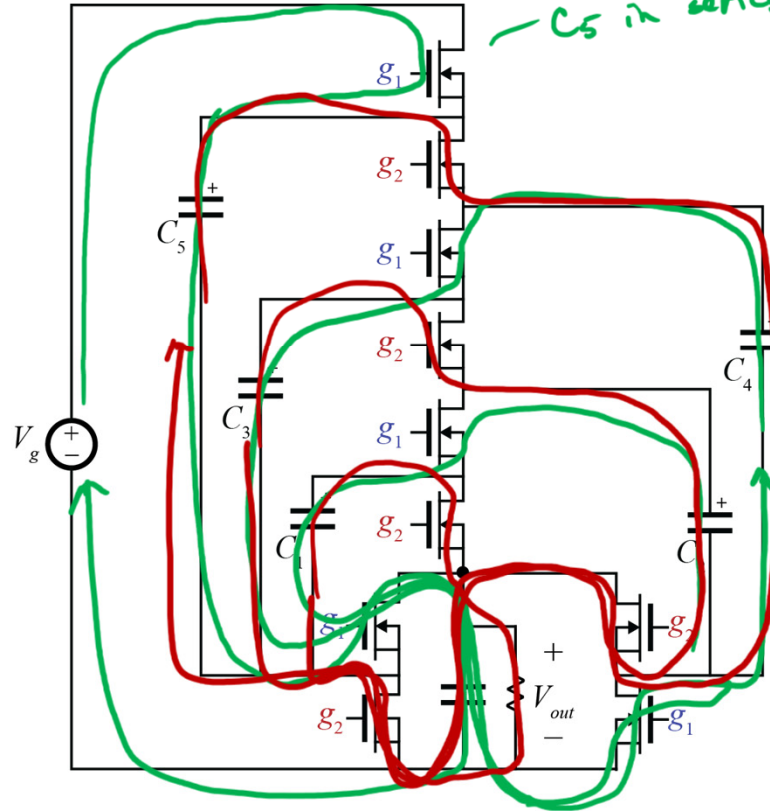


anti-
in series
w/ output

anti-
in series
w/ V_{out}

Dickson Subintervals

I

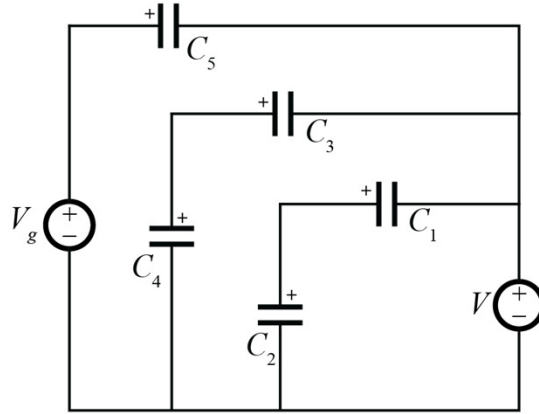

$$V_g = 6V$$

$$V_{C4} = 4V$$


$$V_{C2} = V_{C4} + V = 2V$$

Ideal Analysis :

lossless, let all caps have DC voltage

this is a 6:1 Dickson converter
what is the output resistance?

II

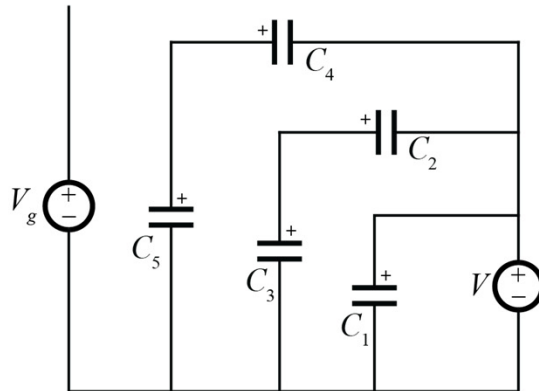


$$V_{C5} = 5V$$


$$V_{C3} = 3V$$

$$V_{C1} = V$$

Dickson Converter Variants

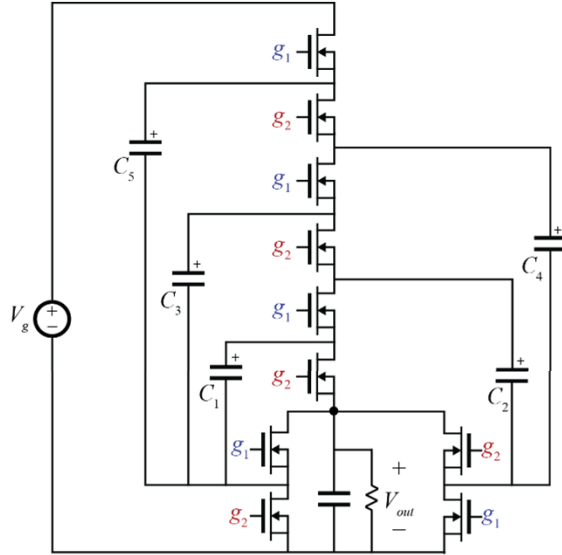


Standard Dickson Converter

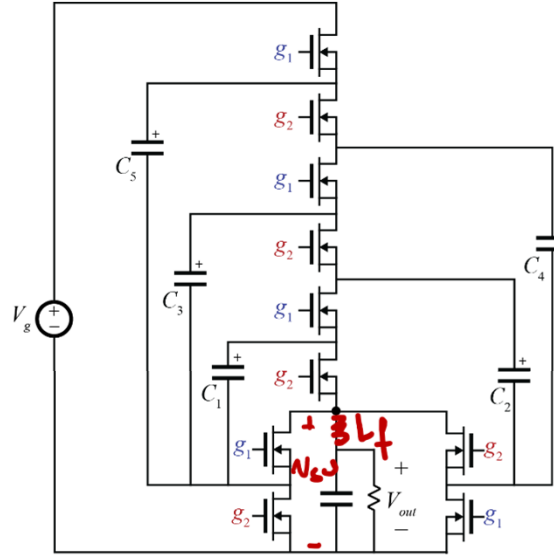


Hybrid Dickson Converter

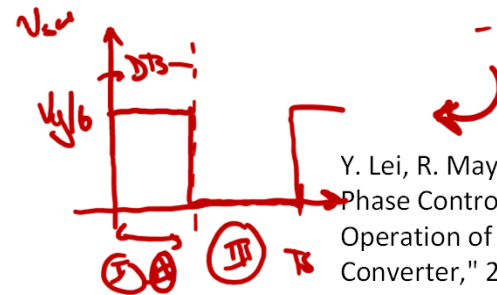- Current sink
- reduces some charge sharing loss
- can add regulation
- from the a buck w/ $\frac{1}{6} V_g$



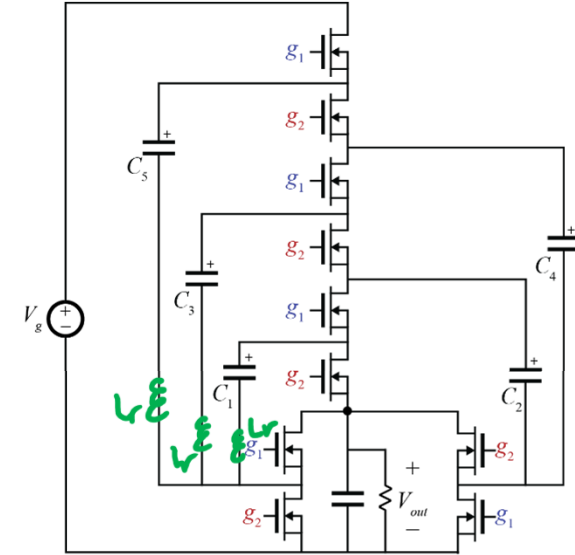Y. Lei, R. May, and R. Pilawa-Podgurski, "Split-Phase Control: Achieving Complete Soft-Charging Operation of a Dickson Switched-Capacitor Converter," 2016




Switched Tank Converter

- still unregulated 6:1
- resonant charging of all caps
- reduced switching losses

Y. Li, X. Lyu, D. Cao, S. Jiang and C. Nan, "A 98.55% Efficiency Switched-Tank Converter for Data Center Application," 2018.

Charge Vector Analysis: Notation

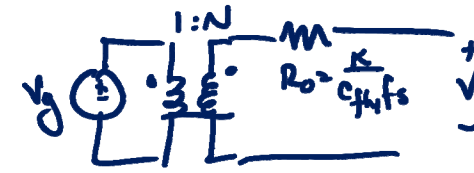Goal: Find $N \times k$ for any switched cap converter



- Apply Cap-Q balance to all caps in the circuit

q_x^I = charge flowing through capacitor x in subinterval I $(q_{c_1}^{\text{II}} = \text{charge through } C_1 \text{ in } \textcircled{\text{II}})$

$a_x^I = \frac{q_x^I}{q_{\text{out}}}$ \rightarrow q_x^I normalized by q_{out} , the total charge delivered to the output
 $q_{\text{out}} = q_{\text{out}}^I + q_{\text{out}}^{\text{II}} + \dots$

$$\bar{a}^I = \begin{bmatrix} a_{\text{in}}^I & \underbrace{a_{c_1}^I \quad a_{c_2}^I \quad \dots \quad a_{c_N}^I}_{\text{for converter w/ } N \text{ flying caps}} & a_{\text{out}}^I \end{bmatrix}$$

input output

$$\bar{v}^I = \begin{bmatrix} V_g & v_{c_1}^I & v_{c_2}^I & \dots & v_{c_N}^I & V \end{bmatrix}$$

V_x^I = Voltage on C_x at the end of subinterval I



Charge Vector Analysis: Rules

- KVL & KCL equations apply
- Cap-Q balance, for all caps $\int_0^{T_0} i_{Cx} dt \rightarrow Q_{Cx} = 0$ in steady state

In a 2-subinterval converter

$$g_{Cx}^I + g_{Cx}^{II} = 0 \rightarrow g_{Cx}^I = -g_{Cx}^{II}$$

same for a_{Cx}