


Charge Vector Analysis: Rules

- KVL & KCL equations apply
- Cap-Q balance, for all caps $\int_0^{T_0} i_{Cx} dt \rightarrow Q_{Cx} = \phi$ in steady state

In a 2-subinterval converter

$$q_{Cx}^I + q_{Cx}^{II} = \phi \rightarrow q_{Cx}^I = -q_{Cx}^{II}$$

same for q_{Lx}

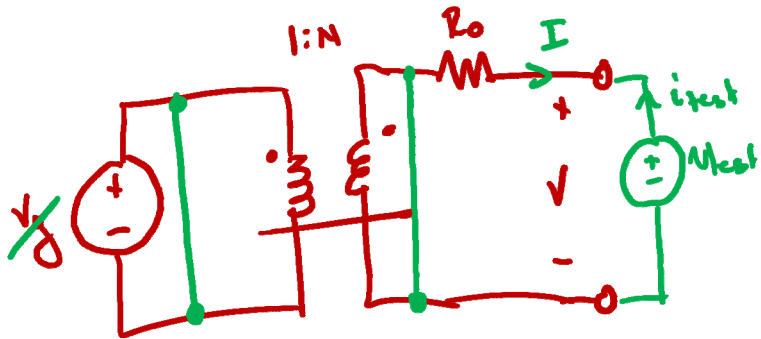


to find R_0 :

shut off all indep. sources

$$R_0 = \frac{v_{test}}{i_{test}} = \frac{V}{-I} \Big|_{v_g = 0}$$

2:1 Converter Charge Vector Analysis

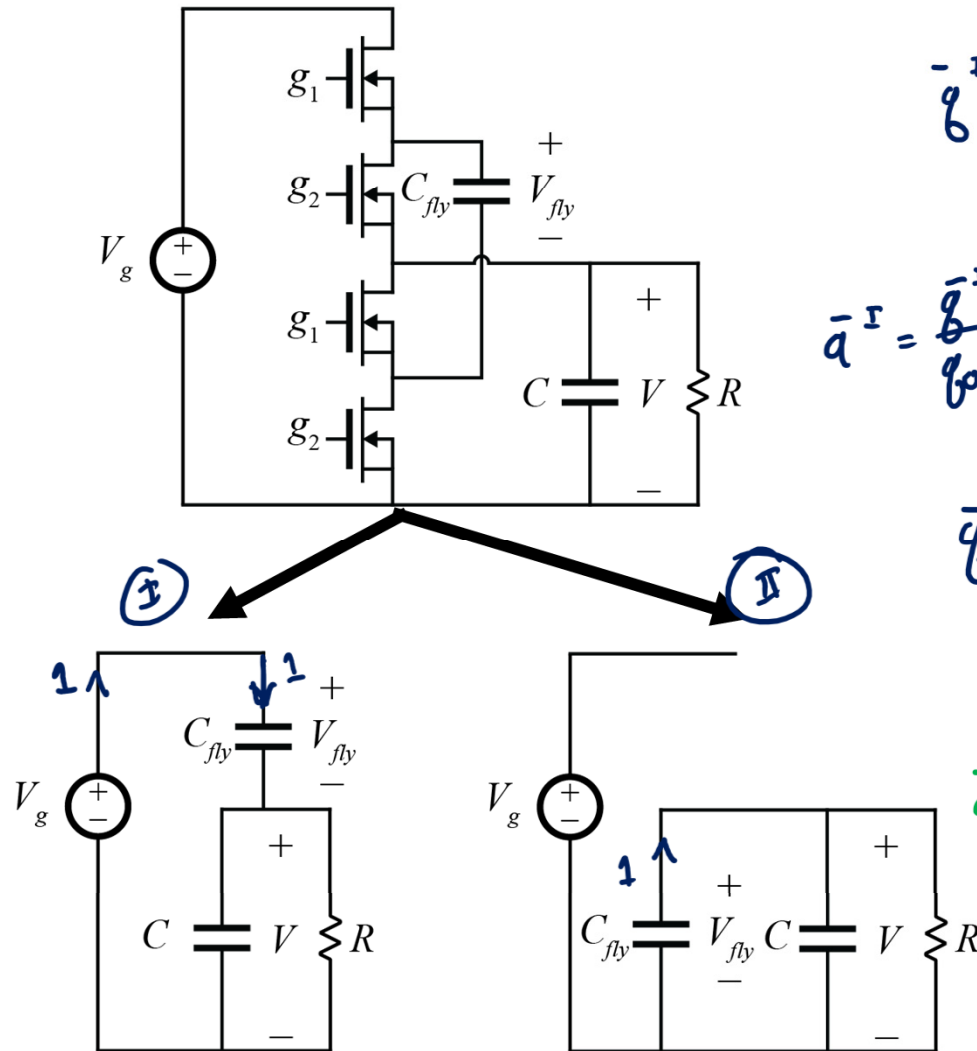

pick value arbitrarily

$$\bar{g}^I = \begin{bmatrix} g_{in}^I & g_{fly}^I & g_{out}^I \end{bmatrix}$$

$$= \begin{bmatrix} -1 & 1 & 1 \end{bmatrix}$$

$$\bar{a}^I = \frac{\bar{g}^I}{g_{out}^I} = \begin{bmatrix} -\frac{1}{2} & \frac{1}{2} & \frac{1}{2} \end{bmatrix}$$

$$\bar{g}^{II} = \begin{bmatrix} g_{in}^{II} & g_{fly}^{II} & g_{out}^{II} \end{bmatrix}$$

$$= \begin{bmatrix} \emptyset & -1 & 1 \end{bmatrix}$$

$$\bar{a}^{II} = \begin{bmatrix} \emptyset & -\frac{1}{2} & \frac{1}{2} \end{bmatrix}$$

$$q_{in} = a_{in}^I + a_{in}^{II} = -\frac{1}{2}$$

$$q_{out} = a_{out}^I + a_{out}^{II} = 1$$

$$M = \frac{1}{2} = \frac{V}{V_g} = \frac{I_g}{I_o}$$

$$m = \frac{V}{V_g} = \frac{-a_{in}}{a_{out}}$$

Tellegen's Theorem

For any valid circuit

$$\sum_{\text{all elements}} V_i I_i = 0$$

V_i = voltage across
 I_i = current through

Passive sign convention is required

for our 2-subinterval switched cap converter

$$\bar{a}^I \bar{v}^I + \bar{a}^II \bar{v}^{II} = 0$$

$$\S \quad \bar{a}^I \bar{v}^I = \bar{a}^{II} \bar{v}^{II} = 0$$

SSL Output Resistance

Apply Tellegen's Theorem:

$$\bar{a}^I \bar{v}^I + \bar{a}^II \bar{v}^II = \phi$$

$$\cancel{(a_{in}^I + a_{in}^{II}) V_g} + \bar{a}_c^I \bar{v}_c^I + \bar{a}_c^{II} \bar{v}_c^{II} + \underbrace{(a_{out}^I + a_{out}^{II}) V}_{=1 \text{ by normalization}} = \phi$$

by application of test circuit for R_o

$$\bar{a}_c^I \bar{v}_c^I + \bar{a}_c^{II} \bar{v}_c^{II} = -V = \sum_{\text{all caps}} a_{ci}^I v_{ci}^I + a_{ci}^{II} v_{ci}^{II}$$

for 2 subintervals $a_{ci}^I = -a_{ci}^{II}$ by cap-Q balance

$$\frac{1}{I_{out}} (-V) = \sum_{\text{all caps}} a_{ci}^I \underbrace{(v_{ci}^I - v_{ci}^{II})}_{\Delta v_{ci} = \frac{g_{ci}}{C_i}} \left(\frac{1}{I_{out}} \right)$$


$$I_{out} = g_{out} f_s$$

$$\frac{-V}{I} = R_o = \sum_{\text{all caps}} a_{ci}^I \left(\frac{g_{ci}}{C_i} \right) \frac{1}{g_{out} f_s} =$$

$$\sum_{\text{all flying caps}} (a_{ci})^2 \frac{1}{C_i f_s} = R_o$$

General for any 2-subinterval switched cap converter in SSL

Output Resistance

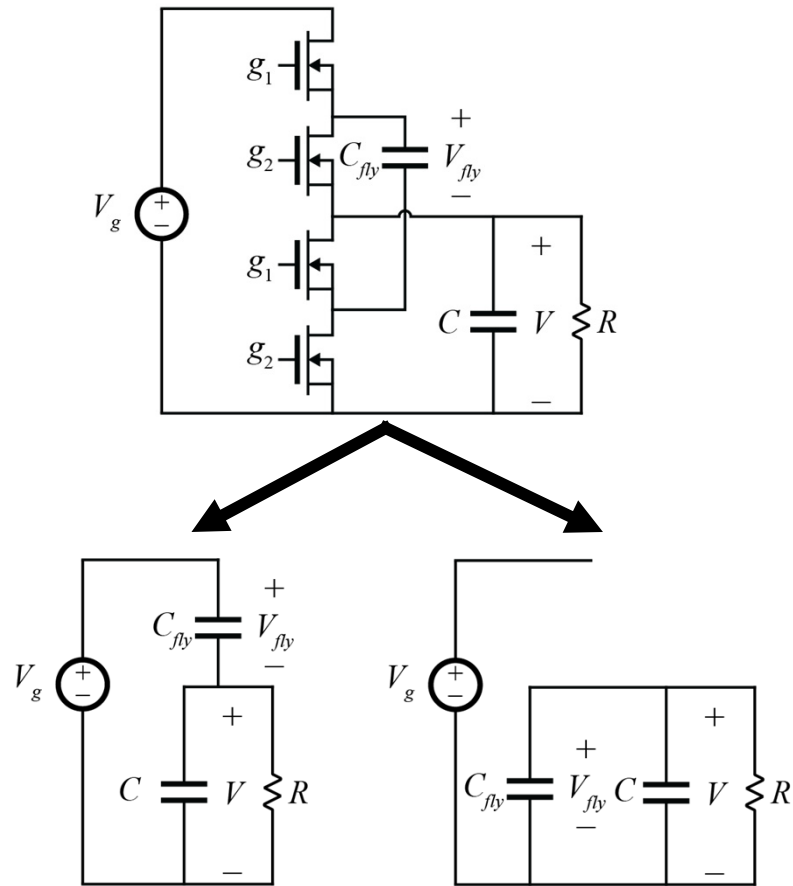


$$\bar{a}^I = \begin{bmatrix} -\frac{1}{2} & \frac{1}{2} & \frac{1}{2} \end{bmatrix}$$

$$\bar{a}^{II} = \begin{bmatrix} 0 & -\frac{1}{2} & \frac{1}{2} \end{bmatrix}$$

$$R_o = \sum_{\text{all flying caps}} (\bar{a}_{cc})^2 \frac{1}{C f_s} = \frac{1}{4} \frac{1}{C_{fly} f_s} = \frac{1}{4 C_{fly} f_s} \quad \checkmark$$

$$R_{o,ssL} = \frac{1}{4 C_{fly} f_s}$$

Dickson Charge Vector Analysis

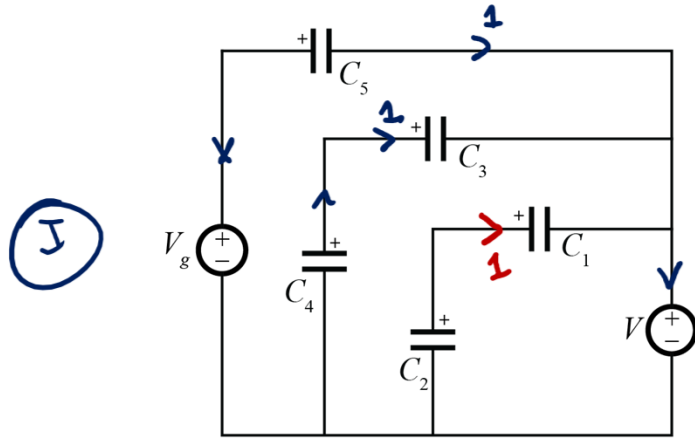


$$\bar{a}^T = \frac{\bar{g}^T}{g_{out}} = \begin{bmatrix} a_{in} & a_{c1} & a_{c2} & a_{c3} & a_{c4} & a_{c5} & a_{out} \end{bmatrix} / g_{out}$$

$$\bar{a}^T = \begin{bmatrix} -1 & 1 & -1 & 1 & -1 & 1 & 3 \end{bmatrix} / g_{out}$$

$$g_{out} = g_{out}^I + g_{out}^P = 6$$

$$\bar{a}^T = \frac{\bar{g}^T}{g_{out}} = \begin{bmatrix} \phi & -1 & 1 & -1 & 1 & -1 & 3 \end{bmatrix} / g_{out}$$
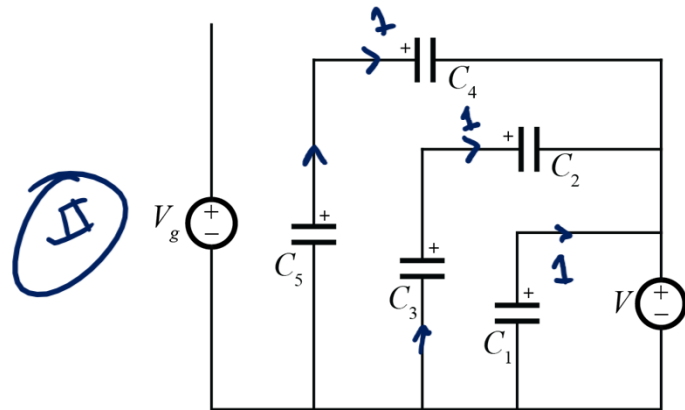
$$\bar{a}^T = \begin{bmatrix} \phi & -\frac{1}{6} & \frac{1}{6} & -\frac{1}{6} & \frac{1}{6} & -\frac{1}{6} & \frac{1}{2} \end{bmatrix}$$



$$M = \frac{-a_{in}}{a_{out}} = \frac{1}{6} \checkmark \quad 6:1 \text{ Dickson}$$

Dickson SSL Output Resistance

$$R_{o,ssl} = \sum_{\substack{\text{flying} \\ \text{caps}}} (a_{ci})^2 \frac{1}{C_i f_s} = \sum_{i=1}^5 \left(\frac{1}{6}\right)^2 \frac{1}{C_{fly} f_s} = \boxed{\frac{5}{36 C_{fly} f_s} = R_{o,ssl}}$$

Assume all caps have $C_i = C_{fly}$, same capacitance

Charge Vector Analysis in FSL

$\bar{a}_r = \frac{\bar{g}_r}{g_{out}} \Rightarrow g_{ri}$ is the charge flowing through transistor i
 Can be extended to any resistor in the circuit
 by limiting to transistors. we're assuming r_{on} dominates
 a_{ri} are generally a linear combination of a_{ci} from before

$R_{O,FSL}$ found by:

In FSL, currents are nearly constant over the subinterval
 for a 2-subinterval converter @ $D=50\%$

$$i_{ri} = g_{ri} \cdot \frac{T_s}{2} \rightarrow$$

$$P_{ri} = (i_{ri})^2 R_i \frac{1}{2} = \left(g_{ri} \frac{T_s}{2}\right)^2 R_i \frac{1}{2}$$


$$P_{ri} = \left(a_{ri} \cdot g_{out} \frac{T_s}{2}\right)^2 R_i \frac{1}{2}$$

$$P_{ri} = a_{ri}^2 4 \frac{1}{2} R_i \cdot g_{out}^2 \frac{T_s^2}{4} = a_{ri}^2 \cdot 2 \cdot R_i I_{out}^2$$

$$P_{total} = \sum_{\text{all } R_i} (a_{ri})^2 \cdot 2 R_i I_{out}^2 \rightarrow$$

$$R_{O,FSL} = \sum_{\text{all } R_i} 2 (a_{ri})^2 R_i$$

Dickson Converter FSL Output Resistance

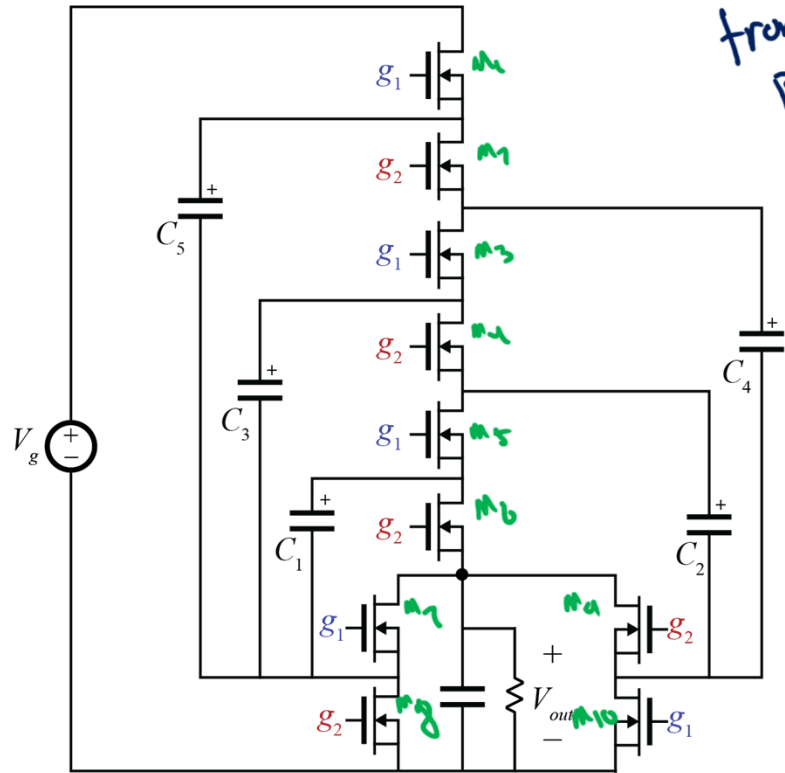

from previous

$$\begin{cases} \bar{a}^I = \begin{bmatrix} -\frac{1}{6} & \frac{1}{6} & -\frac{1}{6} & \frac{1}{6} & -\frac{1}{6} & \frac{1}{6} & \frac{1}{2} \end{bmatrix} \\ \bar{a}^{II} = \begin{bmatrix} 0 & -\frac{1}{6} & \frac{1}{6} & -\frac{1}{6} & \frac{1}{6} & -\frac{1}{6} & \frac{1}{2} \end{bmatrix} \end{cases}$$

$$\bar{a}_r = \begin{bmatrix} \overset{M_1}{\frac{1}{6}} & \overset{M_2}{\frac{1}{6}} & \overset{M_3}{\frac{1}{6}} & \overset{M_4}{\frac{1}{6}} & \overset{M_5}{\frac{1}{6}} & \overset{M_6}{\frac{1}{6}} & \overset{M_7}{\frac{1}{2}} & \overset{M_8}{\frac{1}{2}} & \overset{M_9}{\frac{1}{3}} & \overset{M_{10}}{\frac{1}{3}} \end{bmatrix}$$