

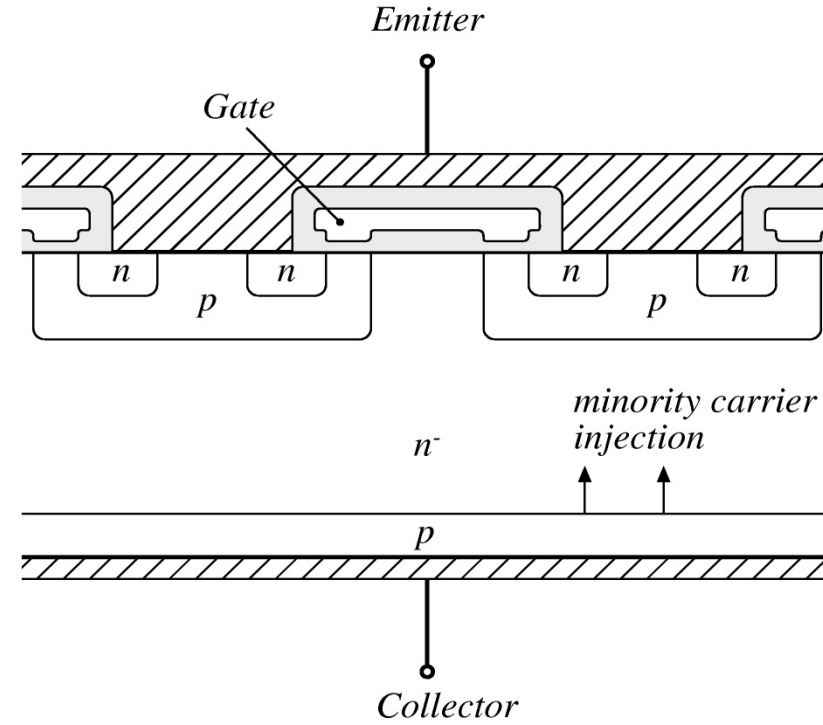


# Charge Storage

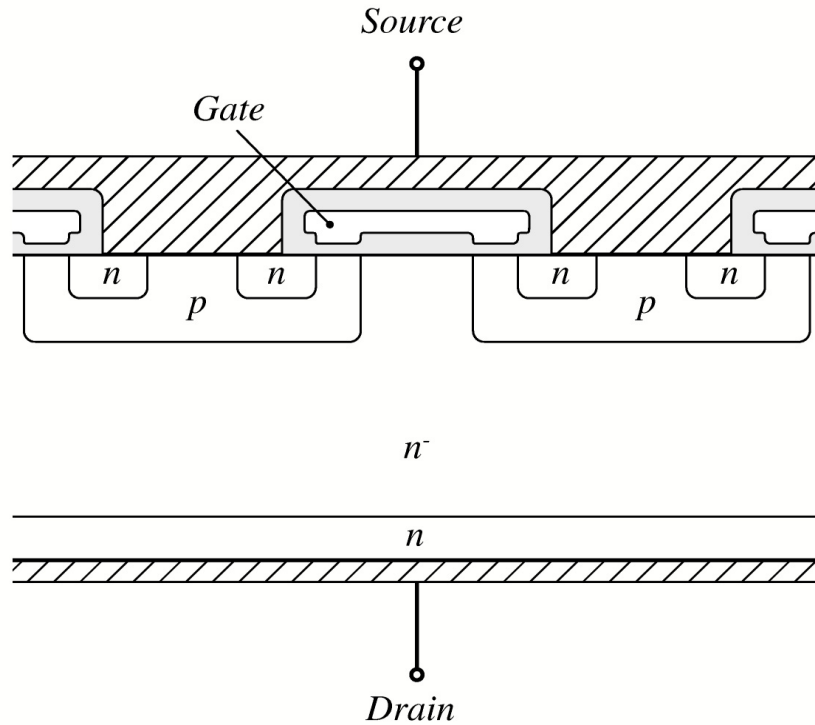


# IGBT Current Tailing

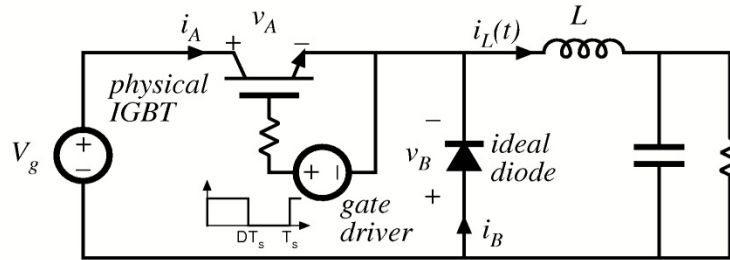

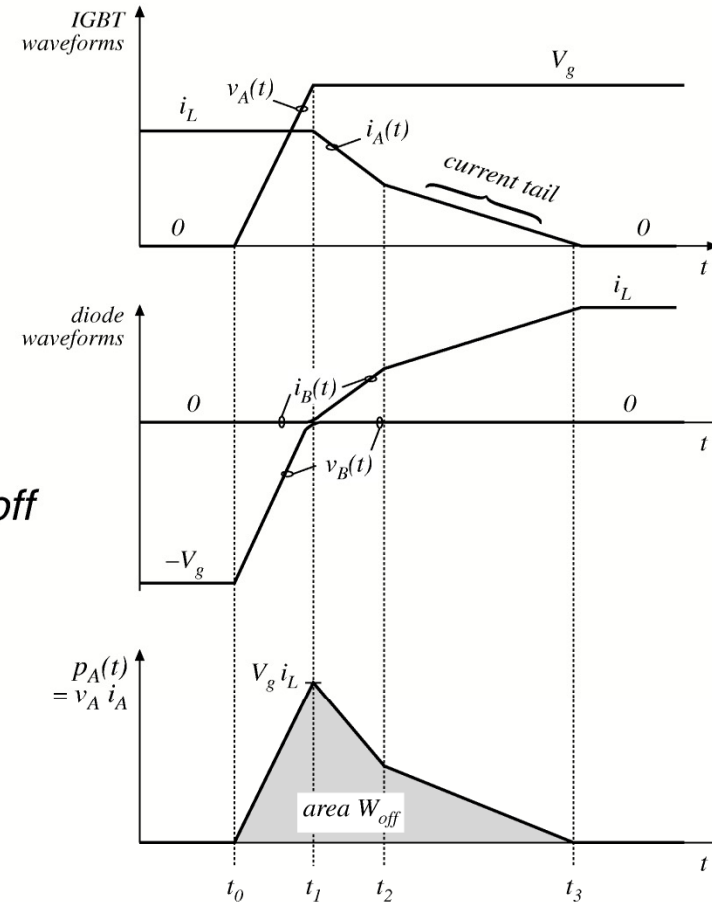
Example: buck converter with IGBT

transistor turn-off  
transition

$$P_{sw} = \frac{1}{T_s} \int_{\text{switching transitions}} p_A(t) dt = (W_{on} + W_{off}) f_s$$




# Schottky Diode

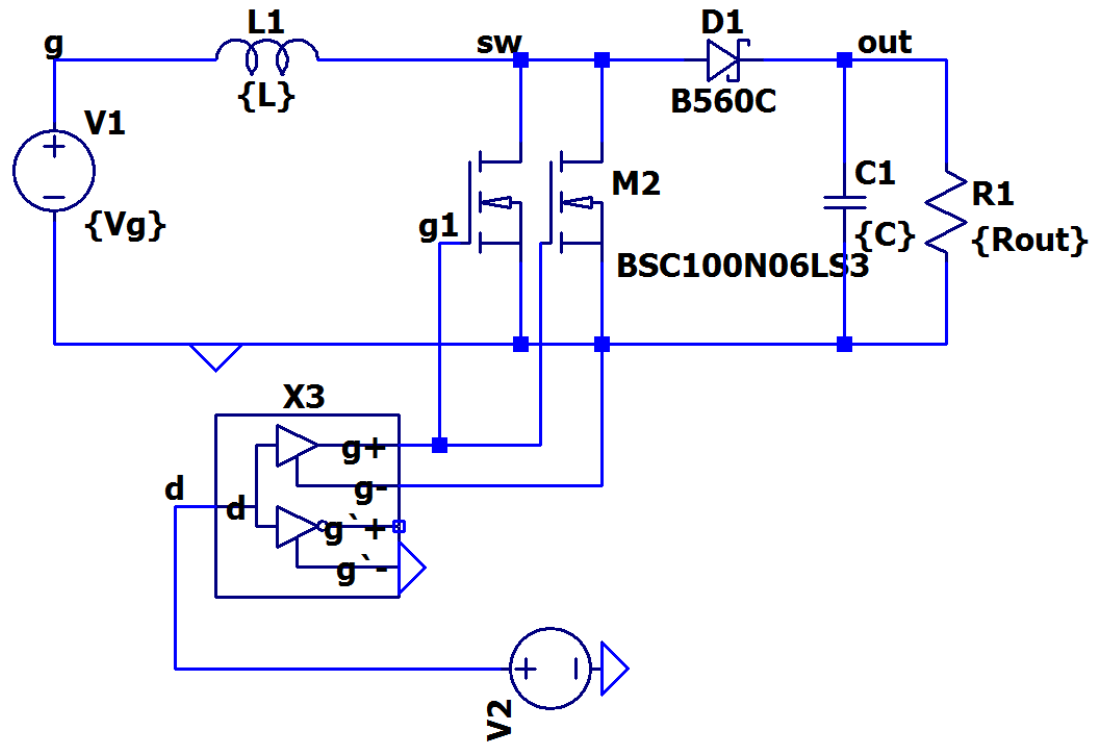


| $L$  | $C_{out}$ | $f_s$ | Diode       | $\eta$ (Sim) |
|------|-----------|-------|-------------|--------------|
| 22uH | 22uF      | 202k  | Si (FR)     | 93.9%        |
| 22uH | 22uF      | 202k  | Si Schottky | 95.8%        |


# Simulation Waveforms

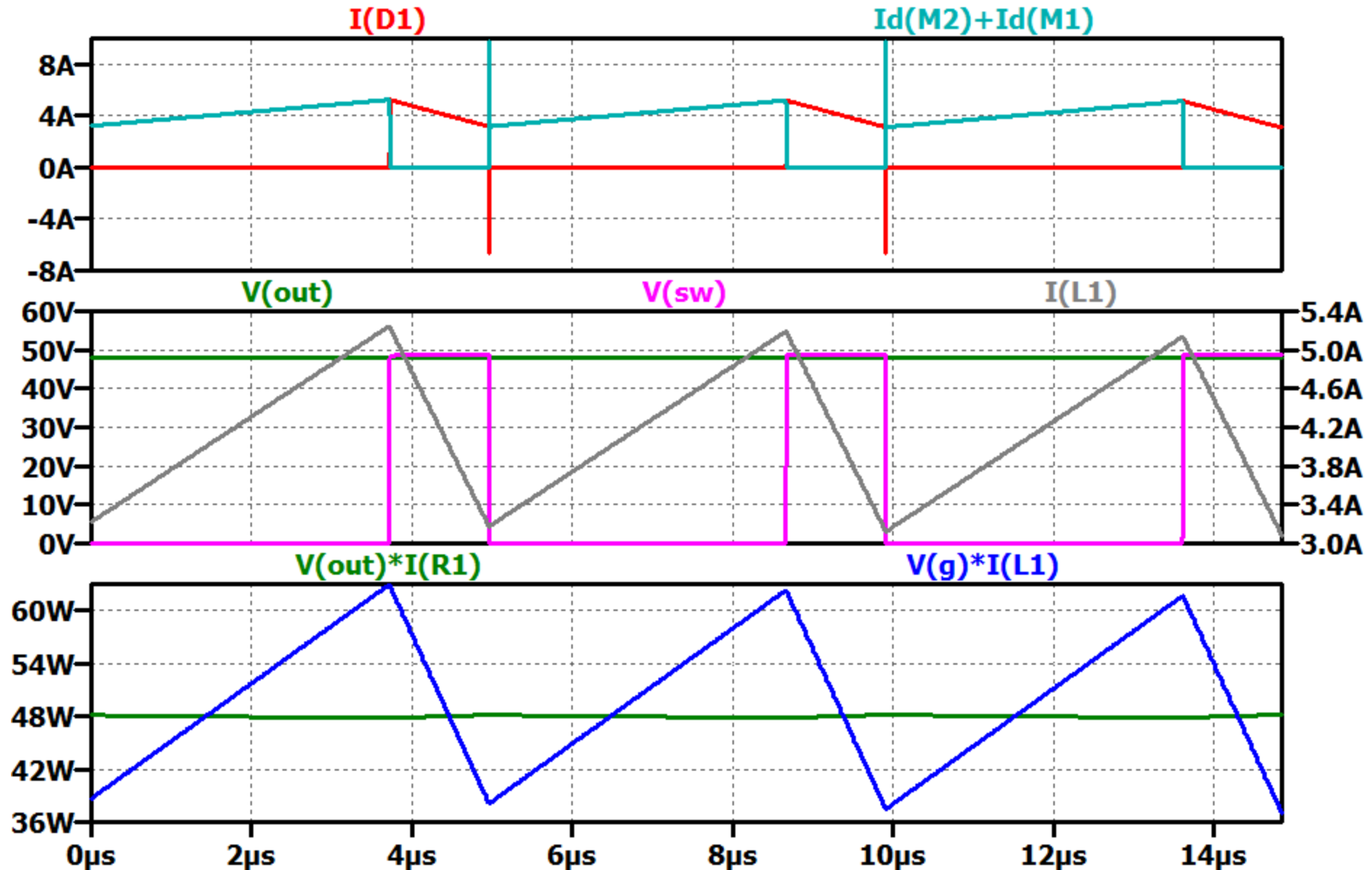

# Switching Transition – FET turn ON

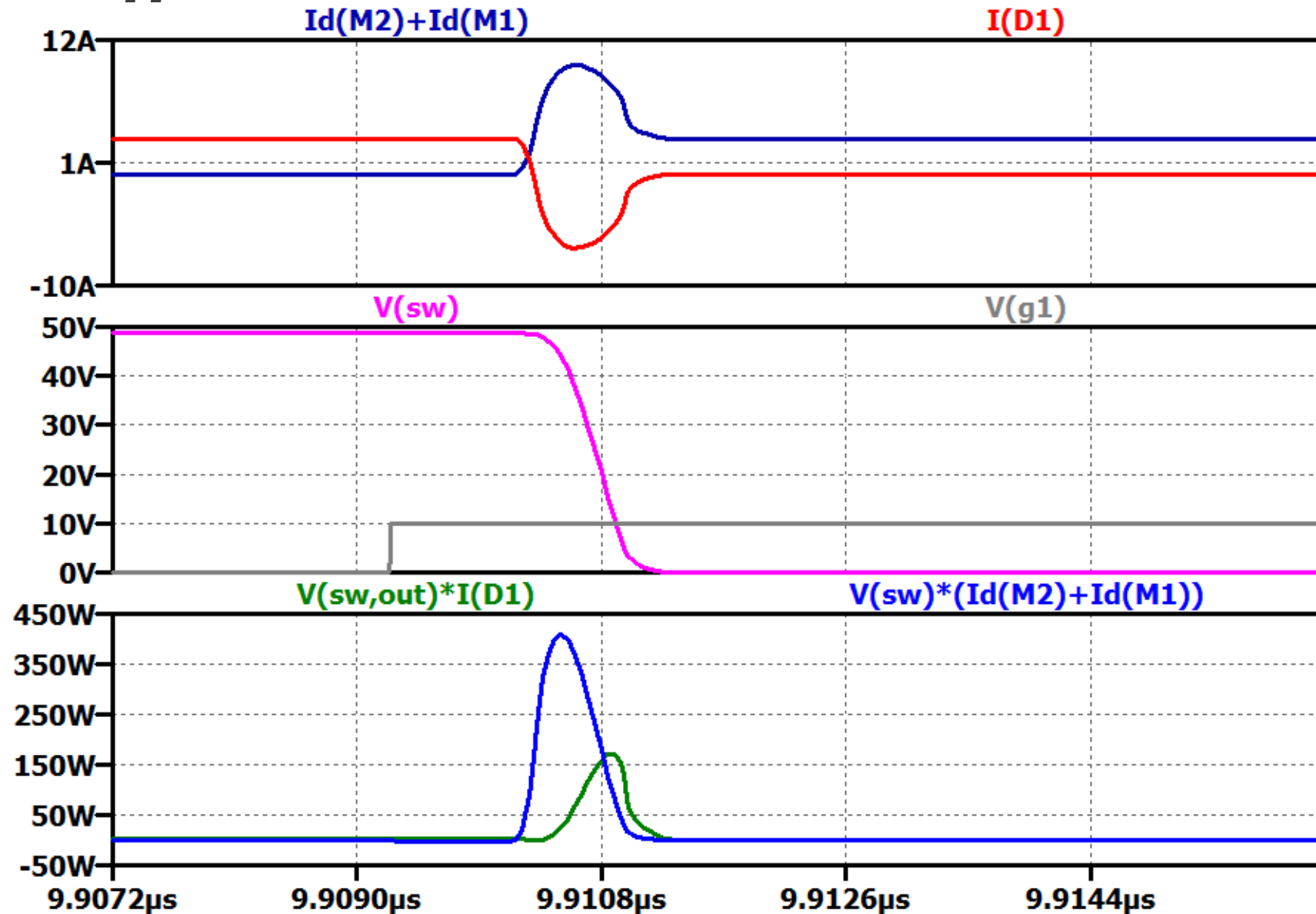

# Switching Transition – FET turn OFF

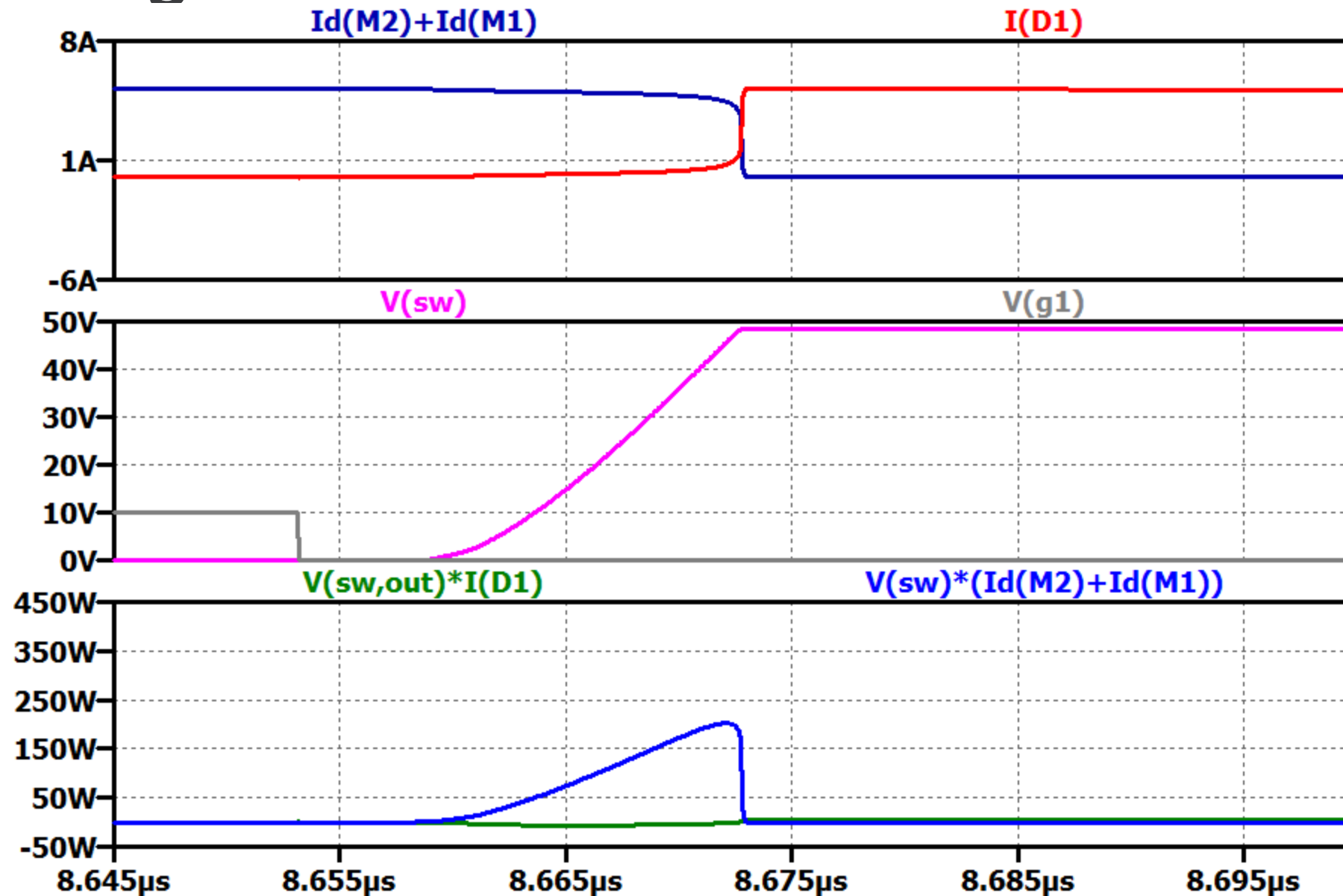


# MOSFET Switching Behaviors

## 5 Typ. output characteristics

$$I_D = f(V_{DS}); T_j = 25^\circ\text{C}$$


parameter:  $V_{GS}$

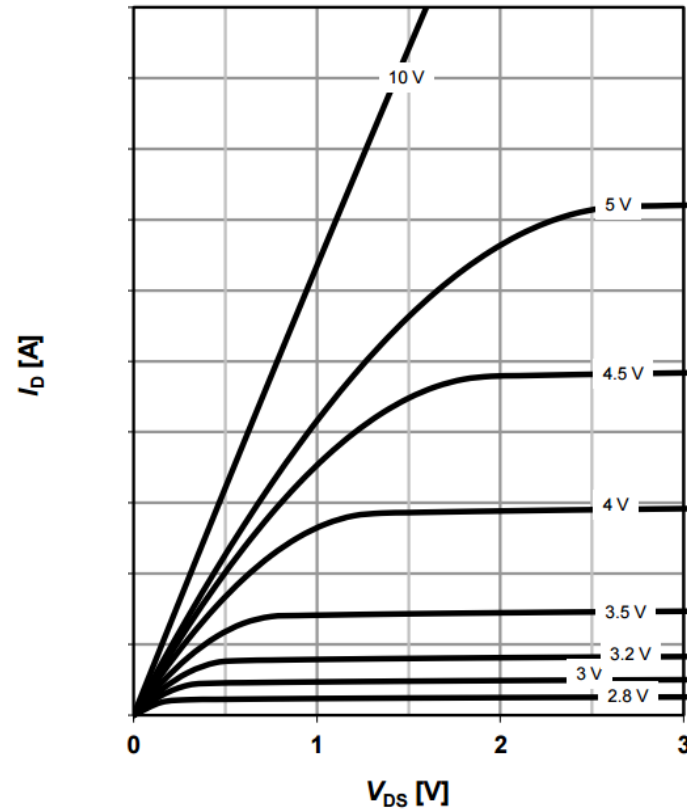





## 6 Typ. drain-source on resistance

$$R_{DS(on)} = f(I_D); T_j = 25^\circ\text{C}$$

parameter:  $V_{GS}$

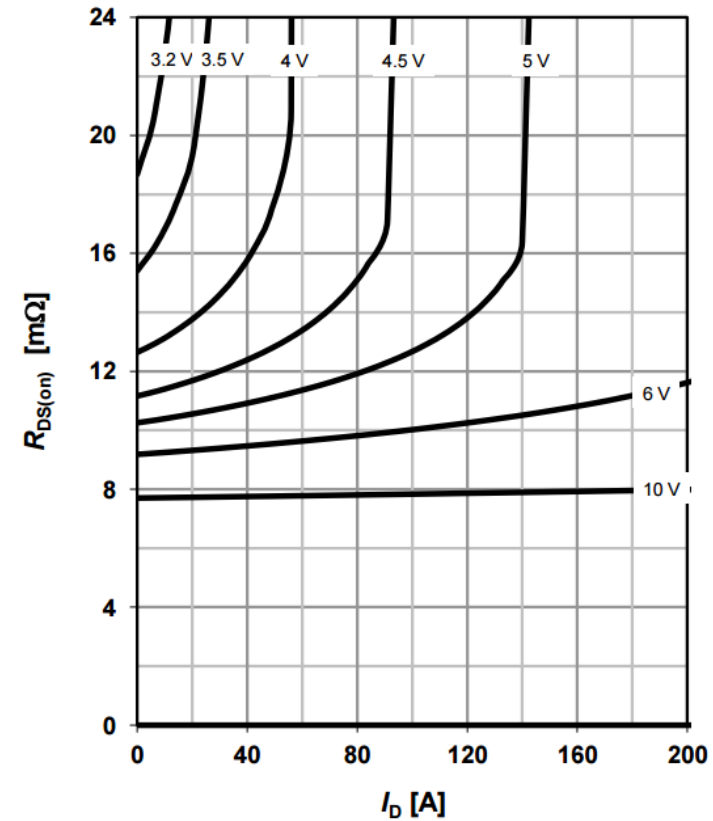

# MOSFET Stored Charge

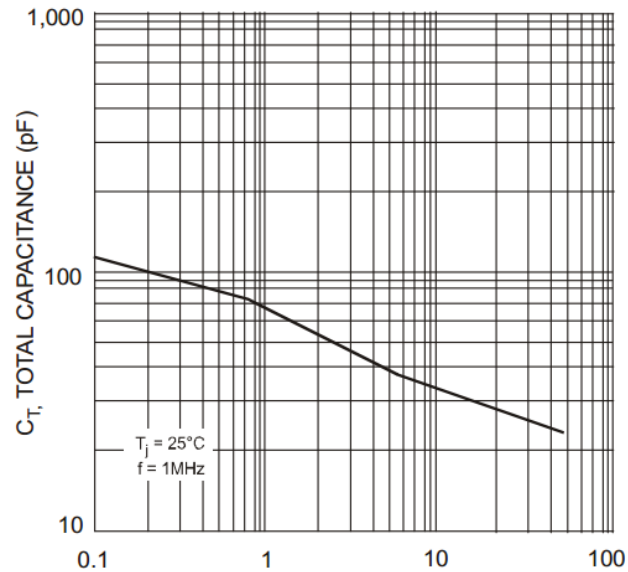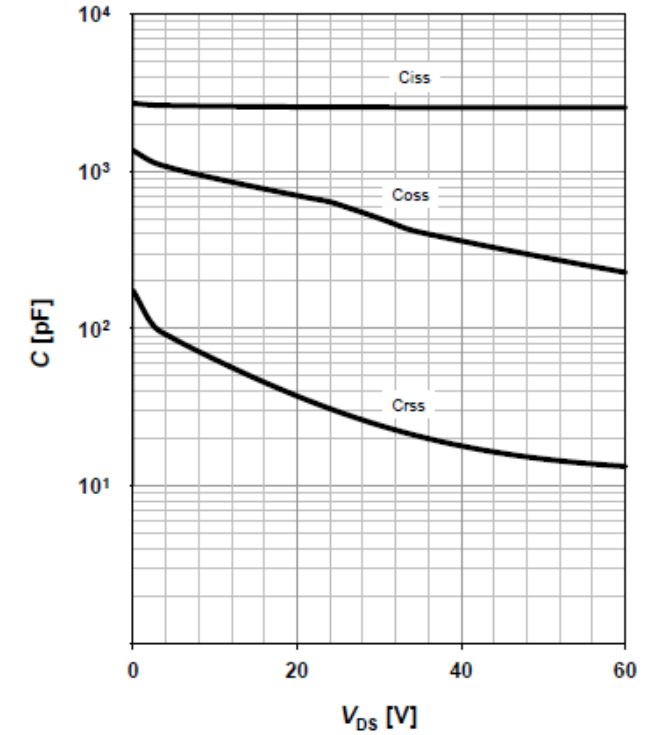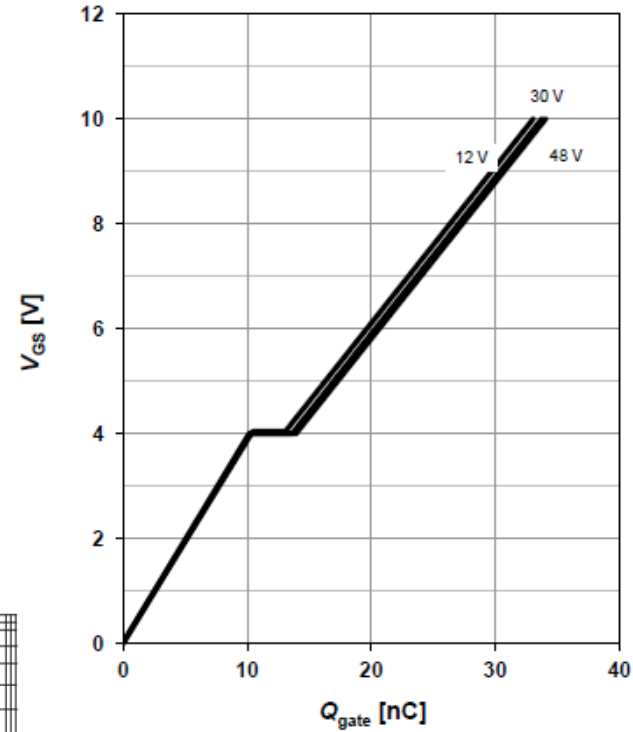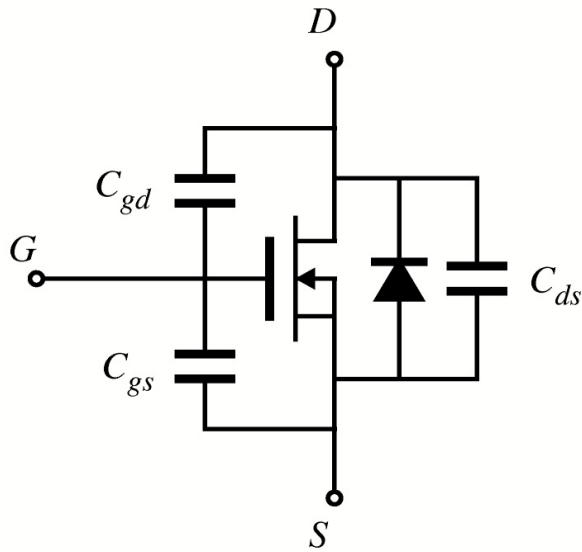

# Device Capacitances

