
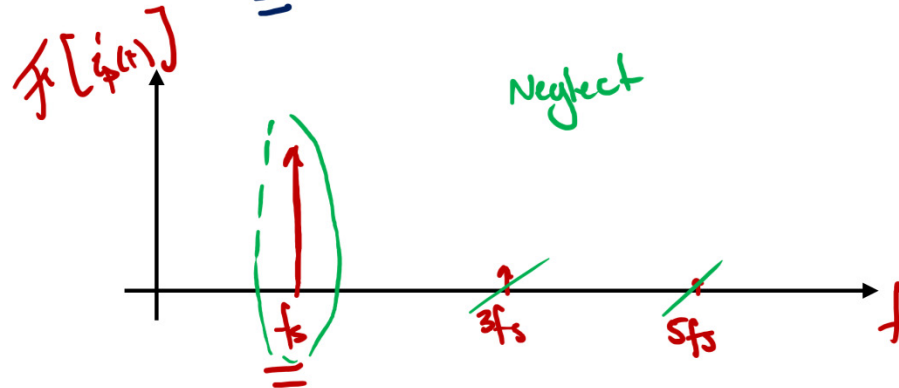


Sinusoidal Analysis (Ch 19)


→ 2nd Edition of Fund. of Power Elec
Chapter 22 in 3rd Edition

Fundamental Harmonic Approximation

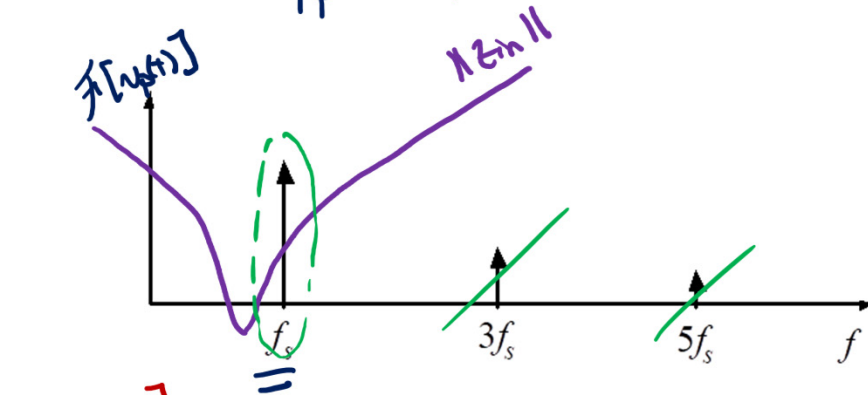


Based on bandpass tech, fundamental even more dominant

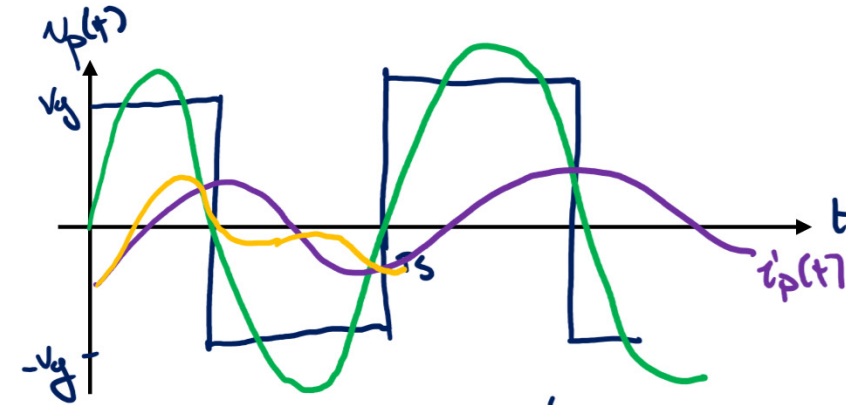Things like ZVS cannot be accurately assessed in FHA




$v_p(t) \rightarrow$ actual waveform

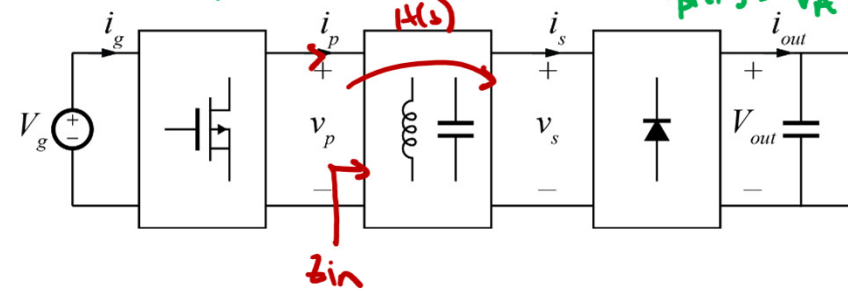$v_{p1}(t) \rightarrow$ fundamental harmonic
 $v_{p1}(t) = V_A \sin(\omega_s t + \varphi)$



for many ac-link converters, $H(s)$ has a bandpass characteristic

for SBE

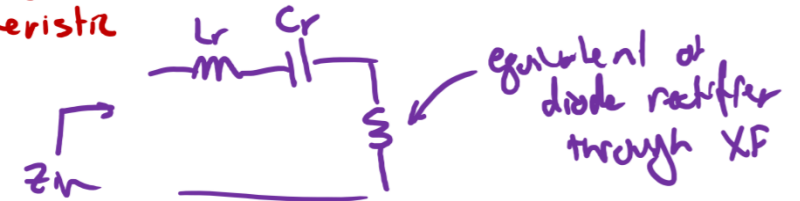

Sinusoidal Analysis: Comments

- Generally most accurate when operating near resonance with a high Q
- Effective quality factor Q_e depends not only on resonant tank, but also on loading
- Analysis neglects switching intervals; can only predict where ZVS **cannot** be obtained


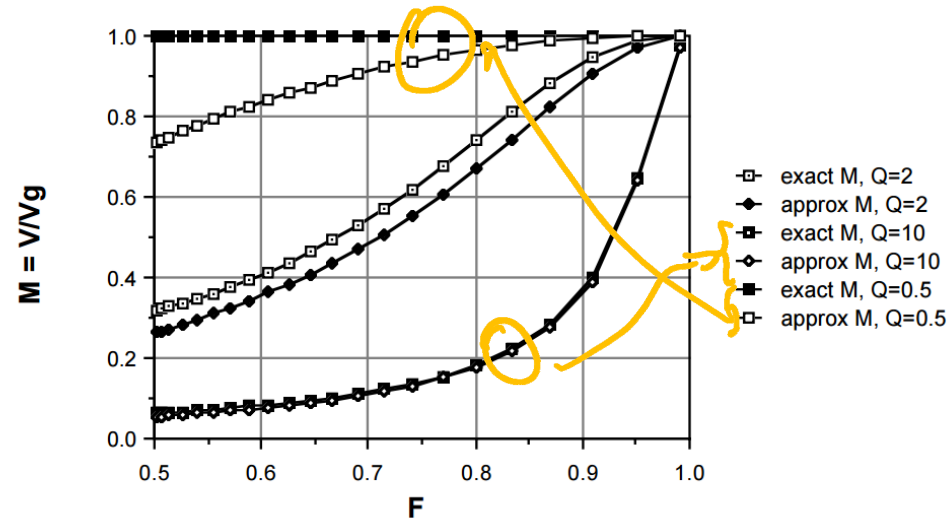



Fig. 2.14. Comparison of exact and approximate series resonant converter characteristics, below resonance.

AC Link Waveforms

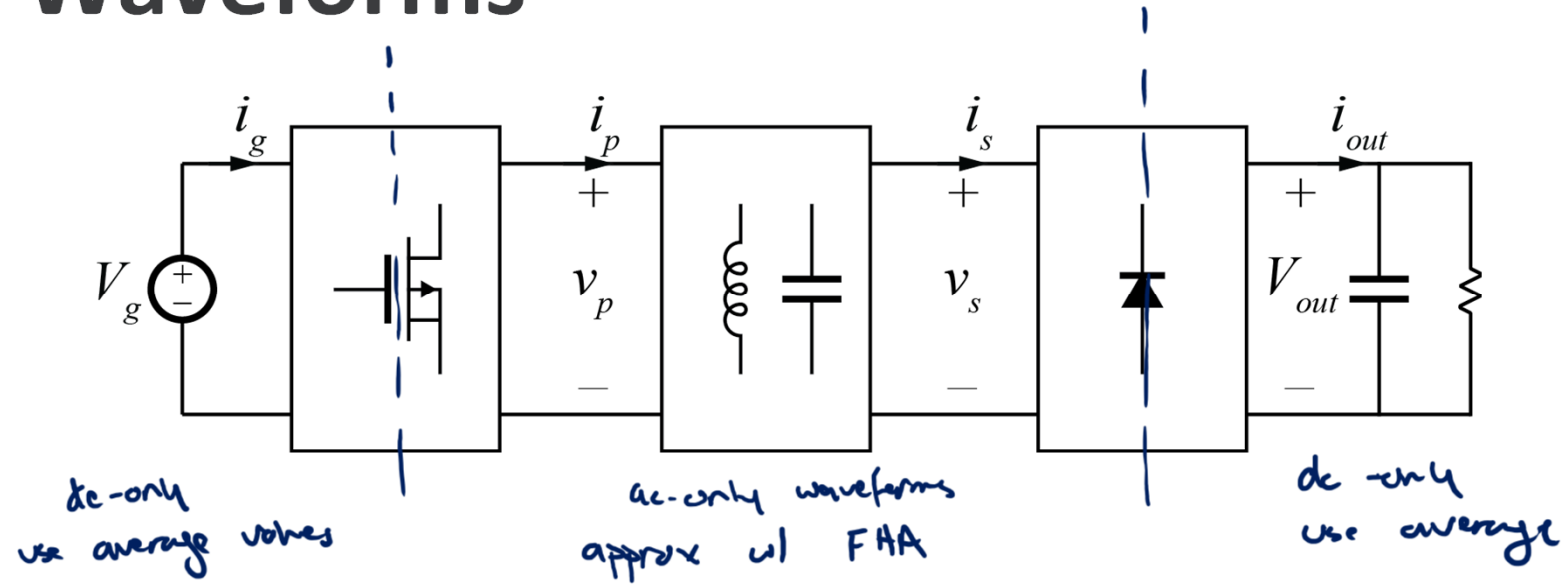

Switch Network Sinusoidal Analysis

Full Bridge Inverter

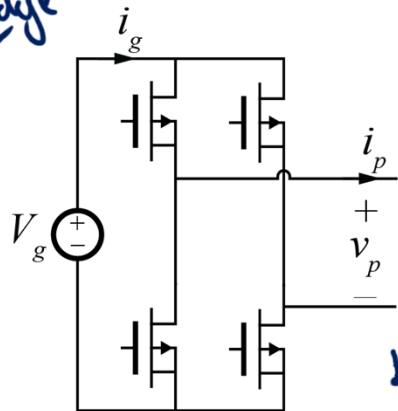

Fourier Series:

$$b_1 = \frac{2}{T_s} \int_0^{T_s} f(x) \sin(2\pi f_s t) dt$$


for $v_p(t)$

$$b_{p1} = \frac{2}{T_s} \int_0^{T_s} v_p(t) \sin(2\pi f_s t) dt$$

$$\begin{aligned} b_{p1} &= 2 \cdot \frac{2}{T_s} \int_0^{T_s/2} V_g \sin(2\pi f_s t) dt \\ &= 2 \cdot \frac{2}{T_s} V_g \left[\frac{1}{2\pi f_s} (-\cos(2\pi f_s t)) \right]_0^{T_s/2} \\ &= 2 \cdot \frac{2}{T_s} V_g \frac{1}{2\pi f_s} (1 + 1) \end{aligned}$$

$$b_{p1} = \frac{4}{\pi} V_g$$
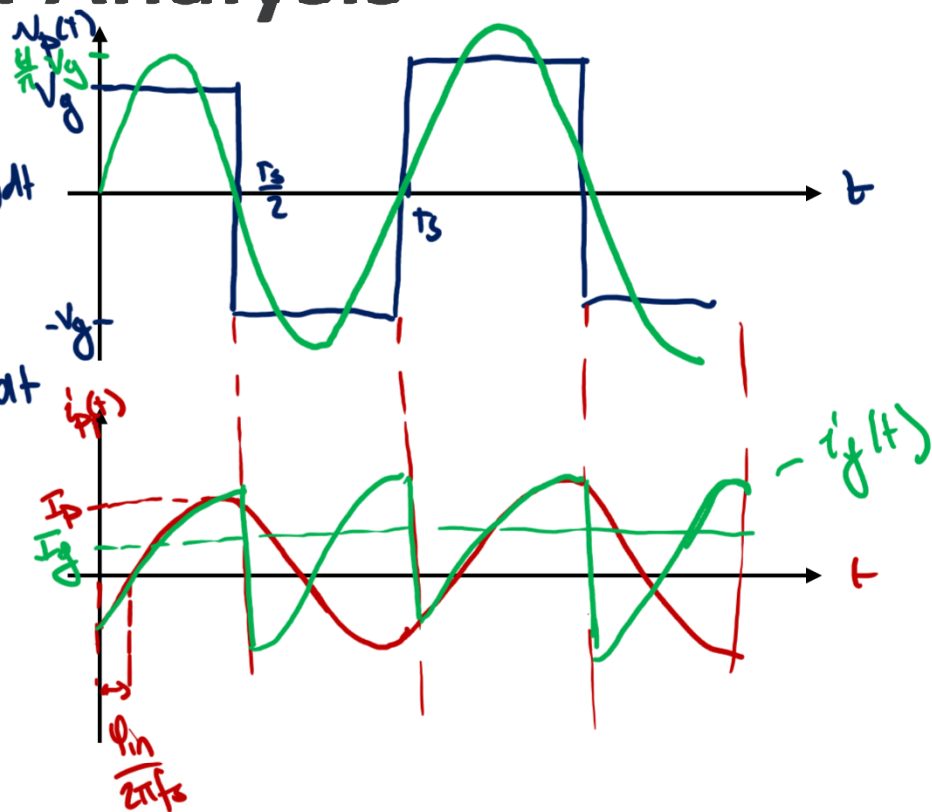
$$v_{p1}(t) = \frac{4}{\pi} V_g \sin(\omega_s t)$$



$i_p(t) \rightarrow$ Dictated by Z_{in}
 $i_p(t) = I_p \sin(\omega_s t + \phi_{in})$

Input Current


for $i_p(t) = I_p \sin(2\pi f_s t + \phi_{in})$

then the DC input current is

$$\begin{aligned} I_g &= \frac{1}{T_s} \int_0^{T_s} i_g(t) dt = \frac{2}{T_s} \int_0^{T_s/2} i_p(t) dt \\ &= \frac{2}{T_s} \int_0^{T_s/2} I_p \sin(2\pi f_s t + \phi_{in}) dt \\ &= \frac{2}{T_s} I_p \left[\frac{1}{2\pi f_s} (-\cos(2\pi f_s t + \phi_{in})) \right]_0^{T_s/2} \\ &= \frac{2}{T_s} I_p \frac{1}{2\pi f_s} (-\cos(\pi + \phi_{in}) + \cos(\phi_{in})) \\ &= \cancel{\frac{2}{T_s}} I_p \cancel{\frac{1}{2\pi f_s}} 2 \cos(\phi_{in}) \end{aligned}$$

$$I_g = \frac{2}{\pi} I_p \cos \phi_{in}$$

Switch Network Equivalent Circuit (FHA)

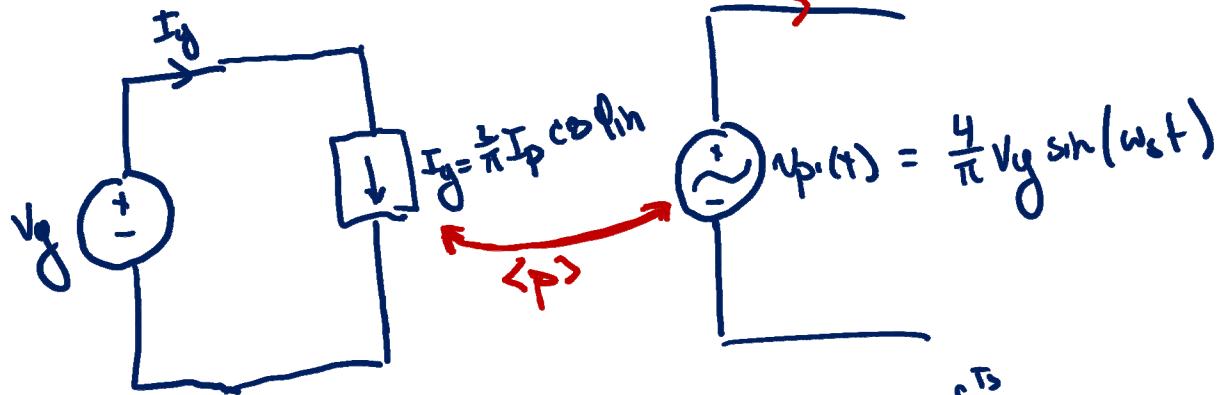

$$P_g = v_g I_g = v_g \frac{2}{\pi} I_p \cos \phi_{in}$$

$$P_{P1} = \frac{1}{T_s} \int_0^{T_s} v_{P1}(t) \cdot i_{P1}(t) dt$$

$$= \frac{1}{T_s} \int_0^{T_s} \frac{4}{\pi} v_g \sin(\omega t) I_p \sin(\omega t + \phi_{in}) dt$$

$$= \frac{1}{T_s} \frac{4}{\pi} v_g I_p \frac{1}{2} \int_0^{T_s} \cos(2\omega t + \phi_{in}) + \cos(-\phi_{in}) dt$$

$$= \cancel{\frac{1}{T_s}} \frac{4}{\pi} v_g I_p \frac{1}{2} \cancel{T_s} \cos(-\phi_{in})$$

$$= \frac{2}{\pi} v_g I_p \cos(\phi_{in})$$

Phasor Model:


$$V_{P1} = \frac{4}{\pi} V_g \angle 0^\circ$$

$$I_{P1} = I_p \angle \phi_{in}$$

$$P_{P1} = \frac{1}{2} \frac{4}{\pi} V_g I_p \cos \phi_{in} \\ = \frac{2}{\pi} V_g I_p \cos \phi_{in}$$

Diode Rectifier Sinusoidal Analysis

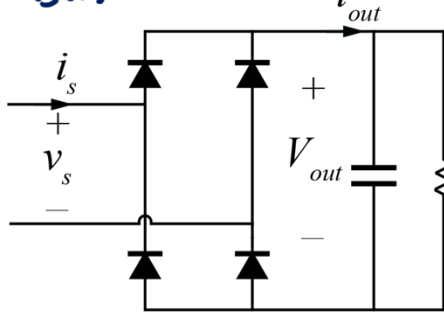Voltage-loaded diode rectifier
 (assume $i_s(t)$ is \approx current source)



By same analysis,

$$v_{s1}(t) = \frac{4}{\pi} V_{out} \sin(2\pi f_s t - \phi_{ps})$$

same analysis w/ $\phi=0$ by ideal diode rectifier

$$I_{out} = \frac{2}{\pi} I_s$$

