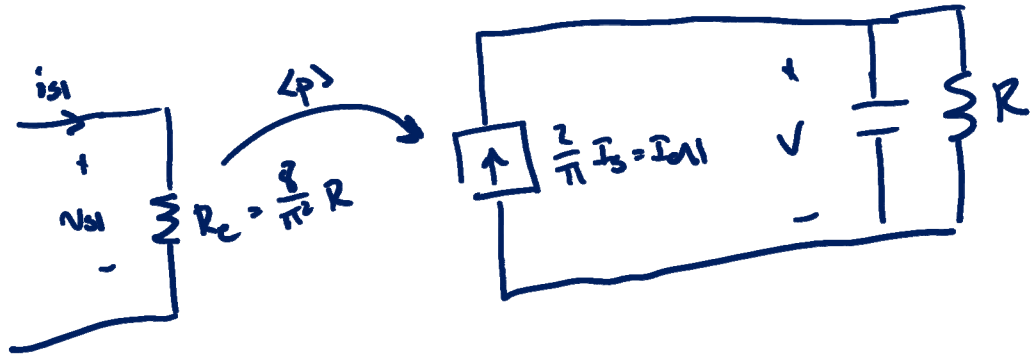


Diode Rectifier Equivalent Circuit



$$v_{s1}(t) = \frac{V_m}{\pi} \sin(2\pi f_s t - \phi_{ps})$$

$$i_{s1}(t) = I_s \sin(2\pi f_s t - \phi_{ps})$$


$$I_{av} = \frac{2}{\pi} I_s$$

$$V_{av} = I_{av} R = \frac{2}{\pi} I_s R$$

for ideal diode rectifier w/ voltage-source output & high- Z input


$$r_{rec} = \frac{v_{s1}(t)}{i_{s1}(t)} = \frac{\frac{4}{\pi} V_{av} \sin(2\pi f_s t - \phi_{ps})}{I_s \sin(2\pi f_s t - \phi_{ps})} = \frac{\frac{4}{\pi} \cdot \left(\frac{2}{\pi} I_s R \right)}{I_s} = \boxed{\frac{8}{\pi^2} R = R_e}$$

Other Implementations

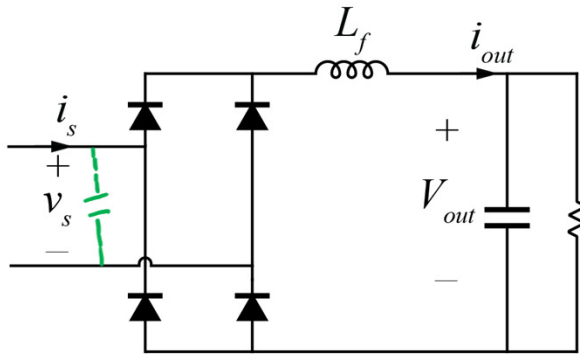

Current-loaded rectifier

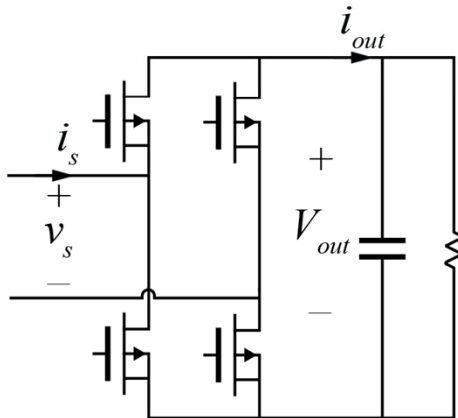current, instead is a squarewave
find fundamental & assume $v_s(t)$ is sinusoidal




Active Rectifier

Can control phase & duty cycle of switching

$$Z_{ee} = R_e + jX_e$$

Complete Equivalent Circuit

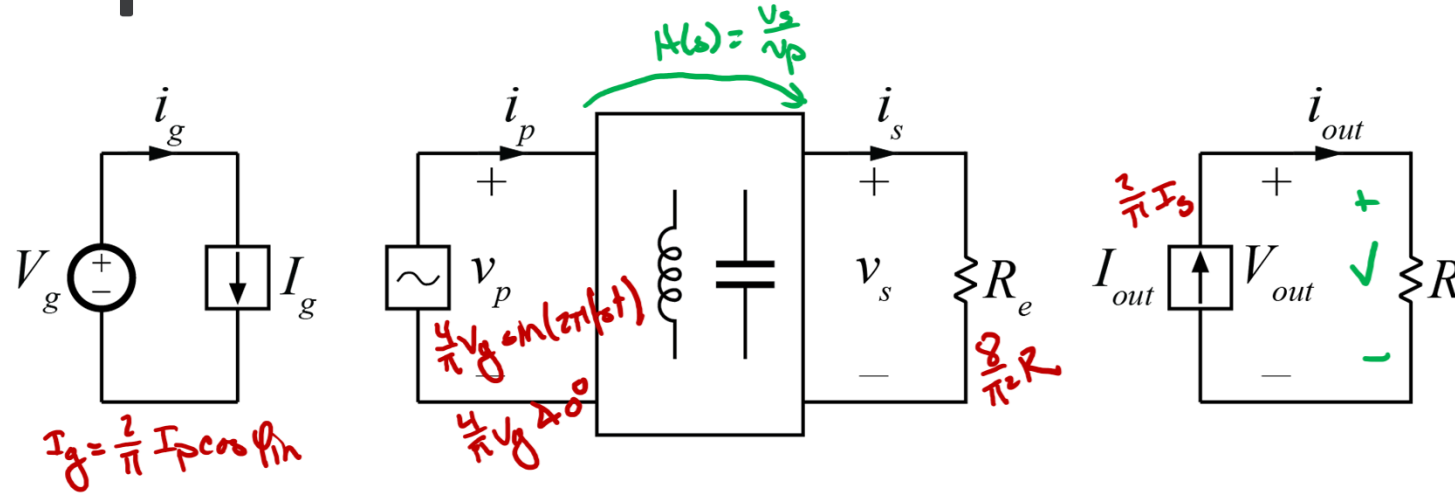

$$M = \frac{V}{v_g} = \frac{V}{I_{out}} \cdot \frac{I_{out}}{I_s} \cdot \frac{I_s}{v_s} \cdot \frac{v_s}{v_p} \cdot \frac{v_p}{v_g}$$




$$M = \cancel{R} \cdot \left(\frac{2}{\pi}\right) \cdot \cancel{\frac{\pi}{8}} \cdot \cancel{\frac{1}{R}} \cdot (|H(s)|) \cdot \cancel{\frac{4}{\pi}}$$

$s \rightarrow j\omega_s$

$$M = |H(s)|$$

$s \rightarrow j\omega_s$

Output Characteristic

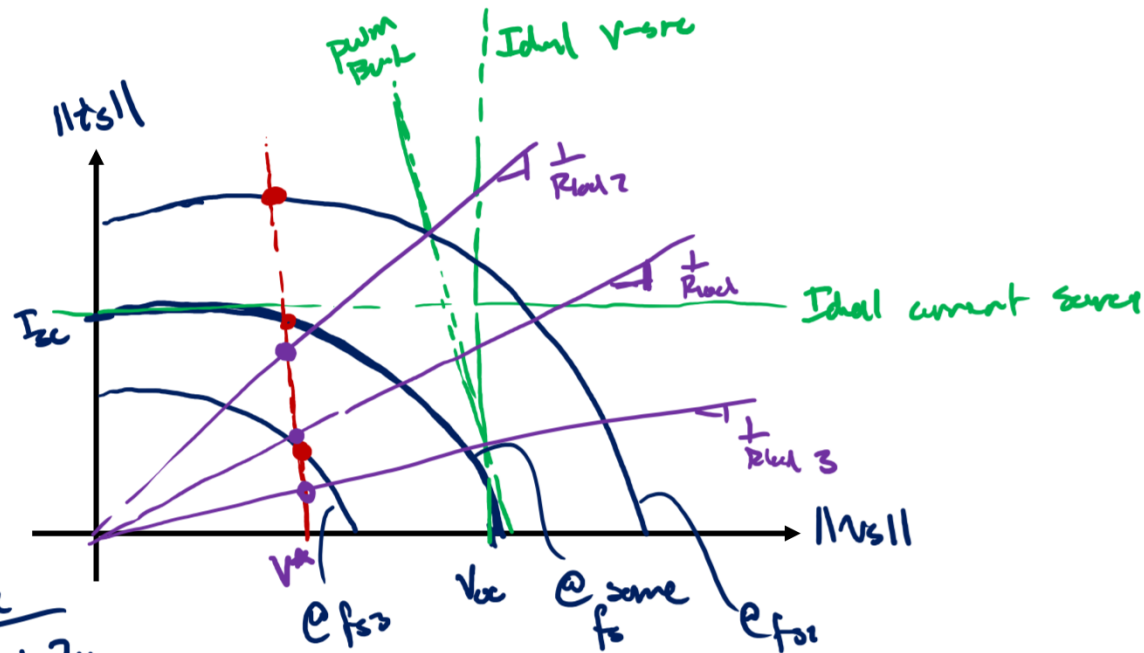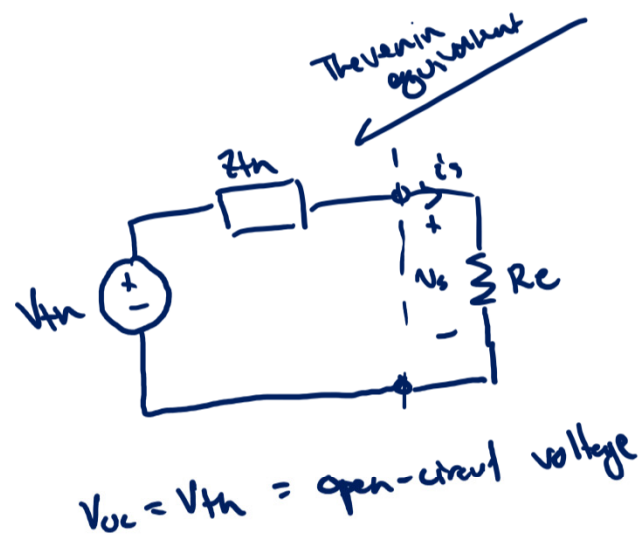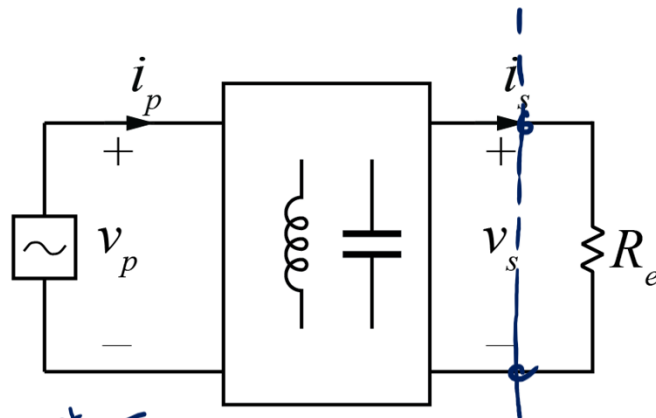

$$V_o = V_{th} \frac{R_e}{R_e + Z_{th}}$$

Assume Z_{th} is dominantly reactive $Z_{th} = \phi + jX_{th}$

$$\|V_o\|^2 = \|V_{th}\|^2 \frac{R_e^2}{R_e^2 + X_{th}^2}$$

$$\frac{\|V_o\|^2 (R_e^2 + X_{th}^2)}{R_e^2 \|V_{th}\|^2} = 1$$

$$\frac{\cancel{R_e^2} \|V_o\|^2 \cancel{R_e^2}}{\cancel{R_e^2} \|V_{th}\|^2} + \frac{\|V_o\|^2 X_{th}^2}{R_e^2 \|V_{th}\|^2} = 1 =$$

$$\boxed{\frac{\|V_o\|^2}{\|V_{oc}\|^2} + \frac{\|i_s\|^2}{\|I_{sc}\|^2} = 1}$$