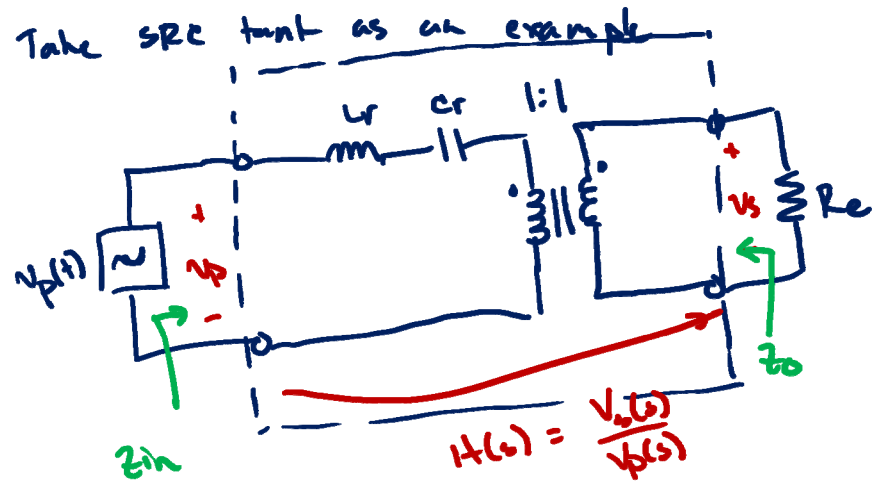


Construction of Tank Transfer Function



$$z_{in} = sL_r + \frac{1}{sC_r} + R_e$$

$$z_o = sL_r + \frac{1}{sC_r}$$

$$H(s) = \frac{R_e}{z_{in}} = \frac{sC_r R_e}{s^2 L_r C_r + sR_e C_r + 1}$$

In standard form

$$H(s) = \frac{\omega_0 / Q_e}{\left(\frac{s}{\omega_0}\right)^2 + \frac{s}{Q_e \omega_0} + 1}$$

Q_e = "loaded Quality factor"

$$Q_e = \frac{R_o}{R_e}$$

$$\omega_0 = \frac{1}{\sqrt{L_r C_r}}, \quad R_o = \sqrt{\frac{L_r}{C_r}}$$

$$M = \|H(s)\|_{s=j\omega_0} = \frac{1}{\sqrt{1 + Q_e^2 \left(\frac{1}{F} - F\right)^2}}$$


Tank Input Impedance

SRC example


$$z_{in} = sL_r + \frac{1}{sC_r} + R_e$$

$$A(s) = \frac{R_e}{z_{in}}$$

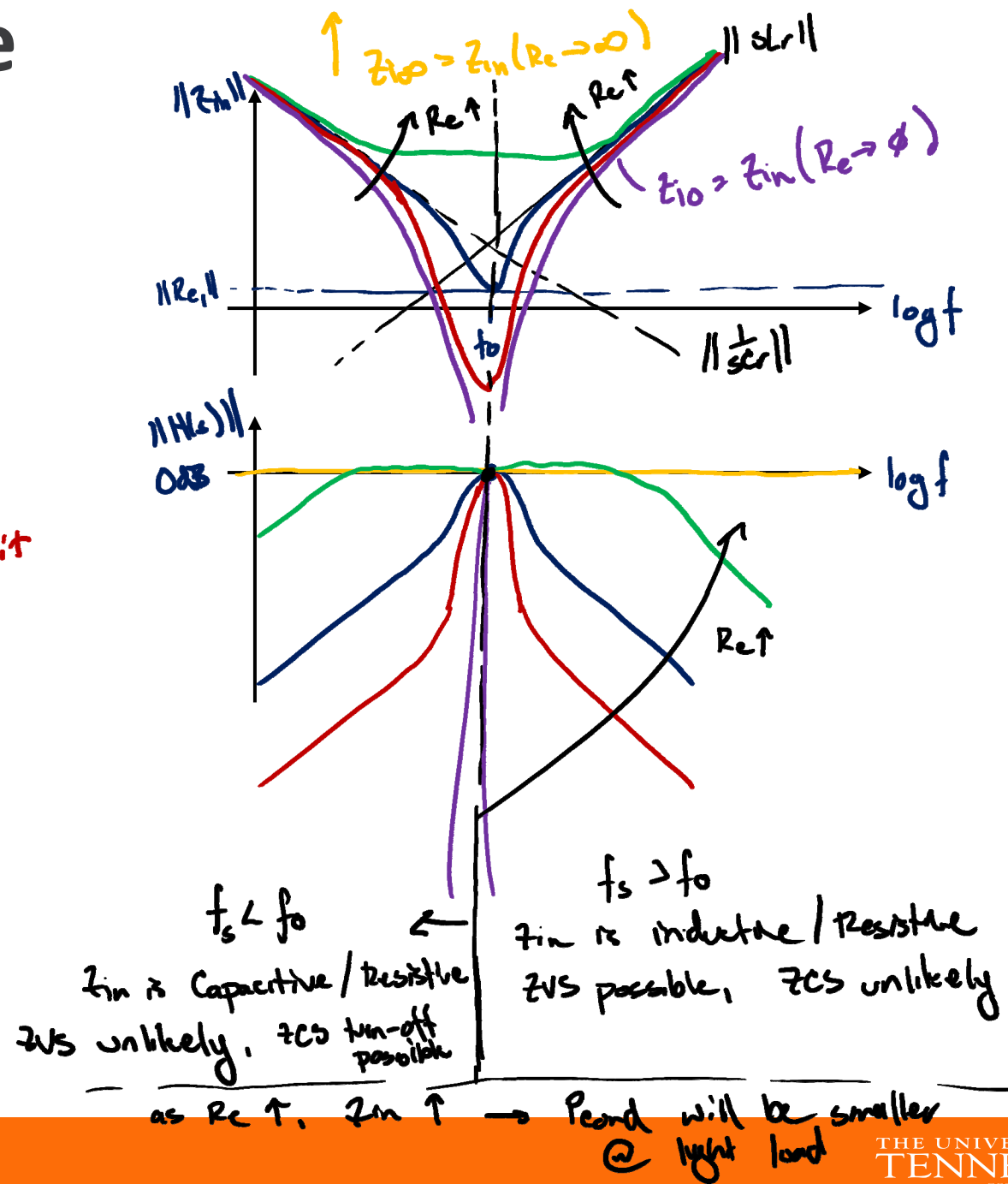
SRC @ $f_0 \rightarrow$
 as $R_e \rightarrow \phi$, $z_{in} \rightarrow \phi$
 meaning circuit cannot tolerate a short-circuit




Series Resonant Tank

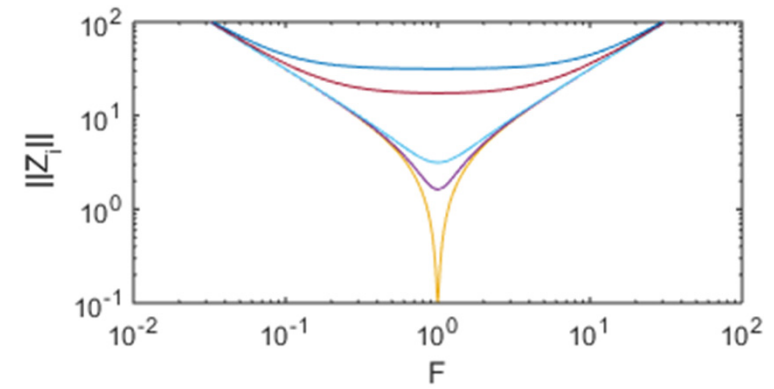


not
by scale

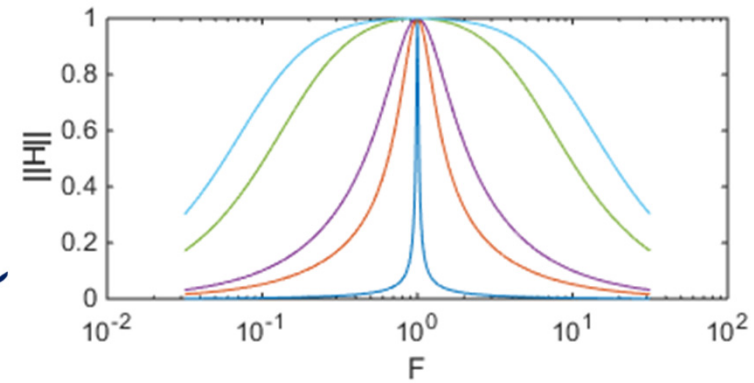

Parallel Resonant Converter

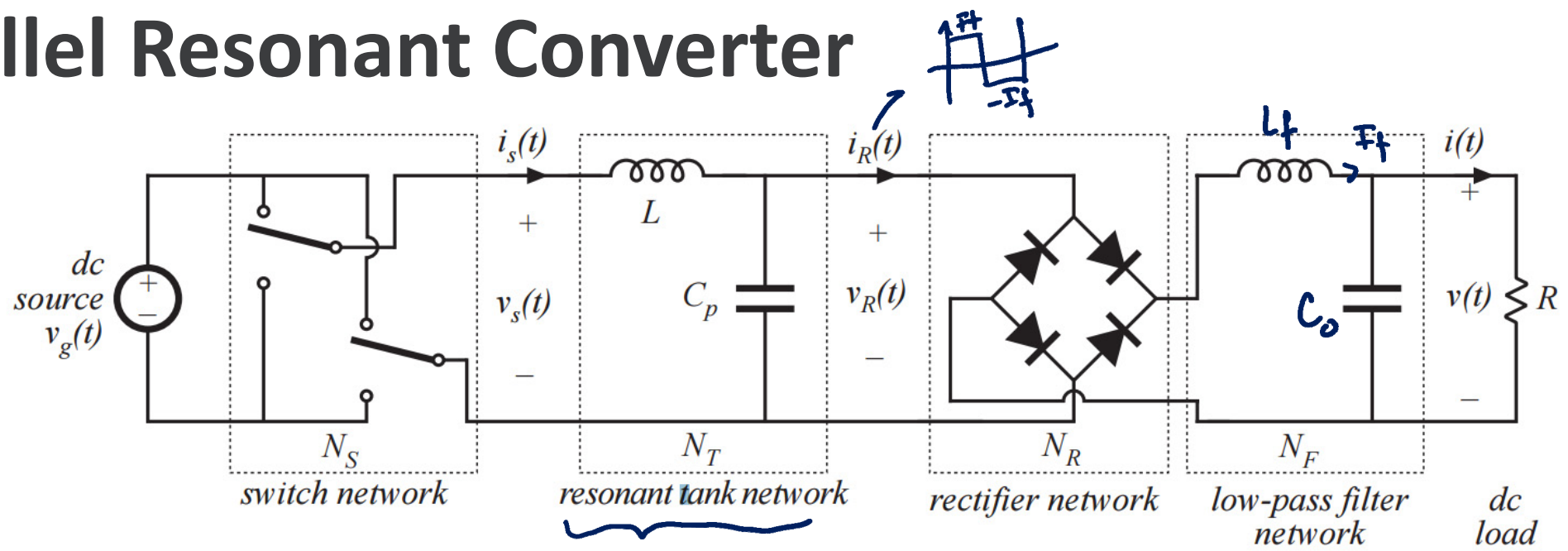


PRC Tank Input Impedance

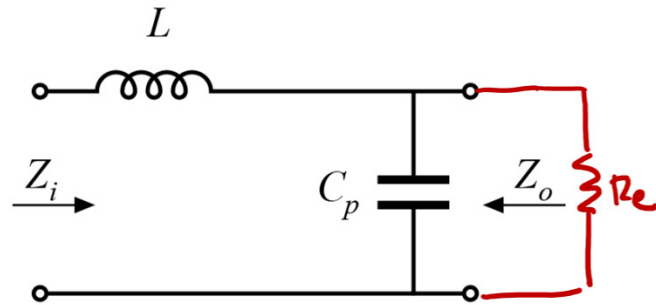

$$Z_{in} = sL + R_e \parallel \frac{1}{sC_p}$$
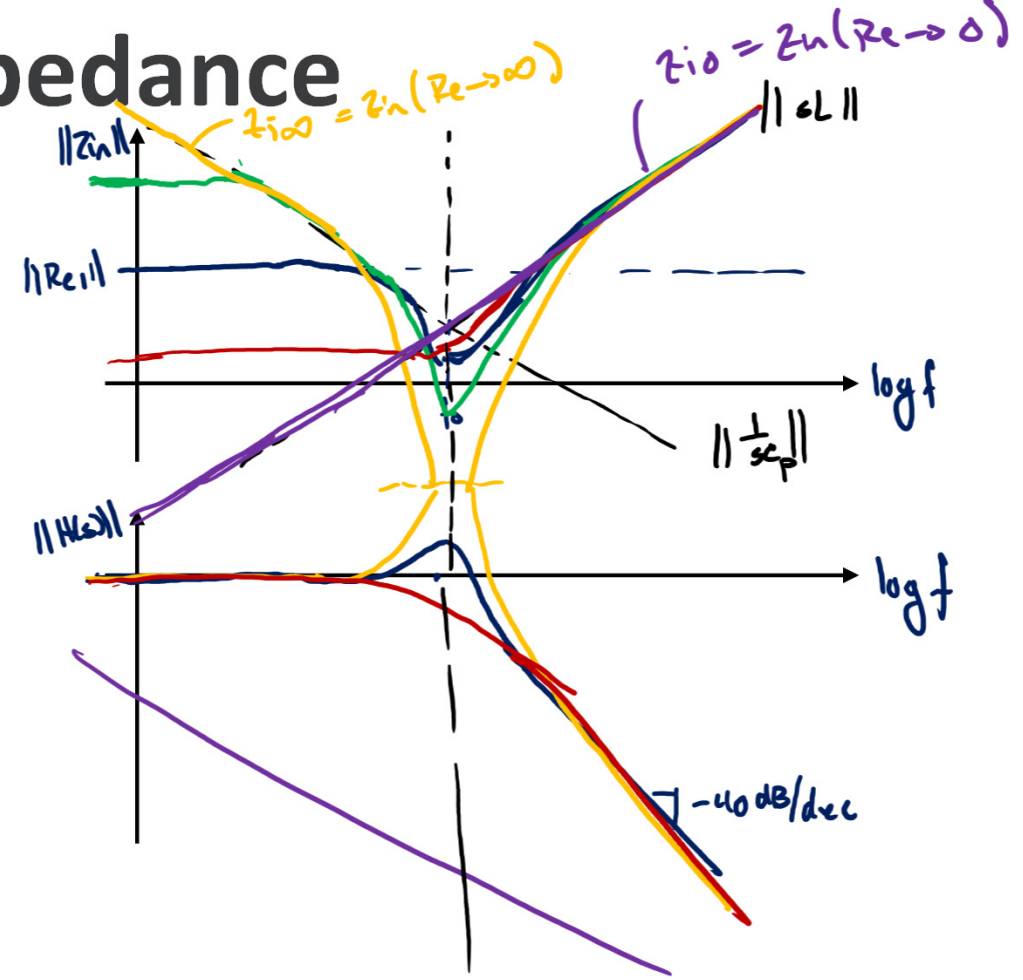
$$H(s) = \frac{R_e \parallel \frac{1}{sC_p}}{Z_{in}}$$



PRC Tank

Textbook (2nd Edition)

Theorem 1 in 19.4.2
(See 22.4 in 3rd Edition)

if tank is a purely reactive $\|Z_i(j\omega)\|$ is
a purely monotonic function of R_e @ any ω_s

Only need to look @ Z_{i0} & $Z_{i\infty}$

