

Chapter 20: Resonant Switch Topologies

2nd Ed.



Chapter 23 in 3rd Edition

- Introduction
- 20.1 The zero-current-switching quasi-resonant switch cell
 - 20.1.1 Waveforms of the half-wave ZCS quasi-resonant switch cell
 - 20.1.2 The average terminal waveforms
 - 20.1.3 The full-wave ZCS quasi-resonant switch cell
- 20.2 Resonant switch topologies
 - 20.2.1 The zero-voltage-switching quasi-resonant switch
 - 20.2.2 The zero-voltage-switching multiresonant switch
 - 20.2.3 Quasi-square-wave resonant switches
- 20.3 Ac modeling of quasi-resonant converters
- 20.4 Summary of key points

The resonant switch concept

General idea:

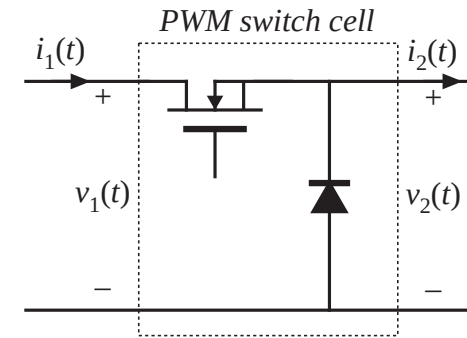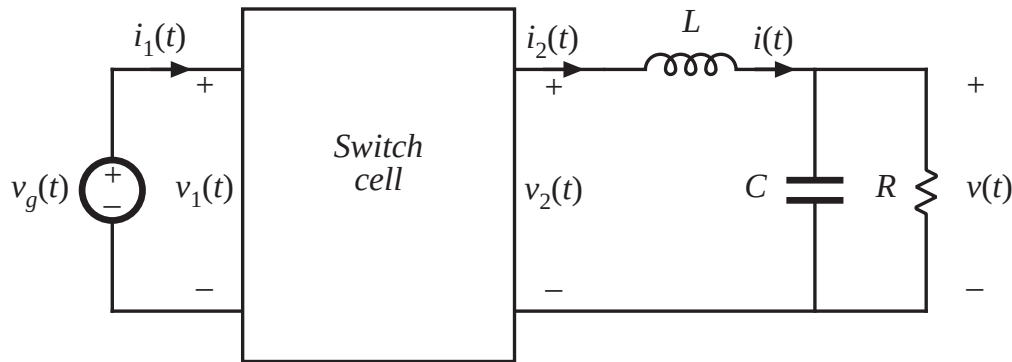- PWM switch network is replaced by a resonant switch network
- This leads to a quasi-resonant or quasi-squarewave version of the original PWM converter




Example: realization of the switch cell in the buck converter

High Frequency Switch Network


Converter examples

High-frequency view of the switch network


Buck

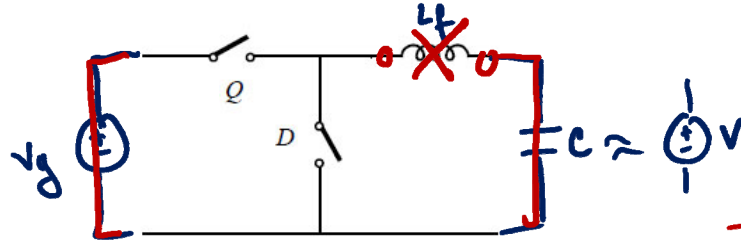



Boost

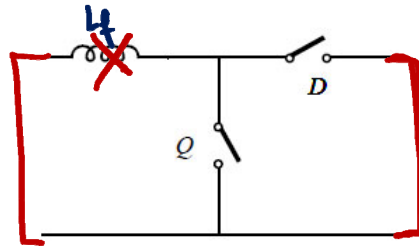

Buck-boost

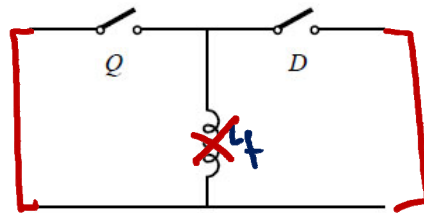

Cuk

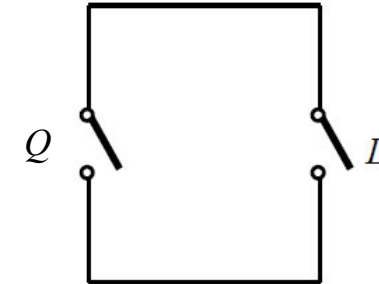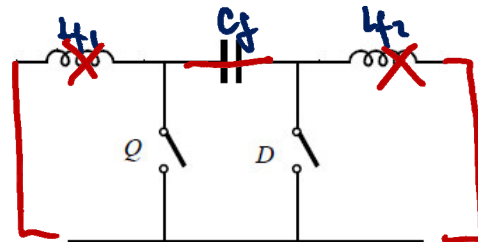


Basic switch implementation options

Q: single-quadrant (transistor)
D: single-quadrant (diode)


Q: current-bidirectional (e.g. MOSFET)
D: current-bidirectional synchronous rectifier
(e.g. MOSFET)

ZVS-QSW: Review

Converter examples

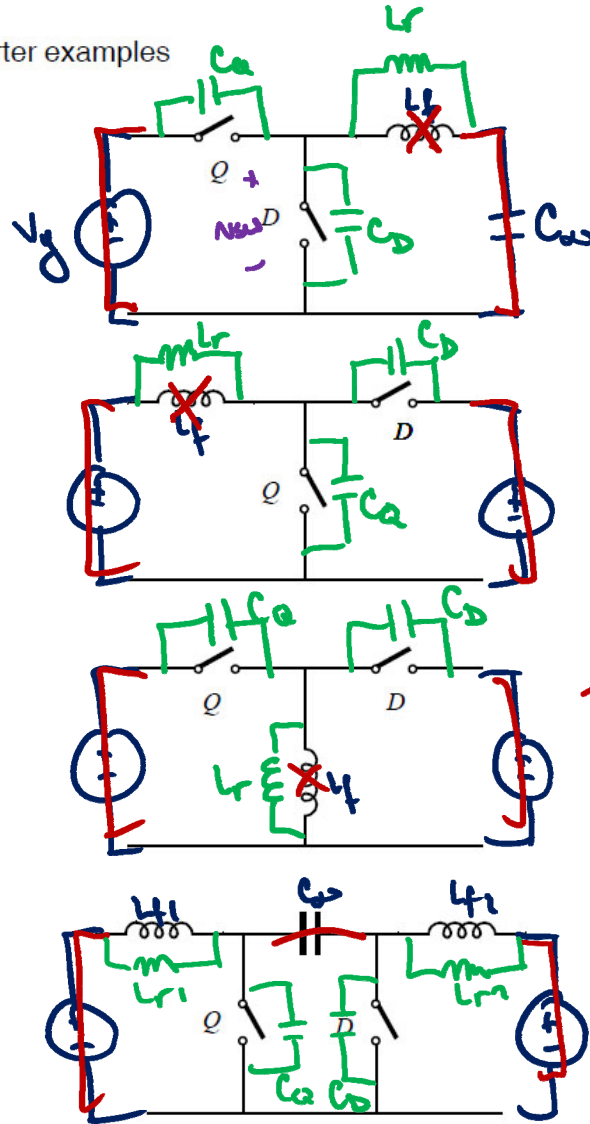

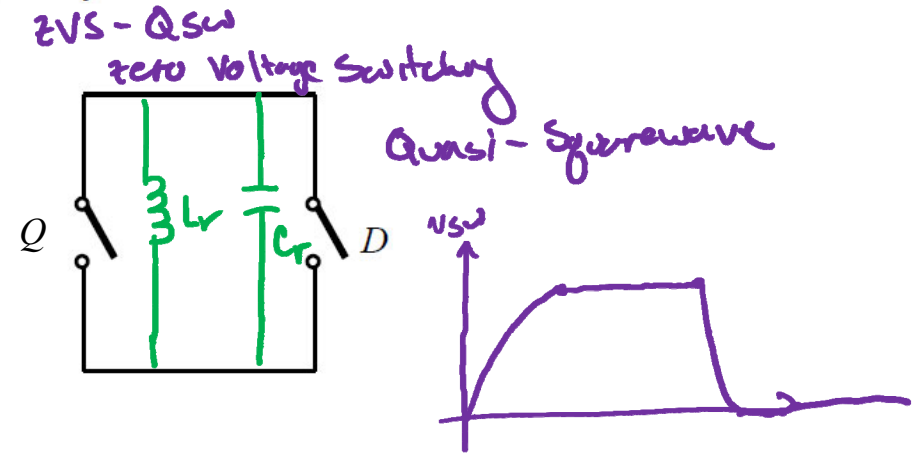High-frequency view of the switch network



Basic switch implementation options

- Q: single-quadrant (transistor)
- D: single-quadrant (diode)
- Q: current-bidirectional (e.g. MOSFET)
- D: current-bidirectional synchronous rectifier (e.g. MOSFET)





Classification of Resonant-Switch Converters

ZVS of Q


ZCS of Q



Discussed in class extensively

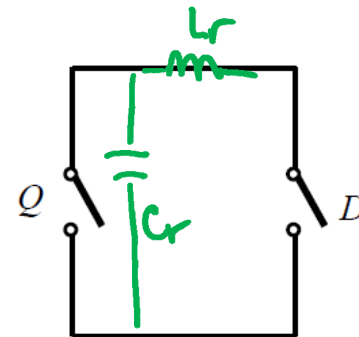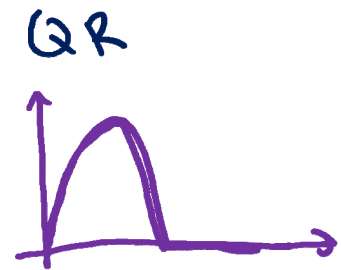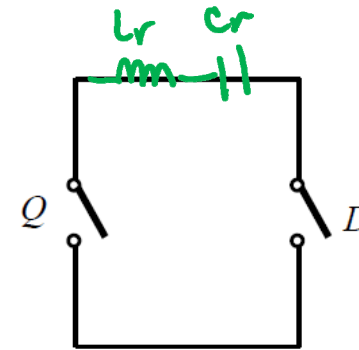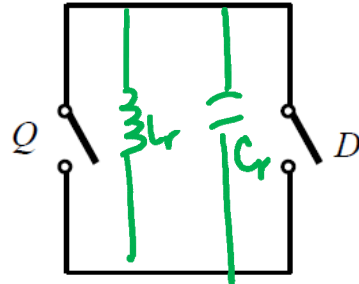


X

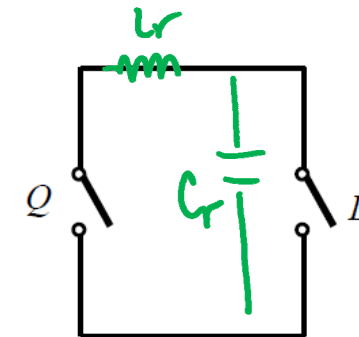



Covered in textbook

ZVS-QR Buck

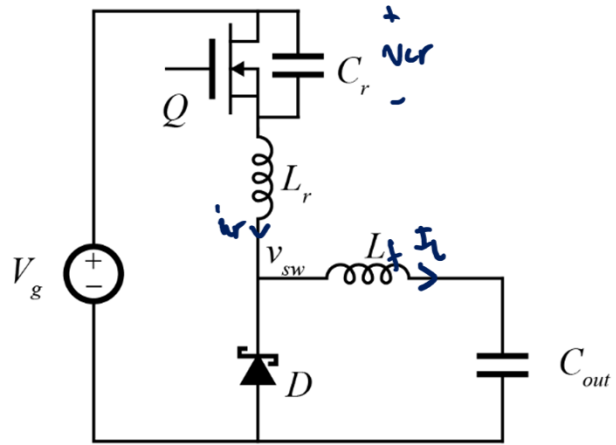

Resonance starts w/ $v_{dy} = v_g$

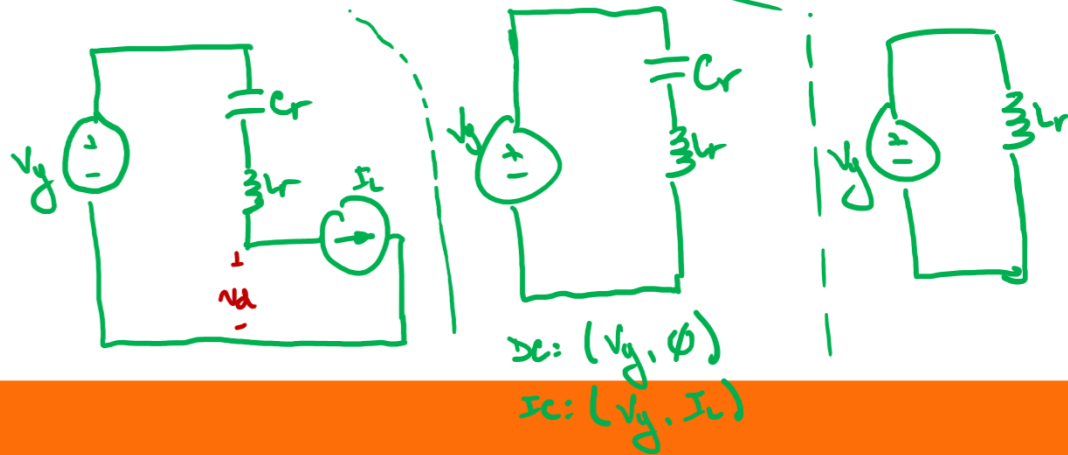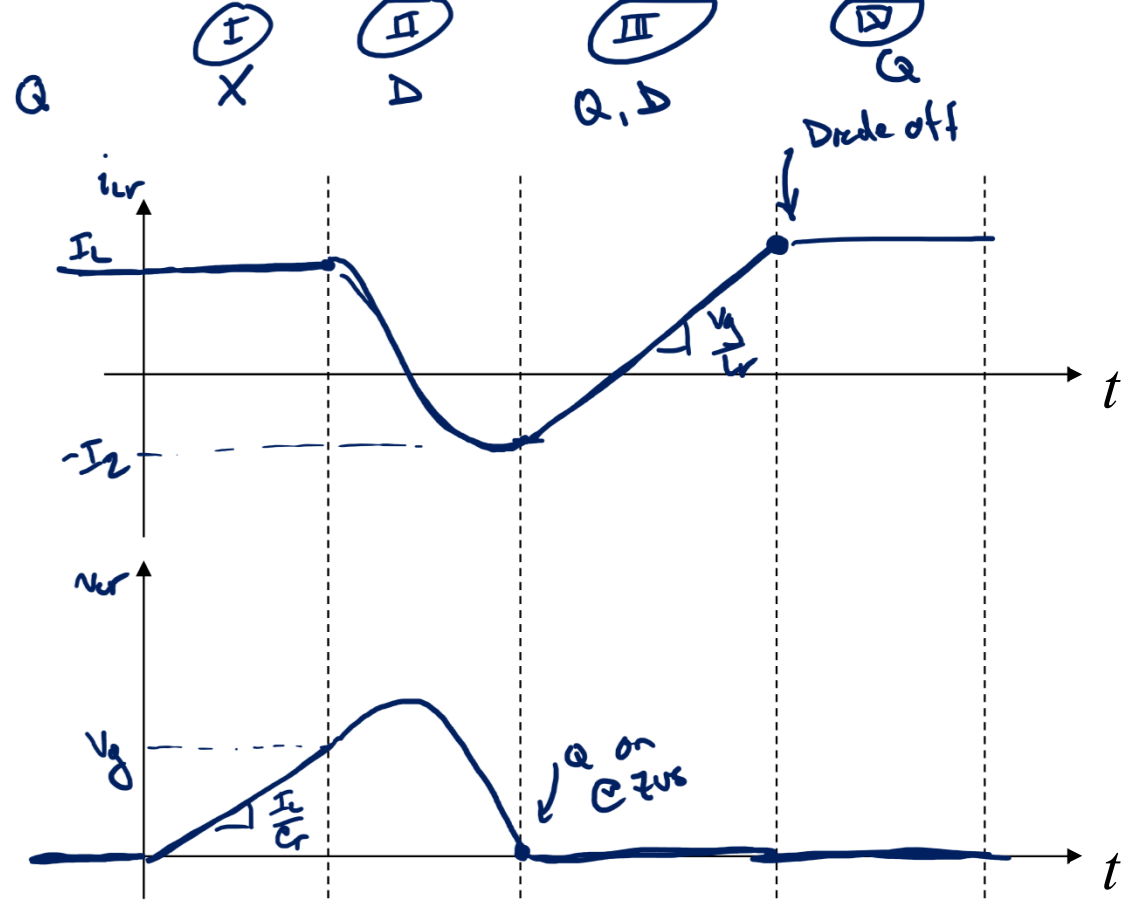- Will increase voltage stress
- + Incorporates power loop inductance & active device capacitance
- Does not integrate diode capacitance
- + I_L is small-ripple
- + $i_{d,avg} = I_L \approx I_{ext}$



ZVS-QR State Plane


$$V_{\text{base}} = V_g \quad I_{\text{base}} = \frac{V_g}{R_0} \quad R_0 = \sqrt{\frac{L_r}{C_r}}$$

(I) $\frac{I_L}{C_r} t_1 = V_g$
 $\theta_1 = \frac{1}{\lambda}$

(II) $\lambda_c^2 = 1 + \lambda_c^2$
 $\beta = \pi + \sin^{-1}\left(\frac{1}{\lambda_c}\right)$

(III) $\frac{V_g}{L_r} t_3 = I_L + I_2$
 $\theta_3 = \lambda_c + \lambda_c$

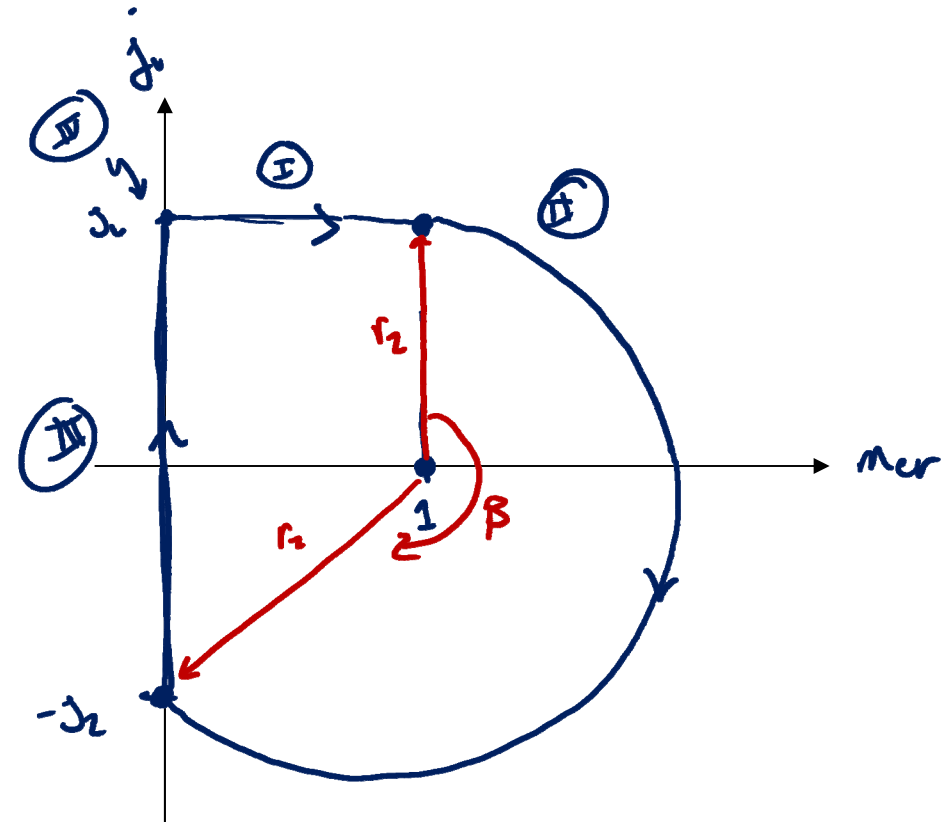(IV) $\theta_1 + \beta + \theta_3 + \theta_4 = \frac{2\pi}{F}$



ZVS condition:

$$r_2 = \lambda_c \geq 1$$

Averaging


2 filter elements

for C_{out} : $\langle i_{co} \rangle = \phi \rightarrow I_L = \frac{V}{R}$

for L_f

$$\langle N_{Lf} \rangle / T_s = \phi = V_g - V - \langle N_{Cr} \rangle / T_s - \langle N_{Lf} \rangle / T_s$$

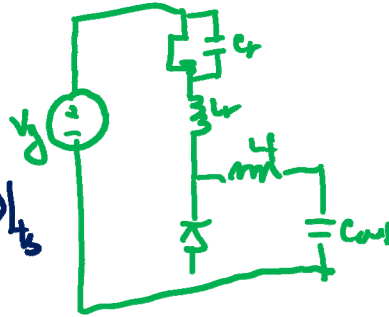
$$N_{Lf}(t) = V_g - N_{Cr}(t) - N_{Lf}(t) - V$$



$$V = V_g - \frac{1}{T_s} \left[\frac{1}{2} V_g t_1 + V_g t_p + L_r (I_L + I_2) \right]$$

$$M = \frac{V}{V_g} = 1 - \frac{1}{T_s} \left[\frac{1}{2} t_1 + t_p + \frac{L_r}{V_g} (I_L + I_2) \right]$$
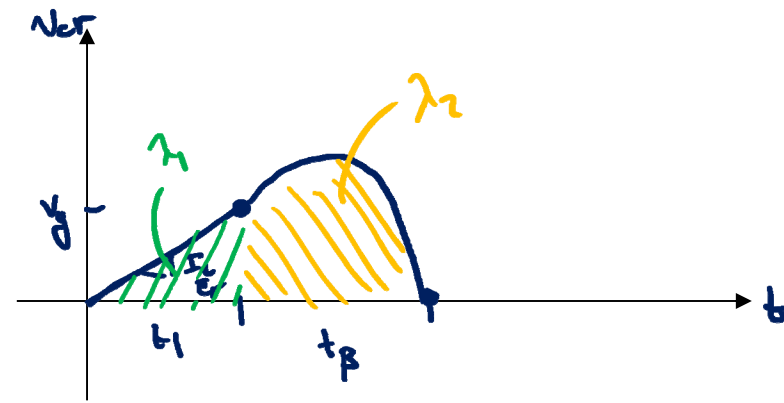
$$M = 1 - \frac{F}{2\pi} \left(\frac{\theta_1}{2} + \beta + \lambda_2 + \lambda_1 \right)$$



$$\langle N_{Cr} \rangle / T_s = \frac{1}{T_s} \int_0^{T_s} N_{Cr}(t) dt = \frac{1}{T_s} [\lambda_1 + \lambda_2]$$

$$\lambda_1 = \frac{1}{2} V_g t_1$$

$$\lambda_2 = \int_{t_1}^{t_1+t_p} (V_g - N_{Cr}) dt = \int_{t_1}^{t_1+t_p} V_g - L_r \frac{di_{Cr}}{dt} dt$$

$$= V_g t_p - L_r (-I_L - I_2)$$