


Complete Solution

$$M = 1 - \frac{F}{2\pi} \left(\frac{Q}{2} + \beta + J_2 + J_0 \right)$$


$$M = 1 - \frac{F}{2\pi} \left(\frac{1}{2J_0} + \pi + \sin^{-1} \left(\frac{1}{J_0} \right) + \sqrt{J_0^2 - 1} - J_0 \right)$$

In book, this is $M = 1 - F \cdot \underline{\underline{P_{1/2}}} \left(\frac{1}{J_0} \right)$

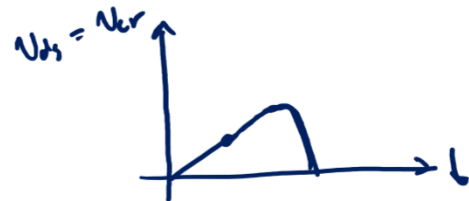The ZVS-QR waveforms we analyzed are for a "half-wave" implementation




the full-wave implementation:

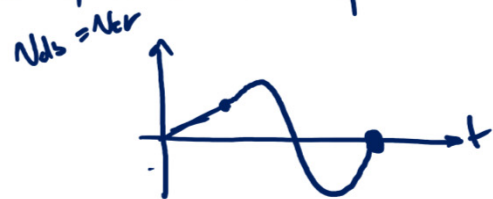

MosFET must be voltage bidirectional

eg.
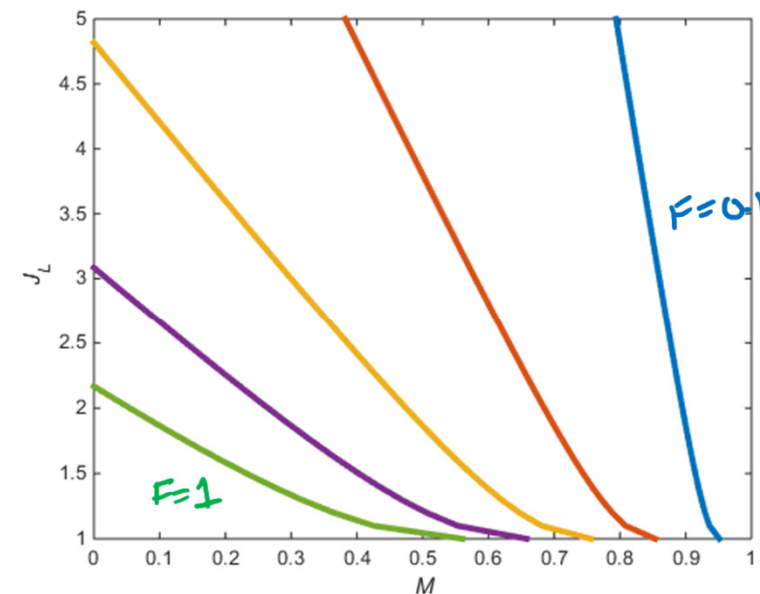
$$M = 1 - F \cdot P \left(\frac{1}{2} \right)$$



MOSFET Voltage Stresses

Peak voltage on transistor $m_{ds,ph} = m_{cr,ph} = 1 + r_2 = 1 + \beta_L$
together with zvs condition $\beta_L \geq 1$

if we get zvs, $v_{ds,ph} \geq 2 \cdot V_g \rightarrow$ only zvs @ full load
if e.g. we want for 80% of load range

at full load $\beta_L = 5$


$$m_{ds,ph} = 1 + 5 = 6$$

$$v_{ds,ph} = 6 \cdot V_g$$



Test Circuit

48-to-16V converter
 $f_s = 1 \text{ MHz}$



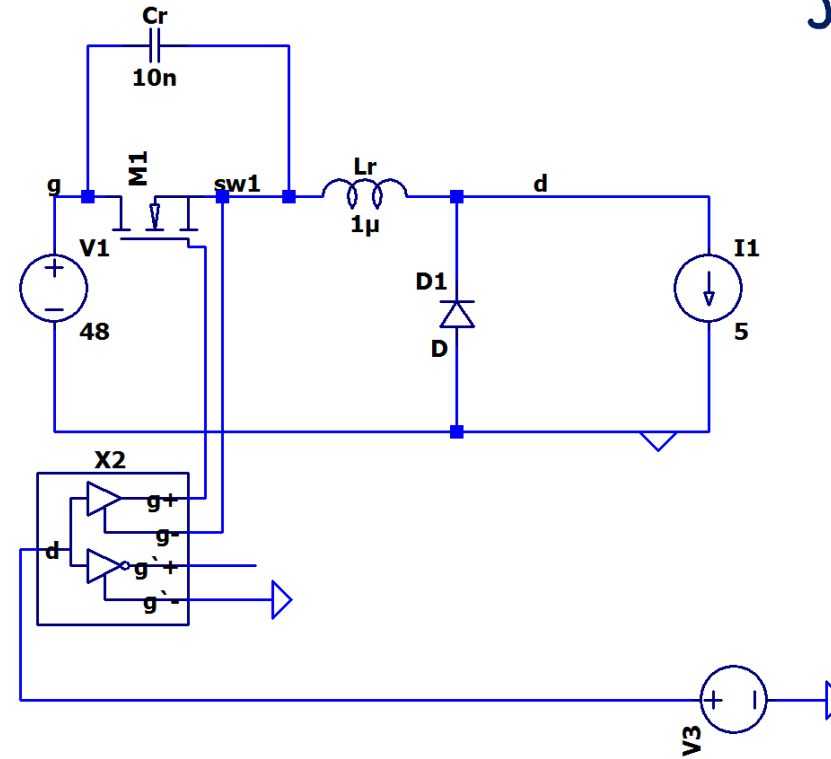
$$J_L = \frac{5A}{48V / \sqrt{\frac{1m}{10n}}} \approx 1 \rightarrow \text{operating @ ZVS bound!}$$




Simulation Results

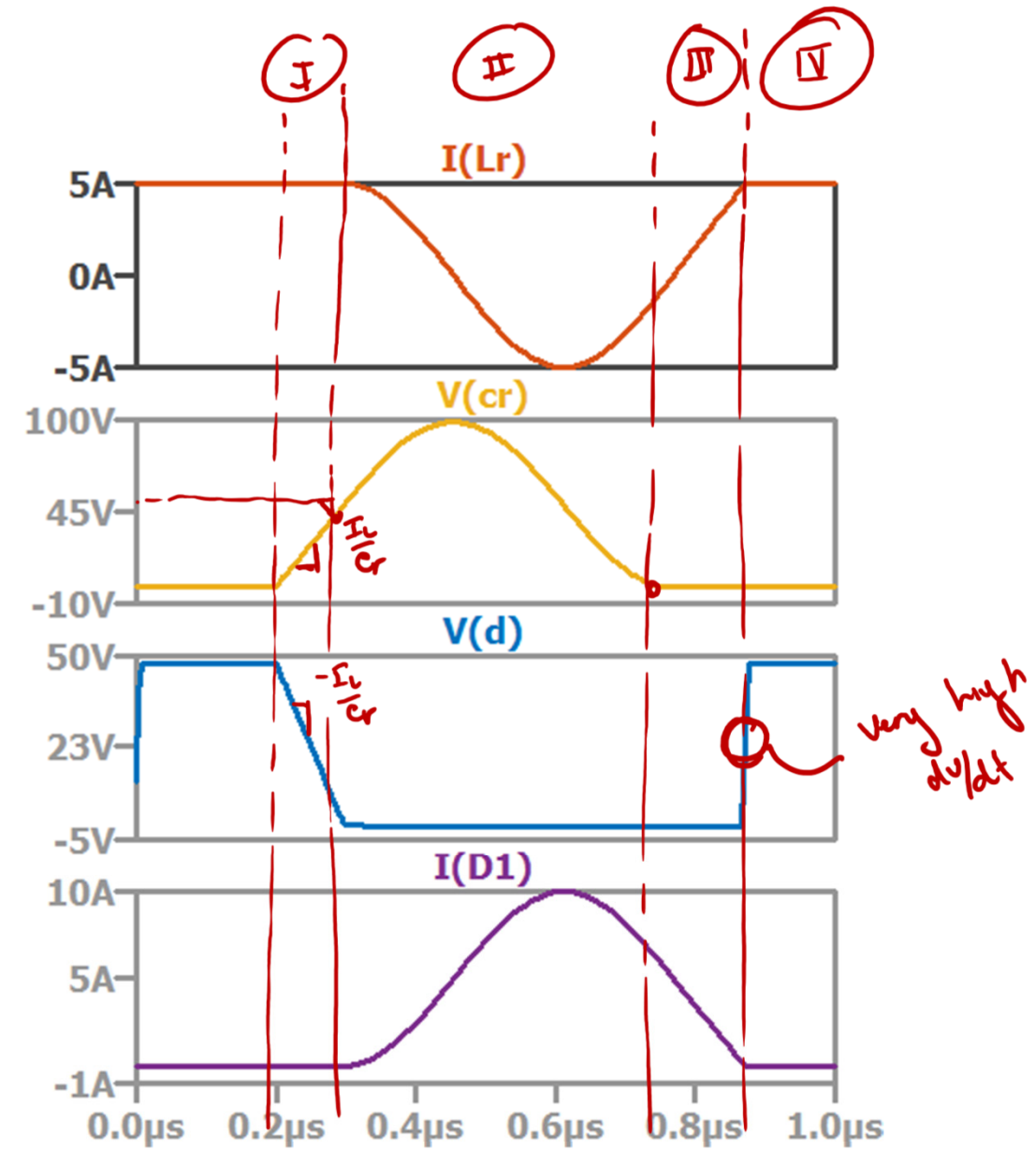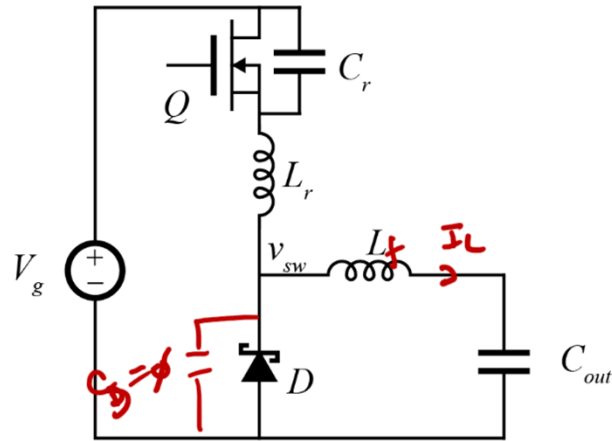


Diode Capacitance

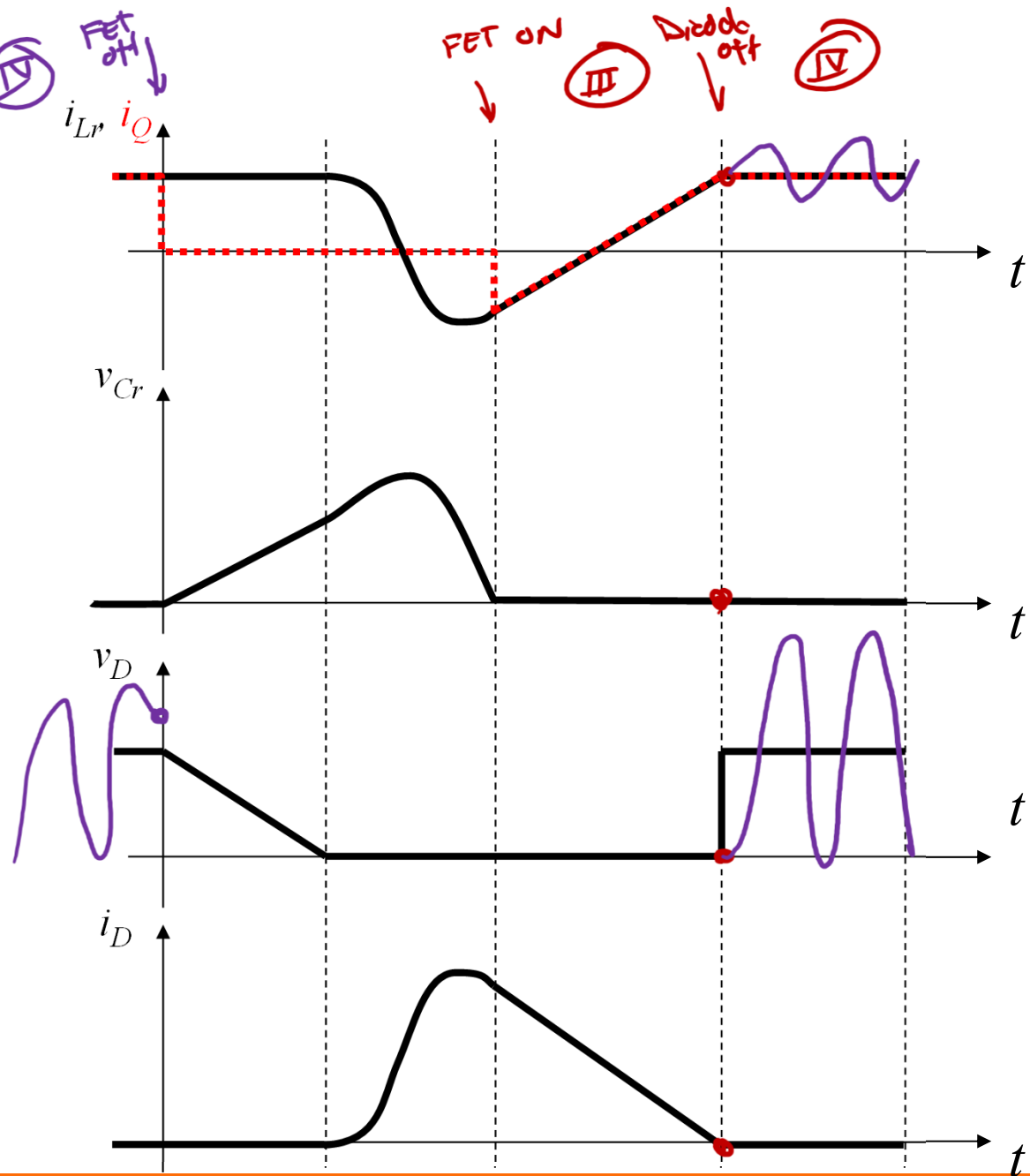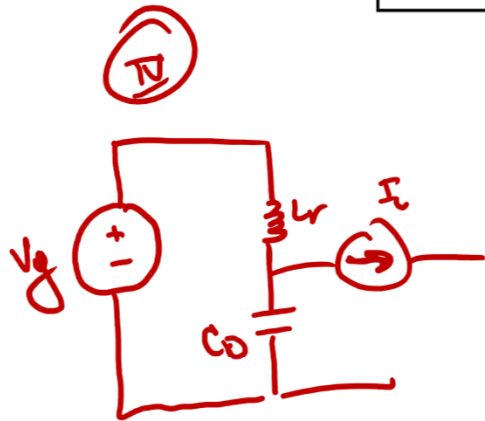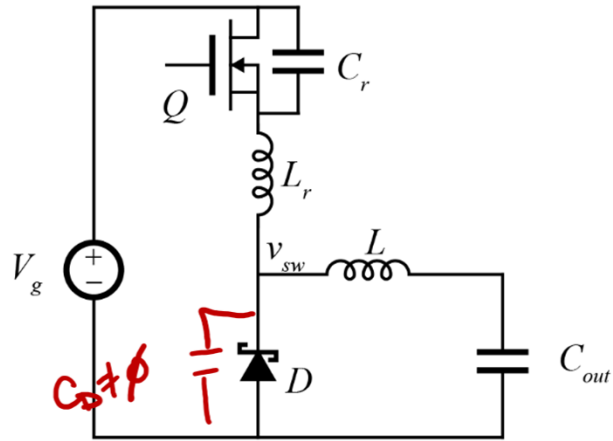

Simulation Results: Diode Capacitance

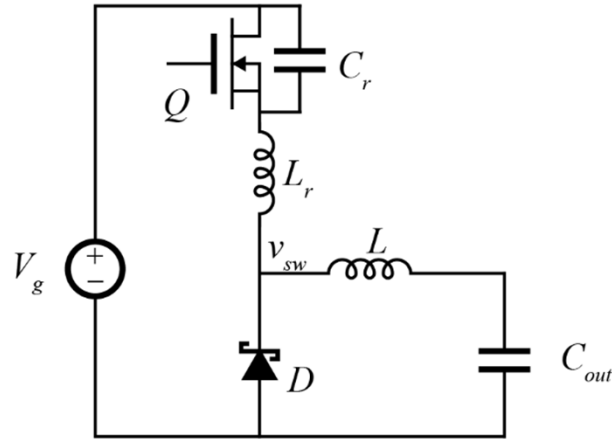


$C_D = 100\text{pF}$
 1nF
 10nF

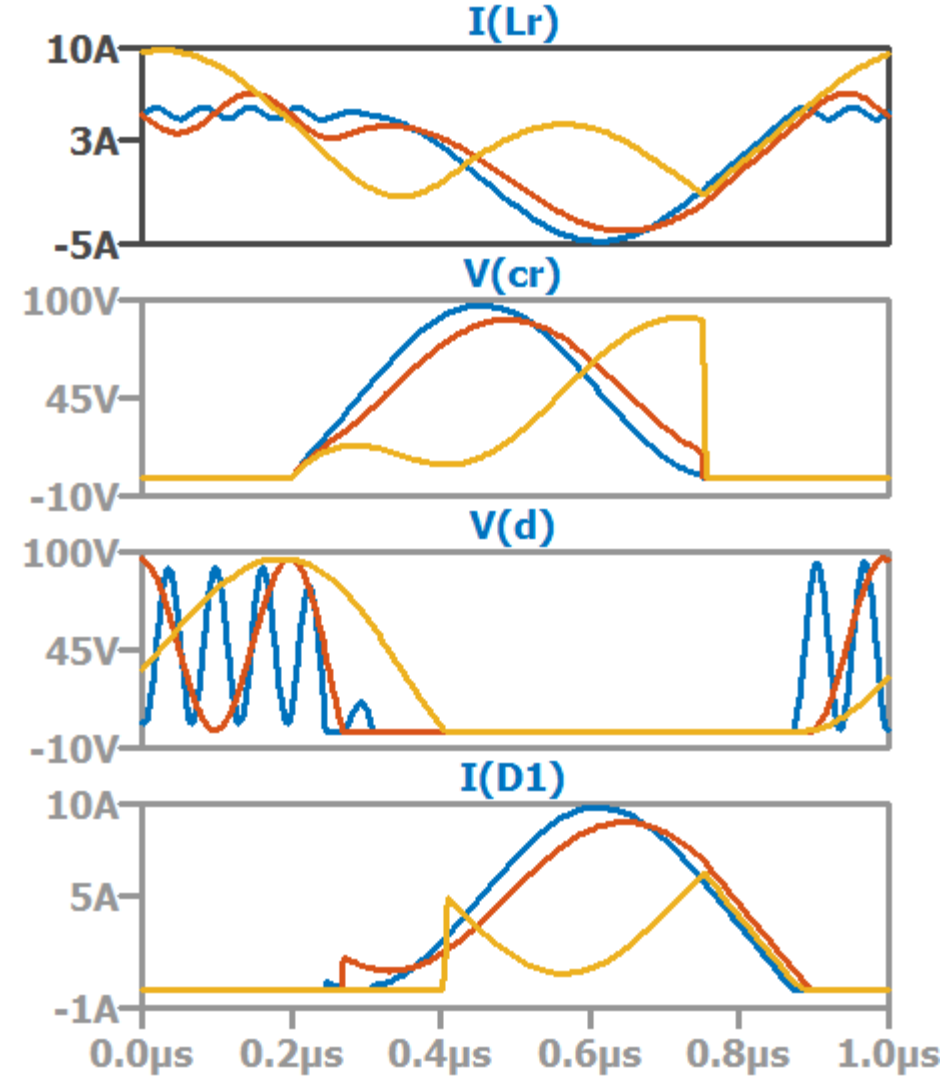


Wishlist: Multi-Resonant

ZVS-MR
switch network

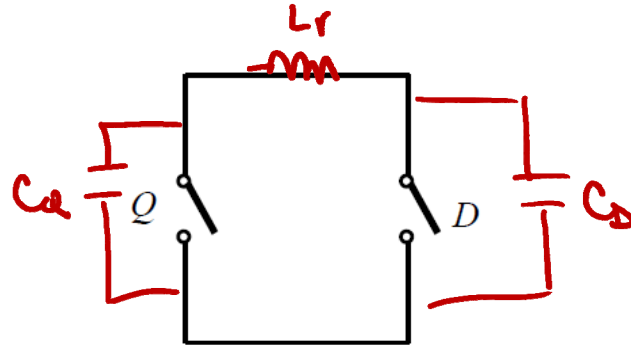

ZVS-MR Buck

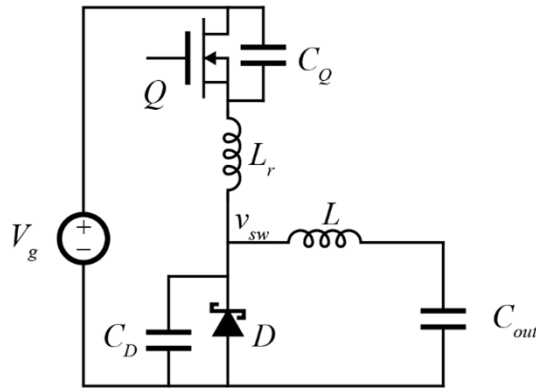

Conducting Devices





Q & D

Q

D

X

EQ circuit

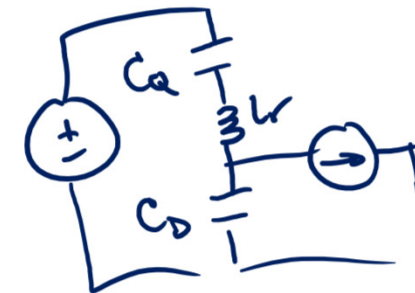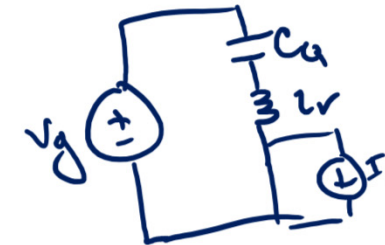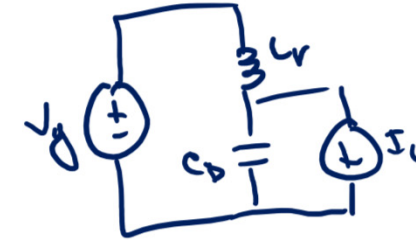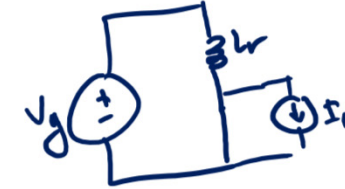

R_o

X
Linear circuit

$$\sqrt{\frac{L_r}{C_D}}$$

$$\sqrt{\frac{L_r}{C_a}}$$

$$\sqrt{\frac{L_r}{C_{eq}}}$$

$$C_{eq} = \frac{C_D C_a}{C_D + C_a}$$

Operating Modes

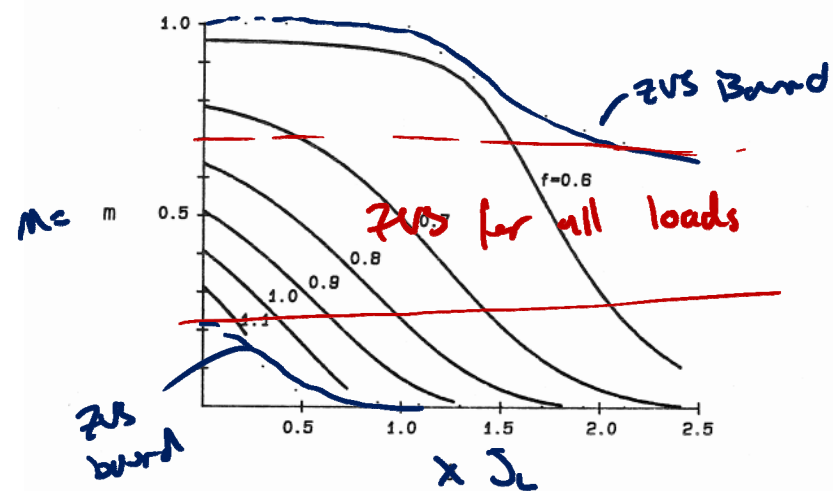


Figure 10.7: Load-to-output DC characteristics of a ZV-MR converter operating in modes (I, II)₁.

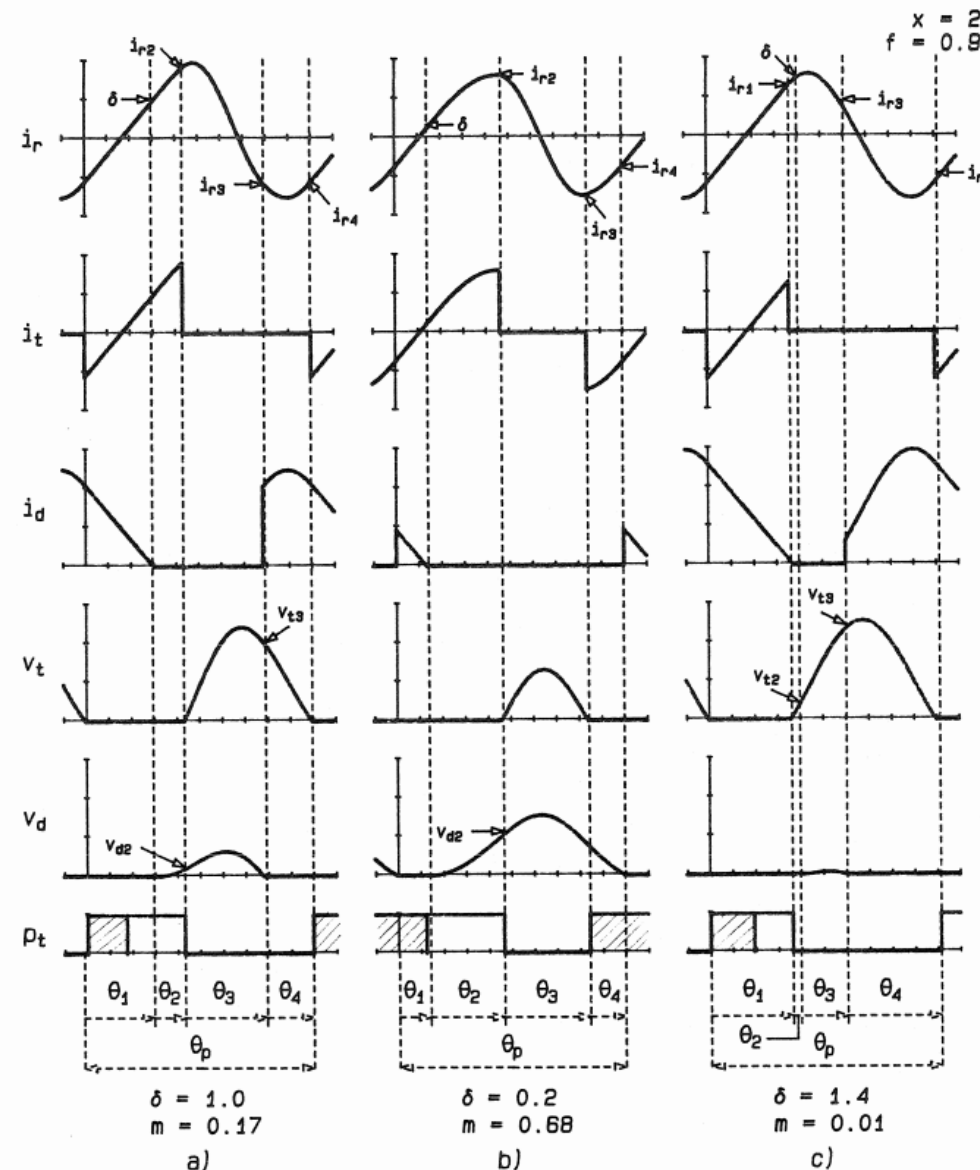
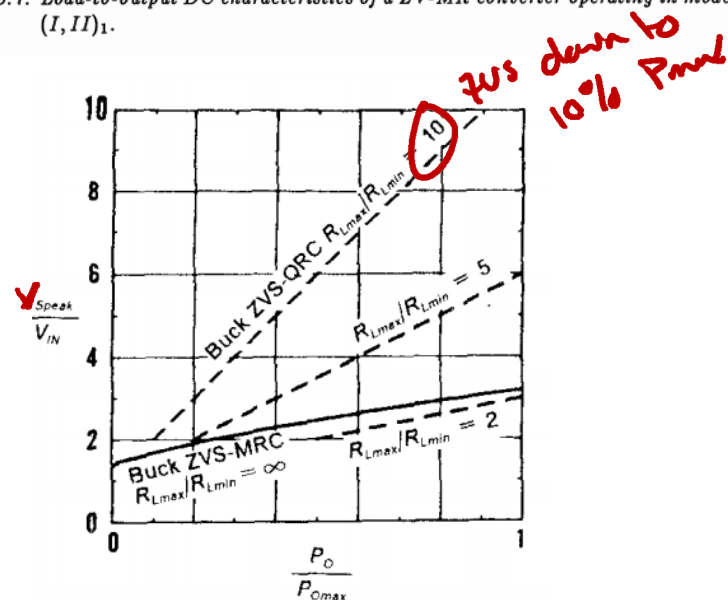


Figure 10.2: Typical waveforms for a ZV-MR converter operating in modes I₁ (a), II₁ (b) or III₁ (c).