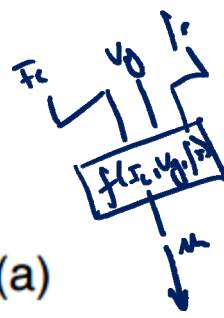


SSM, PWM Case




Textbook, Fig.7.17(a)

for resonant case, replace

$$D \rightarrow M$$

$$\hat{d} \rightarrow \hat{m}$$

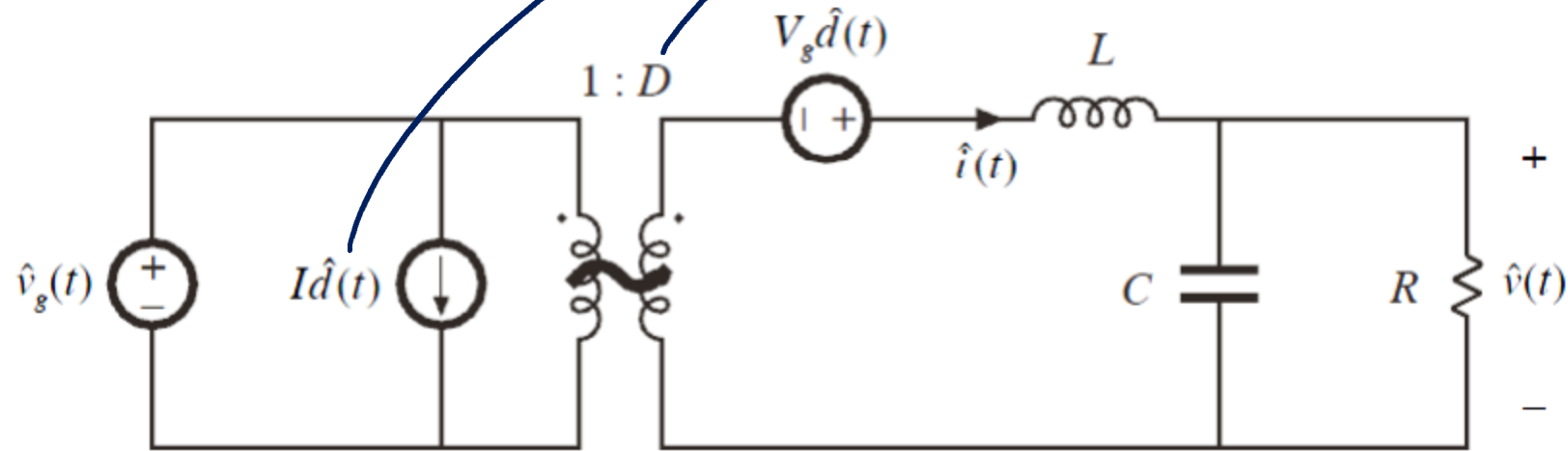

ZVS-QR Switch Cell SSM

$$\mu = 1 - F \cdot \frac{1}{2\pi} \left[\frac{1}{2\lambda} + \pi + \sin^{-1}\left(\frac{1}{\lambda}\right) + \sqrt{\lambda^2 - 1} + \lambda \right] = 1 - F \cdot P_{1/2}\left(\frac{1}{\lambda}\right)$$

$$F = \frac{f_s}{f_0} \quad \lambda = \frac{I_L R_0}{V_g}$$

$$= 1 - \frac{f_s}{f_0} P_{1/2}\left(\frac{V_g}{I_L R_0}\right)$$

$$\mu = f(I_L, V_g, f_s)$$

$$\frac{\partial \mu}{\partial I_L} = - \frac{f_s}{f_0} \frac{\partial P_{1/2}}{\partial \lambda} \cdot \left(\frac{-V_g}{I_L^2 R_0} \right)$$

$$\frac{\partial \mu}{\partial V_g} = - \frac{f_s}{f_0} \cdot \frac{\partial P_{1/2}}{\partial \lambda} \cdot \left(\frac{1}{I_L R_0} \right)$$

$$\frac{\partial \mu}{\partial f_s} = - \frac{1}{f_0} P_{1/2}\left(\frac{1}{\lambda}\right)$$

$$\hat{\mu} = \underbrace{\frac{\partial \mu}{\partial I_L} \hat{I_L}}_{K_i} + \underbrace{\frac{\partial \mu}{\partial V_g} \hat{V_g}}_{K_v} + \underbrace{\frac{\partial \mu}{\partial f_s} \hat{f_s}}_{K_c}$$

$$P_{1/2}\left(\frac{1}{z}\right) = \frac{1}{2\pi} \left[\frac{1}{2z} + \pi + \sin^{-1}\left(\frac{1}{z}\right) + \sqrt{z^2-1} + z \right]$$


$$\frac{\partial P_{1/2}\left(\frac{1}{z}\right)}{\partial z} = \frac{1}{2\pi} \left[\frac{-1}{2z^2} + \left(\frac{-1}{z^2}\right) \cdot \frac{1}{\sqrt{1-\left(\frac{1}{z}\right)^2}} + \frac{1/2}{\sqrt{z^2-1}} (2z) + 1 \right]$$

$$= \frac{1}{2\pi} \left[1 - \frac{1}{2z^2} - \frac{1/z}{\sqrt{z^2-1}} + \frac{z}{\sqrt{z^2-1}} \right]$$


$$= \frac{1}{2\pi} \left[1 - \frac{1}{2z^2} + \frac{1}{z} \frac{z^2-1}{\sqrt{z^2-1}} \right]$$

$$\boxed{\frac{\partial P_{1/2}\left(\frac{1}{z}\right)}{\partial z} = \frac{1}{2\pi} \left[1 - \frac{1}{2z^2} + \frac{1}{z} \sqrt{z^2-1} \right]}$$

SSM, Soft-Switching Buck

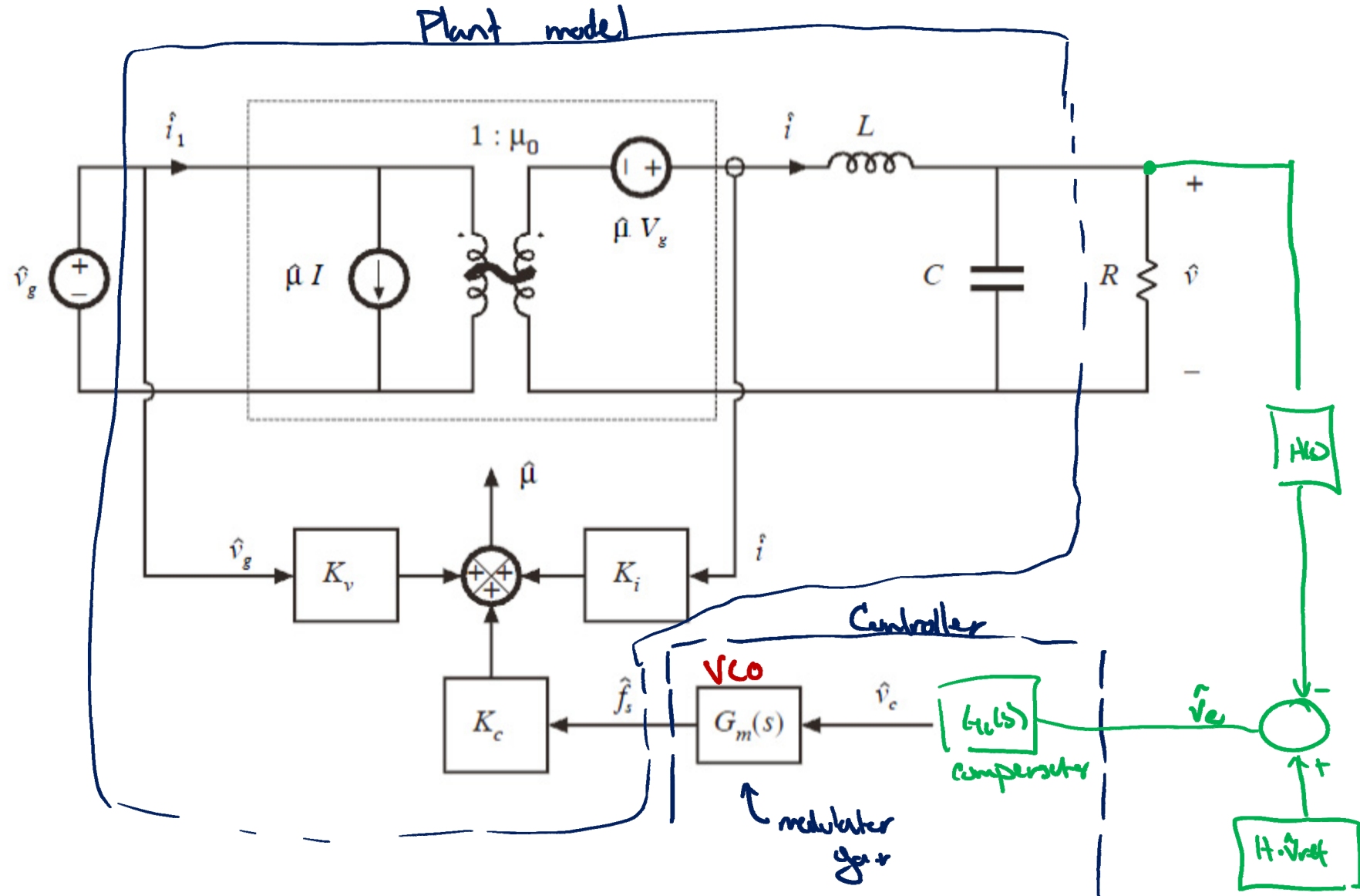


PWM Transfer Functions

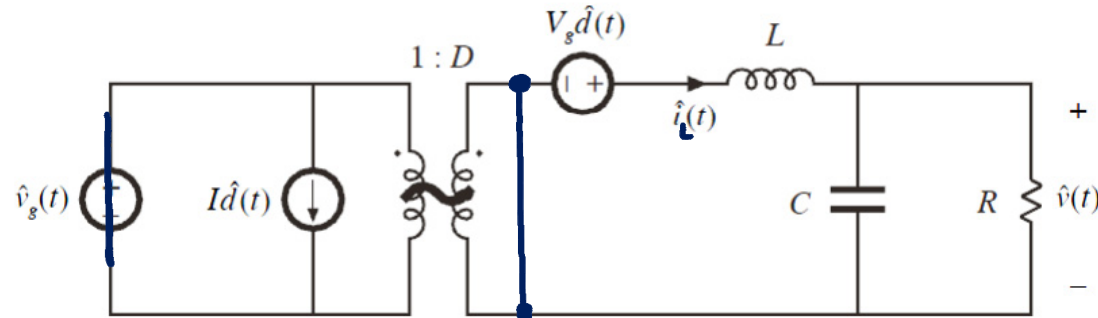


$$G_{va} = \left. \frac{\hat{v}}{\hat{a}} \right|_{\hat{v}_g=0} = V_g \frac{R \parallel \frac{1}{sC}}{sL + R \parallel \frac{1}{sC}} = \frac{V_g}{s^2 LC + s \frac{L}{R} + 1}$$

$$G_{ia} = \left. \frac{\hat{i}_L}{\hat{a}} \right|_{\hat{v}_g=0} = V_g \frac{1}{sL + R \parallel \frac{1}{sC}} = \frac{V_g (1 + sCR)}{s^2 LC + s \frac{L}{R} + 1}$$

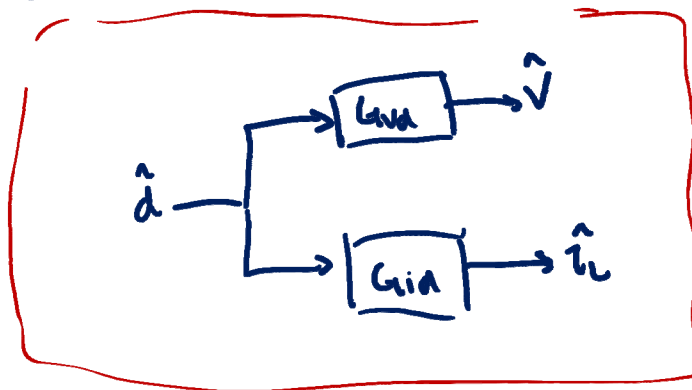

model w/ only $\hat{a}$ as
varying indep. input

QR Transfer Functions

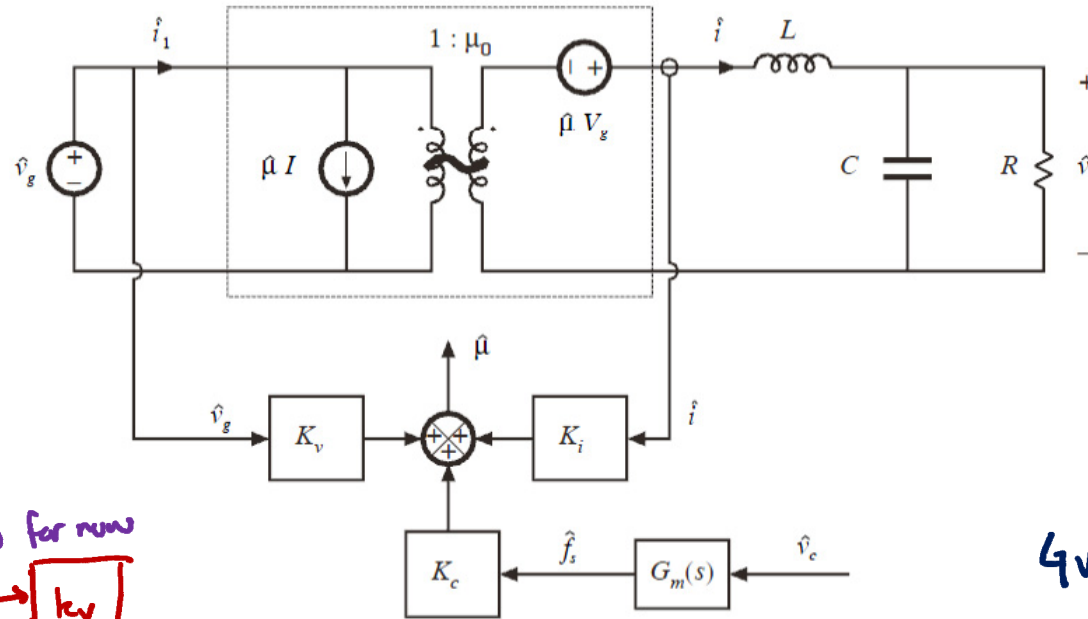


$$G_{vd} = \frac{\hat{v}}{\hat{n}} = G_{vd} \text{ in PWM case}$$

$$G_{VM} = v_g \frac{1}{\epsilon^2 \kappa + \epsilon \frac{\kappa}{R} + 1}$$

$$G_{im} = \frac{\hat{z}}{\hat{m}} = G_{id} \text{ in Pulm case}$$


$$G_{in} = \gamma_g \frac{1 + \frac{S_{RC}}{S_{LC}}}{S_{LC} + S_{RC} + 1}$$
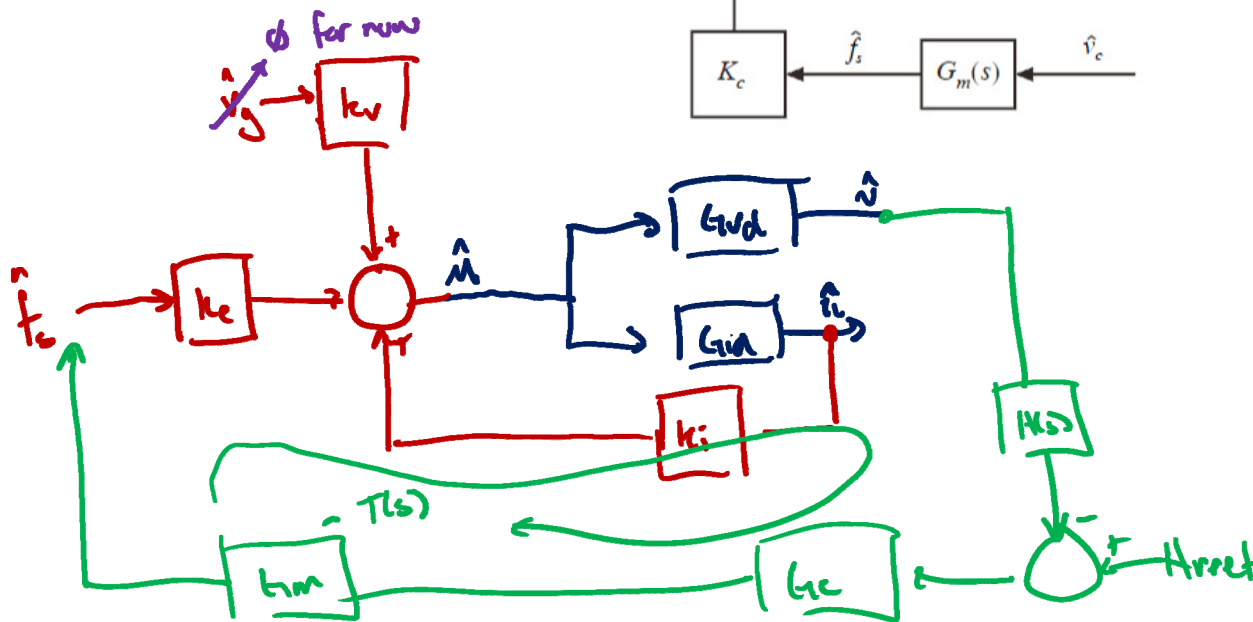
$$G_{vc} = \frac{\hat{v}}{\hat{f}_s} = k_c G_{vd} \cdot \frac{1}{1 - G_{ia} k_i}$$





Example

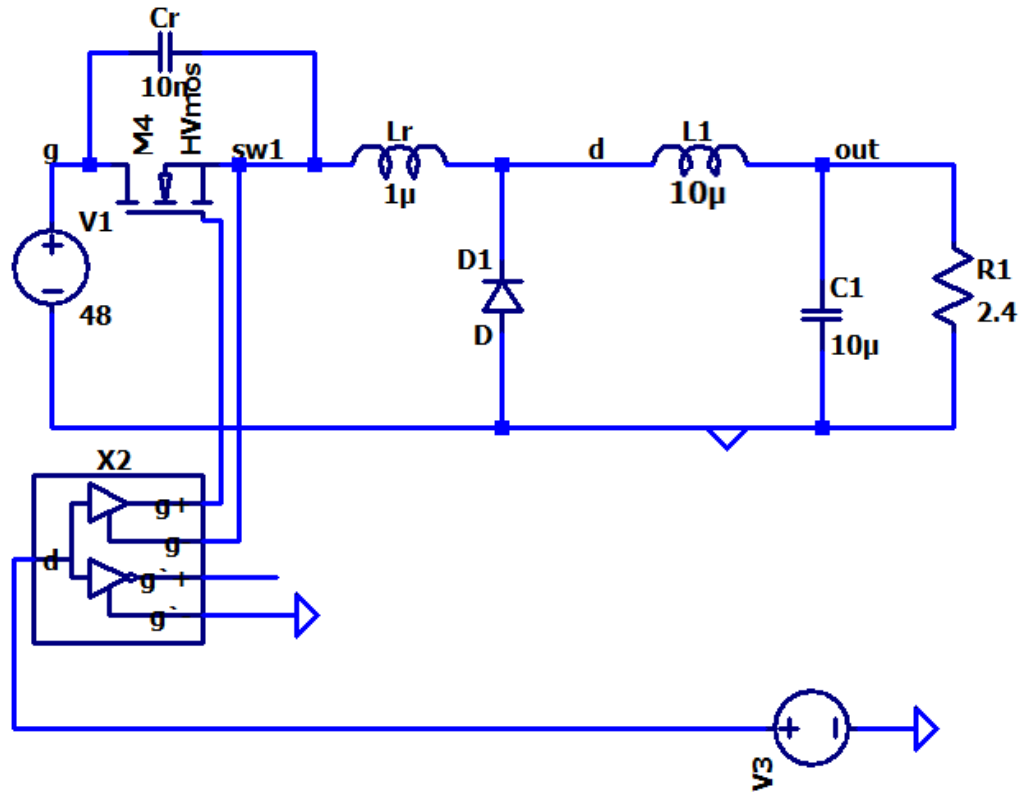

$$f_s = 1 \text{ MHz}$$

$$\beta_c \approx 1$$

$$P_o = 60 \text{ W}$$

$$V = 12 \text{ V}$$


$$F = 0.6$$

$$k_c = 6.24 \times 10^{-12}$$

$$k_i = -0.005$$

$$k_v = 5.6 \times 10^{-4}$$

Control-to-Output Transfer Function

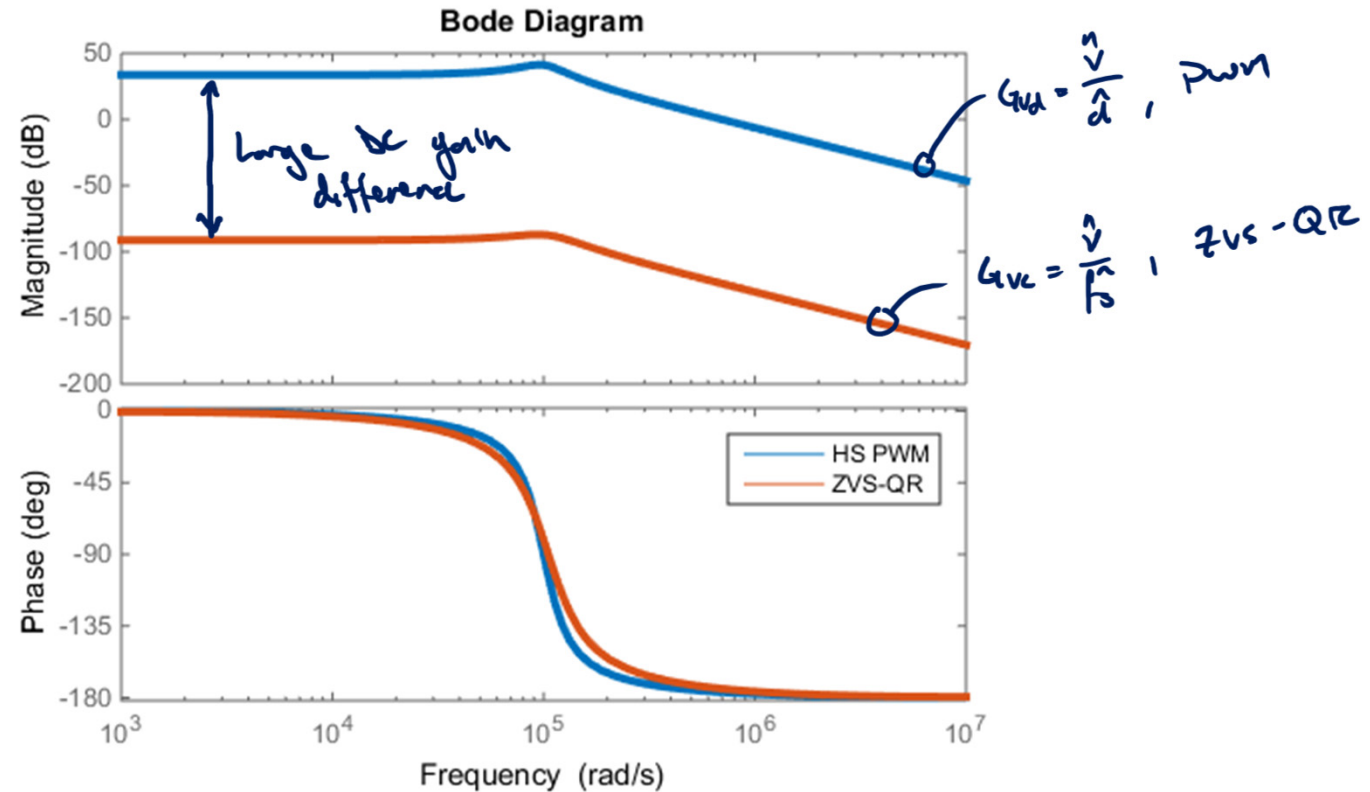

Control-to-Output Transfer Function

