


# **Converter Analysis**

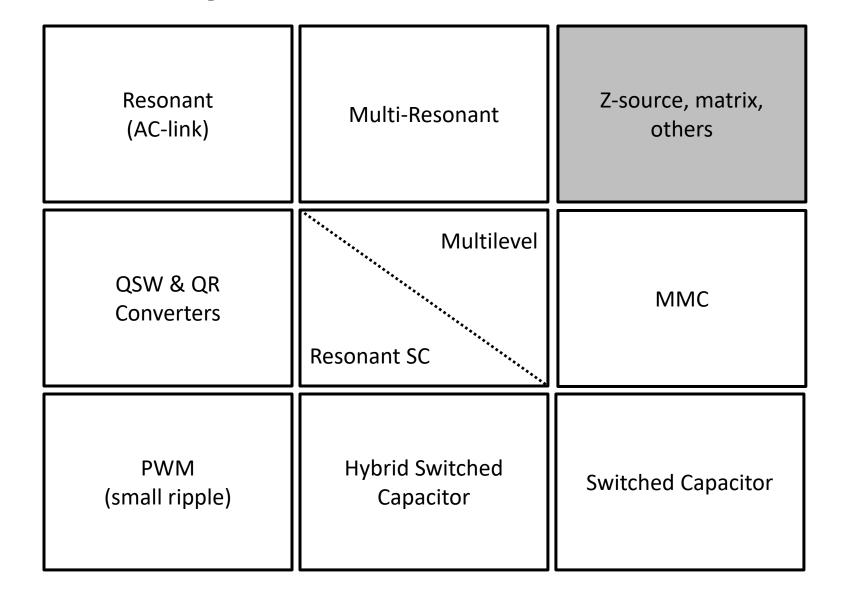


## **Converter Analysis**

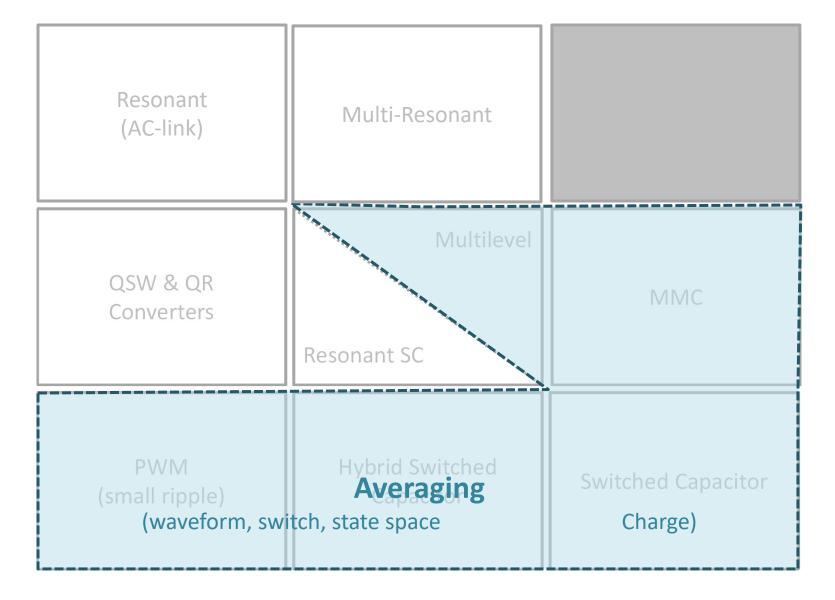

#### **Converter Analysis**

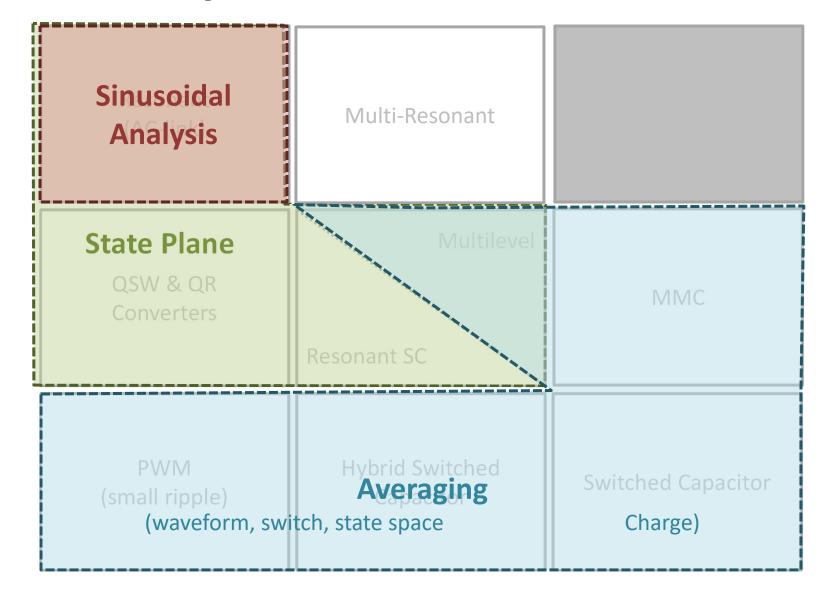

### **Analysis of Switched Systems**

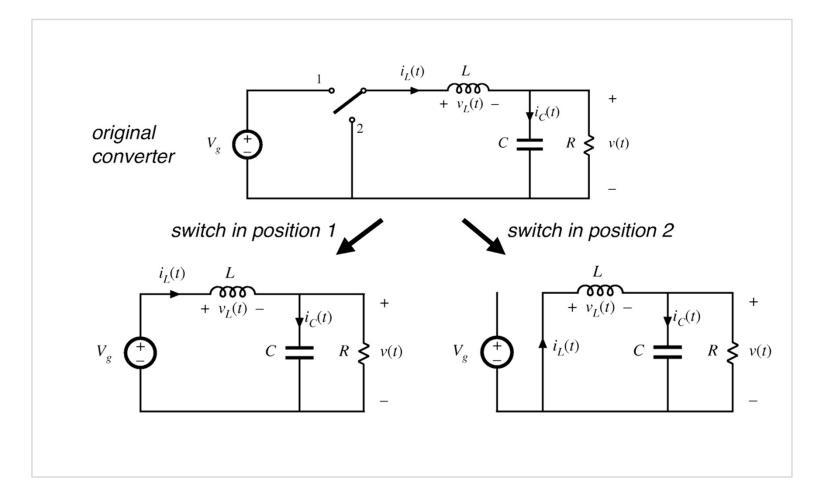

- Every switching subcircuit approximated as a passive, linear circuit
  - Piecewise linear models, if necessary

#### **Historical Perspective**



Robert D Middlebrook
PhD, Standford, 1955
CalTech Professor, 1955-1998

**Slobodan Cúk** PhD CalTech, 1976

CalTech Prof, 1977-1999



Modelling, analysis, and design of switching converters

Model a switched system as an averaged, time-invariant system with

$$\dot{x}(t) = Ax(t) + Bu(t)$$

where


$$A = DA_1 + D'A_2$$

$$\boldsymbol{B} = D\boldsymbol{B_1} + D'\boldsymbol{B_2}$$
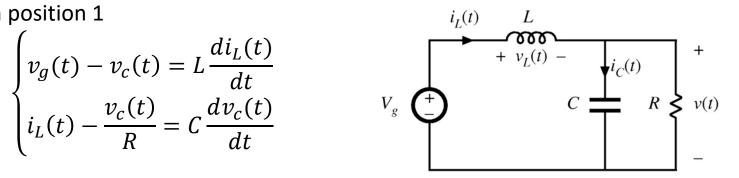
#### **Linear Circuit Modeling Using State Space**

In switch position 1

$$\begin{cases} v_g(t) - v_c(t) = L \frac{di_L(t)}{dt} \\ i_L(t) - \frac{v_c(t)}{R} = C \frac{dv_c(t)}{dt} \end{cases}$$



Which can be written, in state space, form as

$$\frac{d}{dt} \begin{bmatrix} i_L(t) \\ v_c(t) \end{bmatrix} = \begin{bmatrix} 0 & \frac{-1}{L} \\ \frac{1}{C} & \frac{-1}{RC} \end{bmatrix} \cdot \begin{bmatrix} i_L(t) \\ v_c(t) \end{bmatrix} + \begin{bmatrix} 1/L \\ 0 \end{bmatrix} v_g(t)$$

Or, generally,


$$\dot{\boldsymbol{x}}(t) = \boldsymbol{A}_1 \boldsymbol{x}(t) + \boldsymbol{B}_1 \boldsymbol{u}(t)$$

In the second switch position, we will have a new (linear) circuit with

$$\dot{\boldsymbol{x}}(t) = \boldsymbol{A}_2 \boldsymbol{x}(t) + \boldsymbol{B}_2 \boldsymbol{u}(t)$$
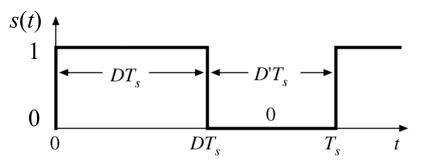
## **Switching Signal**

In a PWM converter with two switch positions, the two linear circuits combine according to a switching function s(t)



$$\dot{x}(t) = [A_1 s(t) + A_2 s'(t)]x(t) + [B_1 s(t) + B_2 s'(t)]u(t)$$

where

$$s(t) = \begin{cases} 1, & \text{if } nT_s < t < (n+D)T_s \\ 0, & \text{if } (n+D)T_s < t < (n+1)T_s \end{cases}$$

$$s'(t) = 1 - s(t)$$

#### **SMPS State Space**

In traditional state space modeling of linear systems

$$\dot{x}(t) = Ax(t) + Bu(t)$$

with u(t) containing a control input. When A and B are constant, this is a linear system. However, we have

$$\dot{x}(t) = [A_1 s(t) + A_2 s'(t)] x(t) + [B_1 s(t) + B_2 s'(t)] u(t)$$

or, equivalently

$$\dot{x}(t) = A(t)x(t) + B(t)u(t)$$

which is nonlinear: how do we deal with it?

#### **Converting to Linear System**

Assume that our system model

$$\dot{x}(t) = [A_1 s(t) + A_2 s'(t)]x(t) + [B_1 s(t) + B_2 s'(t)]u(t)$$

can be approximated by some linear system


$$\dot{\boldsymbol{x}}(t) = \boldsymbol{A}\boldsymbol{x}(t) + \boldsymbol{B}\boldsymbol{u}(t)$$


which removes the nonlinearity of the system

- Nonlinearities came from switching
- Expect that switching dynamics will be lost


Note: This system is now linear in x(t) and u(t), but not in our control signal, s(t)

**Average Modeling** 

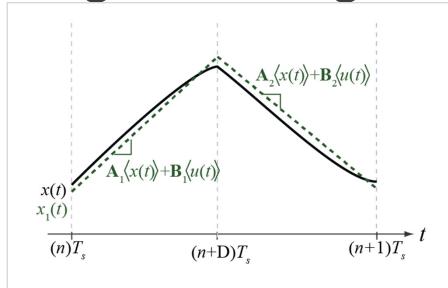

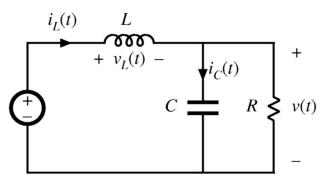
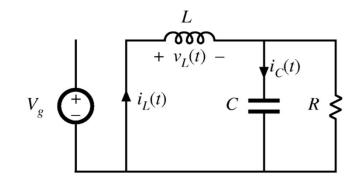
$$\dot{\boldsymbol{x}}(t) = \boldsymbol{A}_1 \boldsymbol{x}(t) + \boldsymbol{B}_1 \boldsymbol{u}(t)$$



$$\dot{\boldsymbol{x}}(t) = \boldsymbol{A}_2 \boldsymbol{x}(t) + \boldsymbol{B}_2 \boldsymbol{u}(t)$$

Approximate waveforms as piecewise linear (PWL)

$$\dot{x}(t) = \begin{cases}
A_1 \langle x(t) \rangle + B_1 \langle u(t) \rangle, & \text{if } nT_S < t < (n+D)T_S \\
A_2 \langle x(t) \rangle + B_2 \langle u(t) \rangle, & \text{if } (n+D)T_S < t < (n+1)T_S
\end{cases}$$

where

$$\langle \mathbf{x}(t) \rangle = \frac{1}{T_s} \int_{0}^{T_s} \mathbf{x}(t) dt = \mathbf{X}$$

so the average slope is

$$\langle \dot{x}(t) \rangle = (\mathbf{D}\mathbf{A}_1 + \mathbf{D}'\mathbf{A}_2)\langle x(t) \rangle + (\mathbf{D}\mathbf{B}_1 + \mathbf{D}'\mathbf{B}_2)\langle u(t) \rangle$$

This equation is now the model of a new, equivalent LTI system

$$\langle \dot{x}(t) \rangle = A \langle x(t) \rangle + B \langle u(t) \rangle$$

## The Averaged System

This equation is now the model of a new, equivalent linear system

$$\dot{\boldsymbol{x}}(t) = \boldsymbol{A}\boldsymbol{x}(t) + \boldsymbol{B}\boldsymbol{u}(t)$$

where


$$A = DA_1 + D'A_2$$
$$B = DB_1 + D'B_2$$

which has averaged behavior over one switching period This approximation is *perhaps* valid, if

- State waveforms are dominantly linear
- Dynamics of interest are at  $f_{bw} \ll f_{s}$
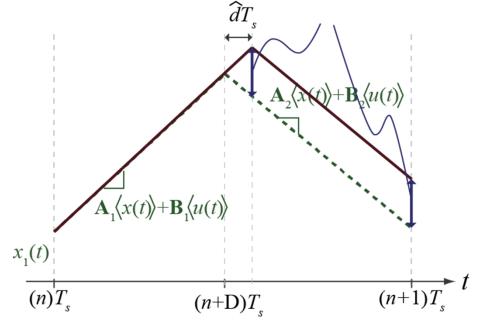
#### **Average Control Response**

$$(\mathbf{A}_1\langle \mathbf{x}(t)\rangle + \mathbf{B}_1\langle u(t)\rangle)\hat{d}T_S - (\mathbf{A}_2\langle \mathbf{x}(t)\rangle + \mathbf{B}_2\langle u(t)\rangle)\hat{d}T_S$$



$$\langle \dot{x}(t) \rangle = A \langle x(t) \rangle + B \langle u(t) \rangle$$

System is LTI with respect to inputs U

Still, the control input (D) is hidden in the state matrices Find dynamic model through small-signal linearization

So, the complete small signal system is

$$\dot{\widehat{x}}(t) = A\widehat{x}(t) + B\widehat{u}(t) + F\widehat{d}(t)$$

with

$$F = ((A_1 - A_2)X + (B_1 - B_2)U)$$


where X and U are defined at the large-signal steady-state operating point

$$\langle \dot{x}(t) \rangle = \mathbf{0} = AX + BU$$

$$X = A^{-1}(-BU)$$
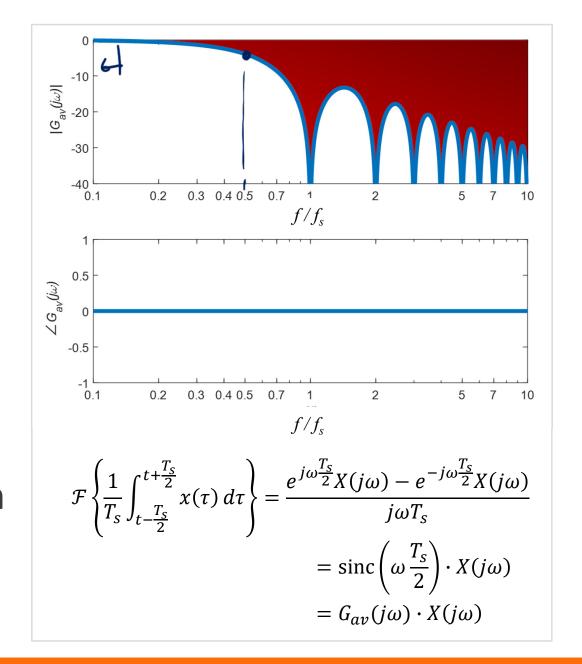
#### **Impacts of Averaging**


- Moving average filter completely attenuates  $f_s$  and harmonics
- Artificial modification of true circuit dynamics
  - Model is incorrect at frequencies approaching  $f_s$
- Minimal impact on systems with only switching ripple at high frequency




## **Limitations of Average Modeling**

- Average modeling only meant to model low-frequency dynamics
- Introduction of the averaging function destroys some internal system dynamics
  - + Switching ripple on dc output ports
  - Resonant and soft switching dynamics
  - ac waveforms
- Inherent sampling behaviors of PWM modulators unmodeled


#### Original System:

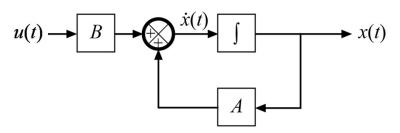
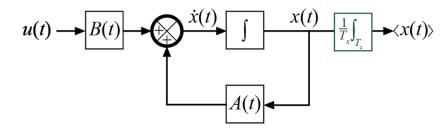
#### **Average States of Original System:**




#### **Averaged System:**

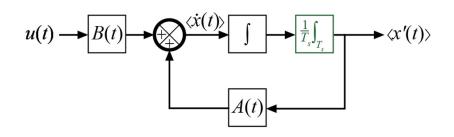

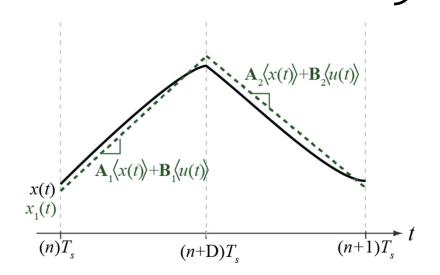
# **Average Modeling**

- Model Error
- Neglected Effects
  - Sampling Effects
  - Delay
  - Quantization




Design  $f_c < f_s/10$ Add HF pole to attenuate switching ripple


#### **Discrete Time Nature of PWM**

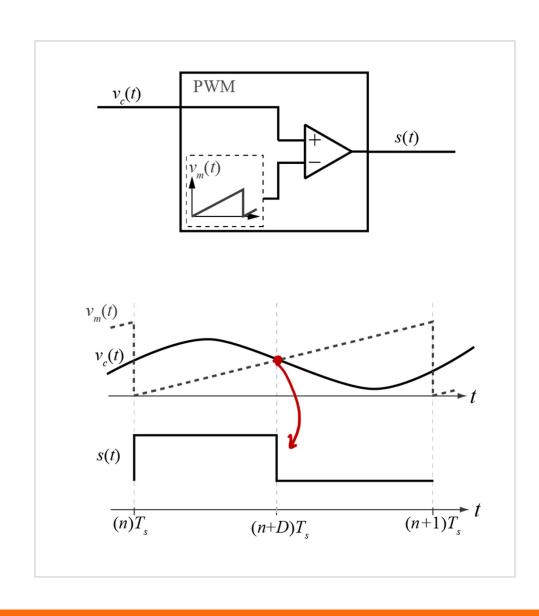


#### **Discrete Time Nature of PWM**

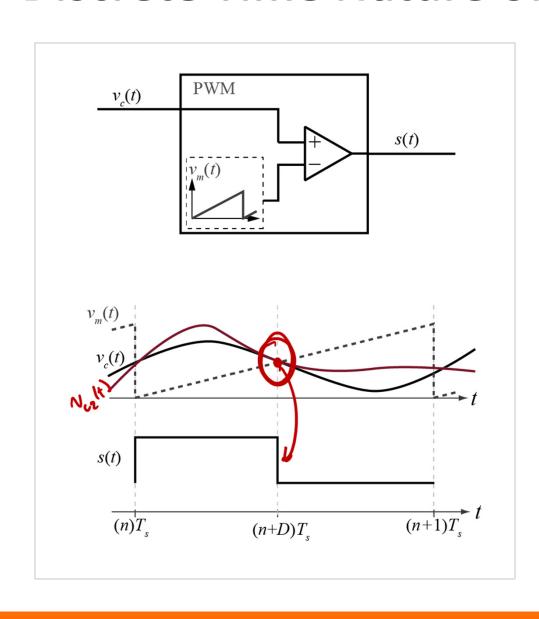

#### **Discrete Time Nature of PWM**

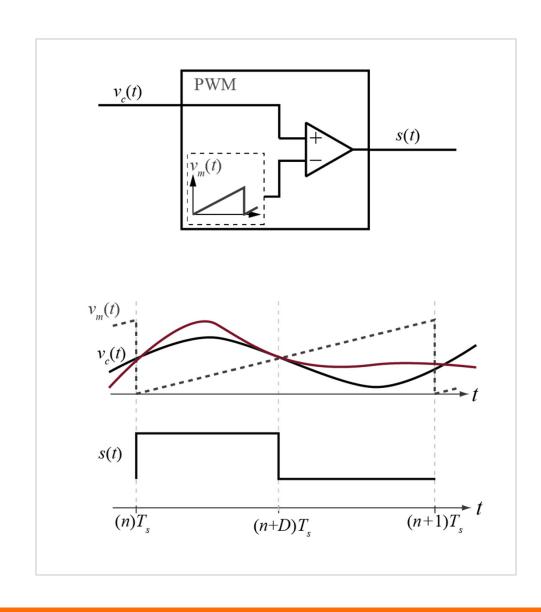

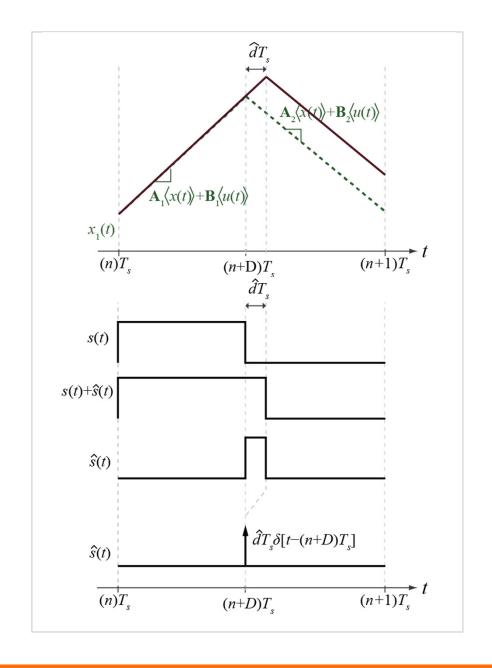

#### **Sampling Phenomena**

- PWM, itself is a sampler
  - Analog PWM is naturally sampled at the comparison point
  - Digital PWMs often uniformly sampled
    - Leading edge, trailing edge, dual edge
    - Shadow registers for  $T_s$  hold
- Additional sampling action from ADC in digitally-controlled converters

#### **Historical Perspective**



Robert D Middlebrook PhD, Standford, 1955 CalTech Professor, 1955-1998

**Slobodan Cúk** PhD CalTech, 1976

976 999

CalTech Prof, 1977-1999

Modelling, analysis, and design of switching converters

Model a switched system as an averaged, time-invariant system with

$$\dot{x}(t) = Ax(t) + Bu(t)$$

where

$$A = DA_1 + D'A_2$$
$$B = DB_1 + D'B_2$$



**Dennis John Packard** PhD, CalTech 1976

Discrete modeling and analysis of switching regulators

Model a switched system as a discrete-time system with


$$x[n+1] = \Phi x[n] + \Psi U[n]$$

where

$$\boldsymbol{\Phi} = \left(\prod_{i=n_{SW}}^{1} e^{\boldsymbol{A}_{i}t_{i}}\right)$$

$$\boldsymbol{\Psi} = \sum_{i=1}^{n_{SW}} \left\{ \left(\prod_{k=n_{SW}}^{i+1} e^{\boldsymbol{A}_{k}t_{k}}\right) \boldsymbol{A}_{i}^{-1} (e^{\boldsymbol{A}_{i}t_{i}} - \boldsymbol{I}) \boldsymbol{B}_{i} \right\}$$

### **Large Signal Modeling of SMPS**

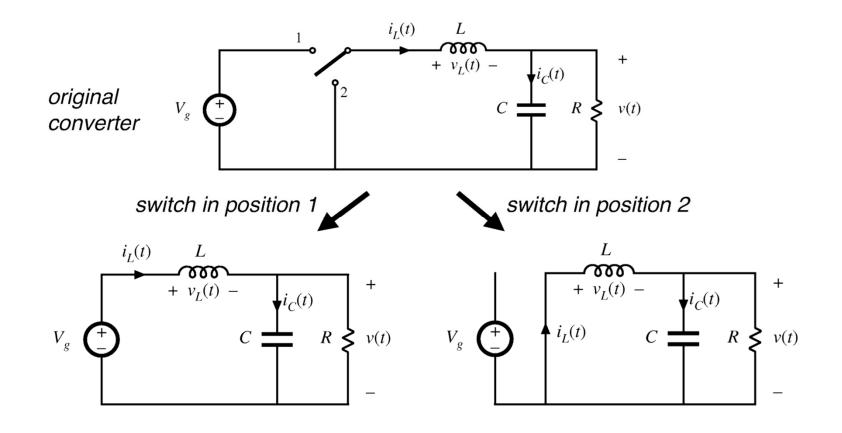

## **Discrete Time Modeling**

- Every subcircuit is a passive, linear circuit
- Passive, linear circuits can be solved in closed-form
  - Can model states at discrete times without averaging
- Only assumption required
  - Independent inputs are DC or slowly varying

# **Solution to State Space Equation**

Closed form solution to state space equation

$$\dot{\boldsymbol{x}}(t) = \boldsymbol{A}\boldsymbol{x}(t) + \boldsymbol{B}\boldsymbol{u}(t)$$

Multiply both sides by  $e^{-At}$ 

$$e^{-At}\dot{x}(t) - e^{-At}Ax(t) = e^{-At}Bu(t)$$

Left-hand side is

$$\frac{d}{dt}(e^{-At}x(t)) = e^{-At}Bu(t)$$

#### **Solution to State Space Equation**

$$\frac{d}{dt}(e^{-At}\mathbf{x}(t)) = e^{-At}\mathbf{B}u(t)$$

Can now be solved by direct integration

$$e^{-At}\mathbf{x}(t) - \mathbf{x}(0) = \int_{0}^{t} e^{-A\tau}\mathbf{B}u(\tau) d\tau$$

Rearranging


$$\mathbf{x}(t) = e^{\mathbf{A}t}\mathbf{x}(0) + \int_{0}^{t} e^{-\mathbf{A}(t-\tau)}\mathbf{B}u(\tau) d\tau$$

## **Matrix Exponential**

Matrix exponential defined by Taylor series expansion

$$e^{At} = I + At + \frac{(At)^2}{2!} + \dots + \frac{(At)^N}{N!} = \sum_{k=0}^{N} \frac{(At)^k}{k!}$$

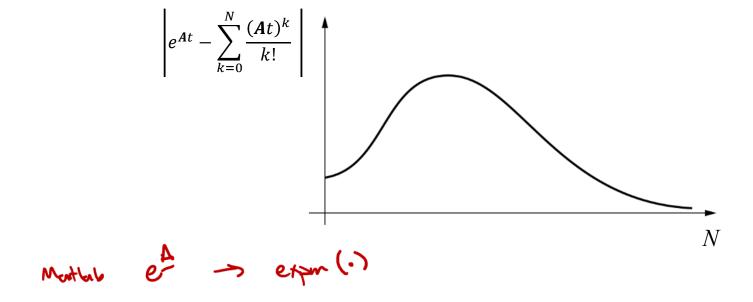Well-known issue with convergence in many cases




## **Properties of the Matrix Exponential**

- Matrix exponential always exists
  - i.e. summation will always converge
- Exponential of any matrix is always invertible, with  $e^A e^{-A} = I$

## First Order Taylor Series Expansion

Linear ripple approximation

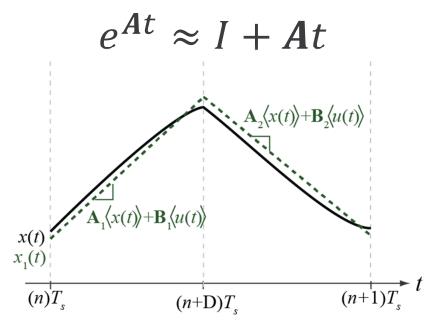


Valid only if switching frequency much faster than system modes


## Simplification for Slow-Varying Inputs


$$\mathbf{x}(t) = e^{At}\mathbf{x}(0) + \int_{0}^{t} e^{-A(t-\tau)}\mathbf{B}u(\tau) d\tau$$

If A is invertible and  $u(\tau) \approx U$ 

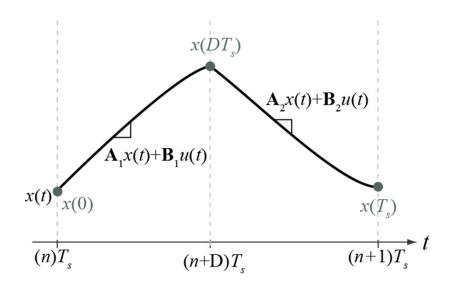
$$x(t) = e^{At}x(0) + A^{-1}(e^{At} - I)BU$$



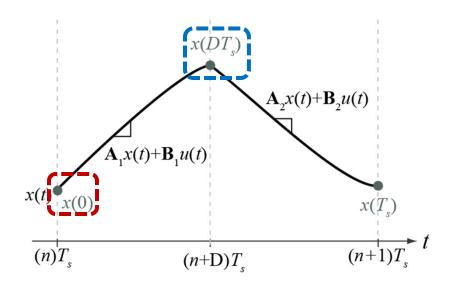

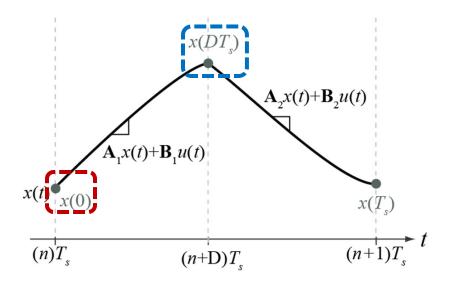

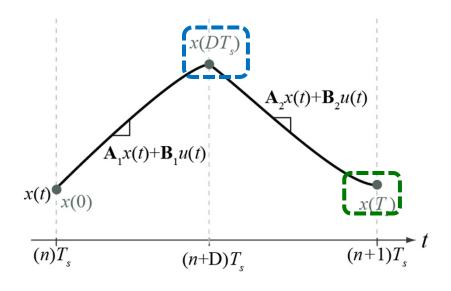
$$\mathbf{x}(DT_S) = e^{\mathbf{A}_1 DT_S} \mathbf{x}(0) + \mathbf{A}_1^{-1} (e^{\mathbf{A}_1 DT_S} - \mathbf{I}) \mathbf{B}_1 U$$



$$\mathbf{x}(DT_S) = e^{\mathbf{A}_1 DT_S} \mathbf{x}(0) + \mathbf{A}_1^{-1} (e^{\mathbf{A}_1 DT_S} - \mathbf{I}) \mathbf{B}_1 U$$
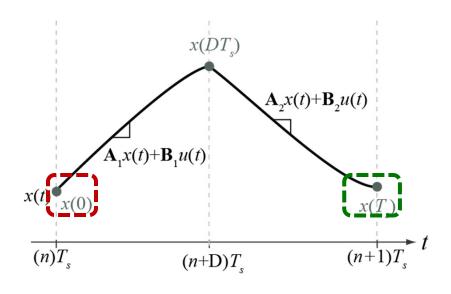
$$\mathbf{x}(T_S) = e^{A_2 D' T_S} \mathbf{x}(DT_S) + A_2^{-1} (e^{A_2 D' T_S} - I) B_2 U$$



$$\mathbf{x}(DT_S) = e^{\mathbf{A}_1 DT_S} \mathbf{x}(0) + \mathbf{A}_1^{-1} (e^{\mathbf{A}_1 DT_S} - \mathbf{I}) \mathbf{B}_1 U$$

$$\mathbf{x}(T_S) = e^{\mathbf{A}_2 D' T_S} \mathbf{x}(DT_S) + \mathbf{A}_2^{-1} (e^{\mathbf{A}_2 D' T_S} - \mathbf{I}) \mathbf{B}_2 U$$

$$\mathbf{x}(T_S) = e^{\mathbf{A}_2 D' T_S} e^{\mathbf{A}_1 D T_S} \mathbf{x}(0) + \mathbf{A}_2^{-1} \left( e^{\mathbf{A}_2 D' T_S} - \mathbf{I} \right) \mathbf{B}_2 U + e^{\mathbf{A}_2 D' T_S} \mathbf{A}_1^{-1} (e^{\mathbf{A}_1 D T_S} - \mathbf{I}) \mathbf{B}_1 U$$

#### **General Form**

Generally, for  $n_{sw}$  separate switching positions

$$\mathbf{x}(T_S) = \left(\prod_{i=n_{SW}}^{1} e^{A_i t_i}\right) \mathbf{x}(0) + \sum_{i=1}^{n_{SW}} \left\{ \left(\prod_{k=n_{SW}}^{i+1} e^{A_k t_k}\right) A_i^{-1} (e^{A_i t_i} - \mathbf{I}) \mathbf{B}_i \right\} U$$

Equation is in the form of a discrete-time system with

$$x[n+1] = \Phi x[n] + \Psi U[n]$$

Again, the effect of changing modulation (i.e.  $t_i$ ) is hidden in nonlinear terms

$$\widehat{\mathbf{x}}[n+1] = \mathbf{\Phi}\widehat{\mathbf{x}}[n] + \mathbf{\Psi}\widehat{\mathbf{u}}[n] + \mathbf{\Gamma}\widehat{\mathbf{d}}[n]$$

Find  $\Gamma$  by small-signal modeling

## **Steady-State Large-Signal Analysis**


$$\mathbf{x}(T_S) = \left(\prod_{i=n_{SW}}^{1} e^{A_i t_i}\right) \mathbf{x}(0) + \sum_{i=1}^{n_{SW}} \left\{ \left(\prod_{k=n_{SW}}^{i+1} e^{A_k t_k}\right) A_i^{-1} (e^{A_i t_i} - \mathbf{I}) B_i \right\} U$$

In steady-state,  $x(T_s) = x(0)$ 


$$\mathbf{x}(T_S) = \left(I - \prod_{i=n_{SW}}^{1} e^{A_i t_i}\right)^{-1} \sum_{i=1}^{n_{SW}} \left\{ \left(\prod_{k=n_{SW}}^{i+1} e^{A_k t_k}\right) A_i^{-1} (e^{A_i t_i} - I) B_i \right\} U$$

Gives explicit solution for steady-state operation of any switching circuit


# **Small Signal Modeling**

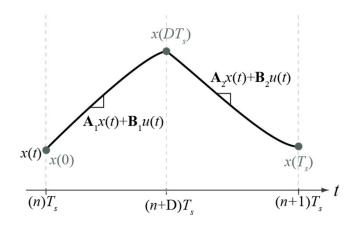

# **Small Signal Modeling**

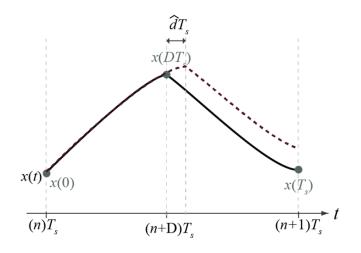

## **Small Signal Modeling**

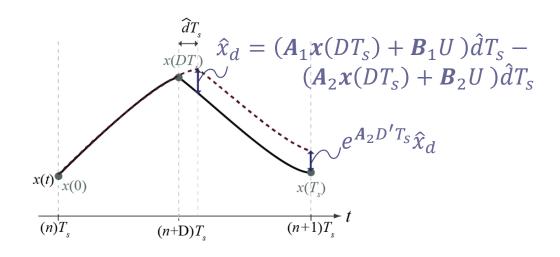

# **Complete Small Signal Model**

This completes the small-signal model


$$\widehat{\mathbf{x}}[n+1] = \mathbf{\Phi}\widehat{\mathbf{x}}[n] + \mathbf{\Psi}\widehat{\mathbf{u}}[n] + \mathbf{\Gamma}\widehat{\mathbf{d}}[n]$$

where


$$\Gamma = e^{A_2 D' T_S} ((A_1 - A_2) X_D + (B_1 - B_2) U) T_S$$

with  $X_D = x(DT_S)$  in steady-state

# **Example Results**

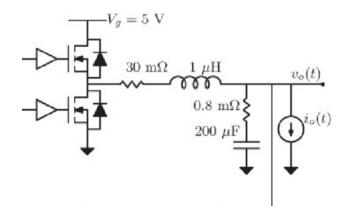

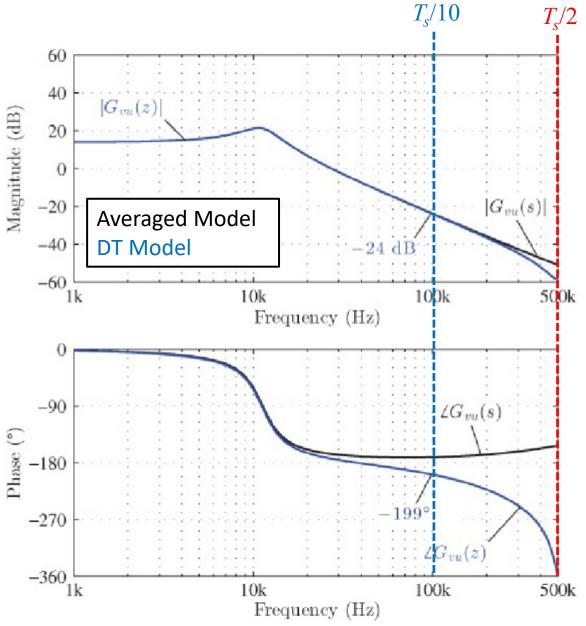\* Includes  $t_d$ =760ns of delay in feedback loop



#### **ECE 692: Discrete Time Power Electronics**

- Taught in alternative Fall semesters with ECE 581
- Covers discrete time modeling for small and large-signal converter analysis and design