



Overlap Time

9 Typ. gate charge




$V_{GS}=f(Q_{gate}); I_D=5.2\text{ A pulsed}$

parameter: V_{DD}


Gate threshold voltage	$V_{GS(th)}$	$V_{DS}=V_{GS}, I_D=0.34\text{ mA}$	2.5	3	3.5	
Gate resistance	R_G	$f=1\text{ MHz, open drain}$	-	1.8	-	Ω

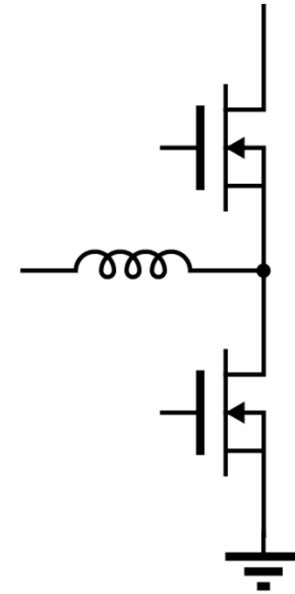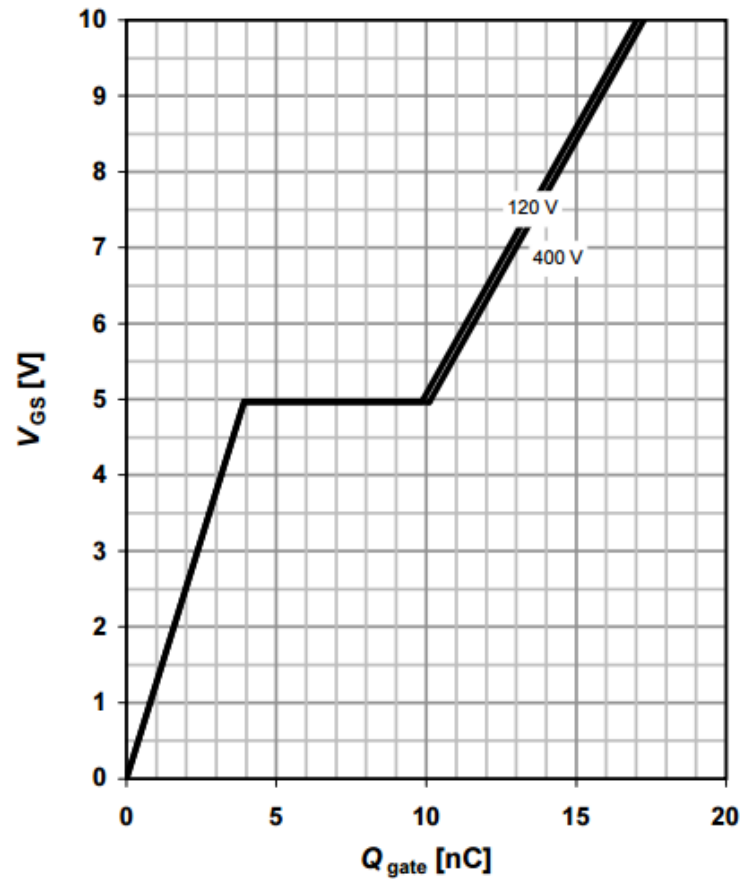

FET Turn-On

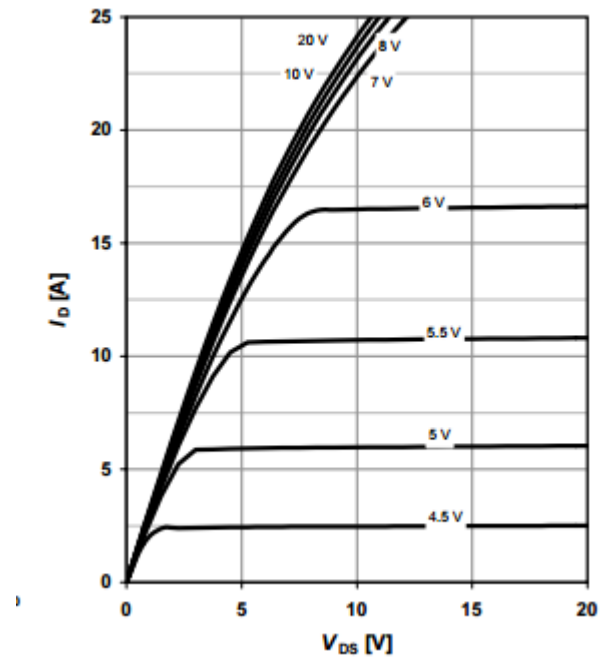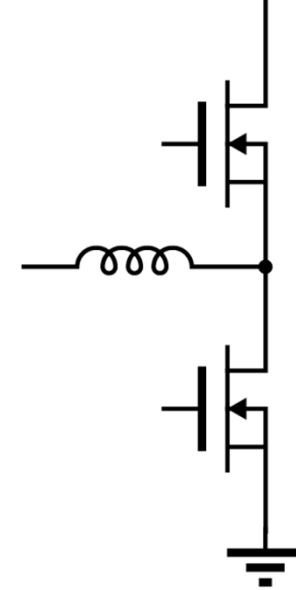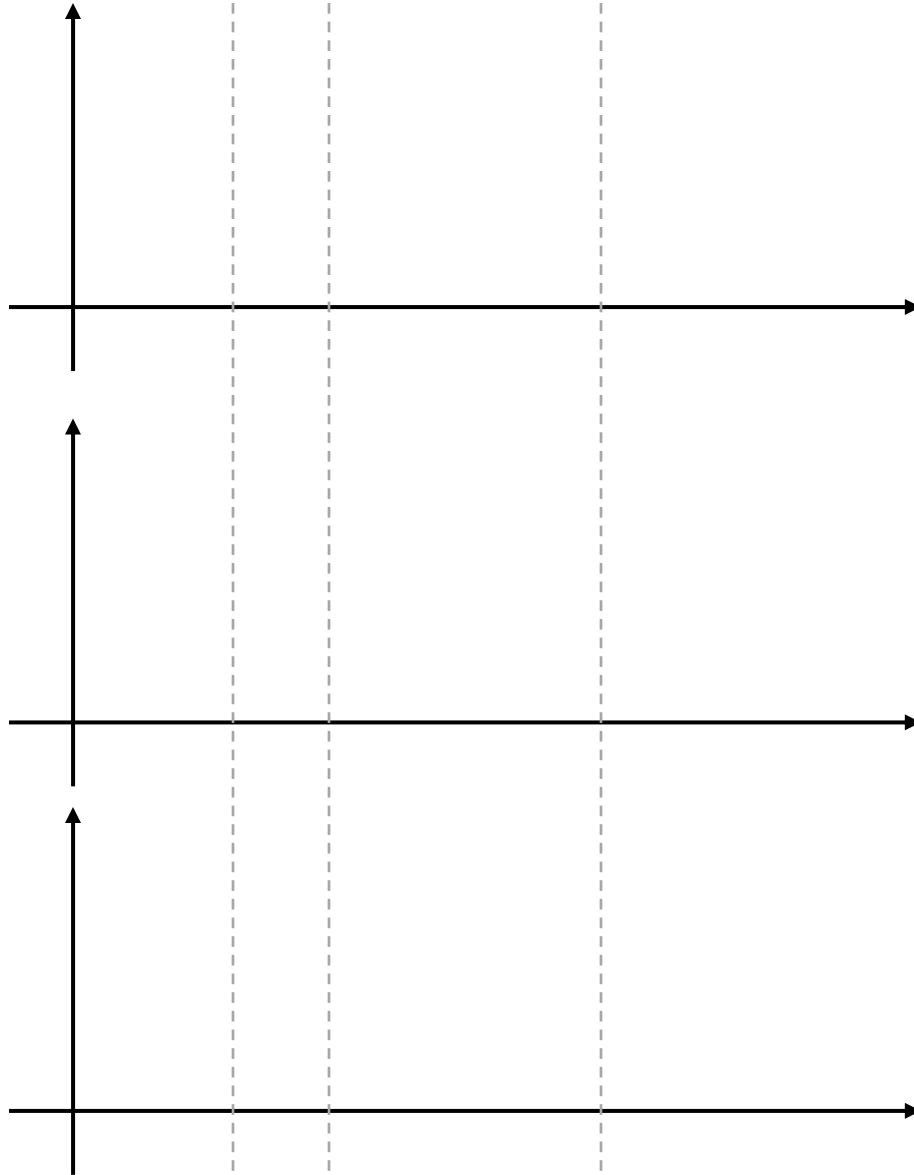


Device Transconductance

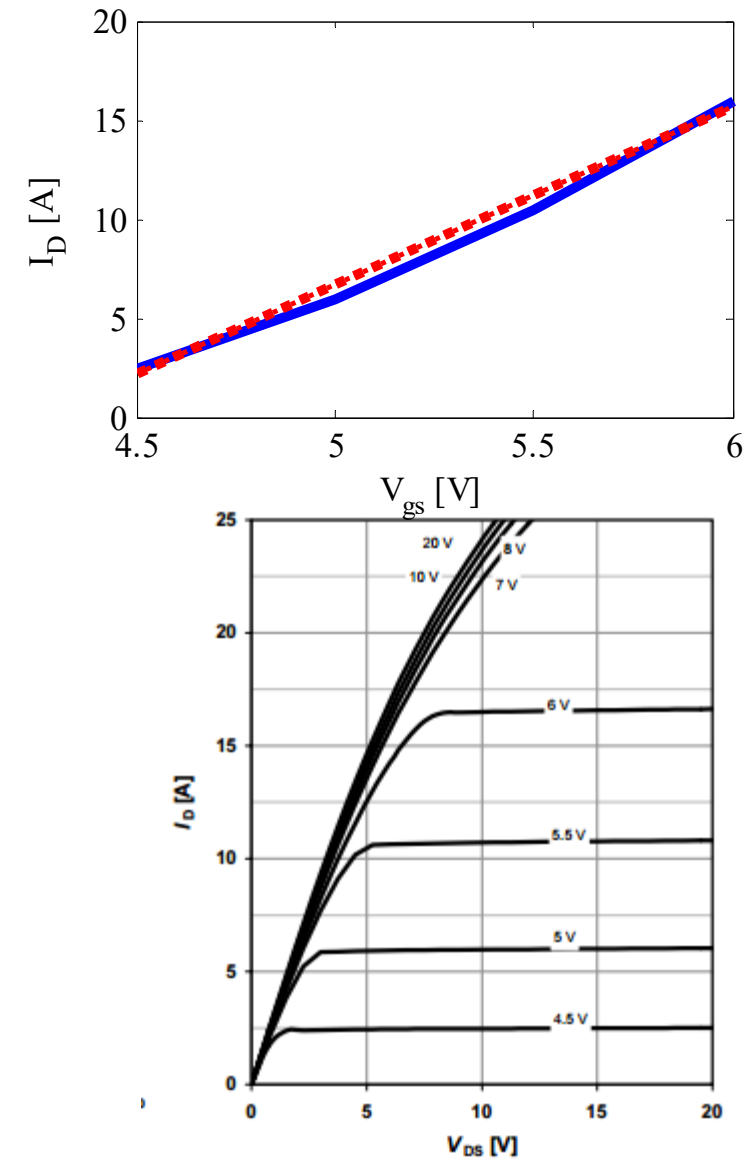

Example Simulation

.ic V(g) = 0

.tran 0 50n 0 1p

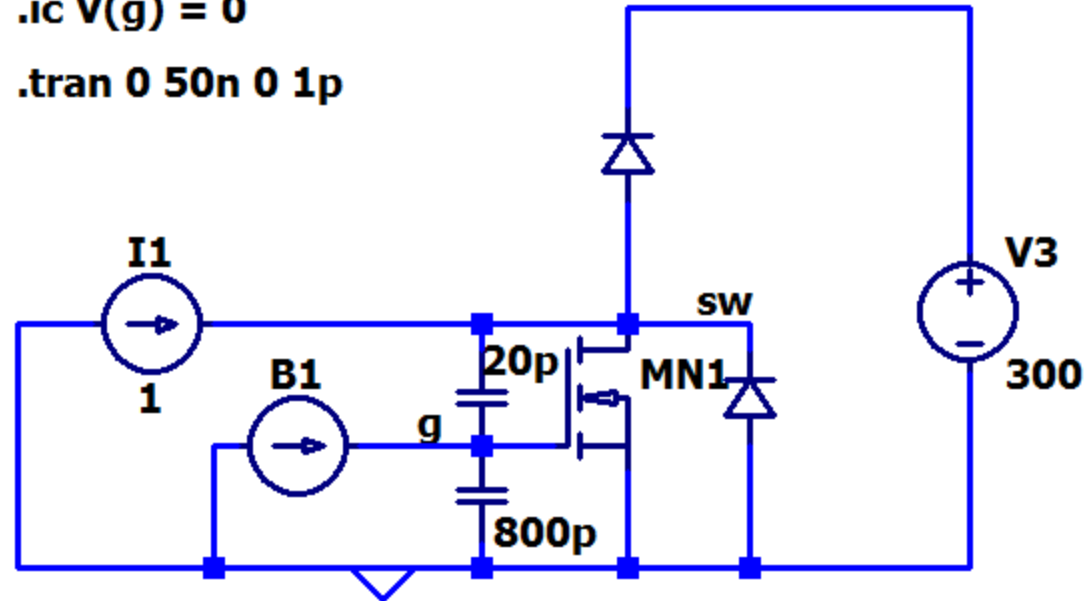


I=IF(V(g)<10,1,0)



.model myD D(n=.01)

**.model testFET VDMOS(Rg=.1 Rd=0 Rs=0 Vto=3 Kp=9 Cgdmax=0p
+ Cgdmin=0p Cgs=0p Cjo=1.5f Is=26p Rb=0m Vds=600 Ron=385m Qg=0n)**


Simulation Waveforms – Turn On

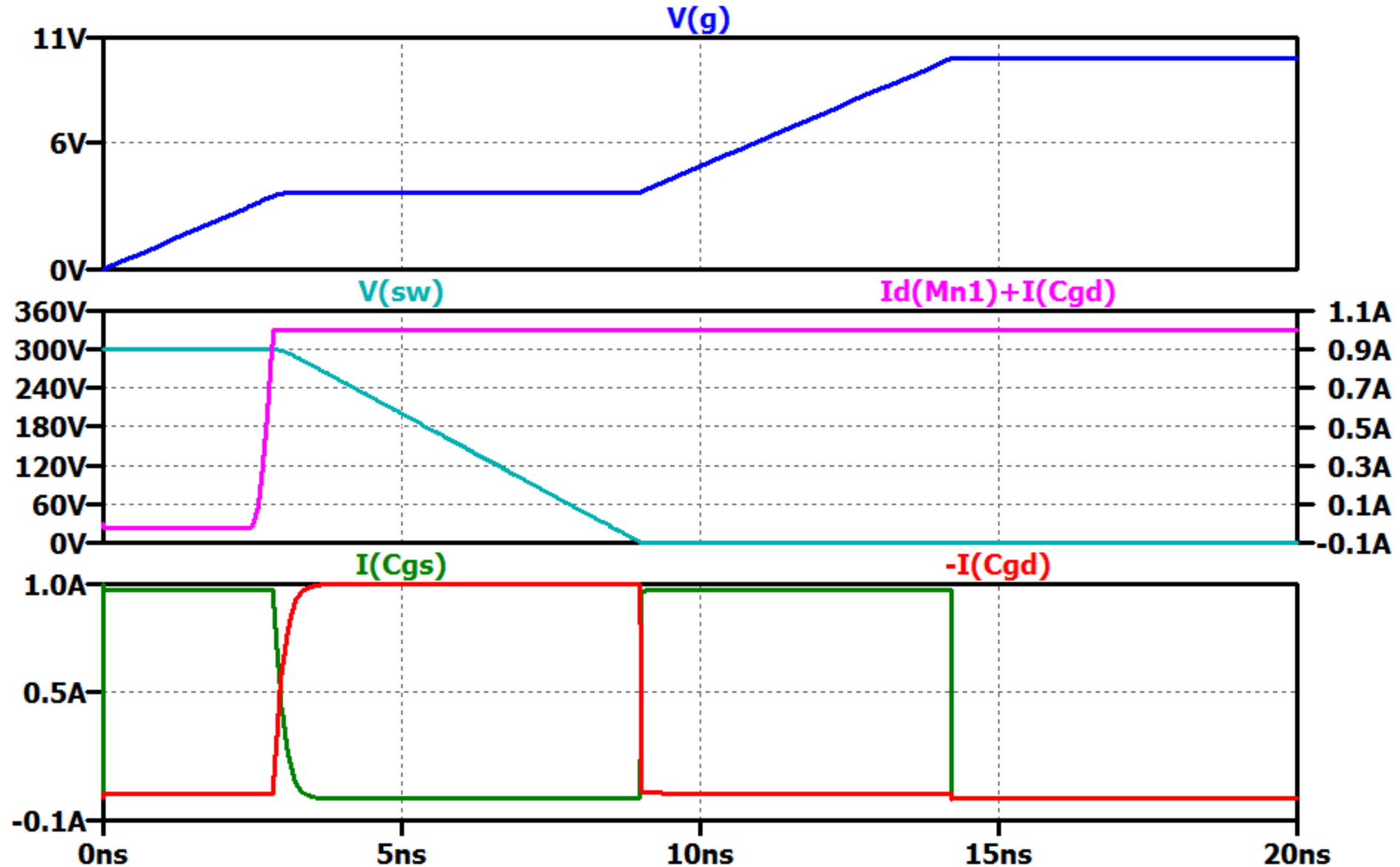


Turn-Off Transition

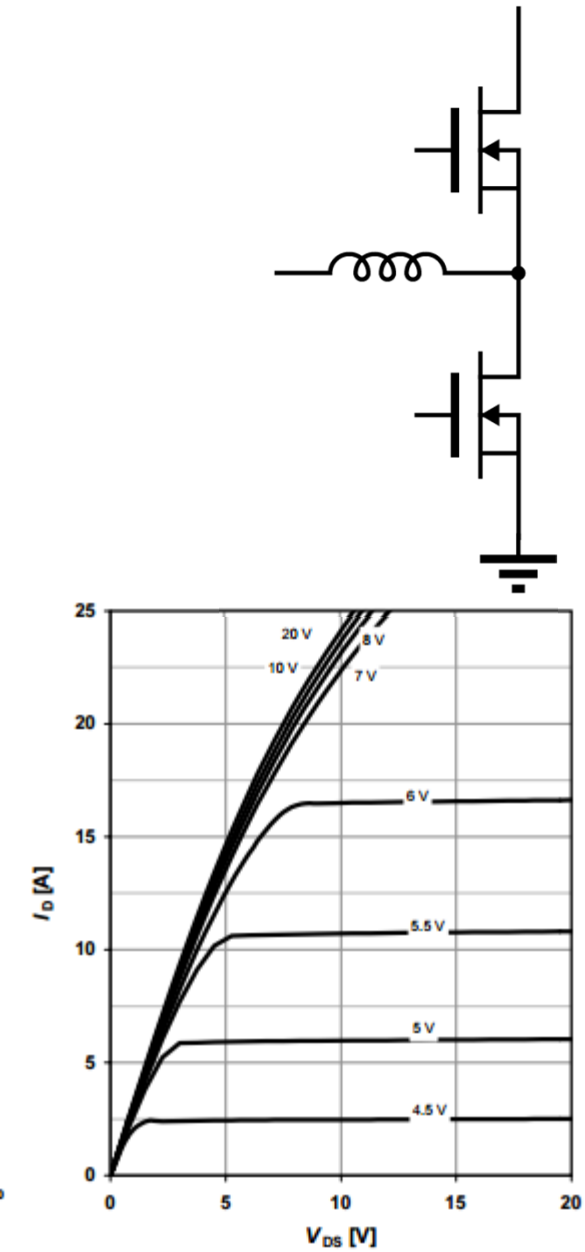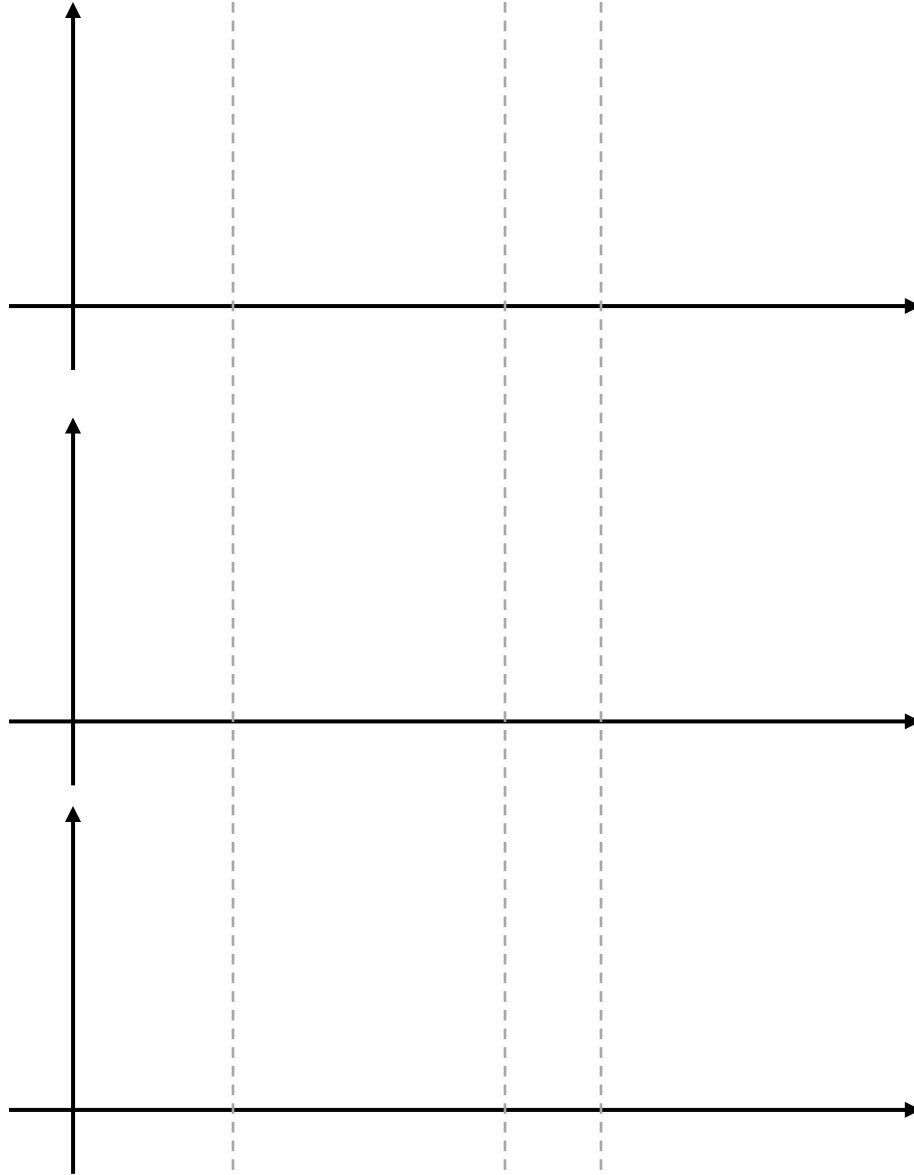

Turn-Off

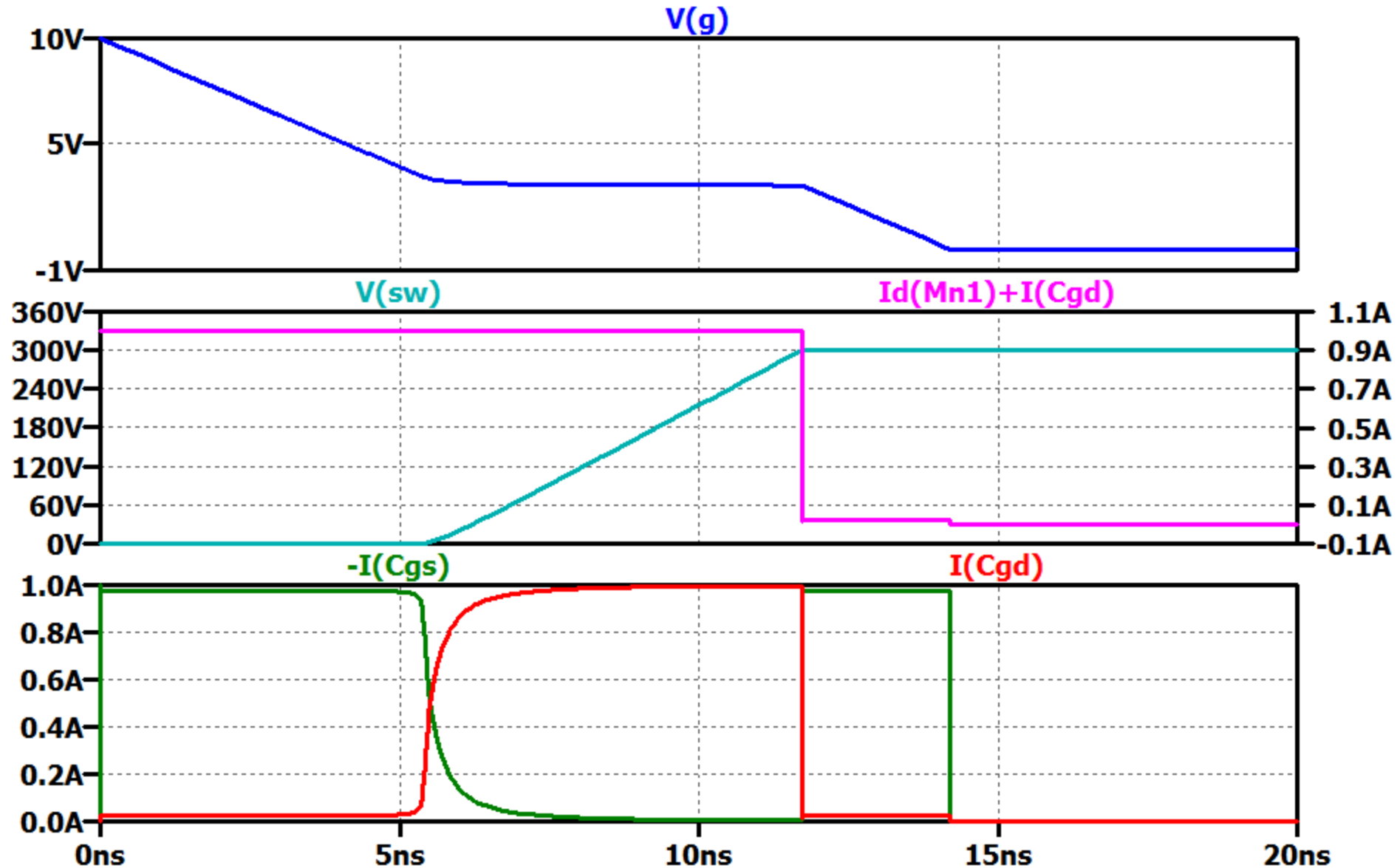

Turn-Off (Drain Dominated)

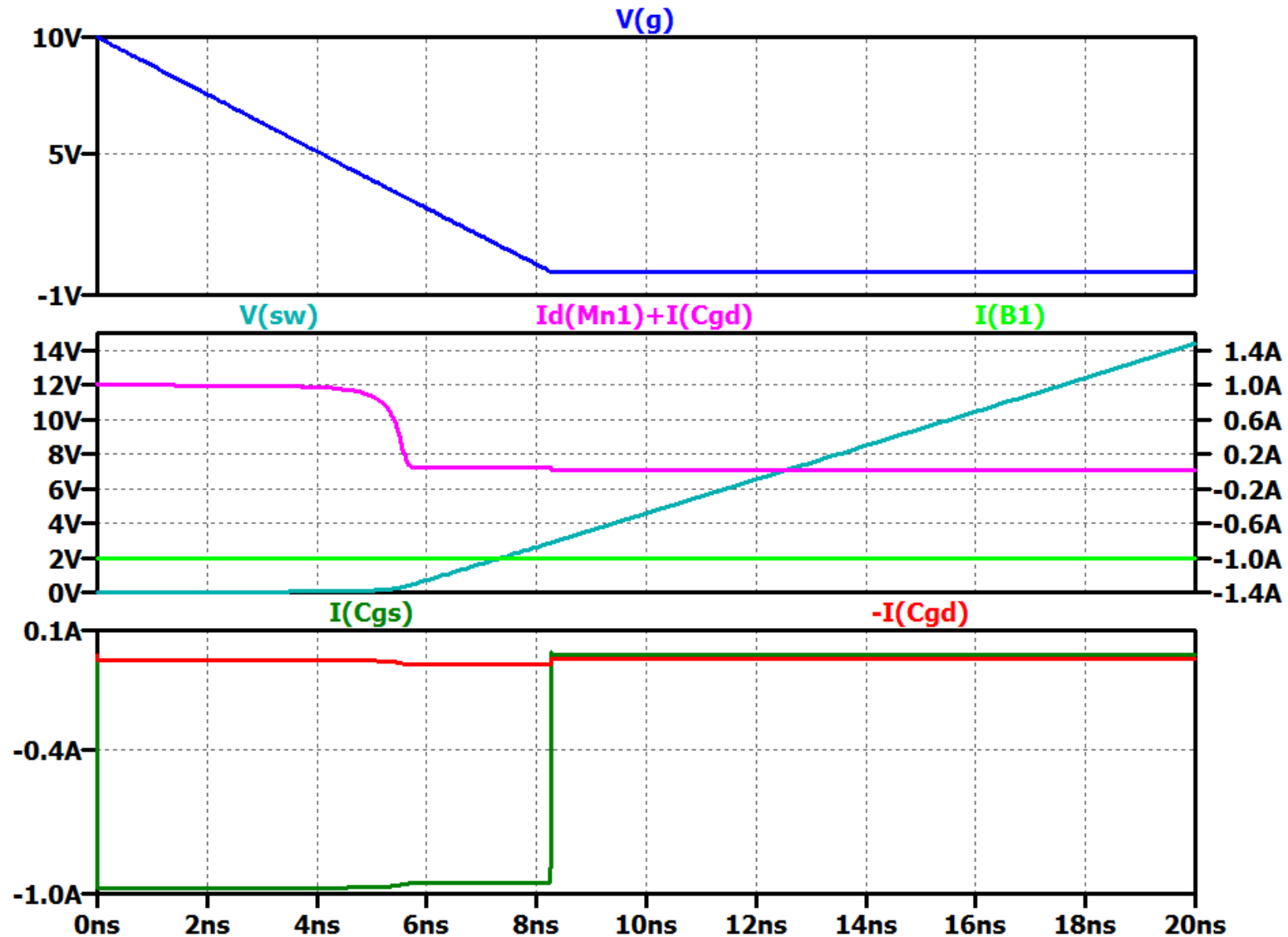

Gate- vs. Drain-Limited Switching