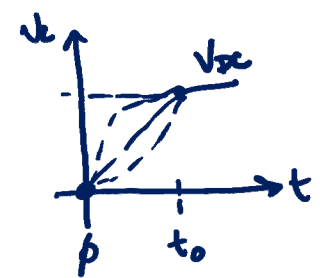


Modeling Nonlinear Capacitances

$$C = \frac{1}{T} \int_0^{T} i_c(t) dt$$



Charge

$$Q = \int_0^{t_0} i_c(t) dt$$

$$Q = \int_0^{t_0} C \frac{dv_c(t)}{dt} dt$$

$$Q = \int_0^{V_{dc}} C dv_c$$

$$Q = C \int_0^{V_{dc}} 1 dv_c$$

$$Q = CV_{dc}$$

$$Q = \int_0^{V_{dc}} C(v_c) dv_c$$

Nonlinear
 $C(v_c)$

cannot simplify further without
(1) analytical expression for $C(v_c)$
(2) numerical result w/ datasheet Coss curve

Energy

$$E = \int_0^{t_0} i_c(t) \cdot v_c(t) dt$$

$$E = \int_0^{t_0} C \frac{dv_c(t)}{dt} \cdot v_c(t) dt$$

$$E = \int_0^{V_{dc}} C v_c dv_c$$

$$E = C \left[\frac{v_c^2}{2} \right]_0^{V_{dc}}$$

$$E = \frac{1}{2} C V_{dc}^2$$

$$E = \int_0^{V_{dc}} C(v_c) \cdot v_c dv_c$$

Linear capacitance
only



Energy and Charge Equivalents

Linear "equivalent" capacitors only correct for a single characteristic

$$E = \frac{1}{2} C_{eq,E} V_{DC}^2 = \int_0^{V_{DC}} C(V_C) \cdot V_C dV_C$$

$$\begin{cases} Q = C_{eq,Q} V_{DC} \\ Q = \int_0^{V_{DC}} C(V_C) dV_C \end{cases}$$

$$C_{eq,Q} = \frac{1}{V_{DC}} \int_0^{V_{DC}} C(V_C) dV_C$$


Capacitor that has the same total charge at V_{DC} as our nonlinear cap

$$\bullet C_{eq,Q} = \langle C \rangle_V$$

$$C_{eq,E} = \frac{2}{V_{DC}^2} \int_0^{V_{DC}} C(V_C) \cdot V_C dV_C$$

same energy @ V_{DC}

C_{oss} Losses in a Half Bridge

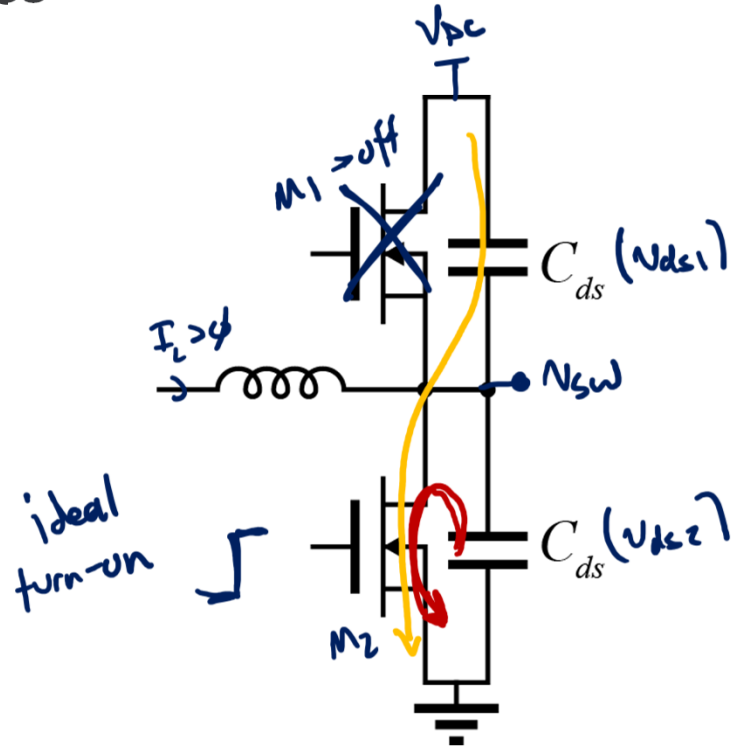


$$N_{sw} = N_{ds2}$$

$$N_{ds1} = V_{DC} - N_{sw}$$

before turn-on $N_{sw} = V_{DC}$

M₂ Energy Loss

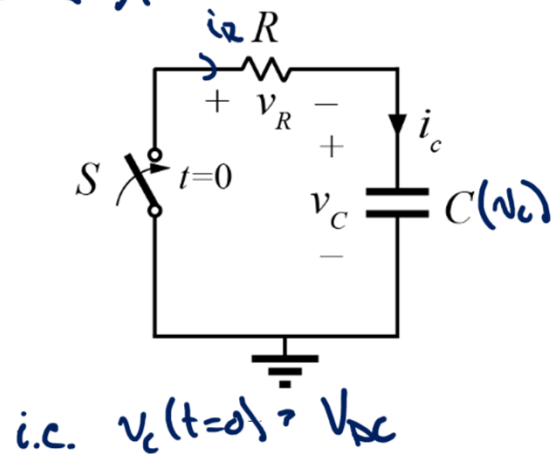

$$\bar{E}_R = \int_0^{\infty} v_R \cdot i_R dt$$

$$\bar{E}_R = \int_0^{\infty} (-v_c) C(v_c) \frac{dv_c}{dt} dt$$

$$\bar{E}_R = \int_{V_{DC}}^0 (-v_c) C(v_c) dv_c$$


$$E_R = \int_0^{V_{DC}} C(v_c) \cdot v_c dv_c$$

$$\boxed{E_R = \frac{1}{2} C_{eq,E} V_{DC}^2}$$

$$v_R = -v_c$$

$$i_R = i_c = C(v_c) \frac{dv_c}{dt}$$

M₁ Energy Loss

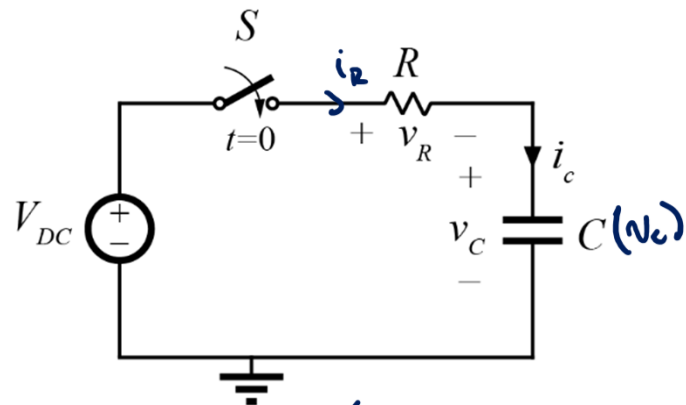

i.e. $v_C(t=0) = 0$

$$E_R = \int_0^{\infty} v_R \cdot i_R dt$$

$$E_R = \int_0^{\infty} (V_{DC} - v_C) \cdot C(v_C) \frac{dv_C}{dt} dt$$

$$E_R = \int_0^{V_{DC}} V_{DC} \cdot C(v_C) dv_C - \int_0^{V_{DC}} C(v_C) \cdot v_C dv_C$$

$$E_R = V_{DC} \cdot \underbrace{\int_0^{V_{DC}} C(v_C) dv_C}_Q - \underbrace{\int_0^{V_{DC}} C(v_C) \cdot v_C dv_C}_E$$

$$E_R = V_{DC} \cdot (C_{eq,0} \cdot V_{DC}) - \frac{1}{2} C_{eq,0} V_{DC}^2$$

$$v_R = V_{DC} - v_C$$

$$i_R = i_C = C(v_C) \frac{dv_C}{dt}$$


Total Half Bridge C_{oss} Loss

$$E_{M_2} = \frac{1}{2} C_{eq,E,M_2} V_{DC}^2 + V_{DC}^2 C_{eq,Q,M_1} - \frac{1}{2} C_{eq,E,M_1} V_{DC}^2$$

If M_1 & M_2 are the same device $C_{eq,E,M_2} = C_{eq,E,M_1}$

$E_{M_2} = V_{DC}^2 C_{eq,Q}$ → Energy loss depends only on charge-equivalent capacitor

Energy Equivalent

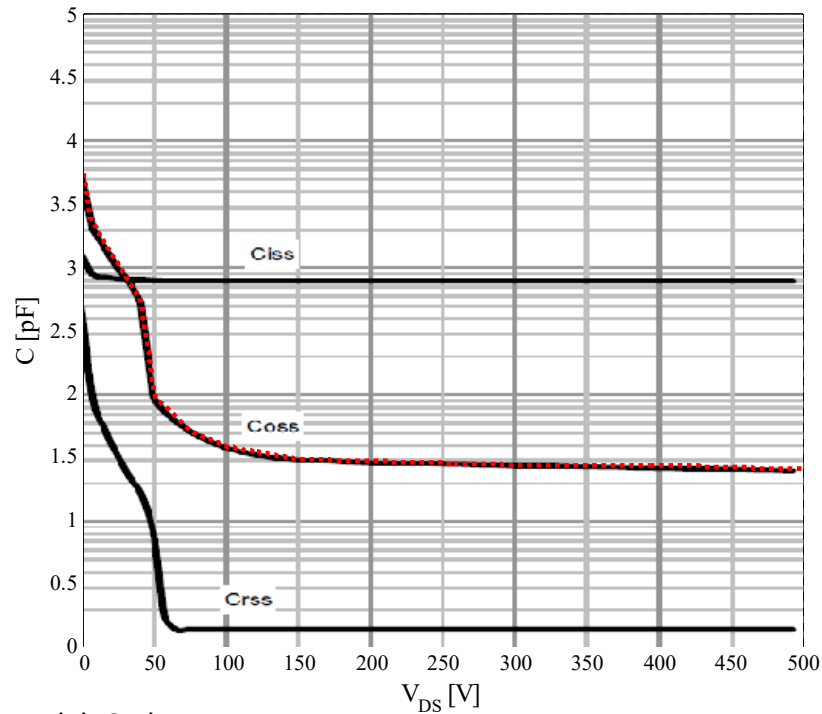


Matlab Code:

Vdc = 550;

```
Vds = [0 5 10 40 50 75 100 150 200 300 400 500 600];
Coss = [5500 2500 1900 550 95 50 38 30 29 27 27 25 24]*1e-12;
```

```
vx = 0.01:.01:Vdc;
Cx = 10.^interp1(Vds,log10(Coss),vx,'linear');
```
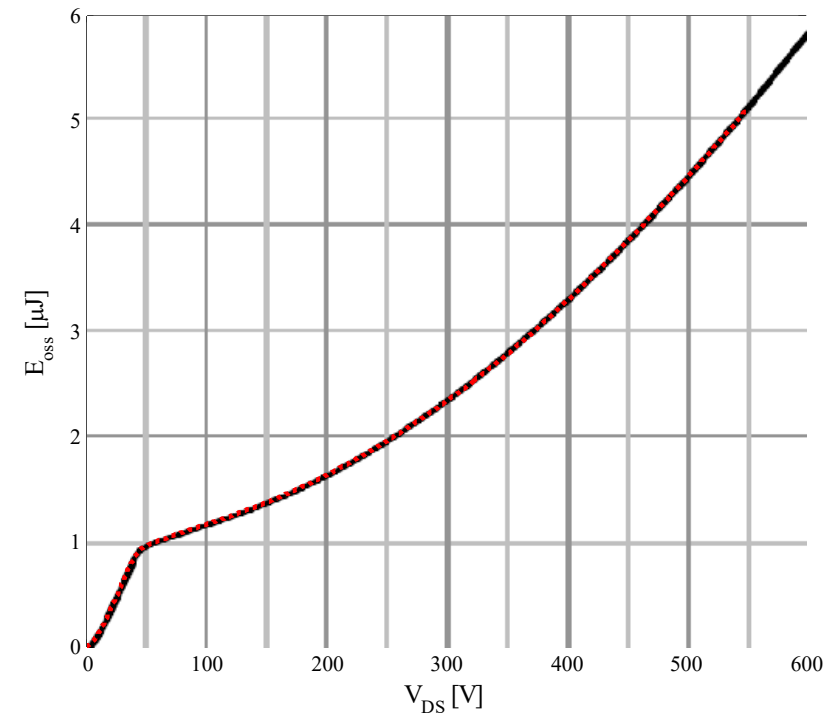
```
E = cumtrapz(vx, Cx.*vx);
Ceq_e = 2*(E)./vx.^2;
```



Nonlinear Capacitance Extraction

- <http://web.eecs.utk.edu/~dcostine/personal/PowerDeviceLib/DigiTest/index.html>

Datasheet Reported Capacitance

Dynamic characteristics

Input capacitance	C_{iss}	$V_{GS}=0\text{ V}$, $V_{DS}=100\text{ V}$, $f=1\text{ MHz}$	-	790	-	pF
Output capacitance	C_{oss}		-	38	-	
Effective output capacitance, energy related ⁶⁾	$C_{o(er)}$	$V_{GS}=0\text{ V}$, $V_{DS}=0\text{ V}$ to 480 V	-	36	-	
Effective output capacitance, time related ⁷⁾	$C_{o(tr)}$		-	96	-	
Turn-on delay time	$t_{d(on)}$	$V_{DD}=400\text{ V}$, $V_{GS}=10\text{ V}$, $I_D=5.2\text{ A}$, $R_G=3.3\ \Omega$	-	10	-	ns
Rise time	t_r		-	5	-	
Turn-off delay time	$t_{d(off)}$		-	40	-	
Fall time	t_f		-	5	-	

⁶⁾ $C_{o(er)}$ is a fixed capacitance that gives the same stored energy as C_{oss} while V_{DS} is rising from 0 to 80% V_{DSS} .

⁷⁾ $C_{o(tr)}$ is a fixed capacitance that gives the same charging time as C_{oss} while V_{DS} is rising from 0 to 80% V_{DSS} .