

Find the time-domain sinusoidal functions corresponding to phasors:  
( $z$  is position.  $Y_0^+$  and  $Y_0^-$  are **real and positive.**)

Make sure you follow conventions adopted in this course.

$$\tilde{Y}_1(z) = Y_0^+ e^{-j\beta z} \quad \Rightarrow \quad y_1(z, t) = Y_0^+ \cos(\omega t - \beta z)$$

$$\tilde{Y}_2(z) = Y_0^- e^{j\beta z} \quad \Rightarrow \quad y_2(z, t) = Y_0^- \cos(\omega t + \beta z)$$

$$\tilde{Y}(z) = -2jY_0^+ \sin(\beta z) \quad \Rightarrow \quad ?$$

Find the time-domain sinusoidal functions corresponding to phasors:  
( $z$  is position.  $Y_0^+$  and  $Y_0^-$  are **real and positive**.)

Make sure you follow conventions adopted in this course.

$$\tilde{Y}_1(z) = Y_0^+ e^{-j\beta z} \quad \Rightarrow \quad y_1(z, t) = Y_0^+ \cos(\omega t - \beta z)$$

$$\tilde{Y}_2(z) = Y_0^- e^{j\beta z} \quad \Rightarrow \quad y_2(z, t) = Y_0^- \cos(\omega t + \beta z)$$

$$\tilde{Y}(z) = -2jY_0^+ \sin(\beta z) \Rightarrow y(z, t) = \text{Re}[-2jY_0^+ \sin(\beta z)e^{j\omega t}] = 2Y_0^+ \sin(\beta z) \sin(\omega t)$$

**This  $j$  means phase  $\pi/2$**

Find the phasor for the following function of position  $z$  and time  $t$ .

( $z$  is position.  $V_0^+$  is **real and positive**)

$$v(z, t) = 2V_0^+ \cos(\beta z) \cos(\omega t)$$

Find the time-domain sinusoidal functions corresponding to phasors:  
( $z$  is position.  $Y_0^+$  and  $Y_0^-$  are **real and positive**.)

Make sure you follow conventions adopted in this course.

$$\tilde{Y}_1(z) = Y_0^+ e^{-j\beta z} \quad \Rightarrow \quad y_1(z, t) = Y_0^+ \cos(\omega t - \beta z)$$

$$\tilde{Y}_2(z) = Y_0^- e^{j\beta z} \quad \Rightarrow \quad y_2(z, t) = Y_0^- \cos(\omega t + \beta z)$$

$$\tilde{Y}(z) = -2jY_0^+ \sin(\beta z) \Rightarrow y(z, t) = \text{Re}[-2jY_0^+ \sin(\beta z)e^{j\omega t}] = 2Y_0^+ \sin(\beta z) \sin(\omega t)$$

**This  $j$  means phase  $\pi/2$**

Find the phasor for the following function of position  $z$  and time  $t$ .

( $z$  is position.  $V_0^+$  is **real and positive**)

$$v(z, t) = 2V_0^+ \cos(\beta z) \cos(\omega t)$$


$$\Rightarrow \quad \tilde{V}(z) = 2V_0^+ \cos(\beta z)$$

**Note:**  $v(z, t) = 2V_0^+ \cos(\beta z) \cos(\omega t) \neq \tilde{V}(z) = 2V_0^+ \cos(\beta z)$

## Standing Wave

Interference between the incident & reflected waves  $\rightarrow$  Standing wave

A string with one end fixed on a wall

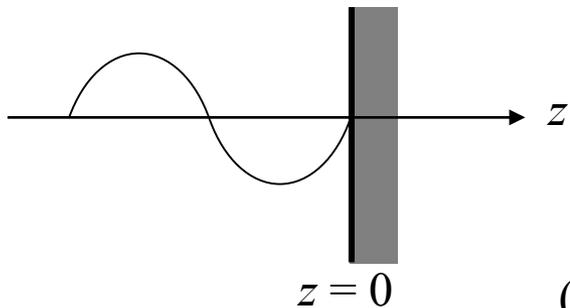

Incident:  $y_1(z, t) = Y_0^+ \cos(\omega t - \beta z)$

$$\tilde{Y}_1(z) = Y_0^+ e^{-j\beta z}$$

(Set the incident wave's phase to be 0, i.e.,  $Y_0^+$  real & positive.)

Reflected:  $y_2(z, t) = |Y_0^-| \cos(\omega t + \beta z + \phi)$

$$\tilde{Y}_2(z) = Y_0^- e^{j\beta z}, \text{ where } Y_0^- = |Y_0^-| e^{j\phi} = |Y_0^-| \angle \phi$$

The total displacement

$$\tilde{Y}(z) = \tilde{Y}_1(z) + \tilde{Y}_2(z) = Y_0^+ e^{-j\beta z} + Y_0^- e^{j\beta z}$$

We must have  $\tilde{Y}(0) = 0 \Rightarrow Y_0^+ + Y_0^- = 0$  i.e.  $Y_0^- = -Y_0^+$

$$\tilde{Y}(z) = Y_0^+ (e^{-j\beta z} - e^{j\beta z})$$

$$\tilde{Y}(z) = Y_0^+ (e^{-j\beta z} - e^{j\beta z})$$

Recall that  $e^{j\theta} - e^{-j\theta} = 2j \sin \theta \quad \Rightarrow \quad \tilde{Y}(z) = -2jY_0^+ \sin(\beta z)$

$$y(z, t) = \text{Re}[-2jY_0^+ \sin(\beta z)] = 2Y_0^+ \sin(\beta z) \underline{\sin(\omega t)} \quad \text{Why sin?}$$

$$\tilde{Y}(z) = Y_0^+ (e^{-j\beta z} - e^{j\beta z})$$

Recall that  $e^{j\theta} - e^{-j\theta} = 2j \sin \theta \quad \Rightarrow \quad \tilde{Y}(z) = -2jY_0^+ \sin(\beta z)$

$$y(z, t) = \text{Re}[-2jY_0^+ \sin(\beta z)] = 2Y_0^+ \sin(\beta z) \sin(\omega t) \quad \text{Why sin?}$$

See Wikipedia Standing Wave animation to get visual picture:  
Harmonic oscillation at each z, with amplitude following  $\sin(\beta z)$




[https://en.wikipedia.org/wiki/Standing\\_wave](https://en.wikipedia.org/wiki/Standing_wave)

This is Homework 1 Problem 4.

Here we just used the phasor tool to do it the easy way.

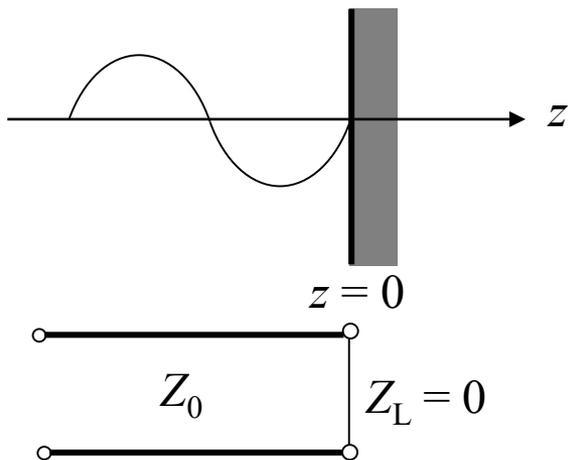Review Homework 1 Problem 4 (and also Quiz 2), relate the physical quantities to the phasors.



$$\tilde{Y}(z) = Y_0^+ (e^{-j\beta z} - e^{j\beta z}) \Rightarrow \boxed{\tilde{Y}(z) = -2jY_0^+ \sin(\beta z)}$$

$$y(z, t) = \text{Re}[-2jY_0^+ \sin(\beta z)] = 2Y_0^+ \sin(\beta z) \sin(\omega t)$$

Similarly, shorted transmission line:


By definition of “short circuit”,  $\tilde{V}(0) = 0 \Rightarrow V_0^+ + V_0^- = 0$

$$V_0^- = -V_0^+$$

$$\boxed{\tilde{V}(z) = -2jV_0^+ \sin(\beta z)}$$

$$v(z, t) = \text{Re}[-2jV_0^+ \sin(\beta z)] = 2V_0^+ \sin(\beta z) \sin(\omega t)$$

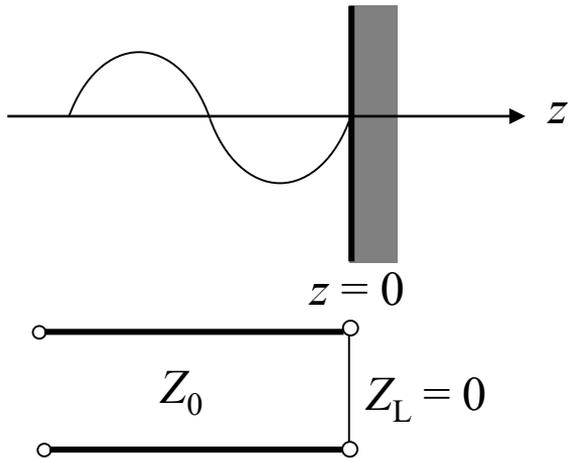Like a mirror. What property of a mirror makes it a mirror?



$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = -1$$

$$\tilde{Y}(z) = Y_0^+ (e^{-j\beta z} - e^{j\beta z}) \Rightarrow \boxed{\tilde{Y}(z) = -2jY_0^+ \sin(\beta z)}$$

$$y(z, t) = \text{Re}[-2jY_0^+ \sin(\beta z)] = 2Y_0^+ \sin(\beta z) \sin(\omega t)$$

Similarly, shorted transmission line:

By definition of “short circuit”,  $\tilde{V}(0) = 0 \Rightarrow V_0^+ + V_0^- = 0$

$$V_0^- = -V_0^+ \quad \Gamma = -1$$

$$\boxed{\tilde{V}(z) = -2jV_0^+ \sin(\beta z)}$$

$$v(z, t) = \text{Re}[-2jV_0^+ \sin(\beta z)] = 2V_0^+ \sin(\beta z) \sin(\omega t)$$

Like a mirror. What property of a mirror makes it a mirror?

$$\text{But, } I_0^- = I_0^+ \quad \frac{I_0^+}{I_0^-} = -\Gamma = 1$$

Find  $\tilde{I}(z)$  and  $i(z, t)$  on your own.

What if the transmission line is terminated in open circuit?

Note: open ended  $\neq$  open circuit for high frequencies!

(You will see how to make an open circuit later.)



$$V_0^- = V_0^+ \quad \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = 1$$

$$\tilde{V}(z) = V_0^+ (e^{-j\beta z} + e^{j\beta z}) = 2V_0^+ \cos(\beta z)$$

Find  $v(z, t)$  on your own.

$$I_0^- = -I_0^+ \quad (\text{since total current is 0, by definition of open circuit})$$

Find  $\tilde{I}(z)$  and  $i(z, t)$  on your own.

In all the above examples,  $\Gamma = \pm 1$ . Completely reflected.

At very high frequencies, we often can only measure the amplitude or power ( $\propto$  amplitude squared), but not the instantaneous values or the waveform.


The following example is for the short circuit. The open circuit is similar (just with a shift of origin).

The amplitude of the voltage wave  $v(z, t)$  at position  $z$  is

$$|\tilde{V}(z)| = \sqrt{\tilde{V}(z)\tilde{V}^*(z)} \quad \text{“Local amplitude” – see the standing wave animation again}$$

$\swarrow$  The “complex amplitude” containing the phase

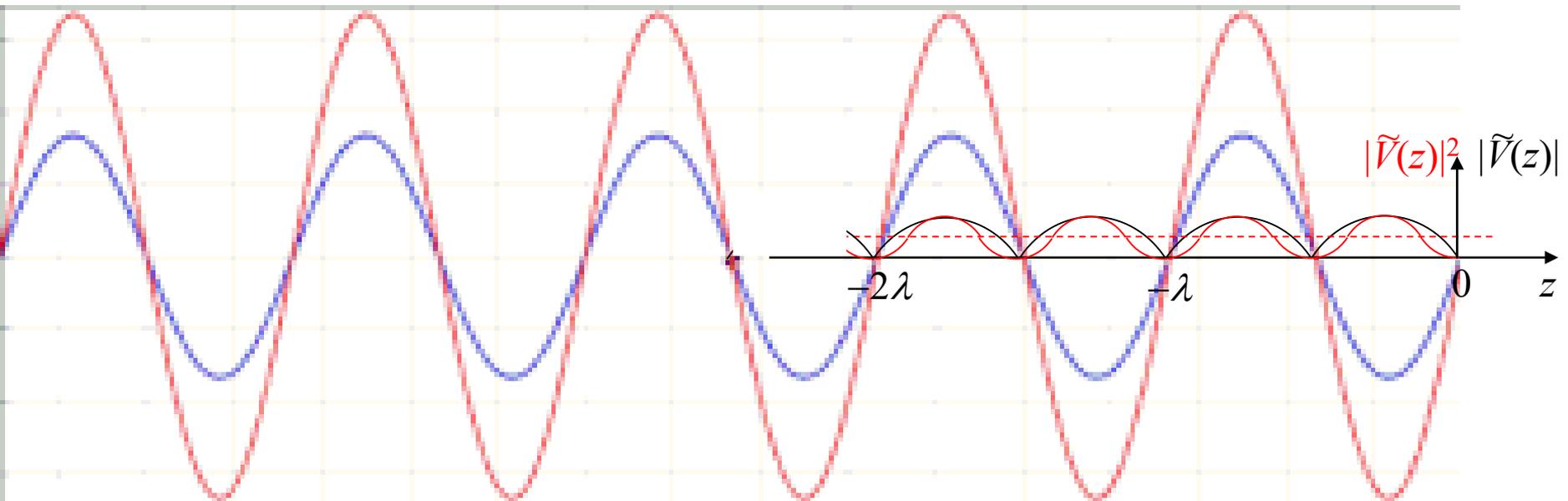[https://en.wikipedia.org/wiki/Standing\\_wave](https://en.wikipedia.org/wiki/Standing_wave)



At very high frequencies, we often can only measure the amplitude or power ( $\propto$  amplitude squared), but not the instantaneous values or the waveform.

The following example is for the **short circuit**. The open circuit is similar (just with a shift of origin).


The amplitude of the voltage wave  $v(z, t)$  at position  $z$  is

$$|\tilde{V}(z)| = \sqrt{\tilde{V}(z)\tilde{V}^*(z)} \quad \text{“Local amplitude” – see the standing wave animation again}$$

↙ The “complex amplitude” containing the phase

$$\tilde{V}(z) = -2jV_0^+ \sin(\beta z)$$

$$\begin{aligned} \Rightarrow |\tilde{V}(z)| &= |-2jV_0^+ \sin(\beta z)| \\ &= 2|V_0^+| |\sin(\beta z)| \end{aligned}$$

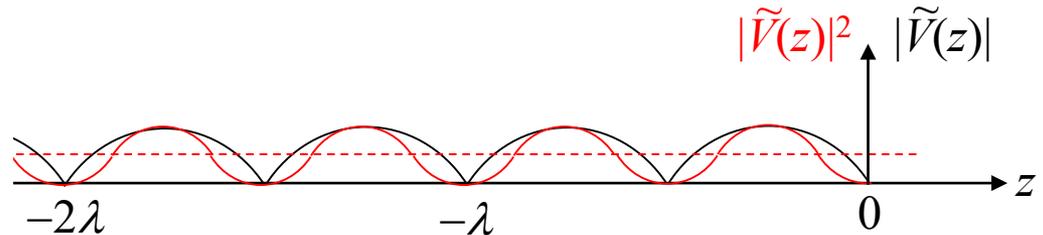

$$|\tilde{V}(z)|^2 = 4|V_0^+|^2 \sin^2(\beta z) = 2|V_0^+|^2 [1 - \cos(2\beta z)]$$

Question: What's the spatial period of the standing wave?

At very high frequencies, we often can only measure the amplitude or power ( $\propto$  amplitude squared), but not the instantaneous values or the waveform.

The following example is for the **short circuit**. The open circuit is similar (just with a shift of origin).

The amplitude of the voltage wave  $v(z, t)$  at position  $z$  is


$$|\tilde{V}(z)| = \sqrt{\tilde{V}(z)\tilde{V}^*(z)} \quad \text{“Local amplitude” – see the standing wave animation again}$$

↙ The “complex amplitude” containing the phase

$$\tilde{V}(z) = -2jV_0^+ \sin(\beta z)$$

$$\Rightarrow |\tilde{V}(z)| = |-2jV_0^+ \sin(\beta z)|$$

$$= 2|V_0^+| |\sin(\beta z)|$$

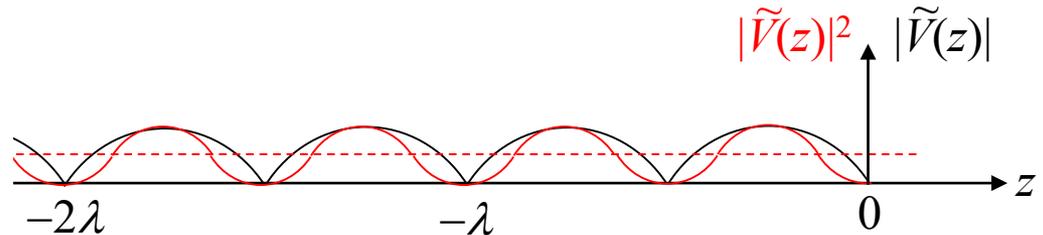

$$|\tilde{V}(z)|^2 = 4|V_0^+|^2 \sin^2(\beta z) = 2|V_0^+|^2 [1 - \cos(2\beta z)]$$


Question: What's the spatial period of the standing wave?

The open circuit: Just a shift of the origin

$$|\tilde{V}(z)| = 2|V_0^+| |\cos(\beta z)|$$

$$|\tilde{V}(z)|^2 = 4|V_0^+|^2 \cos^2(\beta z)$$

$$= 2|V_0^+|^2 [1 + \cos(2\beta z)]$$

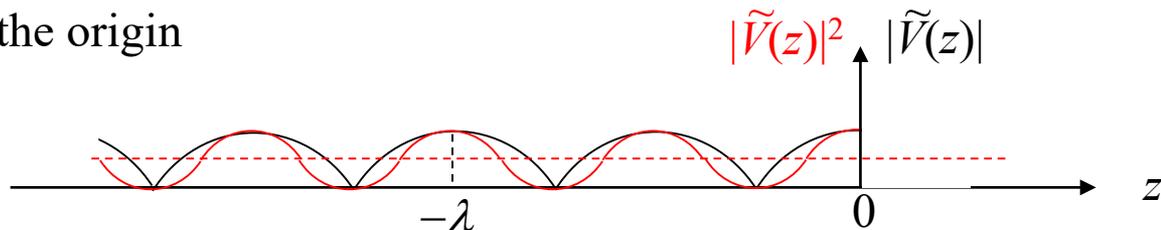

For both the short circuit (SC) and open circuit (OC),

$$|\tilde{V}(z)|_{\max} = 2 |V_0^+|$$

Constructive

$$|\tilde{V}(z)|_{\min} = 0$$

Destructive

$$|\Gamma| = 1$$

Complete reflection. Completely a standing wave.

There are cases where  $|\Gamma| = 1$  but  $\Gamma \neq \pm 1$ .

Also complete reflection. We'll talk about those cases later.

What if  $|\Gamma| \neq 1$  ?

Partially standing, partially traveling.

Now, let's look at the maxima and minima of this combination of a standing wave and a traveling wave.

Recall that, in general,  $\Gamma$  is a complex number:

$$\Gamma = |\Gamma| e^{j\theta_r}$$

$$\tilde{V}(z) = \underbrace{V_0^+ e^{-j\beta z}}_{\text{Incident}} + \underbrace{V_0^- e^{j\beta z}}_{\text{Reflected}} = V_0^+ e^{-j\beta z} + \Gamma V_0^+ e^{j\beta z} = V_0^+ e^{-j\beta z} + |\Gamma| e^{j\theta_r} V_0^+ e^{j\beta z}$$

$$\Gamma = |\Gamma| e^{j\theta_r}$$

$$|\tilde{V}(z)| = \sqrt{\tilde{V}(z) \tilde{V}^*(z)}$$

$$= \sqrt{V_0^+ (e^{-j\beta z} + |\Gamma| e^{j\theta_r} e^{j\beta z}) (V_0^+)^* (e^{j\beta z} + |\Gamma| e^{j\theta_r} e^{-j\beta z})}$$

Notice that  $V_0^+ (V_0^+)^* = |V_0^+|^2$

$V_0^+$  is a complex amplitude

$$\therefore |\tilde{V}(z)| = |V_0^+| \sqrt{(\dots)(\dots)}$$

$$\tilde{V}(z) = \underbrace{V_0^+ e^{-j\beta z}}_{\text{Incident}} + \underbrace{V_0^- e^{j\beta z}}_{\text{Reflected}} = V_0^+ e^{-j\beta z} + \Gamma V_0^+ e^{j\beta z} = V_0^+ e^{-j\beta z} + |\Gamma| e^{j\theta_r} V_0^+ e^{j\beta z}$$

$$\Gamma = |\Gamma| e^{j\theta_r}$$

$$|\tilde{V}(z)| = \sqrt{\tilde{V}(z) \tilde{V}^*(z)}$$

$$= \sqrt{V_0^+ (e^{-j\beta z} + |\Gamma| e^{j\theta_r} e^{j\beta z}) (V_0^+)^* (e^{j\beta z} + |\Gamma| e^{j\theta_r} e^{-j\beta z})}$$

Notice that  $V_0^+ (V_0^+)^* = |V_0^+|^2$

$V_0^+$  is a complex amplitude

$$\therefore |\tilde{V}(z)| = |V_0^+| \sqrt{(\dots)(\dots)}$$

$$= |V_0^+| \sqrt{1 + |\Gamma|^2 + \underbrace{2|\Gamma| \cos(2\beta z + \theta_r)}_{\text{Interference term}}}$$

Interference term

$$\tilde{V}(z) = \underbrace{V_0^+ e^{-j\beta z}}_{\text{Incident}} + \underbrace{V_0^- e^{j\beta z}}_{\text{Reflected}} = V_0^+ e^{-j\beta z} + \Gamma V_0^+ e^{j\beta z} = V_0^+ e^{-j\beta z} + |\Gamma| e^{j\theta_r} V_0^+ e^{j\beta z}$$

$$\Gamma = |\Gamma| e^{j\theta_r}$$

$$|\tilde{V}(z)| = \sqrt{\tilde{V}(z) \tilde{V}^*(z)}$$

$$= \sqrt{V_0^+ (e^{-j\beta z} + |\Gamma| e^{j\theta_r} e^{j\beta z}) (V_0^+)^* (e^{j\beta z} + |\Gamma| e^{j\theta_r} e^{-j\beta z})}$$

Notice that  $V_0^+ (V_0^+)^* = |V_0^+|^2$

$V_0^+$  is a complex amplitude

$$\therefore |\tilde{V}(z)| = |V_0^+| \sqrt{(\dots)(\dots)}$$

$$= |V_0^+| \sqrt{1 + |\Gamma|^2 + \underbrace{2|\Gamma| \cos(2\beta z + \theta_r)}_{\text{Interference term}}}$$



Interference term

Similarly,  $|\tilde{I}(z)| = |I_0^+| \sqrt{1 + |\Gamma|^2 - 2|\Gamma| \cos(2\beta z + \theta_r)}$

It's more convenient to plot  $|\tilde{V}(z)|^2$  and  $|\tilde{I}(z)|^2$  than the amplitudes.


$$2\beta z = 2\pi$$
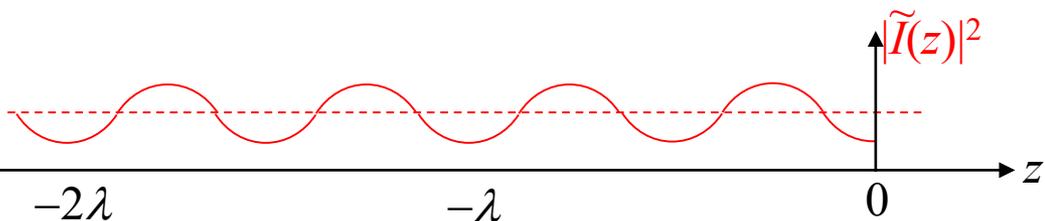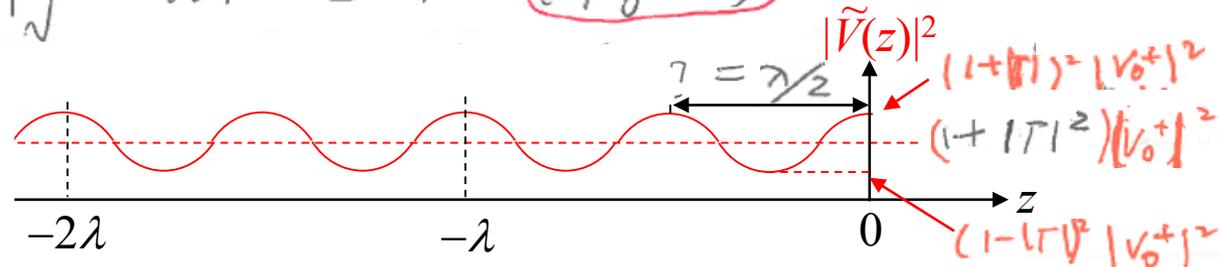
$$\therefore z = \frac{2\pi}{2\beta} = \frac{1}{2} \lambda$$



$$|\tilde{V}(z)| = |V_0^+| \sqrt{(\dots)(\dots)}$$

$$= |V_0^+| \sqrt{1 + |\Gamma|^2 + \underbrace{2|\Gamma| \cos(2\beta z + \theta_r)}_{\text{Interference term}}}$$

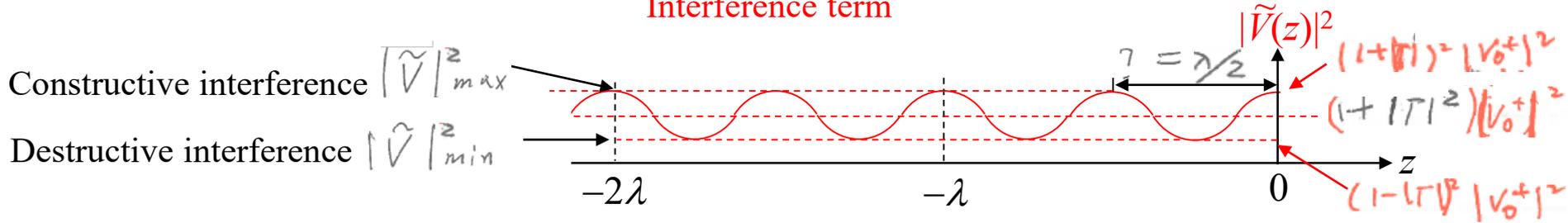


Pay attention to the max,  
min, and average values

In this plot, we have assumed a special case  $\theta_r = 0$ .  
 Can you think of a kind of load that leads to  $\theta_r = 0$ ?  
 Question: In general, what's the condition for  $\theta_r = 0$ ?

We stated that it's more convenient to plot the amplitudes squared than the amplitudes themselves.

But how does the plot of  $|\tilde{V}(z)|$  look?

It looks like this:

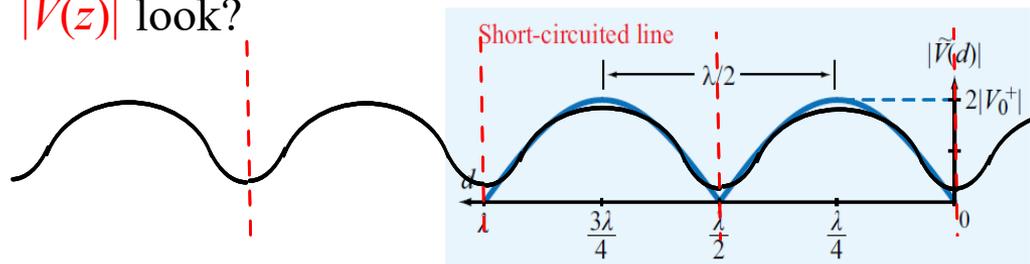


(overlapping the curve for the short circuit case for comparison)

$$|\tilde{V}(z)| = |V_0^+| \sqrt{(\dots)(\dots)}$$

$$= |V_0^+| \sqrt{1 + |\Gamma|^2 + \underbrace{2|\Gamma| \cos(2\beta z + \theta_r)}_{\text{Interference term}}}$$

Work out the max and min values of  $|\tilde{V}(z)|$ .

Notice the important difference between its shape and that of  $|\tilde{V}(z)|^2$ .

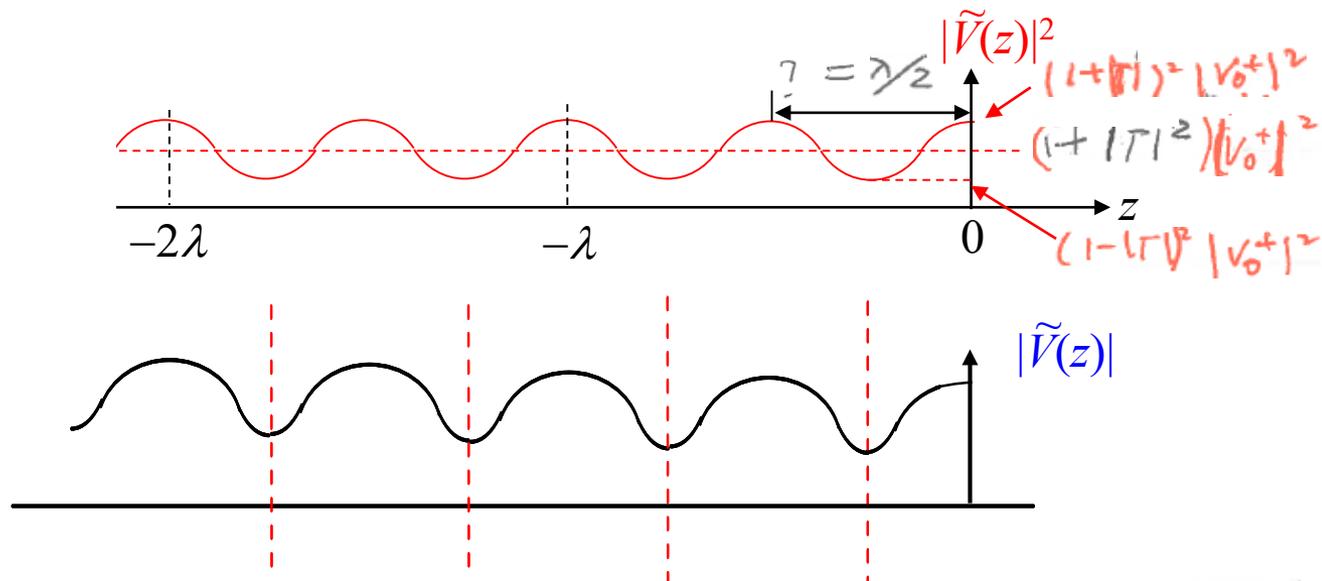

$$|\tilde{V}|_{max} = |V_0^+| \sqrt{1 + |\Gamma|^2 + 2|\Gamma|} = |V_0^+| (1 + |\Gamma|)$$

Constructive, reflection added to incident.

$$|\tilde{V}|_{min} = |V_0^+| \sqrt{1 + |\Gamma|^2 - 2|\Gamma|} = |V_0^+| (1 - |\Gamma|)$$

Destructive, reflection subtracted from incident.

Now we define the **voltage standing wave ratio** (VSWR), or simply standing wave ratio (SWR)

$$S = \frac{|\tilde{V}|_{max}}{|\tilde{V}|_{min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

Special (extreme) cases:

$|\Gamma| = 1, S = \infty \Rightarrow$  All standing wave.  $|\tilde{V}|_{min} = 0$   
 (Recall short & open. Other such cases to be discussed)

$|\Gamma| = 0, S = 1 \Rightarrow$  All traveling wave. No reflection.  
 (What's the condition for this? How does the plot look?)

## Slotted line

A tool to measure impedance. See in the textbook, Fig. 2-16 (pp. 71 in 8/E, pp. 74 in 7/E, pp. 73 in 6/E, or pp. 60 in 5/E). Based on the one-to-one mapping between  $z_L$  and  $\Gamma$ .

The detector measures the local field (proportional to voltage) as a function of longitudinal position  $z$ .


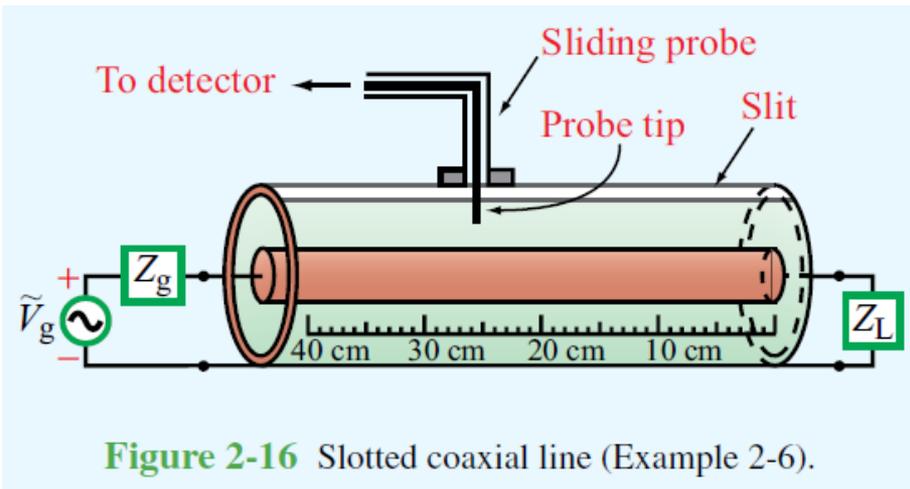


Figure 2-16 Slotted coaxial line (Example 2-6).

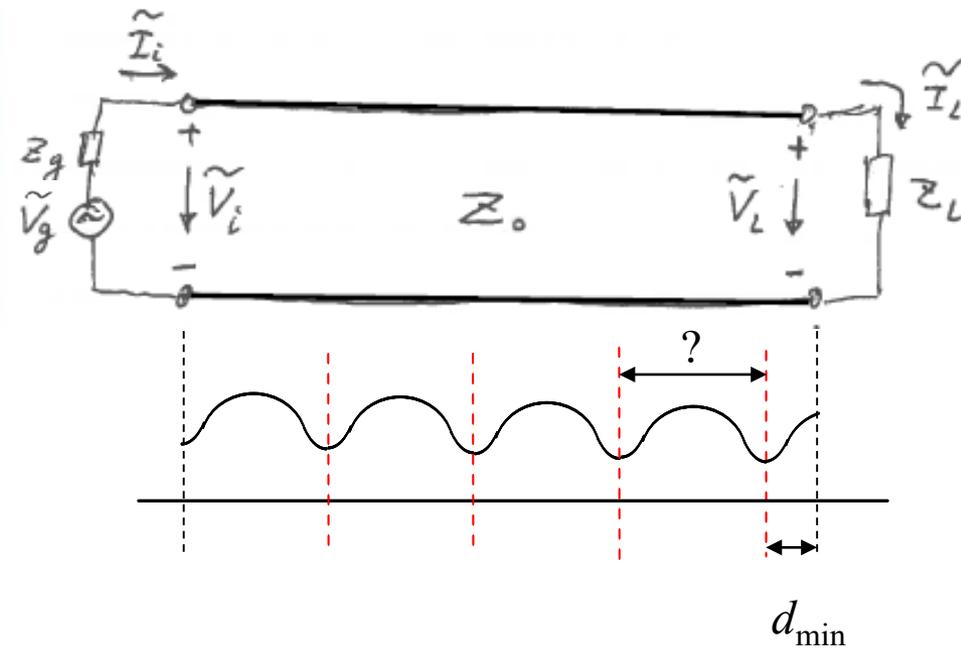Sliding the detector, you find the voltage (amplitude or ac voltage) maxima and minima.



The distance between adjacent minima is \_\_\_\_\_

## Slotted line

**A tool to measure impedance.** See in the textbook, Fig. 2-16 (pp. 74 in 7/E, pp. 73 in 6/E, or pp. 60 in 5/E). **Based on the one-to-one mapping between  $z_L$  and  $\Gamma$ .**

The detector **measures the local field (proportional to voltage)** as a function of longitudinal position  $z$ .

Sliding the detector, you find the voltage maxima and minima.

**The distance between adjacent minima is  $\lambda/2$ .**

You also get the max/min ratio


$$S = \frac{|\tilde{V}|_{\max}}{|\tilde{V}|_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

(You only care about the ratio, not the actual values.)

Solving  $S = \frac{1 + |\Gamma|}{1 - |\Gamma|}$ , you get  $|\Gamma|$ .

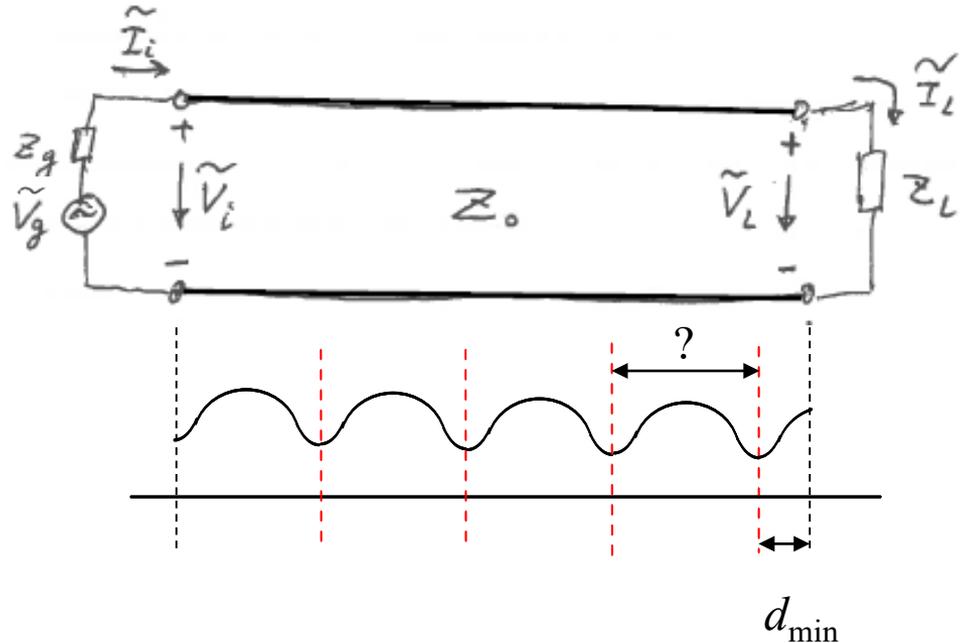**But this is not  $\Gamma$  yet!**

The hope is: If you know  $\Gamma$ , you get  $z_L$  using the one-to-one mapping between the two. (Recall that.) You know  $Z_0$ , thus you can find  $Z_L$ .



The hope is: If you know  $\Gamma$ , you get  $z_L$  using the one-to-one mapping between the two. (Recall that.) You know  $Z_0$ , thus you can find  $Z_L$ .

$$\Gamma = |\Gamma| e^{j\theta_r} \quad \text{We already know } |\Gamma|. \text{ Just need to find } \theta_r.$$

We know  $\frac{\lambda}{2} \xrightarrow{\beta = \frac{2\pi}{\lambda}}$   $\beta$

We know  $z_{\min} = -d_{\min}$


$$2\beta z_{\min} + \theta_r = -\pi$$

$$-2\beta d_{\min} + \theta_r = -\pi$$

$$2\beta d_{\min} - \theta_r = \pi$$

So you find  $\theta_r$ .

$$\Gamma = |\Gamma| e^{j\theta_r} \Rightarrow z_L \Rightarrow Z_L$$

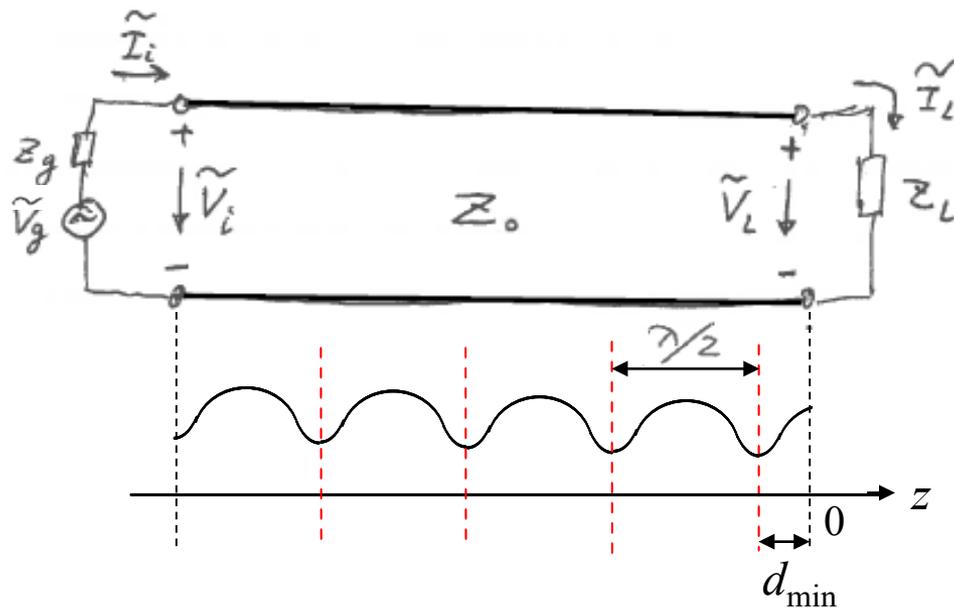

$$|\tilde{V}(z)| = |V_0^+| \sqrt{1 + |\Gamma|^2 + 2|\Gamma| \cos(2\beta z + \theta_r)}$$

Question:


In principle, we can also obtain the result by measuring positions of maxima.

But, in practice, we prefer minima. Why?

We have so far always dealt with negative  $z$ , because we draw the transmission line to the left of the load.

We don't like to always carry the negative sign.

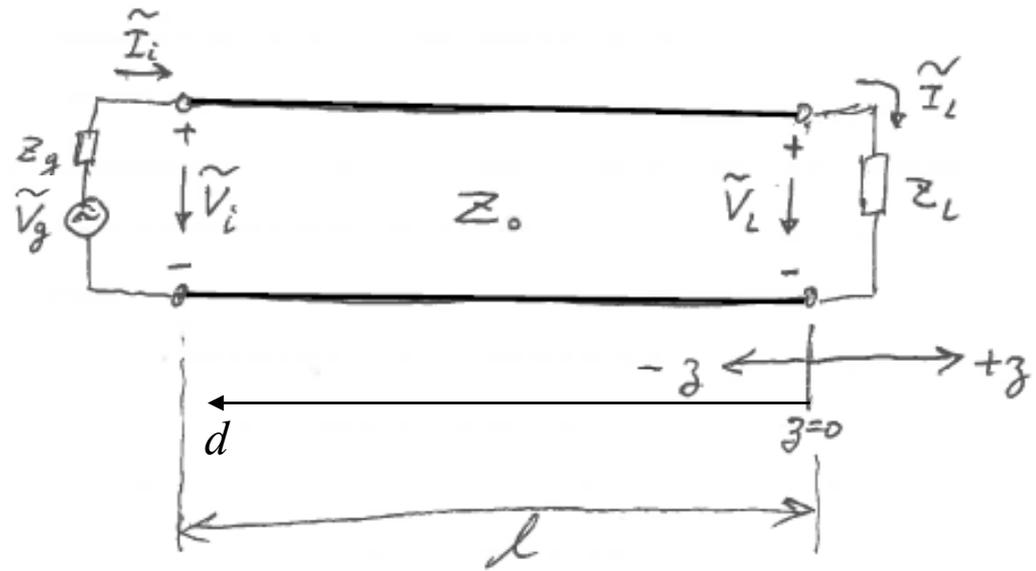So we define  $d = -z$ , the distance from the load.



$$\tilde{V}(z) = \underbrace{V_0^+ e^{-j\beta z}}_{\text{Incident}} + \underbrace{\Gamma V_0^+ e^{j\beta z}}_{\text{Reflected}}$$

$$\tilde{V}(z) = V_0^+ e^{-j\beta z} + \Gamma V_0^+ e^{j\beta z}$$

$$\Rightarrow \tilde{V}(d) = V_0^+ e^{j\beta d} + \Gamma V_0^+ e^{-j\beta d}$$

$$\tilde{I}(z) = I_0^+ e^{-j\beta z} - \Gamma I_0^+ e^{j\beta z}$$


$$\Rightarrow \tilde{I}(d) = I_0^+ e^{j\beta d} - \Gamma I_0^+ e^{-j\beta d}$$

Pay attention to signs.

This sign is the most asked about. Let's focus on the present discussion now. I will give a better explanation later.

$$\tilde{V}(d) = V_0^+ e^{j\beta d} + \Gamma V_0^+ e^{-j\beta d}$$
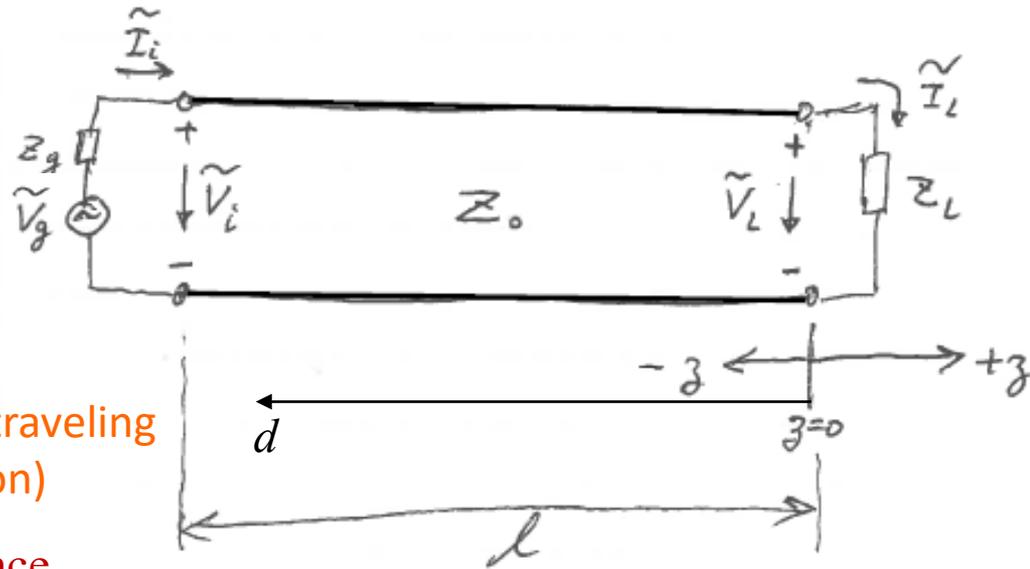
$$\tilde{I}(d) = I_0^+ e^{j\beta d} - \Gamma I_0^+ e^{-j\beta d}$$



$$\frac{\tilde{V}^+(d)}{\tilde{I}^+(d)} = \frac{V_0^+}{I_0^+} = Z_0 \quad (\text{always holds for a traveling wave in one direction})$$

Now let's consider the **equivalent impedance** looking into the transmission line at a distance  $d$  from the load:

$$z(d) = \frac{\tilde{V}(d)}{\tilde{I}(d)} = \frac{V_0^+ (e^{j\beta d} + \Gamma e^{-j\beta d})}{V_0^+ (e^{j\beta d} - \Gamma e^{-j\beta d})} Z_0 = Z_0 \cdot \frac{1 + \Gamma e^{-2j\beta d}}{1 - \Gamma e^{-2j\beta d}} \equiv Z_0 \cdot \frac{1 + \Gamma_d}{1 - \Gamma_d}$$

**Important concept:**  
equivalent impedance at distance  $d$

Compare to  $\frac{Z_L}{Z_0} = \frac{1 + \Gamma}{1 - \Gamma}$ , thus the definition.  $\Gamma_d = \Gamma e^{-2j\beta d}$

$z(d) - \Gamma_d$  one-to-one correspondence exactly same as  $z_L - \Gamma$


$$Z(d) = Z_0 \cdot \frac{1 + \Gamma_d}{1 - \Gamma_d} \Leftrightarrow \Gamma_d = \Gamma e^{-2j\beta d} \quad (\text{equivalent reflection coefficient at } d)$$

How to interpret this?

Say, the incident wave voltage is  $\tilde{V}(d)$  at  $d$  from  $z_L$ .

At the load,  $d$  away **in the propagation direction**,  
the **incident wave** is  $\tilde{V}(d)e^{-j\beta d}$   
-- just a phase shift.

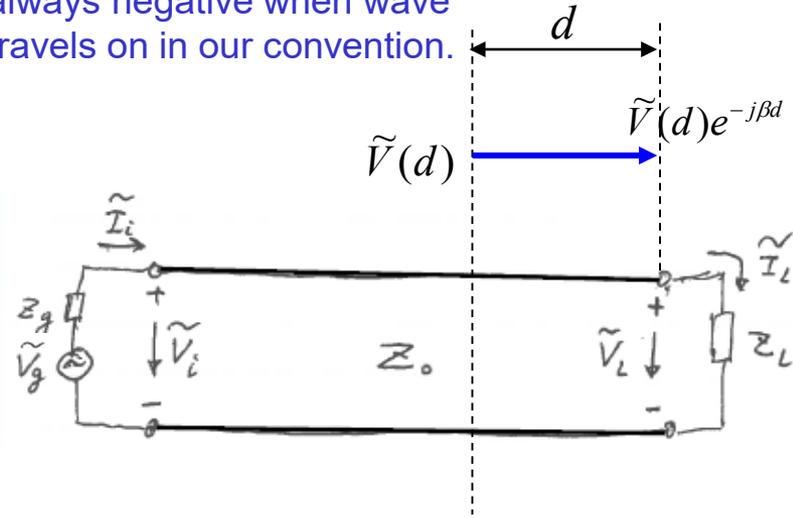Notice this sign. Phase shift  
always negative when wave  
travels on in our convention.



**Note:** This means the phase difference at  
any time is  $-\beta d$ .

**Question:** What is the phase difference between  $v(d, t)$  and  $v(d, t + d/v_p)$ ?

$$Z(d) = Z_0 \cdot \frac{1 + \Gamma_d}{1 - \Gamma_d} \Leftrightarrow \Gamma_d = \Gamma e^{-2j\beta d} \quad (\text{equivalent reflection coefficient at } d)$$


How to interpret this?

Say, the incident wave voltage is  $\tilde{V}(d)$  at  $d$  from  $z_L$ .

At the load,  $d$  away **in the propagation direction**,  
the **incident wave** is  $\tilde{V}(d)e^{-j\beta d}$   
-- just a phase shift.

At the load, the **reflected wave** is  $\tilde{V}(d)\Gamma e^{-j\beta d}$

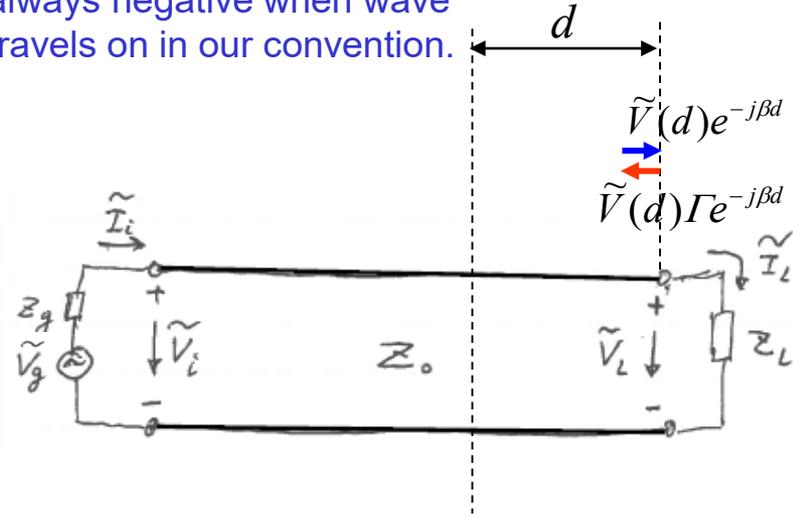Notice this sign. Phase shift  
always negative when wave  
travels on in our convention.



$$Z(d) = Z_0 \cdot \frac{1 + \Gamma_d}{1 - \Gamma_d} \Leftrightarrow \Gamma_d = \Gamma e^{-2j\beta d} \quad (\text{equivalent reflection coefficient at } d)$$

How to interpret this?

Say, the incident wave voltage is  $\tilde{V}(d)$  at  $d$  from  $z_L$ .

Notice this sign. Phase shift always negative when wave travels on in our convention.


At the load,  $d$  away **in the propagation direction**, the **incident wave** is  $\tilde{V}(d)e^{-j\beta d}$   
 -- just a phase shift.

At the load, the **reflected wave** is  $\tilde{V}(d)\Gamma e^{-j\beta d}$

Back at the point  $d$  away from the load, **in the propagation direction** (of the reflection), the reflected wave is

$$\tilde{V}(d)\Gamma e^{-j\beta d} e^{-j\beta d} = \tilde{V}(d)\Gamma e^{-2j\beta d}$$

-- just another phase shift.

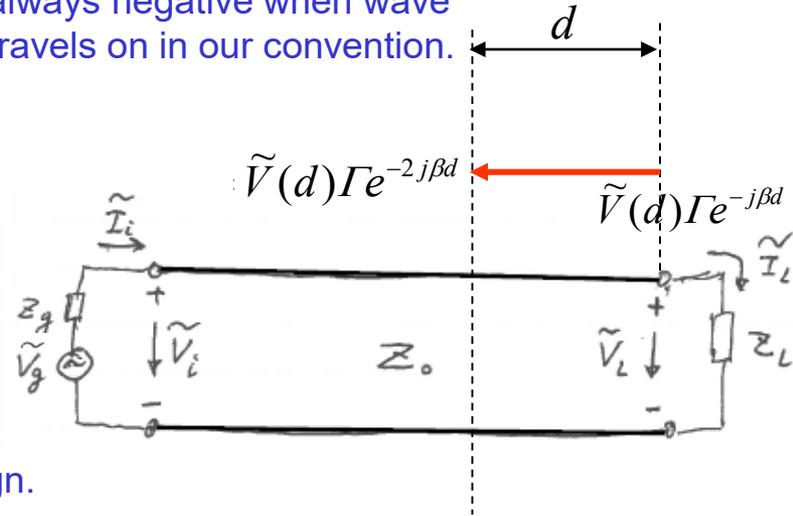

Notice this sign.

$$z(d) = z_0 \cdot \frac{1 + \Gamma_d}{1 - \Gamma_d} \Leftrightarrow \Gamma_d = \Gamma e^{-2j\beta d} \quad (\text{equivalent reflection coefficient at } d)$$

How to interpret this?

Say, the incident wave voltage is  $\tilde{V}(d)$  at  $d$  from  $z_L$ .

Notice this sign. Phase shift always negative when wave travels on in our convention.

At the load,  $d$  away **in the propagation direction**, the **incident wave** is  $\tilde{V}(d)e^{-j\beta d}$   
 -- just a phase shift.

At the load, the **reflected wave** is  $\tilde{V}(d)\Gamma e^{-j\beta d}$


Back at the point  $d$  away from the load, **in the propagation direction** (of the reflection), the reflected wave is

$$\tilde{V}(d)\Gamma e^{-j\beta d} e^{-j\beta d} = \tilde{V}(d)\Gamma e^{-2j\beta d}$$

-- just another phase shift.

Thus the equivalent reflection coefficient at  $d$  is

$$\Gamma_d = \Gamma e^{-2j\beta d}$$

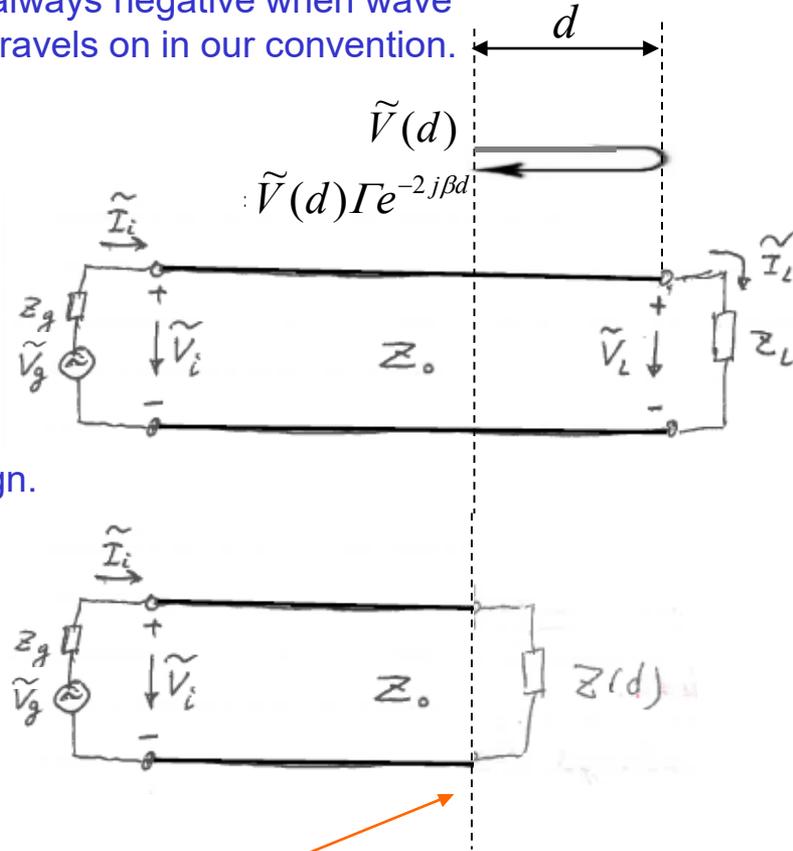

Notice this sign.





Just imagine the interface is at  $d$ . We have the equivalent circuit.

$z(d)$  corresponds to  $\Gamma_d$  in exactly the same manner as any  $z_L$  to  $\Gamma$ .

$Z(d)$  corresponds to  $\Gamma_d$  in exactly the same manner as any  $Z_L$  to  $\Gamma$ .

Therefore the equivalent circuit.

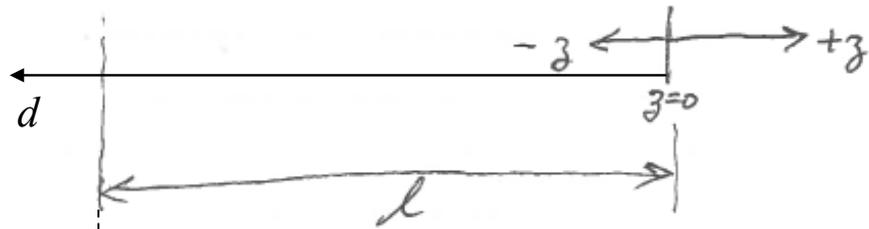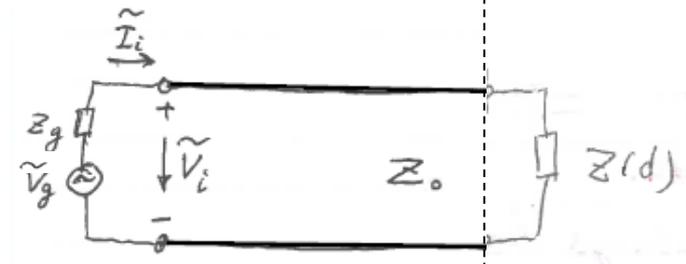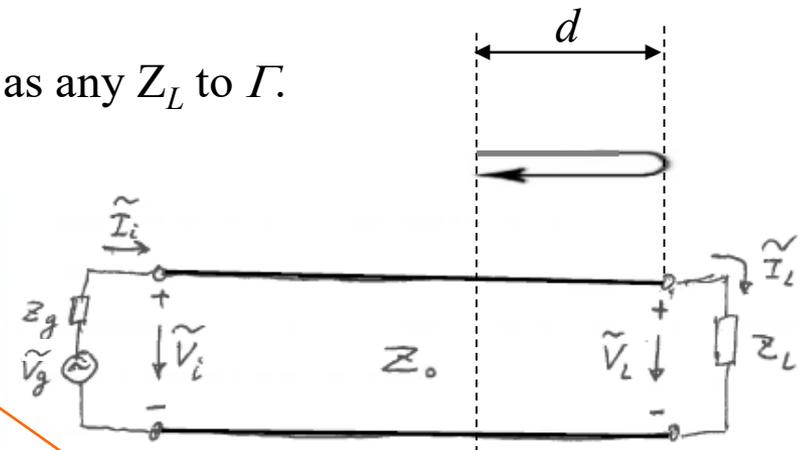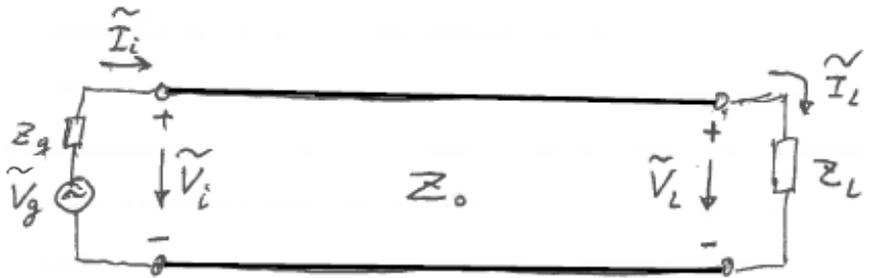You can have such an equivalent circuit at any  $d$ , all the way up to  $l$  for the entire transmission line:



At the input end of the transmission line,

$$Z_{in} = Z(l) = Z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L}$$

This way, you turn the transmission line problem in to a simple circuit problem.


Question: Given  $\tilde{V}_g$  and  $Z_g$ , how do you find  $\tilde{V}_i$ ?



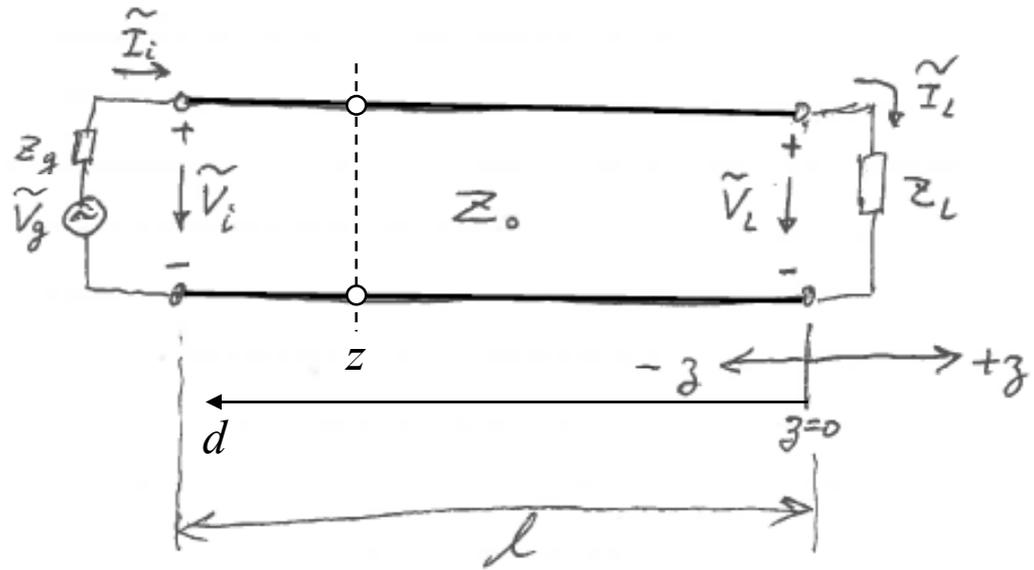
# About That Negative Sign

$$\tilde{V}(z) = \underbrace{V_0^+ e^{-j\beta z}}_{\text{Incident}} + \underbrace{\Gamma V_0^+ e^{j\beta z}}_{\text{Reflected}}$$

$$\tilde{I}(z) = \underbrace{I_0^+ e^{-j\beta z}}_{\text{Incident}} - \underbrace{\Gamma I_0^+ e^{j\beta z}}_{\text{Reflected}}$$



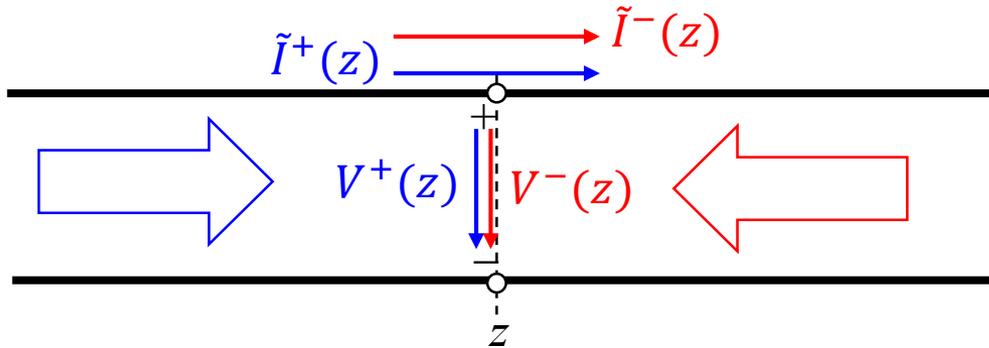More generally, for a traveling wave going towards  $+z$  and another one going  $-z$ :  
(not necessarily the incident and the reflected)



We have learned

$$\frac{\tilde{V}^+(z)}{\tilde{I}^+(z)} = \frac{V_0^+ e^{-j\beta z}}{I_0^+ e^{-j\beta z}} = \frac{V_0^+}{I_0^+} = Z_0$$


The traveling wave going towards  $-z$  must follow the same physics:

This negative sign is due to the way we define the polarity of  $\tilde{I}^-$

$$\frac{\tilde{V}^-(z)}{-\tilde{I}^-(z)} = \frac{V_0^- e^{j\beta z}}{-I_0^- e^{j\beta z}} = \frac{V_0^-}{-I_0^-} = Z_0$$

$$\frac{\tilde{V}^-(z)}{\tilde{I}^-(z)} = \frac{V_0^- e^{j\beta z}}{I_0^- e^{j\beta z}} = \frac{V_0^-}{I_0^-} = -Z_0$$

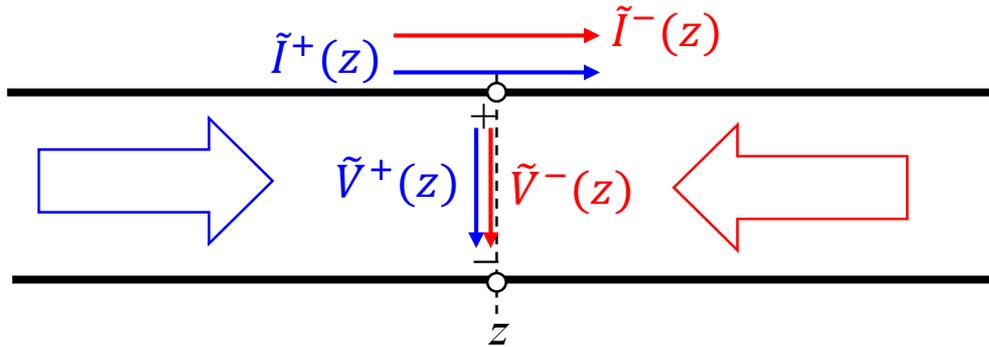
Our **convention** for a traveling wave going towards  $+z$  and **another one** going  $-z$ :  
 (not necessarily the incident and the reflected)



$$\frac{\tilde{V}^+(z)}{\tilde{I}^+(z)} = \frac{V_0^+ e^{-j\beta z}}{I_0^+ e^{-j\beta z}} = \frac{V_0^+}{I_0^+} = Z_0$$

$$\frac{\tilde{V}^-(z)}{-\tilde{I}^-(z)} = \frac{V_0^- e^{j\beta z}}{-I_0^- e^{j\beta z}} = \frac{V_0^-}{-I_0^-} = Z_0 \iff \frac{\tilde{V}^-(z)}{\tilde{I}^-(z)} = \frac{V_0^- e^{j\beta z}}{I_0^- e^{j\beta z}} = \frac{V_0^-}{I_0^-} = -Z_0$$

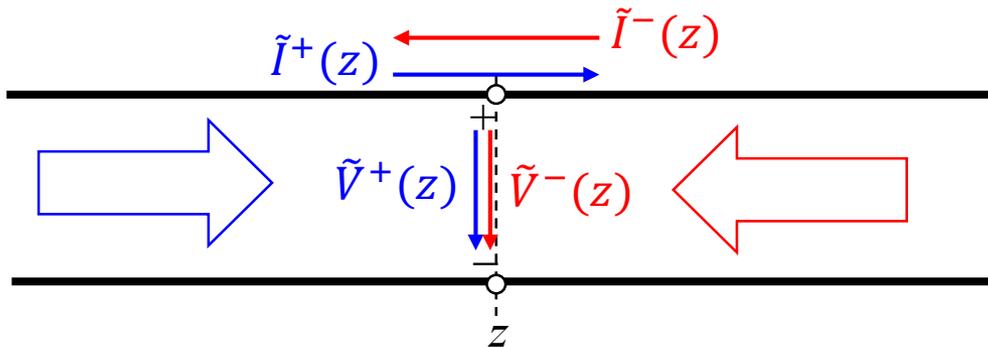If we *wanted* to be fair with the two waves, we could use a different convention:




$$\frac{\tilde{V}^+(z)}{\tilde{I}^+(z)} = \frac{V_0^+ e^{-j\beta z}}{I_0^+ e^{-j\beta z}} = \frac{V_0^+}{I_0^+} = Z_0$$

$$\frac{\tilde{V}^-(z)}{\tilde{I}^-(z)} = \frac{V_0^- e^{j\beta z}}{I_0^- e^{j\beta z}} = \frac{V_0^-}{I_0^-} = Z_0$$

Both conventions give us the same  $Z(z)/Z_0$  (or  $Z(d)/Z_0$  with  $d = -z$ ).

Now, in the context of reflection

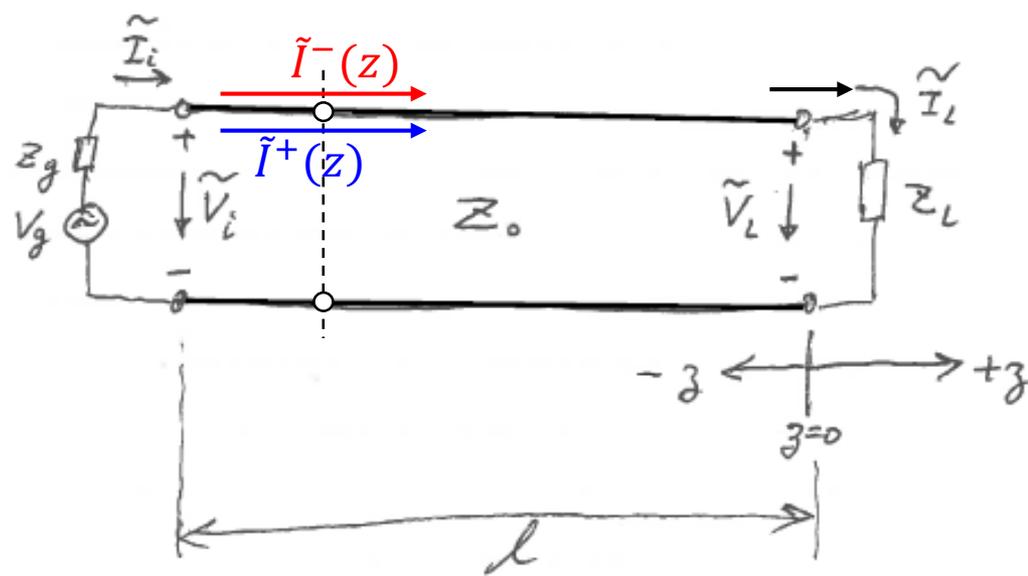

What if  $Z_L \neq Z_0$ ?

The load says 
$$\frac{\tilde{V}(0)}{\tilde{I}(0)} = \frac{\tilde{V}_L}{\tilde{I}_L} = Z_L$$

If there were only the incident wave, 
$$\frac{\tilde{V}^+(0)}{\tilde{I}^+(0)} = \frac{V_0^+}{I_0^+} = Z_0$$

Something has to happen to resolve this “conflict.” That something is reflection.

$$\begin{aligned} \tilde{V}_L &= \tilde{V}(z=0) = V_0^+ + V_0^- \\ \tilde{I}_L &= \tilde{I}(z=0) = I_0^+ + I_0^- = \frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0} \end{aligned}$$

Sign due to convention

$$\frac{V_0^-}{I_0^-} = -Z_0$$

By definition, 
$$Z_L = \frac{\tilde{V}_L}{\tilde{I}_L} = \left( \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \right) Z_0$$

Solve it and we have 
$$V_0^- = \frac{Z_L - Z_0}{Z_L + Z_0} V_0^+$$

This sounds like the reflection is just due to our sign convention, doesn't it? If we used **the fair alternative convention**, would there be no reflection?

In the *fair* alternative convention

$$\tilde{I}(z) = \tilde{I}^+(z) - \tilde{I}^-(z)$$



The load says  $\frac{\tilde{V}(0)}{\tilde{I}(0)} = \frac{\tilde{V}_L}{\tilde{I}_L} = Z_L$

If there were only the incident wave,  $\frac{\tilde{V}^+(0)}{\tilde{I}^+(0)} = \frac{V_0^+}{I_0^+} = Z_0$


Something has to happen to resolve this “conflict.” That something is reflection.

$$\tilde{V}_L = \tilde{V}(z=0) = V_0^+ + V_0^-$$

$$\tilde{I}_L = \tilde{I}(z=0) = I_0^+ - I_0^- = \frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0}$$

By definition,  $Z_L = \frac{\tilde{V}_L}{\tilde{I}_L} = \left( \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \right) Z_0$

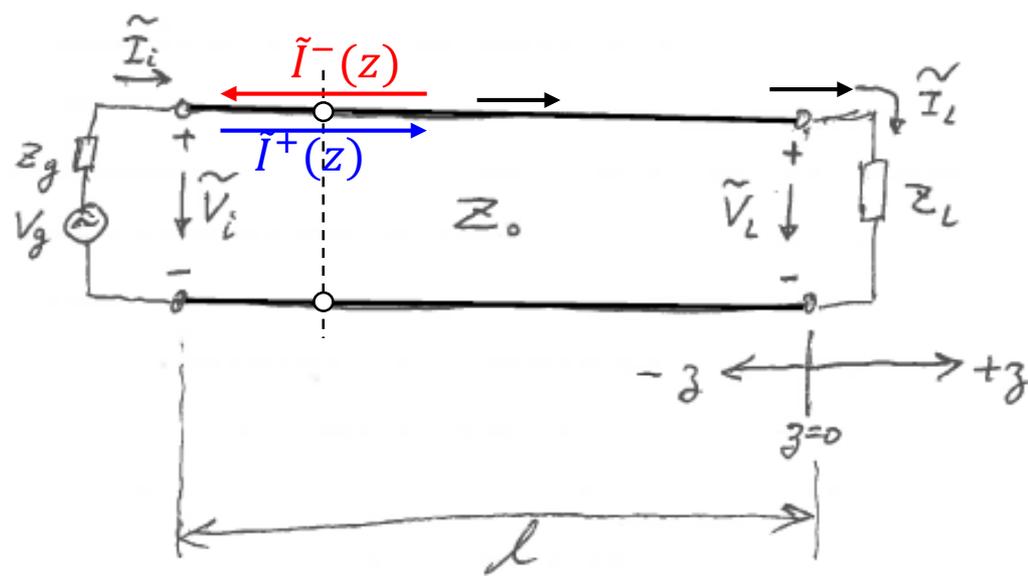Solve it and we have  $V_0^- = \frac{Z_L - Z_0}{Z_L + Z_0} V_0^+$



In the *fair* convention  $\frac{V_0^-}{I_0^-} = Z_0$

We end up with exactly the same thing!

Review textbook Sections 2-6, 2-7.  
Do HW2 up to Problem 9.

Notice that we take a different approach than in the textbook (again).  
We started from special cases: short and open circuit terminations.  
Then we moved on to the general case.  
Now we are going back to the special cases, but not that special.


Short circuit  $\Gamma = -1$ . Open circuit  $\Gamma = 1$ .  
There are cases where  $|\Gamma| = 1$  but  $\Gamma \neq \pm 1$ .  
Also complete reflection, but neither short nor open.

What loads make those cases?

All cases of  $|\Gamma| = 1$

There are cases where  $|\Gamma| = 1$  but  $\Gamma \neq \pm 1$ .  
Also complete reflection, but neither short  
nor open.

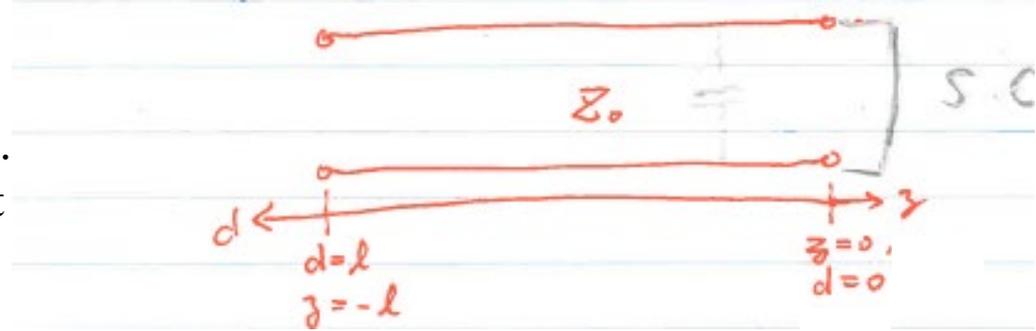**A quarter wavelength** away from a short,  
the equivalent circuit is an open.  
(See next slide – an old one)



At very high frequencies, we often can only measure the amplitude or power ( $\propto$  amplitude squared), but not the instantaneous values or the waveform.

The amplitude of the voltage wave  $v(z, t)$  at position  $z$  is  $|\tilde{V}(z)| = \sqrt{\tilde{V}(z)\tilde{V}^*(z)}$

The “complex amplitude” containing the phase


Short

$$\tilde{V}(z) = -2jV_0^+ \sin(\beta z)$$

$$\Rightarrow |\tilde{V}(z)| = |-2jV_0^+ \sin(\beta z)|$$

$$= 2|V_0^+| |\sin(\beta z)|$$

$$|\tilde{V}(z)|^2 = 4|V_0^+|^2 \sin^2(\beta z) = 2|V_0^+|^2 [1 - \cos(2\beta z)]$$

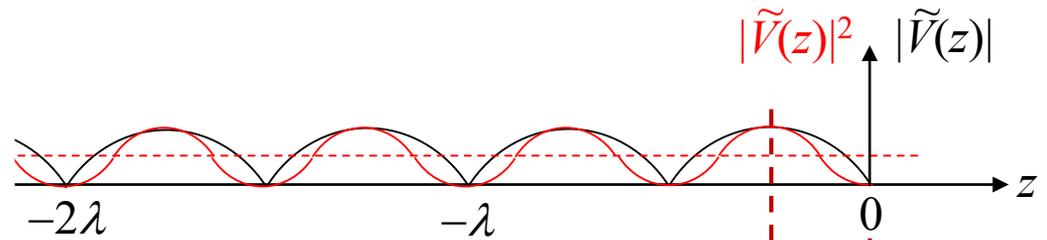


Open

$$|\tilde{V}(z)| = 2|V_0^+| |\cos(\beta z)|$$

$$|\tilde{V}(z)|^2 = 4|V_0^+|^2 \cos^2(\beta z)$$

$$= 2|V_0^+|^2 [1 + \cos(2\beta z)]$$

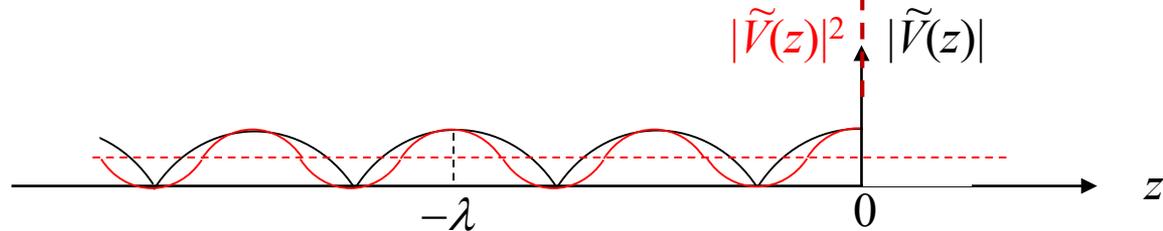

Between short and open: Just a shift of the origin by  $\lambda/4$ .

All cases of  $|\Gamma| = 1$

There are cases where  $|\Gamma| = 1$  but  $\Gamma \neq \pm 1$ .  
Also complete reflection, but neither short nor open.

A quarter wavelength away from a short, the equivalent circuit is an open.  
(See next slide – an old one)

What is the equivalent impedance anywhere in between?

Let's have a closer look at the short circuit.

$$\tilde{V}_{sc}(d) = V_0^+ (e^{j\beta d} - e^{-j\beta d})$$

$$= 2jV_0^+ \sin \beta d$$


$$\tilde{I}_{sc}(d) = \frac{V_0^+}{Z_0} (e^{j\beta d} + e^{-j\beta d}) = \frac{2V_0^+}{Z_0} \cos \beta d$$

$$Z_{sc}(d) = \frac{\tilde{V}_{sc}(d)}{\tilde{I}_{sc}(d)}$$

$$= jZ_0 \tan \beta d$$

Pay attention to signs. We are using  $d$  now.

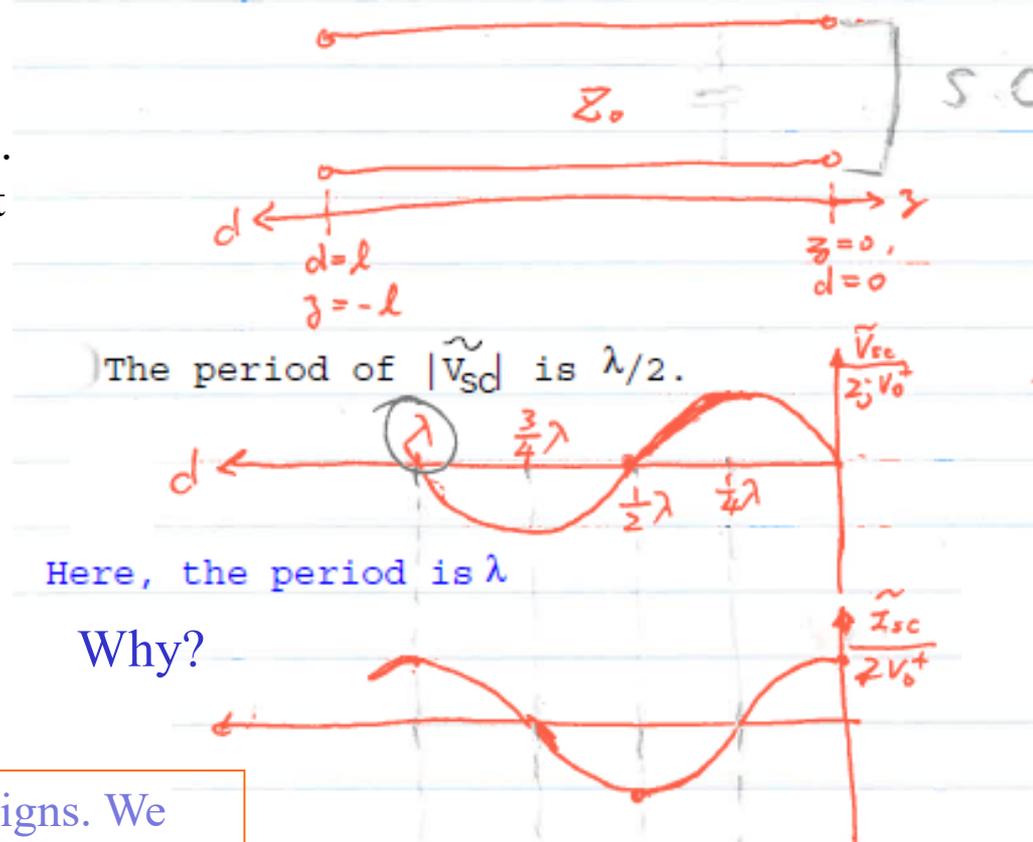Compare these Equations to those in first 4 slides of this ppt.



To visualize  $Z(d)$ , we now plot  $\tilde{V}(d)$  and  $\tilde{I}(d)$ .

Previously, we plotted either  $|\tilde{V}(d)|^2$  and  $|\tilde{I}(d)|^2$  or  $|\tilde{V}(d)|$  and  $|\tilde{I}(d)|$  because they are measurable.

All cases of  $|\Gamma| = 1$

There are cases where  $|\Gamma| = 1$  but  $\Gamma \neq \pm 1$ . Also complete reflection, but neither short nor open.

A quarter wavelength away from a short, the equivalent circuit is an open. (See next slide – an old one)

What is the equivalent impedance anywhere in between?

Let's have a closer look at the short circuit.

$$\tilde{V}_{sc}(d) = V_0^+ (e^{j\beta d} - e^{-j\beta d})$$

$$= 2jV_0^+ \sin \beta d$$


$$\tilde{I}_{sc}(d) = \frac{V_0^+}{Z_0} (e^{j\beta d} + e^{-j\beta d}) = \frac{2V_0^+}{Z_0} \cos \beta d$$

$$Z_{sc}(d) = \frac{\tilde{V}_{sc}(d)}{\tilde{I}_{sc}(d)}$$

$$= jZ_0 \tan \beta d$$

Pay attention to signs. We are using  $d$  now.

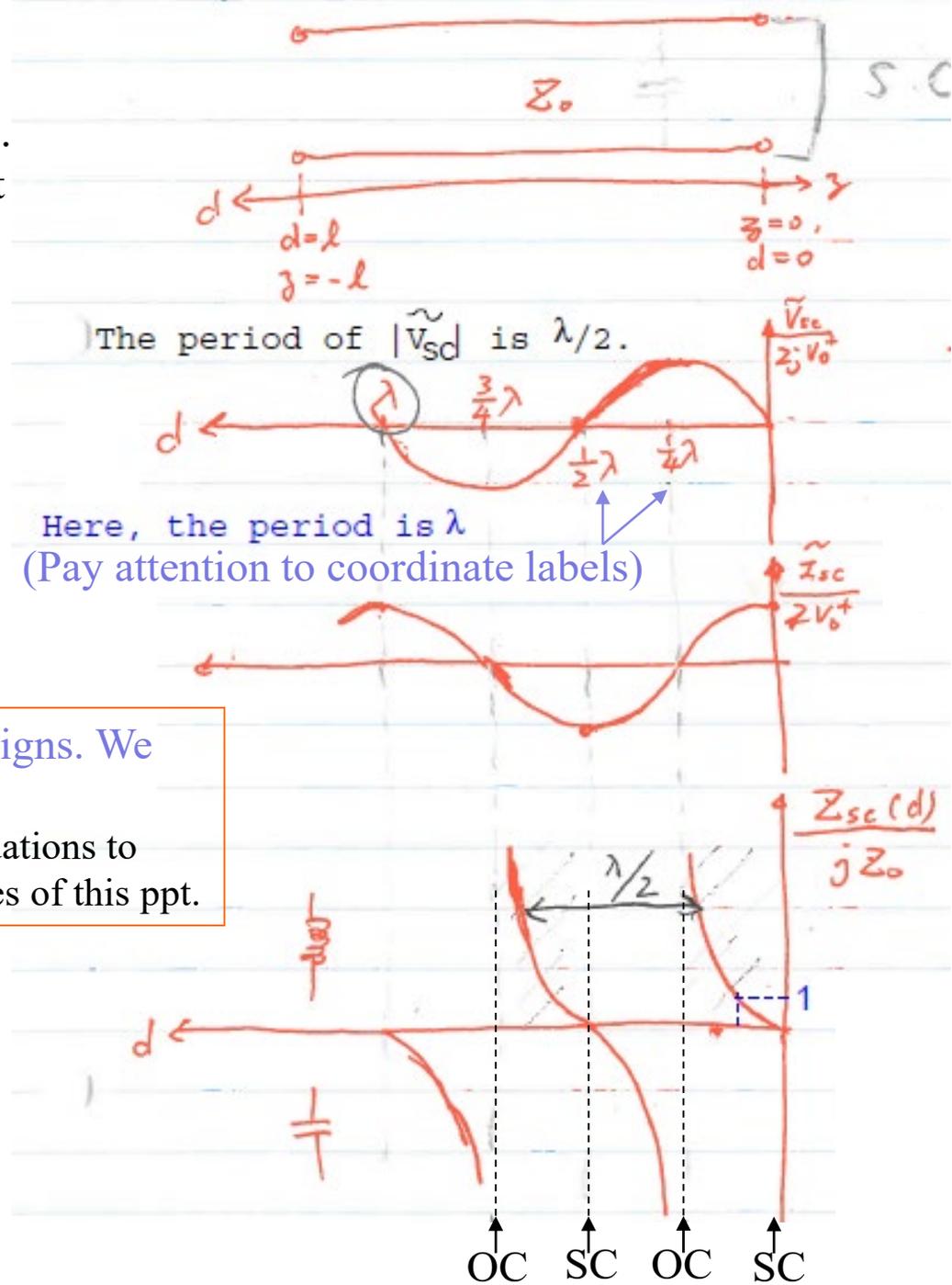Compare these Equations to those in first 4 slides of this ppt.



$$Z_{sc}(d) = \frac{\tilde{V}_{sc}(d)}{\tilde{I}_{sc}(d)}$$

$$= j Z_0 \tan \beta d$$

Understand this from a physics point of view:

Reactive loads don't dissipate power.  
Thus complete reflection.  
The difference is just in the phase.

Equivalent impedance


For  $\tan \beta d > 0$

$$j\omega L_{eq} = j Z_0 \tan \beta d \Rightarrow L_{eq} = \frac{Z_0}{\omega} \tan \beta d$$

For  $\tan \beta d < 0$

$$\frac{1}{j\omega C_{eq}} = j Z_0 \tan \beta d \Rightarrow C_{eq} = -\frac{1}{\omega Z_0 \tan \beta d}$$


Notice frequency dependence.

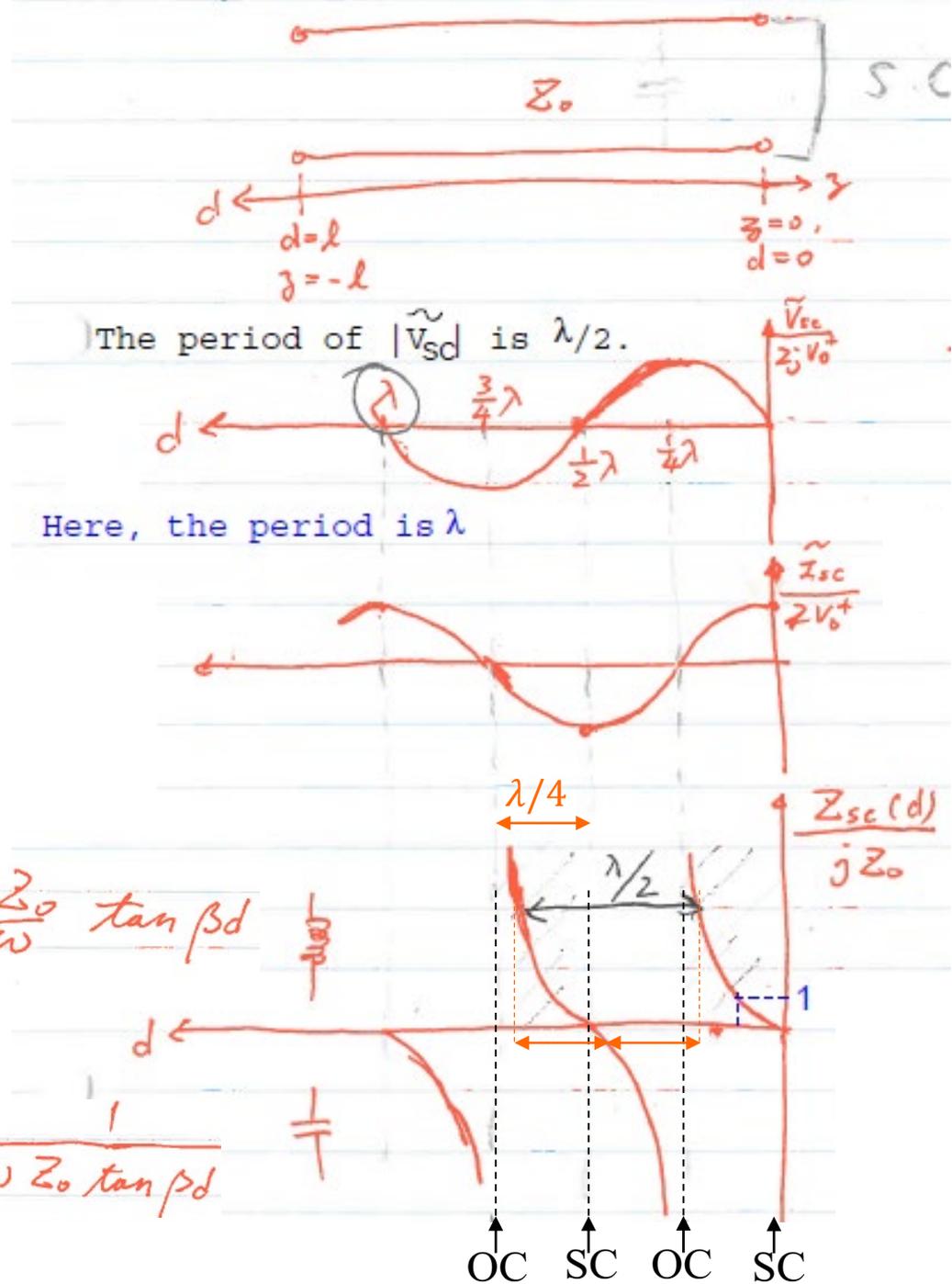
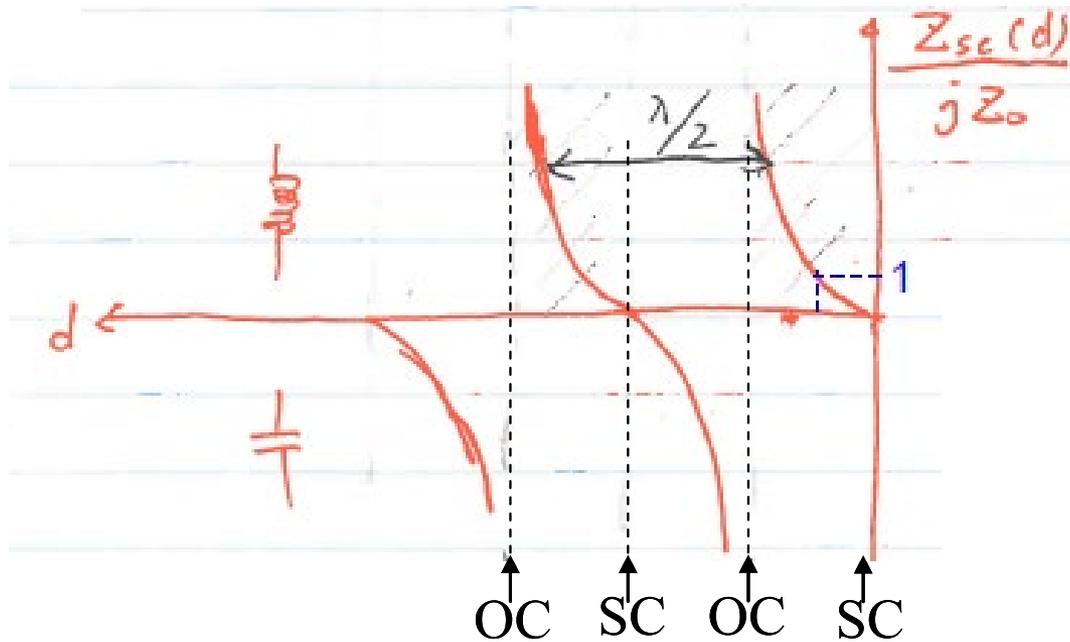
## The case of open circuit termination

Now that we already know the case of short circuit termination, what's the easiest way to work out the open circuit termination case?

Leaving a transmission line open ended does not make an open circuit termination.



With a short circuit, you can make an open circuit.

(For complete solution, see Fig. 2-21 in textbook, pp. 77 in 8/E pp. 81 in 7/E or pp. 82 in 6/E)

Now let's go back to the general case and look at the equivalent input impedance.

$$Z_{in} = Z(d=l) = Z_0 \frac{e^{j\beta l} + \Gamma e^{-j\beta l}}{e^{j\beta l} - \Gamma e^{-j\beta l}}$$


(make sure you understand how this is arrived at)

Insert

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$e^{j\beta l} = \cos \beta l + j \sin \beta l$$
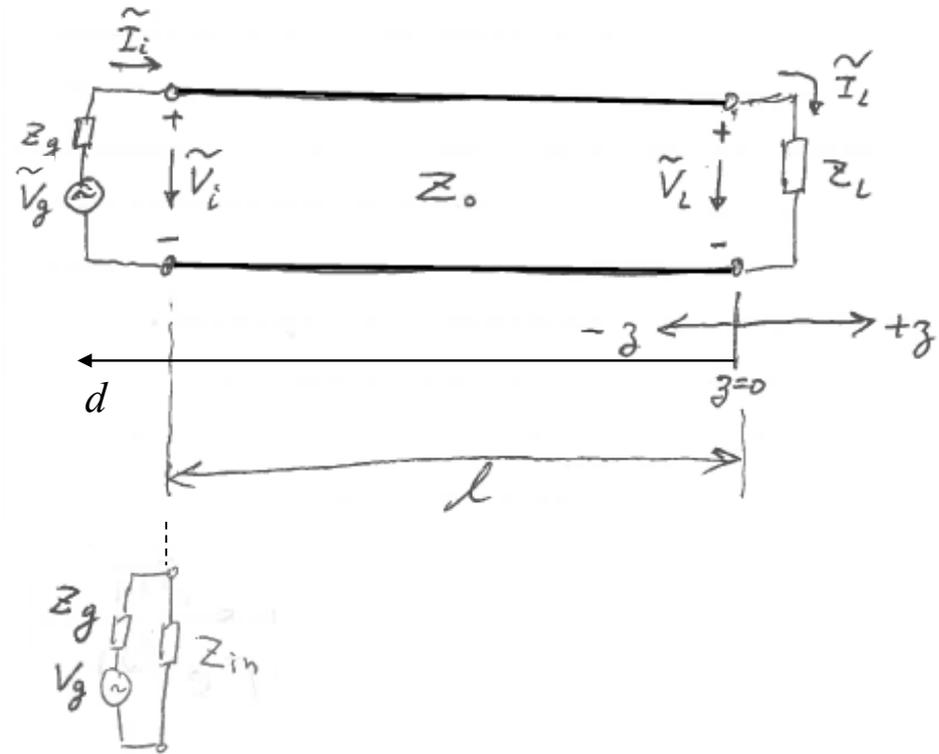
$$e^{-j\beta l} = \cos \beta l - j \sin \beta l$$



and you get

$$Z_{in} = \frac{Z_L \cos \beta l + jZ_0 \sin \beta l}{Z_0 \cos \beta l + jZ_L \sin \beta l} Z_0$$

or in the normalized form:

$$z_{in} = \frac{z_L \cos \beta l + j \sin \beta l}{\cos \beta l + j z_L \sin \beta l}$$

Recall that  $z_L = \frac{Z_L}{Z_0}$

Questions: What is the unit of  $z_L$ ? What is the unit of  $z_{in}$ ?

Do not confuse “input” with “incident”

$\tilde{V}_i$  or  $\tilde{V}_{in}$  is the voltage at the input end. It is the sum of incident and reflected waves **there**.

$$\tilde{V}_{in} = \frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} = V_o^+ (e^{j\beta l} + \Gamma e^{-j\beta l})$$

incident                      reflected

The incident wave voltage at the input end is


$$\tilde{V}_{inc}(l) = V_o^+ e^{j\beta l}$$

At this point read textbook Sections 2-7, 2-8.1, 2-8.2 & 2-8.3.

We changed the sequence of the contents here for easier understanding – Special/extreme cases (short & open) are often easier to understand.

Finish HW2 (P10).

Work on HW3 Problems 1-3.

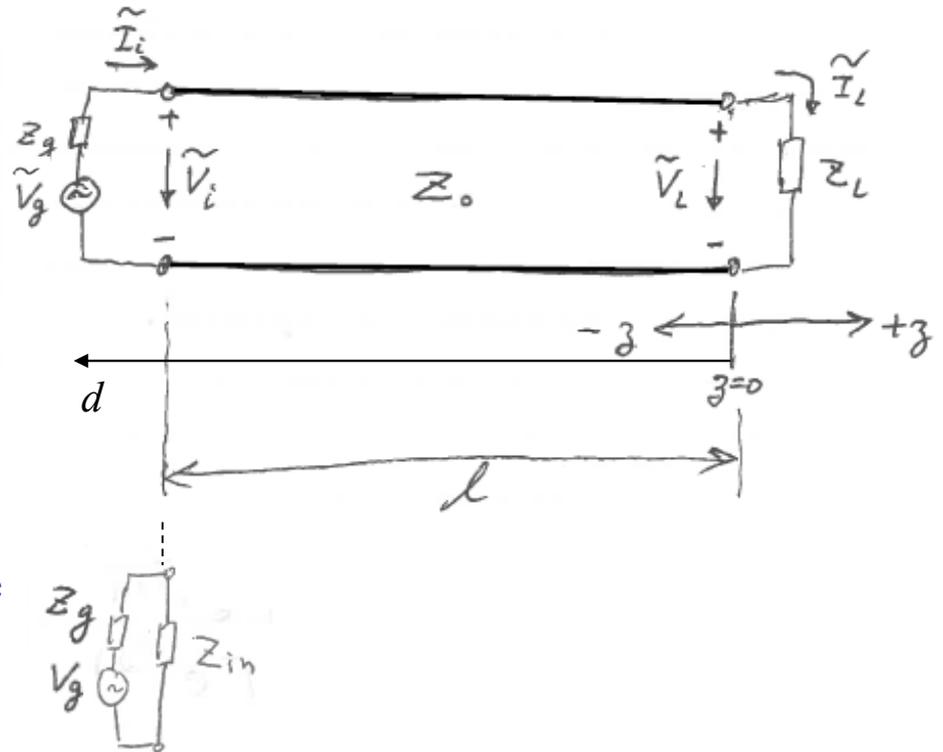

# The quarter wavelength magic

(Textbook Section 2-8.4)

$$Z_{in} = \frac{Z_L \cos \beta l + jZ_0 \sin \beta l}{Z_0 \cos \beta l + jZ_L \sin \beta l} Z_0$$

For  $\beta l = n\pi$ ,

i.e.  $l = n \cdot \frac{\lambda}{2}$

$$Z_{in} = Z_L$$


Periodic. This is for generic  $Z_L$ .

For the special case of purely reactive loads, see slides 38 & 41.

For  $\begin{cases} \cos \beta l = 0 \\ \sin \beta l = \pm 1 \end{cases}$  i.e.  $\beta l = n\pi + \frac{1}{2}\pi$ ,

i.e.  $l = n \cdot \frac{\lambda}{2} + \frac{\lambda}{4}$

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

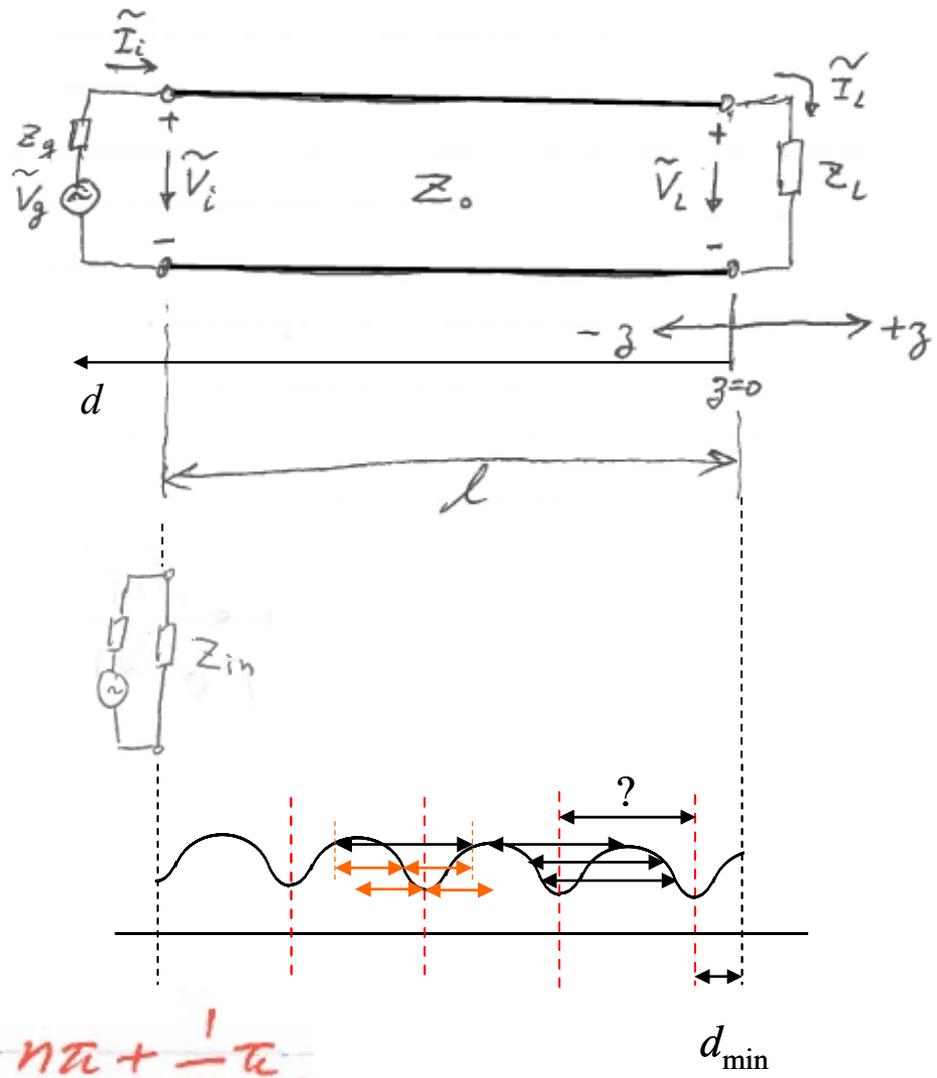

$l$	$\beta l$
$\lambda$	$2\pi$
$\lambda/2$	$\pi$
$\lambda/4$	$\pi/2$

For  $l = n \cdot \frac{\lambda}{2} + \frac{\lambda}{4}$ ,



$$Z_{in} = \frac{Z_0^2}{Z_L}$$

or

$$Z_0 = \sqrt{Z_{in} \cdot Z_L}$$

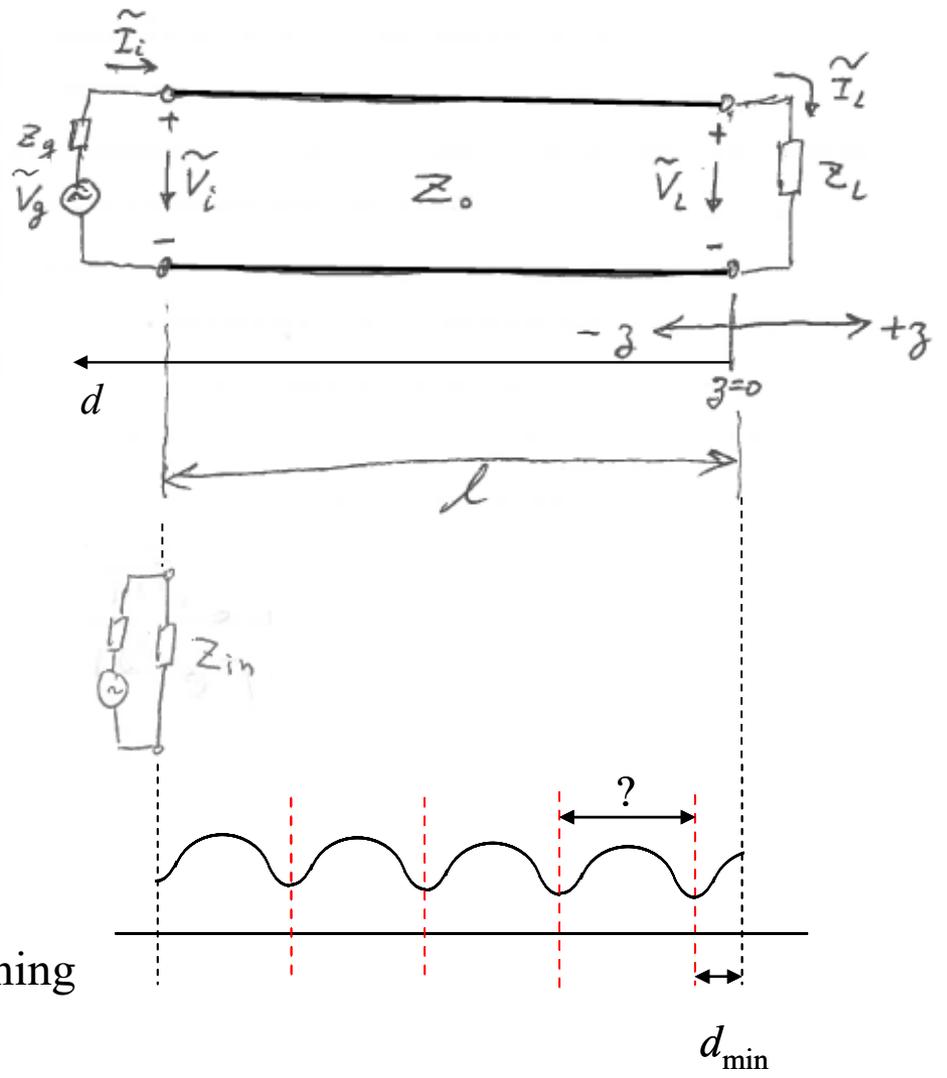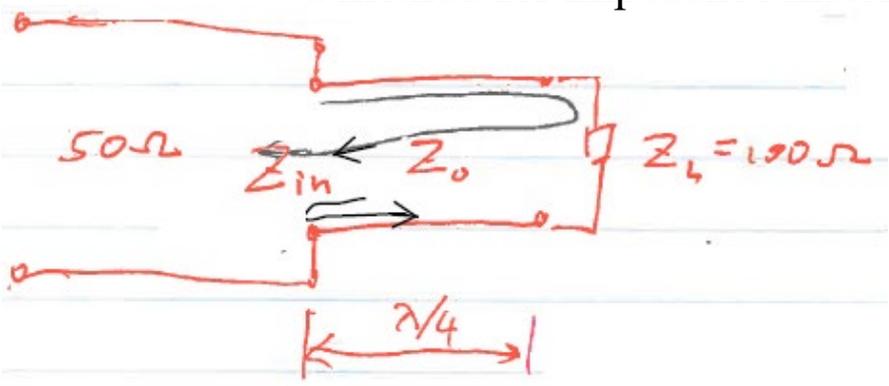Question: What are the equivalent "normalized" forms?

The quarter wavelength transformer  
 -- a method for impedance matching




# The quarter wavelength transformer

$$Z_{in} = \frac{Z_0^2}{Z_L} \quad \text{or} \quad Z_0 = \sqrt{Z_{in} \cdot Z_L}$$

In the “normalized” forms:
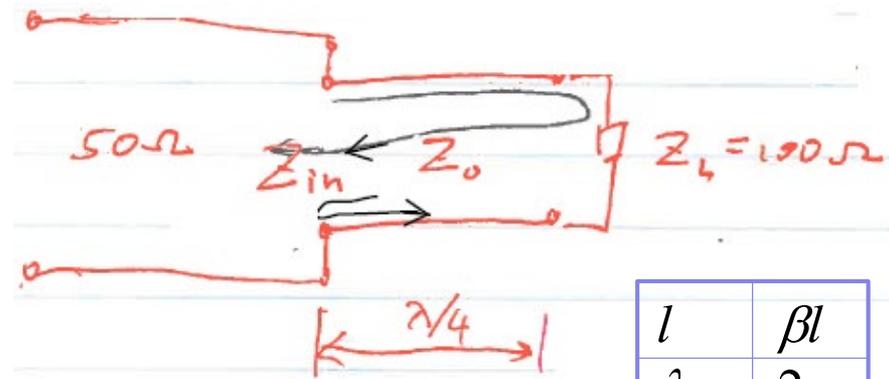
$$z_{in} = \frac{1}{z_L} \quad \text{or} \quad z_{in} z_L = 1$$




$l$	$\beta l$
$\lambda$	$2\pi$
$\lambda/2$	$\pi$
$\lambda/4$	$\pi/2$

To better understand why it works, let's look at its optical analog.
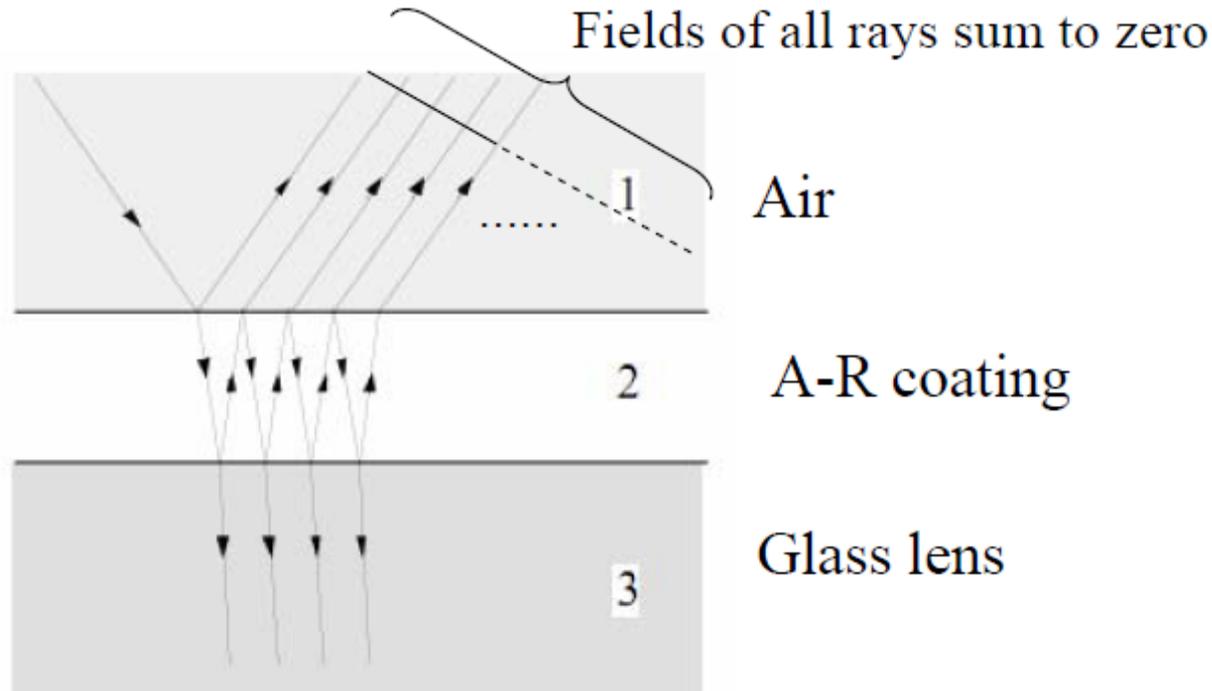
## Anti-reflection coating




WITHOUT ANTI-REFLECTIVE      WITH ANTI-REFLECTIVE



The quarter wavelength magic explained in the multiple reflection point of view

Optical analog: the AR coating

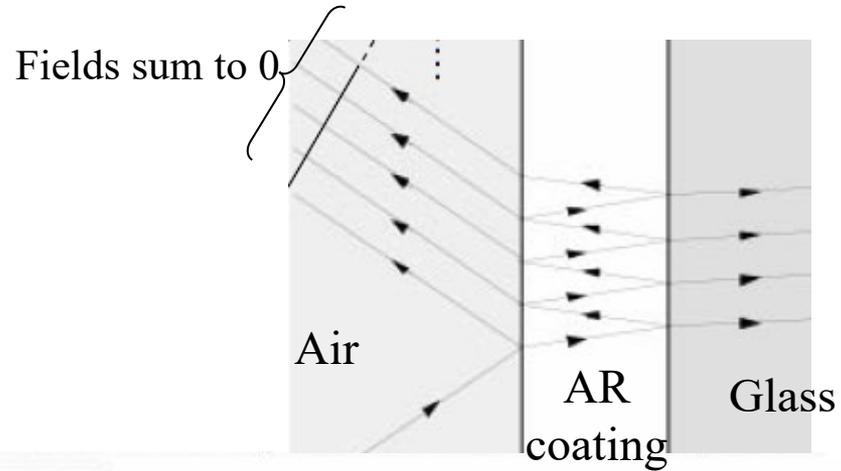


$$\Gamma_1 = \frac{Z_1 - Z_o}{Z_1 + Z_o}$$

$$\Gamma_2 = \frac{Z_0 - Z_1}{Z_0 + Z_1}$$


$$\Gamma_3 = \frac{R_L - Z_1}{R_L + Z_1}$$

$$T_1 = \frac{2Z_1}{Z_1 + Z_o}$$

$$T_2 = \frac{2Z_o}{Z_1 + Z_o}$$

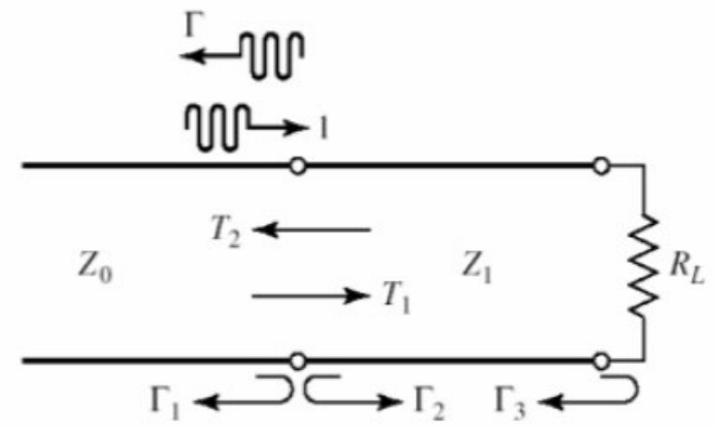

Voltages (or fields) sum to 0

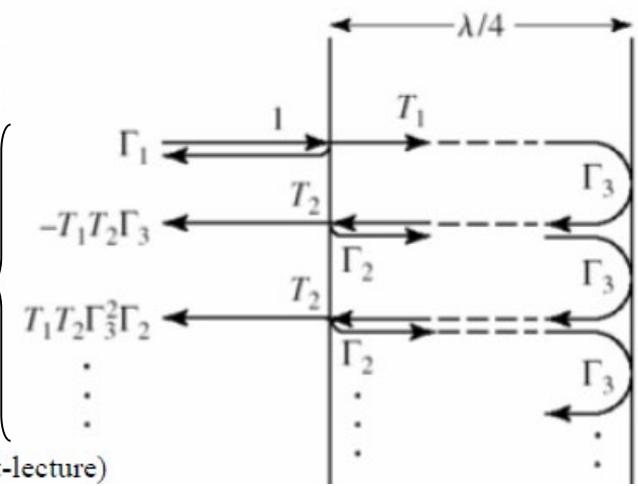

$l$	$\beta l$
$\lambda$	$2\pi$
$\lambda/2$	$\pi$
$\lambda/4$	$\pi/2$

(Adapted from: Naveed Ramzan, <http://www.slideshare.net/nramzan19/smith-chart-lecture>)

## Take-home messages

- Standing waves are simply due to **interference** between incident & reflected waves.
- The variations of real positive amplitudes (of voltage & current) and modulus squares of amplitudes (  $|\tilde{V}(d)|^2$  and  $|\tilde{I}(d)|^2$  ) with position (i.e. distance from load) are **periodic**, analogous to interference stripes in optics and are indeed one-dimensional interference patterns.
- The period of the **(observed) patterns** is **half wavelength**.
- The reflected wave amplitude is a fraction ( $\leq 1$ ) of the incident, and its **phase is shifted** relative to the incident, **right upon reflection**. Thus the reflection coefficient is complex.
- In general, voltage and current of a transmission line are combinations of a traveling wave and a standing wave.
- When the load is **purely reactive** (including short and open), **complete reflection** happens. What's in common is absence of energy dissipation. Thus you can obtain any desired reactance value by terminating a transmission line in any reactive component; you only need to have the right distance from the load. This equivalence is **frequency specific**.
- At any distance  $d$  from the load, you have an **equivalent impedance**  $Z(d)$ , such that you feel as if the transmission line is terminated in  $Z(d)$  right there.
- $Z(\lambda/4)$  and  $Z_L$  [or more generally  $Z(d + \lambda/4)$  and  $Z(d)$ ] have a special relation, which is used as **a method for impedance matching**. This method eliminates reflection because multiple reflections sum up to 0.

Finish reading textbook Section 2-8.

Do Homework 3 through Problem 5.