

CS 160, Fall 2006

Dr Beck

HW #1: Boolean algebra and logic

Due 9/12

1. (10 pts)

a) Write an expression for the function F in sum-of-minterms form

$$F(x,y) = \overline{xy} + \overline{xy}$$

b) Give the truth table for the above function.

2. (20 pts) Prove these expressions equivalent using standard identities given in Table A.4 on page 670 of Hamacher.

a. $xyz + (\overline{xy} + \overline{xyz}) = y$

b. $(x + y)(\overline{x} + \overline{y}) = \overline{xy} + \overline{xy}$

c. $x(\overline{yz} + \overline{zw}) + x = ((\overline{yz} + \overline{zw}) + ((\overline{y} + z)(\overline{z} + w))) x$

d. $\overline{xyz} + xyz + \overline{xz} = x$

e. $\overline{xy} + \overline{yz} + \overline{zx} = \overline{xy} + \overline{zx}$

3. (30 pts) Use a Karnaugh maps to find minimal SOP expressions for the functions described in Problems A.6 - A.9 in Hamacher. For each of A.6 - A.9, show a circuit that is lower cost than the minimal SOP form if one exists.

4. (20 pts) Using a PAL of the type shown in Figure A.42 in Hamacher, show how to implement

a) The function from problem 1.

b) The majority function of three inputs

$F(x,y,z)$ = value taken by the majority of x , y , and z

5. (20 pts) Use a Karnaugh map to derive a boolean expression in minimal SOP form that is equivalent to each truth table. Show the map and rectangles.

a)

x1	x2	x3	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

b)

x1	x2	x3	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1