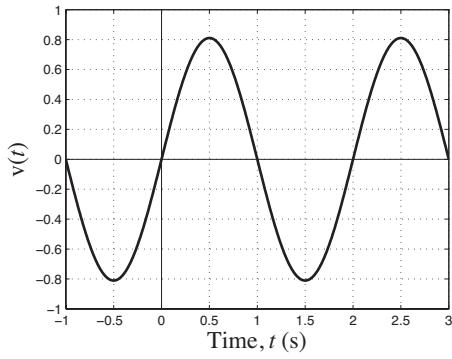



# Chapter 10 Answers to Assigned Homework

(These are my answers but they are not guaranteed to be right. Please report any errors you find.)


2. (a)  $10.12 \cos(50t - 164.6^\circ)$   
(b)  $17.142 \sin(100t + 50^\circ)$
4. (a)  $v_1$  lags  $i_1$  by  $-125^\circ$   
(b)  $v_1$  lags  $i_1$  by  $-205^\circ$  or better  $+155^\circ$   
(c)  $v_1$  lags  $i_1$  by  $-165^\circ$   
(d)  $v_1$  lags  $i_1$  by  $-85^\circ$   
(e)  $v_1$  lags  $i_1$  by  $-234$  or better  $+126^\circ$
5. (a) sin lags cosine by  $90^\circ$   
(b)  $\cos(4t - 80^\circ)$  lags  $\cos(4t)$  by  $80^\circ$   
(c)  $\cos(4t)$  lags  $\cos(4t + 80^\circ)$  by  $80^\circ$   
(d)  $\cos(5t + 2^\circ)$  lags  $-\sin(5t)$  by  $88^\circ$   
(e) Neither is lagging; they are in phase
8. (a)  $v(0.25) = 0.5$   
(b)  $v(0.25) = 0.573$   
(c)  $v(0.25) = 0.4865$   
(d)



(e)

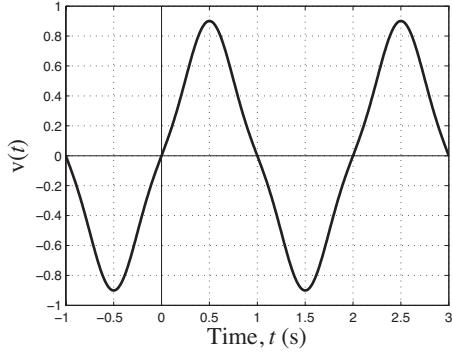

(f)

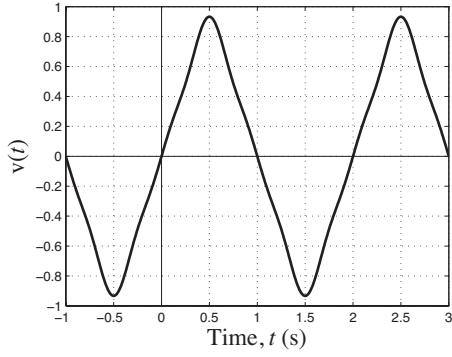

9. (a) Proof

$$110 \text{ V}_{rms} \Rightarrow V_m = 155.56$$

$$(b) \quad 115 \text{ V}_{rms} \Rightarrow V_m = 162.63$$


$$120 \text{ V}_{rms} \Rightarrow V_m = 169.71$$

16. (a)  $50\angle -75^\circ = 12.941 - j48.3$

$$(b) \quad 19e^{j30^\circ} = 16.45 + j9.5 \quad , \quad 2.5\angle -30^\circ + 0.5\angle 45^\circ = 2.519 - j0.896$$

- (c)  $(2 + j2)(2 - j2) = 8\angle 0^\circ$
- (d)  $(2 + j2)(5\angle 22^\circ) = 14.142\angle 1.169 = 14.142\angle 67^\circ$
17. (a)  $2 + e^{j35^\circ} = 2.877\angle 11.5^\circ$
- (b)  $(j)(j)(-j) = j = 1\angle 90^\circ$
- (c)  $1 = 1\angle 0^\circ$
- (d)  $2 + e^{j35^\circ} = 2.8192 + j0.5736$
- (e)  $-j9 + 5\angle 55^\circ = 2.867 - j4.904$
19. (a)  $3(3\angle 30^\circ) = 7.794 + j4.5$
- (b)  $2\angle 25^\circ + 5\angle -10^\circ = 6.737 - j0.023$
- (c)  $(12 + j90) - 5\angle 30^\circ = 7.67 + j87.5$
- (d)  $\frac{10 + j5}{8 - j} + 2\angle 60^\circ + 1 = 3.154 + j2.501$
- (e)  $(10 + j5)(10 - j5)(3\angle 40^\circ) + 2 = 289.27 + j241.05$
21.  $v_C(t) = 0.383e^{-j175.6^\circ}e^{j20t} = 0.383e^{j(20t-175.6^\circ)}$   
 $i_C(t) = 0.9958e^{j(20t-85.6^\circ)}$
24.  $i_L(t) = 1.1288e^{j(35t+108.3^\circ)}$
25. (a)  $75.928\angle 0^\circ$
- (b)  $5\angle -42^\circ$
- (c)  $1\angle 104^\circ$
- (d)  $8.04\angle -78.44^\circ$

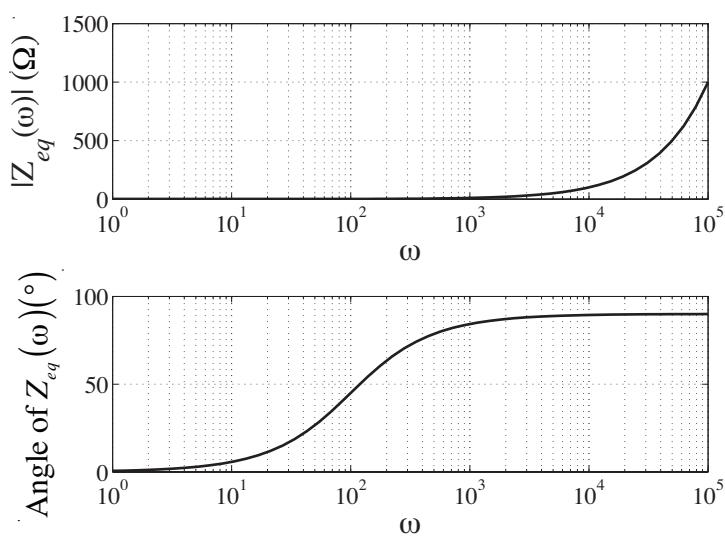
27. (a)  $9\cos(2000\pi t + 65^\circ)$  V  
 (b)  $0.5\cos(2000\pi t + 6^\circ)$  A  
 (c)  $14.669\cos(2000\pi t + 3.7726^\circ)$
34. (a) The element must be an inductor for the voltage to lead the current by  $90^\circ$ .  
 (b) 20 mH
35. (a) A resistor of  $2.5 \Omega$ .  
 (b)  $V_s = 100\angle 35^\circ$ .
36. (a)  $Z_{eq} = 1 + j0.01\omega$   
 (b) and (c)



39. (a)  $31.23\angle -38.66^\circ$  mS  
 (b)  $64\angle -51.34^\circ$  mS  
 (c)  $19.95\angle 89.89^\circ$  S  
 (d)  $1\angle -89.94^\circ$  mS  
 (e)  $999.999\angle 89.94^\circ$  S
40. (a)  $23.25\angle -12.9^\circ$


- (b)  $12.09 \angle -13.82^\circ$
- (c)  $11.145 \angle 1.576^\circ$
43. (a)  $29.99 \angle -0.294^\circ$
- (b)  $25.43 \angle 22.75^\circ$
- (c)  $30 \angle 0.025^\circ$
- (d) 30
- (e) 30
44.  $i(t) = 2.981 \cos(100t - 46.57^\circ)$

47.

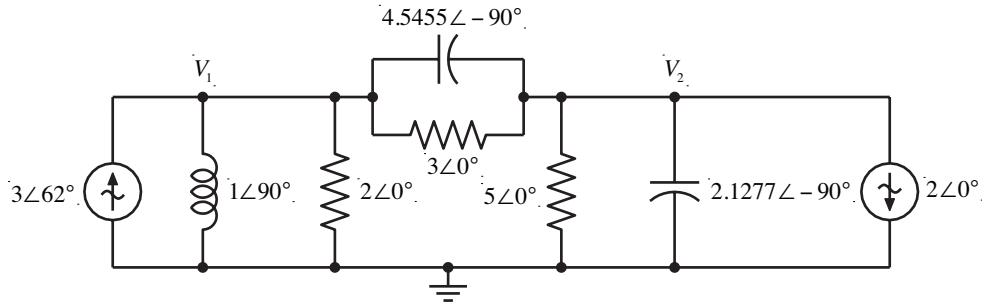

$$v_1(t) = 2.838 \cos(100t + 131.08^\circ) \text{ and } v_2(t) = 3.562 \cos(100t + 122.11^\circ)$$

48.

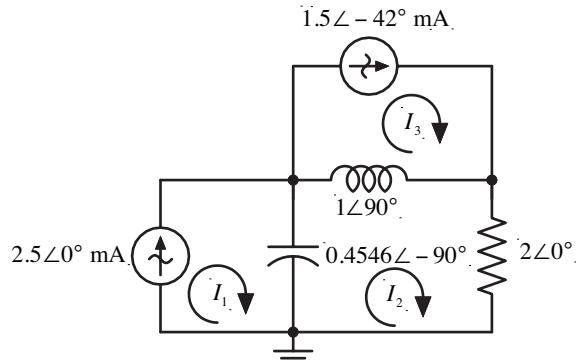

$$i_1(t) = 2.5 \cos(10t) \text{ mA}, \quad i_2(t) = 0.4843 \cos(10t - 16.5^\circ) \text{ mA}, \quad i_3(t) = 1.5 \cos(10t - 42^\circ) \text{ mA}$$

52.

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0.349\angle 11.5^\circ \\ 0.4024\angle 38.07^\circ \end{bmatrix}$$

$$i_1(t) = 0.349 \cos(10t + 11.5^\circ) \text{ and } i_2(t) = 0.4024 \cos(10t + 38.07^\circ)$$

56.  $i_x(t) = 1.1358 \cos(20t + 12.161^\circ)$

59. (a)  $\frac{V_o}{V_s} = -\frac{j\omega A R_f C_1}{A + j\omega R_f C_1 + 1}$

$$\lim_{A \rightarrow \infty} \frac{V_o}{V_s} = -j\omega R_f C_1$$

(b)  $\frac{V_o}{V_s} = -\frac{j\omega A R_f C_1}{A(j\omega R_f C_f + 1) + j\omega R_f C_1 + j\omega R_f C_f + 1}$

$$\lim_{A \rightarrow \infty} \frac{V_o}{V_s} = -\frac{j\omega R_f C_1}{j\omega R_f C_f + 1}$$

64.

$$V_{Th} = 9.619\angle 64.55^\circ$$

$$Z_{Th} = 4.773\angle 34.37^\circ$$

$$I_1 = 0.654\angle -58.57^\circ$$

66. (a)  $V_{Th} = 295.68\angle 112.88^\circ \text{ V}$        $Z_{Th} = 13.44\angle 82.88^\circ \Omega$

(b)  $I_N = 22\angle 30^\circ \text{ A}$

(c)  $I_{ab} = 20.72\angle 60.28^\circ \text{ A}$

73.  $I_L = 57.26\angle -76.76^\circ$

$$I_R = 25.607\angle -140.19^\circ$$

$$I_C = 51.213\angle -50.25^\circ$$

$$V_L = 143.15\angle 13.24^\circ$$

$$V_R = V_C = 51.214\angle -140.19^\circ$$

