

# Chapter 12 Answers to Assigned Homework

1. (a)  $V_{cb} = 8.35 \text{ V}$   
 (b)  $P_{be} = 0.65 \mu\text{W}$
  
3. (a)  $V_{cn} = 400 \angle -87^\circ$   
 (b)  $V_{an} - V_{bn} = 692.82 \angle 3^\circ$   
 (c)  $V_{ax} = 569.2 \angle 72.28^\circ$   
 (d)  $V_{bx} = 724.53 \angle 135.71^\circ$
  
7. (a)  $I_{ab} = -9 \text{ A}$  ,  $I_{cd} = 8 \text{ A}$  ,  $I_{de} = 9 \text{ A}$  ,  $I_{fe} = -10 \text{ A}$  ,  $I_{be} = 1 \text{ A}$   
 (b)  $R_{ab} = 13.89 \Omega$
  
11. (a)  $V_{an} = 110 \angle 0^\circ$  and  $V_{bn} = 110 \angle 180^\circ$   
 (b)  $V_{ab} = 220 \angle 0^\circ$   
 (c)  $I_{aA} = 3.586 \angle 17.76^\circ \text{ Arms}$   
 $P_{V_{an}} = 375.66 \text{ W supplied}$   
 $I_{Bb} = 2.237 \angle 17.76^\circ$   
 $P_{V_{nb}} = 234.34 \text{ W supplied}$   
 (d)  $R = 100$  and  $C = 29.47 \mu\text{F}$
  
13. (a)  $PF = 0.981$ .  
 (b)  $C = 30.607 \mu\text{F}$
  
15. (a) Proof  
 (b) Positive phase sequence
  
17. Phase Voltages:  $V_{an} = 208 \angle 0^\circ$  ,  $V_{bn} = 208 \angle -120^\circ$  ,  $V_{cn} = 208 \angle 120^\circ$   
 Line Voltages:  $V_{ab} = 360.27 \angle 30^\circ$   $V_{bc} = 360.27 \angle -90^\circ$   $V_{ca} = 360.27 \angle 150^\circ$   
 (a)  $I_{aA} = 0.208 \angle 0^\circ$        $I_{bB} = 0.208 \angle -120^\circ$        $I_{cC} = 0.208 \angle 120^\circ$   
 (b)  $I_{aA} = 1.8752 \angle -25.64^\circ$        $I_{bB} = 1.8752 \angle -145.64^\circ$        $I_{cC} = 1.8752 \angle 94.36^\circ$   
 (c)  $I_{aA} = 1.8752 \angle 25.64^\circ$        $I_{bB} = 1.8752 \angle -94.36^\circ$        $I_{cC} = 1.8752 \angle 145.64^\circ$
  
20. The phase voltage magnitude is  $100 / \sqrt{3} = 57.735 \text{ V}$ .  
 (a)  $|I_{aA}| = 6.7924 \text{ A}$        $Z_p = 8.5 \angle 31.8^\circ \Omega$   
 (b)  $|I_{aA}| = 5.648 \text{ A}$        $Z_p = 10.22 \angle -23.07^\circ \Omega$

22. (a) The load power factor is 0.8944 .  
 $|V_{an}| = 106.483 \text{ V}$        $|V_{ab}| = 184.434 \text{ V}$
27. (a)  $I_{AB} = 1256.635 \angle 89.96^\circ \text{ A}$   
 (b)  $I_{nA} = 2176.6 \angle 59.96^\circ \text{ A}$   
 (c)  $V_{AB} = 400 \angle 0^\circ$  .  
 (d)  $PF = 0.0006981$   
 (e)  $P = 1052.8 \text{ W}$
28.  $V_{an} = 400 \angle 0^\circ \text{ V}$ ,  $V_{ab} = 692.82 \angle 30^\circ \text{ V}$ ,  $Z_L = 217.04 \angle 64.273^\circ \Omega$   
 Y-Connection:  $I_{na} = 1.843 \angle -64.273^\circ$ ,  $PF = \cos(-64.273^\circ) = 0.4341$   
 $\Delta$ -Connection:  
 $I_{AB} = 3.1921 \angle -34.273^\circ \text{ A}$   
 $V_{CA} = 692.82 \angle 150^\circ \text{ V}$   
 $I_{AC} = 3.1921 \angle -94.273^\circ \text{ A}$   
 $I_{na} = 5.5289 \angle -64.273^\circ$   
 $PF = 0.4341$
31.  $R_w = 0.665 \Omega$
35.  $V_{an} = 138.564 \angle 0^\circ \text{ Vrms}$   
 $\Delta$ -connected load:  $I_{AB} = 19.93 \angle 25.24^\circ \text{ mA}$        $I_{aA} = 34.52 \angle -4.76^\circ \text{ mA}$   
 Y-connected load:  $I_{aA} = 23.76 \angle -30.96^\circ \text{ mA}$   
 Overall:  $I_{aA} = 55.9 \angle -15.63^\circ$   
 Total power taken by the combined load:  $P = 22.4 \text{ W}$
36. (a) The wattmeter reads the power absorbed by the 10 ohm resistor (without reversing the leads). The wattmeter reading is  $P = 1.539 \text{ kW}$   
 (b) The wattmeter reads the power absorbed by all the passive elements (without reversing the leads).  $P_{\text{total}} = 2.153 \text{ kW}$   
 (c) The wattmeter reads the power absorbed by the parallel combination of the inductor and the 20 ohm resistor (without reversing the leads).  
 $P_{20} = 614 \text{ W}$
39. Wattmeter A:  $P_A = 849.6 \text{ W}$   
 Wattmeter B:  $P_B = 225.15 \text{ W}$   
 Powers absorbed by the impedances:  
 $Z_A$ :  $P_{Z_A} = 500 \text{ W}$      $Z_B$ :  $P_{Z_B} = 200 \text{ W}$      $Z_C$ :  $P_{Z_C} = 375.45 \text{ W}$