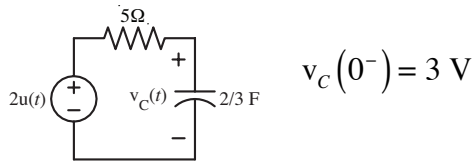


Chapter 15 Solutions to Assigned Homework


4. (a) $v(t) = [4.531e^{-2.454t} - 1.031e^{-t}]u(t)$
 (b) $v(t) = -(1.031e^{-t} + 3.569e^{-2.454t})u(t)$

5. $V_C(s) = \frac{2}{s} + \frac{1}{s+0.3} \Rightarrow v(t) = (2 + e^{-0.3t})u(t)$



7. $Z_{in}(s) = 0.5 \frac{s^2 + 1.2121s + 8}{s + 1.2121}$

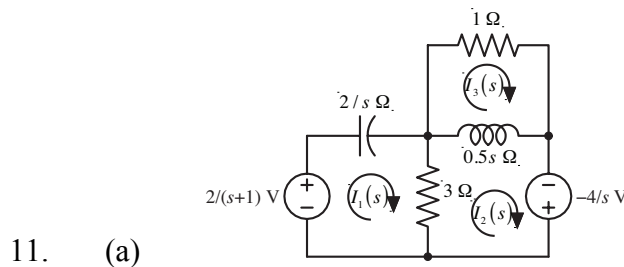8. $Y(s) = 0.667 \frac{s^2 + 3.6453s + 1.7632}{s^2 + 4.736s + 5.5278}$



(b)

$$\begin{bmatrix} \frac{2}{s} + 3 & -3 & 0 \\ -3 & 3 + 0.5s & -0.5s \\ 0 & -0.5s & 1 + 0.5s \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \\ I_3(s) \end{bmatrix} = \begin{bmatrix} \frac{2}{s+1} \\ -\frac{4}{s} \\ 0 \end{bmatrix}$$

(c)

$$i_1(t) = [-0.5714e^{-t} + 3.243e^{-1.333t} \cos(1.4907t + 103.6^\circ)]u(t)$$

$$i_2(t) = [-0.8572e^{-t} - 1.333 + 2.648e^{-1.333t} \cos(1.4907t + 85.875^\circ)]u(t)$$

$$i_3(t) = [0.8571e^{-t} + 3.243e^{-1.333t} \cos(1.4907t + 151.78^\circ)]u(t)$$

$$13. \quad \left(\frac{1}{0.8} + \frac{s}{5} + \frac{s^2}{4} \right) V_x(s) = -\frac{2}{0.8s} + \frac{3s}{4}$$

$$v_x(t) = [-2 + 5e^{-0.4t} \cos(2.2t + 42.27^\circ)] u(t)$$

$$15. \quad p_1(t) = \frac{v_1^2(t)}{1} = [4.667e^{-t} + 5.669e^{-t/4} \cos(1.5612t + 178.38^\circ)]^2 u(t)$$

$$16. \quad p_3(t) = \frac{v_2^2(t)}{3} = \frac{(4.65 - 1.05e^{-t})^2}{3} u(t)$$

$$20. \quad v_2(1\text{ms}) = 0.0001938(e^{-0.02882} - e^{0.21276}) = -51.45 \mu\text{V}$$

$$v_2(100\text{ms}) = 0.0001938(e^{-2.882} - e^{21.276}) = -336.82 \text{ kV}$$

$$v_2(10\text{s}) = 0.0001938(e^{-288.2} - e^{2127.6}) = -0.0001938e^{2127.6} \quad (\text{as a practical matter, negative infinity})$$

$$21. \quad V_{Th} = \frac{6}{17} \frac{s^2}{(s+1)(s+2)(s^2 + (47/34)s + 15/17)}$$

$$Z_{Th} = 12 \frac{s + 35/34}{s^2 + (47/34)s + 15/17}$$

$$25. \quad (a) \quad Z_{Th} = 6.5 \frac{s}{s+1.3}$$

$$(b) \quad i_L(t) = 2.6907(1 - e^{-0.7879t}) u(t)$$

$$27. \quad V_{Th} = 0 \text{ V}, \quad R_{Th} = 5/6 \Omega$$

$$28. \quad v_1(t) = \left[\begin{array}{l} -0.0205e^{-1.0123t} + 0.1491e^{-0.2051t} + 0.2982 \cos(2t - 86.06^\circ) \\ + 0.0283e^{-0.41352t} \cos(0.89t - 96.09^\circ) \end{array} \right] u(t)$$

$$31. \quad (a) \quad \text{Zero at } s = 0, \text{ Pole at } s = -12.5$$

$$(b) \quad \text{Zeros at } s = 0 \text{ and } s = -1, \text{ Poles at } s = -5 \text{ and } s = -3$$

$$(c) \quad \text{Zero at } s = -4 \text{ and } s \rightarrow \infty, \text{ Poles at } s = -1 \text{ and } s = -7$$

$$(d) \quad \text{Zeros at } s = 2 \text{ and } s = -1, \text{ Poles at } s = 0, s = -7 \text{ and } s = -1$$

$$33. \quad (a) \quad \text{Zero at } s = -0.2, \text{ Pole at } s = 0$$

- (b) Zeros at $s = 0$, $s = -1$ and $s = -4$, Poles at $s = -5$ and $s = -3$ and $s = -3$
- (c) No finite zeros, Poles at $s = \pm j2$
- (d) Zeros at $s = \pm 6$, Poles at $s = \pm j$

34. (a) $H(s) = \frac{s}{s+1/RC}$

- (b) Zero at $s = 0$, Pole at $s = -1/RC$

35. (a) $H(s) = \frac{R}{L} \frac{1}{s + R/L} \Rightarrow$ (b) No finite zeros, Pole at $s = -R/L$

(a) $H(s) = \frac{s}{s + R/L} \Rightarrow$ (b) Zero at $s = 0$, Pole at $s = -R/L$

38. (a) $V_{out}(s) = \frac{3}{s^2 + 8s + 7}$

(b) $V_{out}(s) = \frac{25s}{(s^2 + 8s + 7)(s + 2)}$


(c) $V_{out}(s) = \frac{4e^s}{s^2 + 8s + 7}$

(d) $V_{out}(s) = \frac{10s}{(s^2 + 8s + 7)(s^2 + 25)}$

40. Zeros at $s = -2$ and $s = -1/3$, Poles at $s = -3.351$ and $s = -0.149$

41. $x(t) * y(t) = 3(t-1)u(t-1)$


$f(t) * g(t)$

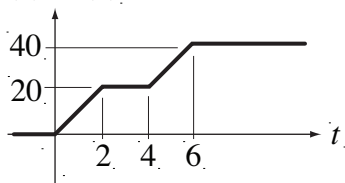


43.

44. $y(t) = \frac{2}{3}(1 - 4e^{-3t})u(t)$


48.

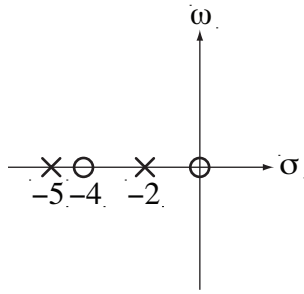


(a)

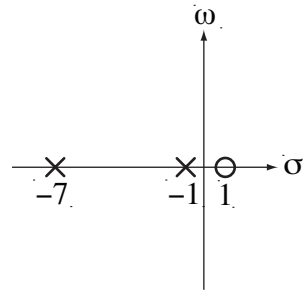

(b)

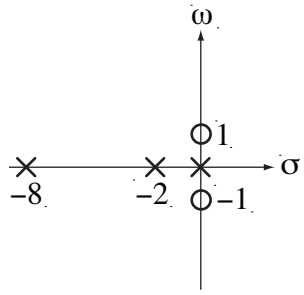

(c)

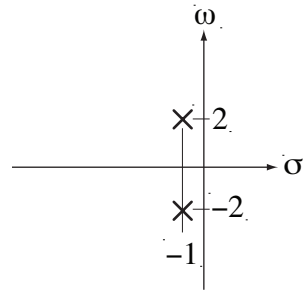


(d)

49. (a) $H(s) = \frac{5}{2} \frac{s+2}{s^2 + 2s + 5}$

(b) $H(s) = -\frac{25}{2} \frac{s+2}{s^2 + 2s + 5}$

(c) Stable.

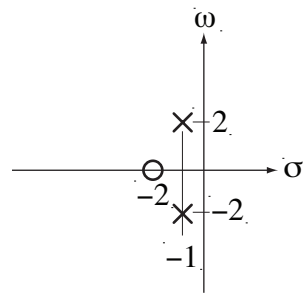


51.

(a)

(b) $H(j\omega) = 100 \frac{j\omega + 2}{-\omega^2 + j2\omega + 5}$


(c) $|H(j\omega)| = 100 \sqrt{\frac{4 + \omega^2}{(5 - \omega^2)^2 + 4\omega^2}}$

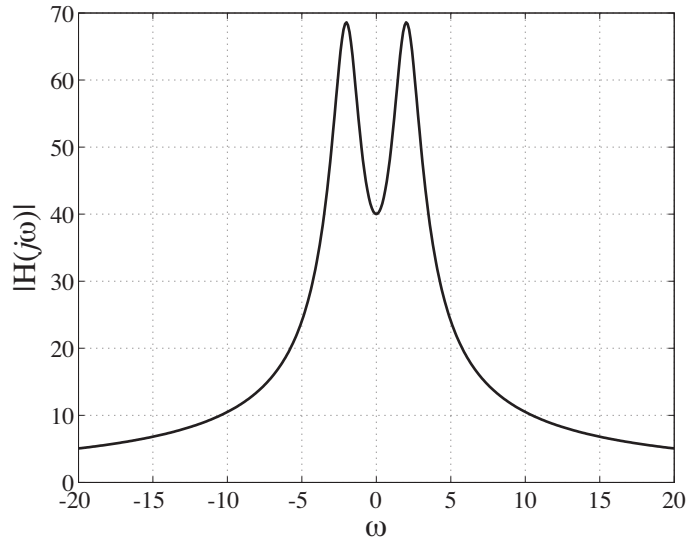

(d)


(e) $\omega_{\max} = 2.0155$.

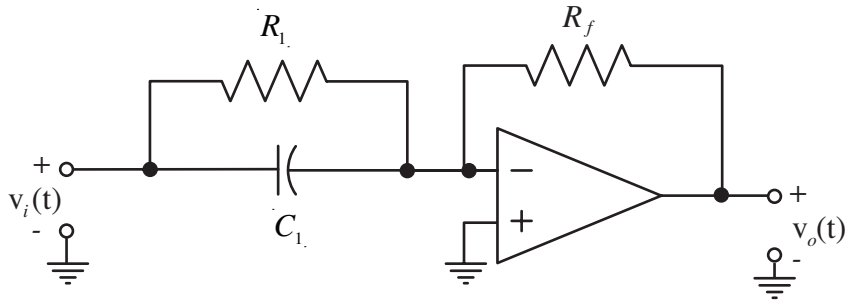54. Pole at $s = -\frac{1}{(R_1 + R_2)C}$



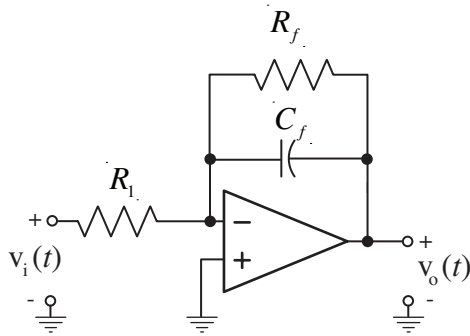
56. (a)

Choose $R_f = 5R_1$ and $R_1C_1 = 1$. (Complete except for the minus sign.)




(b)

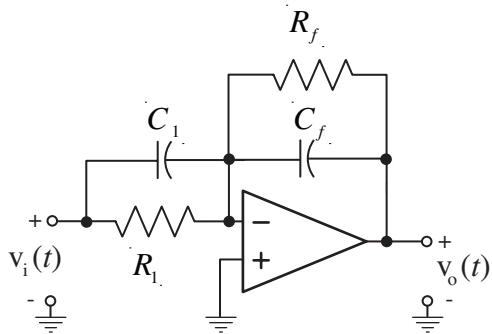Choose $R_f = 5R_1$ and $R_fC_f = 1$. (Complete except for the minus sign.)



(c)

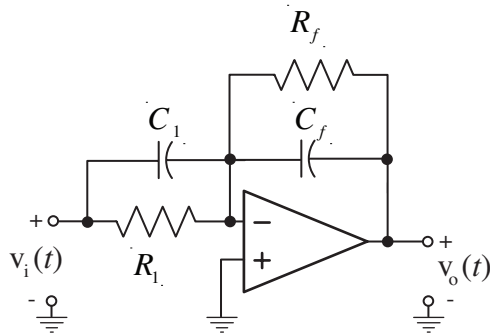Choose $C_1 = 5C_f$ and $R_1C_1 = 1$ and $R_fC_f = 1/2$. (Complete except for the minus sign.)



58.

Let $C_f = 1\text{nF}$. Then $C_1 = 5\text{nF}$, $R_1 = 20\text{ k}\Omega$ and $R_f = 5\text{ k}\Omega$. (Complete except for the minus sign.)

60. (a) $H(s) = -5 \frac{s}{s + 10^5}$
- (b) $H(s) = -0.2 \frac{s + 10^5}{s}$
- (c) $H(s) = -10 \frac{s + 10^4}{s + 10^5}$