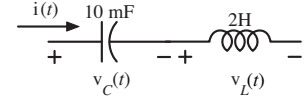


Solution of EECS 300 Test 6 F08

1. A current $i(t) = (3t + 4)$ A is flowing through a 10 mF capacitor and a 2H inductor in series. The voltage $v_c(t)$ across the capacitor at time $t = 0$ is 1200 V. Find the numerical values of the capacitor voltage and the inductor voltage at time $t = 5$ s.



$$v_c(t) = 1200\text{V} + \frac{1}{C} \int_0^t i_c(\tau) d\tau = \left(1200 + 100 \int_0^t (3\tau + 4) d\tau \right) \text{V}$$


$$v_c(t) = \left(1200 + 100 \left[3\tau^2 / 2 + 4\tau \right]_0^t \right) \text{V}$$

$$v_c(t) = \left(1200 + 300t^2 / 2 + 400t \right) \text{V}$$

$$v_c(5) = \left(1200 + 300(25) / 2 + 400(5) \right) \text{V} = 6950\text{V}$$

$$v_L(t) = L \frac{di}{dt} = (2\text{H})(3 \text{ A/s}) = 6\text{V} \Rightarrow v_L(5) = 6\text{V}$$

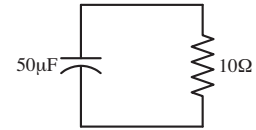
2. In the circuit below, the initial capacitor voltage at time $t = 0$ is 24V. The energy decays toward zero as time passes. How much energy will be dissipated in the resistor over the time range $0 < t < \infty$?




All the initial energy in the capacitor must be dissipated in the resistor. The initial energy stored in the capacitor is

$$E_C = (1/2)CV^2 = (1/2)50\mu\text{F}(24\text{V})^2 = 14.4\text{mJ}$$

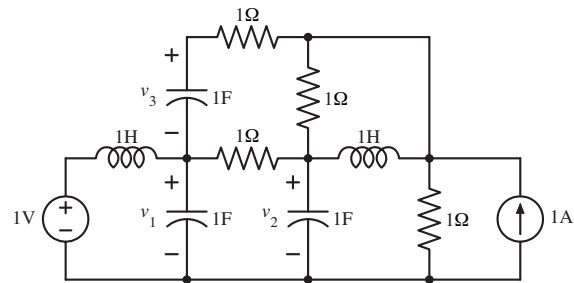3. The voltage source in the circuit below is a constant 1V and the current source is a constant 1A. Find the numerical values of the voltages v_1 , v_2 and v_3 .



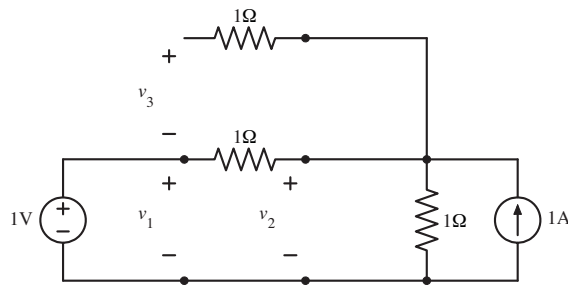We can simplify the circuit for this problem by replacing all capacitors by open circuits and all inductors by short circuits. Also the upper-right hand resistor is shorted out and can be removed without changing any voltages or currents.



Due to the 1V source acting alone:

Current source is open-circuited. Current flows through the middle resistor path and down through the right hand resistor. Half of the 1V source voltage appears across each of the two resistors in that path.

$$v_1 = 1\text{V} \quad , \quad v_2 = 0.5\text{V} \quad \text{and} \quad v_3 = -0.5\text{V}$$


Due to the 1A source acting alone:

Voltage source is short-circuited. The source current splits between the right-hand resistor and the middle resistor, 1/2A going each way. v_1 is zero because it is across a short circuit. v_2 is 0.5V and v_3 is 0.5V.

Including both sources: $v_1 = 1\text{V} \quad , \quad v_2 = 1\text{V} \quad \text{and} \quad v_3 = 0$

Solution of EECS 300 Test 6 F08

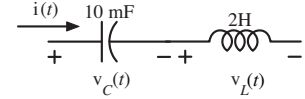1. A current $i(t) = (5t + 2)$ A is flowing through a 10 mF capacitor and a 2H inductor in series. The voltage $v_c(t)$ across the capacitor at time $t = 0$ is 1000 V. Find the numerical values of the capacitor voltage and the inductor voltage at time $t = 5$ s.



$$v_c(t) = 1000\text{V} + \frac{1}{C} \int_0^t i_c(\tau) d\tau = \left(1000 + 100 \int_0^t (5\tau + 2) d\tau \right) \text{V}$$


$$v_c(t) = \left(1000 + 100 \left[5\tau^2 / 2 + 2\tau \right]_0^t \right) \text{V}$$

$$v_c(t) = \left(1000 + 500t^2 / 2 + 200t \right) \text{V}$$

$$v_c(5) = \left(1000 + 500(25) / 2 + 200(5) \right) \text{V} = 8250\text{V}$$

$$v_L(t) = L \frac{di}{dt} = (2\text{H})(5 \text{ A/s}) = 10\text{V} \Rightarrow v_L(5) = 10\text{V}$$

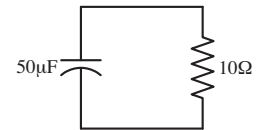
2. In the circuit below, the initial capacitor voltage at time $t = 0$ is 16V. The energy decays toward zero as time passes. How much energy will be dissipated in the resistor over the time range $0 < t < \infty$?




All the initial energy in the capacitor must be dissipated in the resistor. The initial energy stored in the capacitor is

$$E_C = (1/2) C v^2 = (1/2) 50 \mu\text{F} (16\text{V})^2 = 6.4 \text{mJ}$$

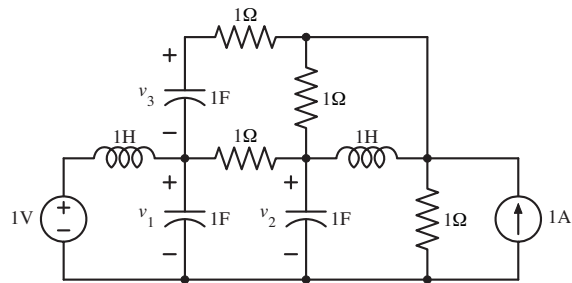3. The voltage source in the circuit below is a constant 1V and the current source is a constant 1A. Find the numerical values of the voltages v_1 , v_2 and v_3 .



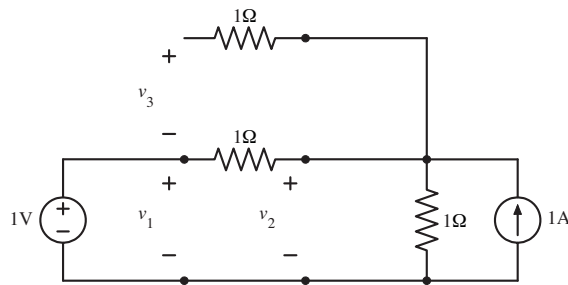We can simplify the circuit for this problem by replacing all capacitors by open circuits and all inductors by short circuits. Also the upper-right hand resistor is shorted out and can be removed without changing any voltages or currents.



Due to the 1V source acting alone:

Current source is open-circuited. Current flows through the middle resistor path and down through the right hand resistor. Half of the 1V source voltage appears across each of the two resistors in that path.

$$v_1 = 1\text{V} \quad , \quad v_2 = 0.5\text{V} \quad \text{and} \quad v_3 = -0.5\text{V}$$

Due to the 1A source acting alone:

Voltage source is short-circuited. The source current splits between the right-hand resistor and the middle resistor, 1/2A going each way. v_1 is zero because it is across a short circuit. v_2 is 0.5V and v_3 is 0.5V.

Including both sources: $v_1 = 1\text{V} \quad , \quad v_2 = 1\text{V} \quad \text{and} \quad v_3 = 0$