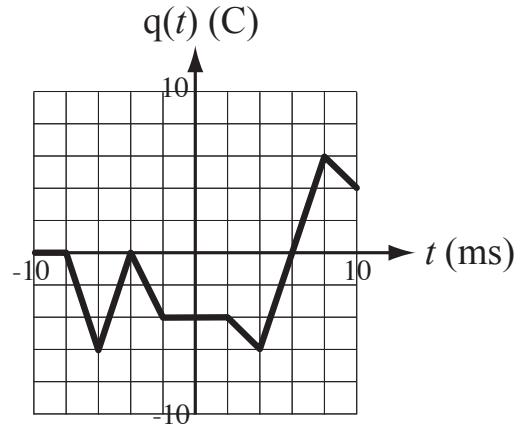


Solution of ECE 300 Test 1 S11

- Below is a graph of the amount of charge $q(t)$ that has passed a point in a circuit versus time. Find the numerical current in amperes at that same point in the circuit at the following times.




$$i(1 \text{ ms}) = 0$$

$$i(6 \text{ ms}) = 12 \text{ C} / 4 \text{ ms} = 3000 \text{ A}$$

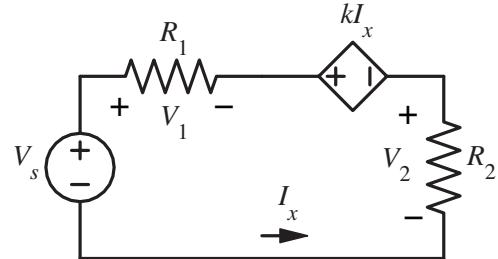2. Find the numerical current I_x , the numerical voltage across and absorbed power in watts for each circuit element.

$$V_s = 33V, R_1 = 14\Omega, R_2 = 9\Omega, k = 12$$




$$\text{KVL: } -V_s + V_1 + kI_x + V_2 = 0 \Rightarrow -V_s - R_1 I_x + kI_x - R_2 I_x = 0 \Rightarrow I_x = \frac{V_s}{k - R_1 - R_2}$$

$$I_x = \frac{33}{12 - 14 - 9} = -3A \Rightarrow V_1 = 42V, V_2 = 27V, kI_x = -36V$$

$$P_{V_s,abs} = V_s I_x = 33 \times (-3) = -99W, P_{R_1,abs} = I_x^2 R_1 = (-3)^2 \times 14 = 126W, P_{R_2,abs} = I_x^2 R_2 = (-3)^2 \times 9 = 81W$$

$$P_{kI_x,abs} = -kI_x \times I_x = -12(-3)^2 = -108W$$

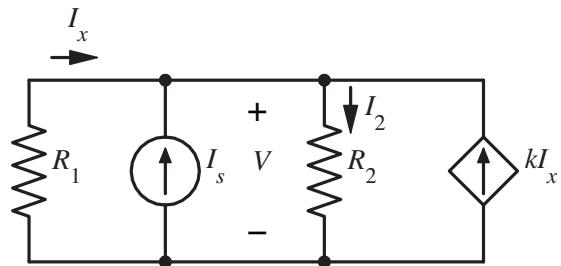3. Find the numerical current through and absorbed power in watts for each circuit element.



$$\text{KCL: } I_x + I_s - I_2 + kI_x = 0 \Rightarrow -\frac{V}{R_1} + I_s - \frac{V}{R_2} + 2\left(-\frac{V}{R_1}\right) = 0 \Rightarrow V = \frac{I_s}{3G_1 + G_2}$$

$$V = \frac{0.05}{3 \times 10^{-4} + 7.6923 \times 10^{-5}} = 132.6531 \Rightarrow I_x = -0.01327 \text{ A}, I_2 = 0.0102 \text{ A}$$


$$P_{I_s,abs} = -VI_s = -132.6531 \times 0.05 = -6.6327 \text{ W} \quad P_{R_1,abs} = I_x^2 R_1 = (-0.01327)^2 \times 10^4 = 1.7609 \text{ W}$$

$$P_{R_2,abs} = I_2^2 R_2 = (0.0102)^2 \times 1.3 \times 10^4 = 1.3525 \text{ W}$$

$$P_{kI_x,abs} = -V k I_x = -132.6531 \times 2 \times (-0.01327) = 3.5206 \text{ W}$$

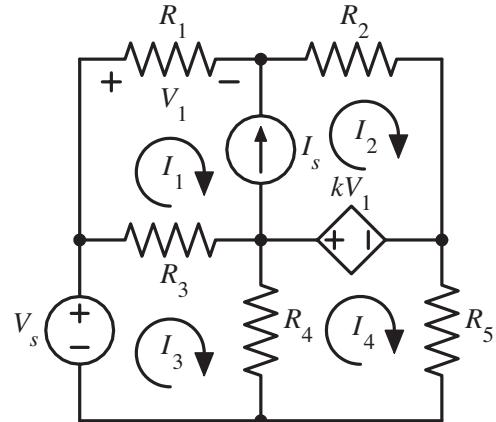4. Fill in the blanks in these mesh-current equations with numbers.

$$V_s = 18V, I_s = 30mA, R_1 = 90\Omega, R_2 = 140\Omega, R_3 = 120\Omega, R_4 = 200\Omega, R_5 = 80\Omega, k = 2$$



$$\begin{bmatrix} R_1 + R_3 & R_2 & -R_3 & 0 \\ -R_3 & 0 & R_3 + R_4 & -R_4 \\ 0 & 0 & -R_4 & R_4 + R_5 \\ -1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} kV_1 \\ V_s \\ -kV_1 \\ I_s \end{bmatrix}$$


$$V_1 = I_1 R_1$$

$$\begin{bmatrix} R_1 + R_3 - kR_1 & R_2 & -R_3 & 0 \\ -R_3 & 0 & R_3 + R_4 & -R_4 \\ kR_1 & 0 & -R_4 & R_4 + R_5 \\ -1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 0 \\ V_s \\ 0 \\ I_s \end{bmatrix}$$

$$\begin{bmatrix} 30 & 140 & -120 & 0 \\ -120 & 0 & 320 & -200 \\ 180 & 0 & -200 & 280 \\ -1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 18 \\ 0 \\ 0.03 \end{bmatrix}$$

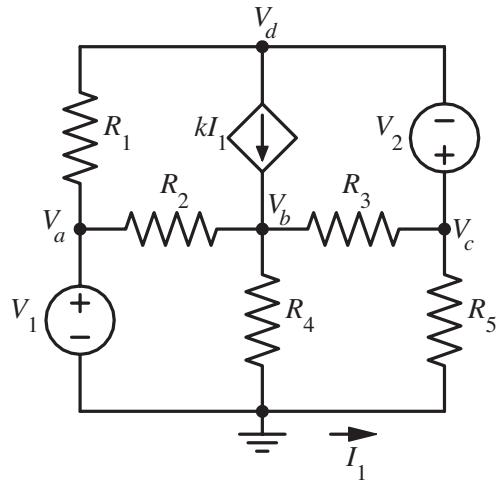5. Fill in the blanks in the node-voltage equations with numbers.

$$V_1 = 8V, V_2 = 13V, R_1 = 9\Omega, R_2 = 16\Omega, R_3 = 11\Omega, R_4 = 5\Omega, R_5 = 20\Omega, k = -1.5$$



$$\begin{bmatrix} -G_2 & G_2 + G_3 + G_4 & -G_3 & 0 \\ -G_1 & -G_3 & G_3 + G_5 & G_1 \\ 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \\ V_d \end{bmatrix} = \begin{bmatrix} kI_1 \\ -kI_1 \\ V_1 \\ V_2 \end{bmatrix}$$


$$I_1 = -V_c G_5$$

$$G_1 = 0.1111, G_2 = 0.0625, G_3 = 0.0909, G_4 = 0.2, G_5 = 0.05$$

$$\begin{bmatrix} -0.0625 & 0.3534 & -0.1659 & 0 \\ -0.1111 & -0.0909 & 0.2159 & 0.1111 \\ 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \\ V_d \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 8 \\ 13 \end{bmatrix}$$

Solution of ECE 300 Test 1 S11

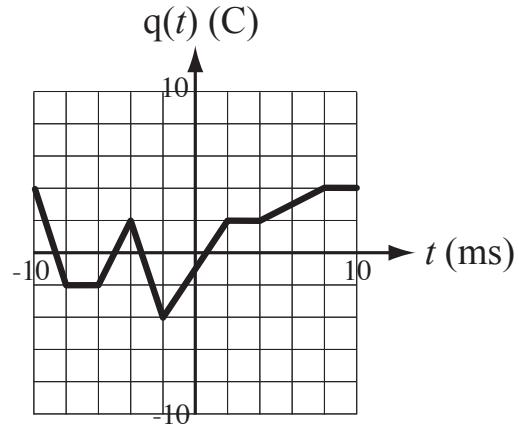- Below is a graph of the amount of charge $q(t)$ that has passed a point in a circuit versus time. Find the numerical current in amperes at that same point in the circuit at the following times.




$$i(-3 \text{ ms}) = -6 \text{ C} / 2 \text{ ms} = -3000 \text{ A}$$

$$i(3 \text{ ms}) = 0$$

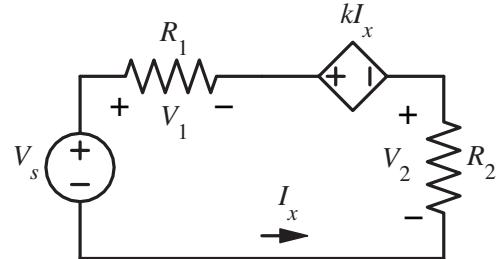2. Find the numerical current I_x , the numerical voltage across and absorbed power in watts for each circuit element.

$$V_s = 22\text{V} , R_1 = 14\Omega , R_2 = 9\Omega , k = 12$$



$$\text{KVL: } -V_s + V_1 + kI_x + V_2 = 0 \Rightarrow -V_s - R_1 I_x + kI_x - R_2 I_x = 0 \Rightarrow I_x = \frac{V_s}{k - R_1 - R_2}$$


$$I_x = \frac{22}{12 - 14 - 9} = -2\text{A} \Rightarrow V_1 = 28\text{V} , V_2 = 18\text{V} , kI_x = -24\text{V}$$

$$P_{V_s,abs} = V_s I_x = 22 \times (-2) = -44\text{W} , P_{R_1,abs} = I_x^2 R_1 = (-2)^2 \times 14 = 56\text{W} , P_{R_2,abs} = I_x^2 R_2 = (-2)^2 \times 9 = 36\text{W}$$

$$P_{kI_x,abs} = -kI_x \times I_x = -12(-2)^2 = -48\text{W}$$

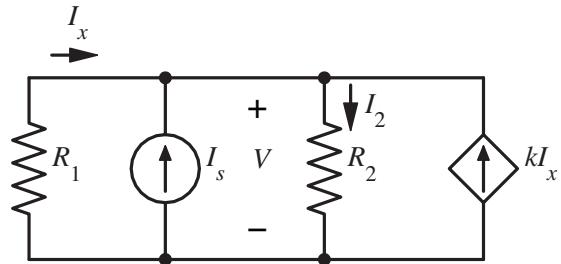3. Find the numerical current through and absorbed power in watts for each circuit element.

$$I_s = 25\text{mA} , R_1 = 10k\Omega , R_2 = 13k\Omega , k = 2$$



$$\text{KCL: } I_x + I_s - I_2 + kI_x = 0 \Rightarrow -\frac{V}{R_1} + I_s - \frac{V}{R_2} + 2\left(-\frac{V}{R_1}\right) = 0 \Rightarrow V = \frac{I_s}{3G_1 + G_2}$$

$$V = \frac{0.025}{3 \times 10^{-4} + 7.6923 \times 10^{-5}} = 66.3265 \Rightarrow I_x = -0.0066\text{A} , I_2 = 0.0051\text{A}$$


$$P_{I_s,abs} = -VI_s = -66.3265 \times 0.025 = -1.6582\text{W} \quad P_{R_1,abs} = I_x^2 R_1 = (-0.0066)^2 \times 10^4 = 0.4402\text{W}$$

$$P_{R_2,abs} = I_2^2 R_2 = (0.0051)^2 \times 1.3 \times 10^4 = 0.3381\text{W}$$

$$P_{kI_x,abs} = -V k I_x = -66.3265 \times 2 \times (-0.0066) = 0.8801\text{W}$$

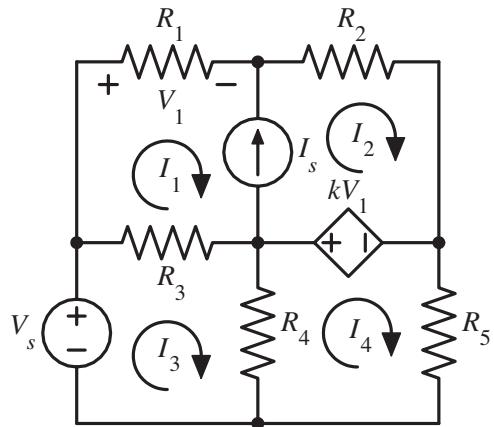4. Fill in the blanks in these mesh-current equations with numbers.

$$V_s = 15V, I_s = 50mA, R_1 = 110\Omega, R_2 = 100\Omega \\ R_3 = 130\Omega, R_4 = 220\Omega, R_5 = 70\Omega, k = 3$$



$$\begin{bmatrix} R_1 + R_3 & R_2 & -R_3 & 0 \\ -R_3 & 0 & R_3 + R_4 & -R_4 \\ 0 & 0 & -R_4 & R_4 + R_5 \\ -1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} kV_1 \\ V_s \\ -kV_1 \\ I_s \end{bmatrix}$$


$$V_1 = I_1 R_1$$

$$\begin{bmatrix} R_1 + R_3 - kR_1 & R_2 & -R_3 & 0 \\ -R_3 & 0 & R_3 + R_4 & -R_4 \\ kR_1 & 0 & -R_4 & R_4 + R_5 \\ -1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 0 \\ V_s \\ 0 \\ I_s \end{bmatrix}$$

$$\begin{bmatrix} -90 & 100 & -130 & 0 \\ -130 & 0 & 350 & -220 \\ 330 & 0 & -220 & 290 \\ -1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 15 \\ 0 \\ 0.05 \end{bmatrix}$$

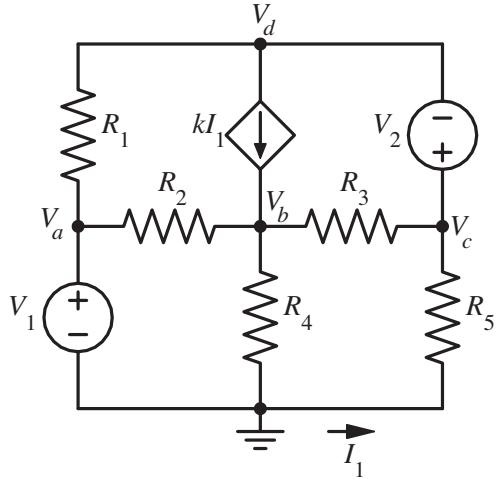5. Fill in the blanks in the node-voltage equations with numbers.

$$V_1 = 12V, V_2 = 18V, R_1 = 7\Omega, R_2 = 13\Omega, R_3 = 9\Omega, R_4 = 11\Omega, R_5 = 15\Omega, k = -2.5$$



$$\begin{bmatrix} -G_2 & G_2 + G_3 + G_4 & -G_3 & 0 \\ -G_1 & -G_3 & G_3 + G_5 & G_1 \\ 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \\ V_d \end{bmatrix} = \begin{bmatrix} kI_1 \\ -kI_1 \\ V_1 \\ V_2 \end{bmatrix}$$

$$I_1 = -V_c G_5$$


$$\begin{bmatrix} -G_2 & G_2 + G_3 + G_4 & -G_3 - 2.5G_5 & 0 \\ -G_1 & -G_3 & G_3 + G_5 + 2.5G_5 & G_1 \\ 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \\ V_d \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ V_1 \\ V_2 \end{bmatrix}$$

$$G_1 = 0.1429, G_2 = 0.0769, G_3 = 0.1111, G_4 = 0.0909, G_5 = 0.0667$$

$$\begin{bmatrix} -0.0769 & 0.2789 & -0.2778 & 0 \\ -0.1429 & -0.1111 & 0.3444 & 0.1429 \\ 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \\ V_d \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 12 \\ 18 \end{bmatrix}$$

Solution of ECE 300 Test 1 S11

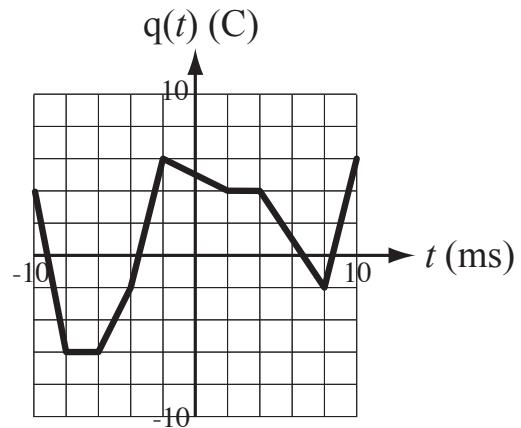- Below is a graph of the amount of charge $q(t)$ that has passed a point in a circuit versus time. Find the numerical current in amperes at that same point in the circuit at the following times.




$$i(-3 \text{ ms}) = 8 \text{ C} / 2 \text{ ms} = 4000 \text{ A}$$

$$i(3 \text{ ms}) = 0$$

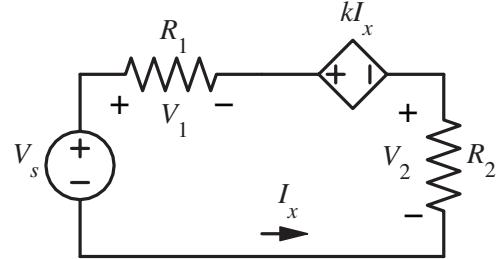2. Find the numerical current I_x , the numerical voltage across and absorbed power in watts for each circuit element.

$$V_s = 11\text{V} , R_1 = 14\Omega , R_2 = 9\Omega , k = 12$$



$$\text{KVL: } -V_s + V_1 + kI_x + V_2 = 0 \Rightarrow -V_s - R_1 I_x + kI_x - R_2 I_x = 0 \Rightarrow I_x = \frac{V_s}{k - R_1 - R_2}$$


$$I_x = \frac{11}{12 - 14 - 9} = -1\text{A} \Rightarrow V_1 = 14\text{V} , V_2 = 9\text{V} , kI_x = -12\text{V}$$

$$P_{V_s,abs} = V_s I_x = 11 \times (-1) = -11\text{W} , P_{R_1,abs} = I_x^2 R_1 = (-1)^2 \times 14 = 14\text{W} , P_{R_2,abs} = I_x^2 R_2 = (-1)^2 \times 9 = 9\text{W}$$

$$P_{kI_x,abs} = -kI_x \times I_x = -12(-1)^2 = -12\text{W}$$

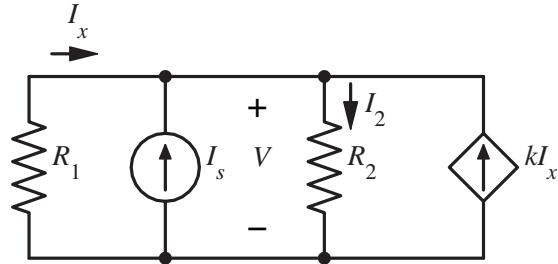3. Find the numerical current through and absorbed power in watts for each circuit element.

$$I_s = 100\text{mA} , R_1 = 10k\Omega , R_2 = 13k\Omega , k = 2$$



$$\text{KCL: } I_x + I_s - I_2 + kI_x = 0 \Rightarrow -\frac{V}{R_1} + I_s - \frac{V}{R_2} + 2\left(-\frac{V}{R_1}\right) = 0 \Rightarrow V = \frac{I_s}{3G_1 + G_2}$$

$$V = \frac{0.1}{3 \times 10^{-4} + 7.6923 \times 10^{-5}} = 265.3062 \Rightarrow I_x = -0.0265\text{A} , I_2 = 0.0204\text{A}$$


$$P_{I_s,abs} = -VI_s = -265.3062 \times 0.1 = -26.5306\text{W} \quad P_{R_1,abs} = I_x^2 R_1 = (-0.0265)^2 \times 10^4 = 7.0436\text{W}$$

$$P_{R_2,abs} = I_2^2 R_2 = (0.0204)^2 \times 1.3 \times 10^4 = 5.41\text{W}$$

$$P_{kI_x,abs} = -VkI_x = -265.3062 \times 2 \times (-0.0265) = 14.0824\text{W}$$

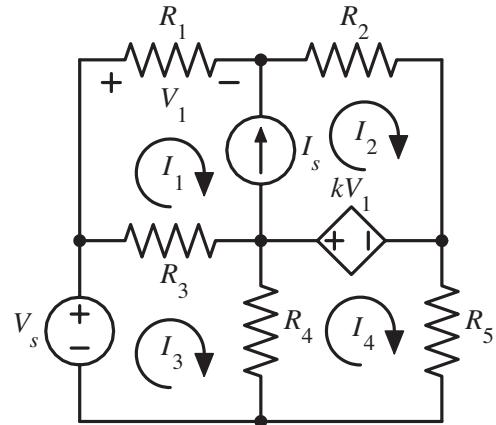4. Fill in the blanks in these mesh-current equations with numbers.

$$V_s = 9\text{V} , I_s = 80\text{mA} , R_1 = 50\Omega , R_2 = 110\Omega \\ R_3 = 170\Omega , R_4 = 140\Omega , R_5 = 60\Omega , k = 1.5$$



$$\begin{bmatrix} R_1 + R_3 & R_2 & -R_3 & 0 \\ -R_3 & 0 & R_3 + R_4 & -R_4 \\ 0 & 0 & -R_4 & R_4 + R_5 \\ -1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} kV_1 \\ V_s \\ -kV_1 \\ I_s \end{bmatrix}$$


$$V_1 = I_1 R_1$$

$$\begin{bmatrix} R_1 + R_3 - kR_1 & R_2 & -R_3 & 0 \\ -R_3 & 0 & R_3 + R_4 & -R_4 \\ kR_1 & 0 & -R_4 & R_4 + R_5 \\ -1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 0 \\ V_s \\ 0 \\ I_s \end{bmatrix}$$

$$\begin{bmatrix} 145 & 110 & -170 & 0 \\ -170 & 0 & 310 & -140 \\ 75 & 0 & -140 & 200 \\ -1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 9 \\ 0 \\ 0.08 \end{bmatrix}$$

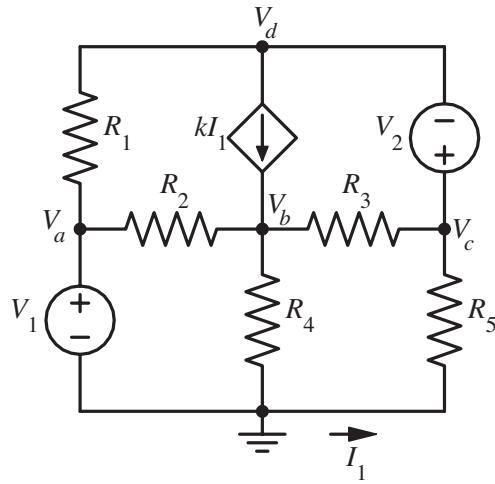5. Fill in the blanks in the node-voltage equations with numbers.

$$V_1 = 6V, V_2 = 4V, R_1 = 15\Omega, R_2 = 8\Omega, R_3 = 7\Omega, R_4 = 16\Omega, R_5 = 18\Omega, k = -0.5$$



$$\begin{bmatrix} -G_2 & G_2 + G_3 + G_4 & -G_3 & 0 \\ -G_1 & -G_3 & G_3 + G_5 & G_1 \\ 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \\ V_d \end{bmatrix} = \begin{bmatrix} kI_1 \\ -kI_1 \\ V_1 \\ V_2 \end{bmatrix}$$

$$I_1 = -V_c G_5$$

$$\begin{bmatrix} -G_2 & G_2 + G_3 + G_4 & -G_3 - 0.5G_5 & 0 \\ -G_1 & -G_3 & G_3 + G_5 + 0.5G_5 & G_1 \\ 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \\ V_d \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ V_1 \\ V_2 \end{bmatrix}$$

$$G_1 = 0.0667, G_2 = 0.125, G_3 = 0.1429, G_4 = 0.0625, G_5 = 0.0556$$

$$\begin{bmatrix} -0.125 & 0.3304 & -0.1706 & 0 \\ -0.0667 & -0.1429 & 0.2262 & 0.0667 \\ 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \\ V_d \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 6 \\ 4 \end{bmatrix}$$