


Solution of ECE 300 Test 2 S11

1. Find the numerical value of I_x with

(a) V_s acting alone $I_x = V_s / (R_1 + R_2) = \frac{14\text{V}}{12\Omega + 23\Omega} = 0.4\text{A}$


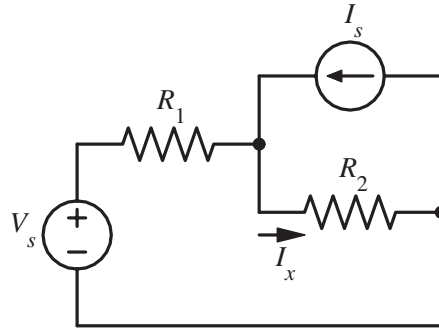
(b) I_s acting alone $I_x = \frac{R_1}{R_1 + R_2} I_s = \frac{12\Omega}{12\Omega + 23\Omega} 2.5\text{A} = 0.8571\text{A}$

$$V_s = 14\text{V} , I_s = 2.5\text{A} , R_1 = 12\Omega , R_2 = 23\Omega$$



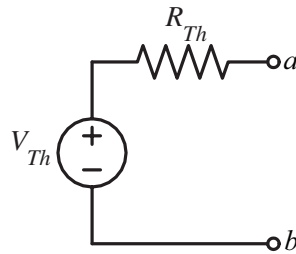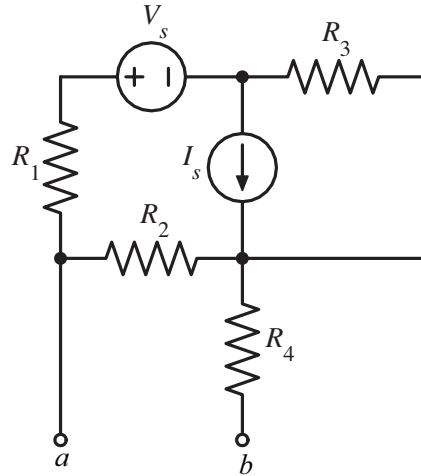2. The Thevenin equivalent of the first circuit at terminals a and b is the second circuit shown below. Find the numerical values of V_{Th} and R_{Th} .


$$V_s = 15\text{V} , I_s = 2\text{A} , R_1 = 8\Omega , R_2 = 3\Omega , R_3 = 10\Omega , R_4 = 12\Omega$$



$$V_{Th} = V_s \frac{R_2}{R_1 + R_2 + R_3} - I_s \frac{R_3}{R_1 + R_2 + R_3} R_2 = 15 \frac{3}{8 + 3 + 10} - 2 \frac{10}{8 + 3 + 10} 3 = \frac{45}{21} - \frac{60}{21} = -\frac{15}{21} = -0.7143 \text{ V}$$


$$R_{Th} = R_4 + (R_1 + R_3) \parallel R_2 = 12 + \frac{18 \times 3}{21} = 14.5714 \Omega$$

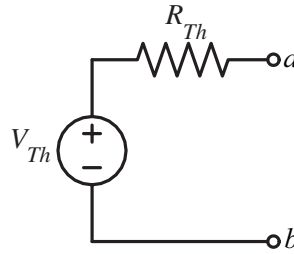3. If $V_{Th} = 22\text{V}$ and $R_{Th} = 50\Omega$, what is the maximum amount of power that could be delivered to a resistive load R_L connected between a and b by this practical voltage source?



$$R_L = R_{Th} = 50\Omega, \quad V_L = V_{Th} / 2 = 11\text{V}, \quad P_L = (11)^2 / 50 = 121 / 50 = 2.42 \text{ W}$$

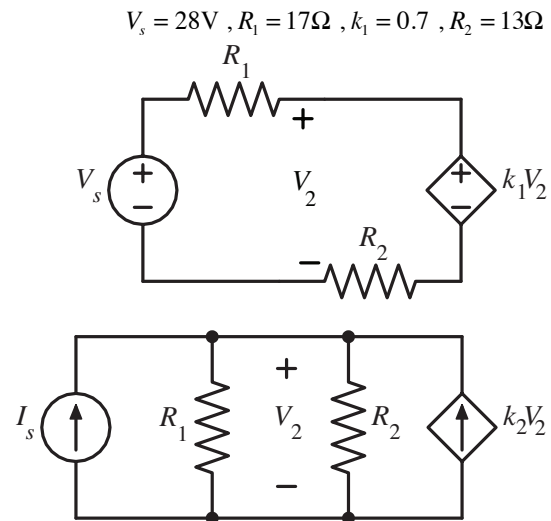
4. The second circuit below was formed by source transformation on the first circuit below where V_s and R_1 form one practical voltage source and k_1V_2 and R_2 form the other practical voltage source. Find the numerical values of I_s and k_2 .



$$I_s = V_s / R_1 = \frac{28}{17} = 1.6471 \text{ A}$$

$$k_2V_2 = k_1V_2 / R_2 = \frac{0.7}{13}V_2 = 0.0538V_2 \Rightarrow k_2 = 0.0538$$

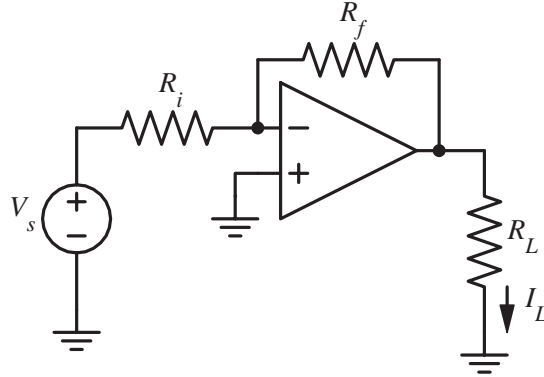
5. If $V_s = 18\text{V}$, $R_i = 10\text{k}\Omega$, $R_f = 85\text{k}\Omega$ and $R_L = 200\Omega$ find the numerical value of I_L .



$$I_L = \frac{V_s \left(-\frac{R_f}{R_i} \right)}{R_L} = \frac{18 \left(-\frac{85}{10} \right)}{200} = -0.765 \text{ A}$$

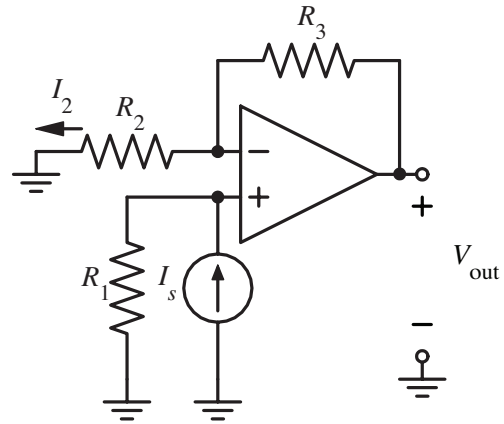6. Find the numerical values of I_2 and V_{out} .

$$I_s = 10\text{mA} , R_1 = 200\Omega , R_2 = 2\text{k}\Omega , R_3 = 11\text{k}\Omega$$




$$V_{out} = I_s R_1 \left(1 + \frac{R_3}{R_2} \right) = 0.01 \times 200 \times \left(1 + \frac{11}{2} \right) = 13 \text{ V}$$

$$I_2 = I_s R_1 / R_2 = 0.01 \times 200 / 2000 = 1\text{mA}$$

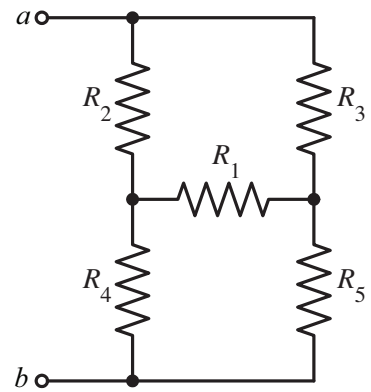7. Find the numerical resistance between terminals a and b .

$$R_1 = R_2 = R_3 = 10\Omega, R_4 = R_5 = 5\Omega$$



If we convert the top π to a T, the three elements of the T are all equal and are all

$$\frac{10 \times 10}{10 + 10 + 10} = \frac{10}{3} \Omega. \text{ Then the } ab \text{ resistance is}$$

$$R_{ab} = (5 + 10/3) \parallel (5 + 10/3) + 10/3 = 22.5/3 = 7.5\Omega$$


Solution of ECE 300 Test 2 S11

1. Find the numerical value of I_x with

(a) V_s acting alone $I_x = V_s / (R_1 + R_2) = \frac{7\text{V}}{12\Omega + 23\Omega} = 0.2\text{A}$


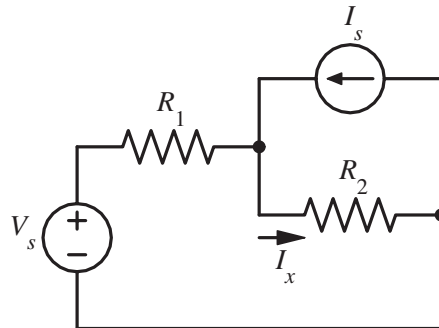
(b) I_s acting alone $I_x = \frac{R_1}{R_1 + R_2} I_s = \frac{12\Omega}{12\Omega + 23\Omega} 5\text{A} = 1.7142\text{ A}$

$$V_s = 7\text{V} , I_s = 5\text{A} , R_1 = 12\Omega , R_2 = 23\Omega$$



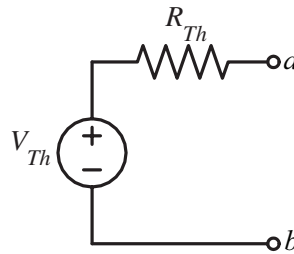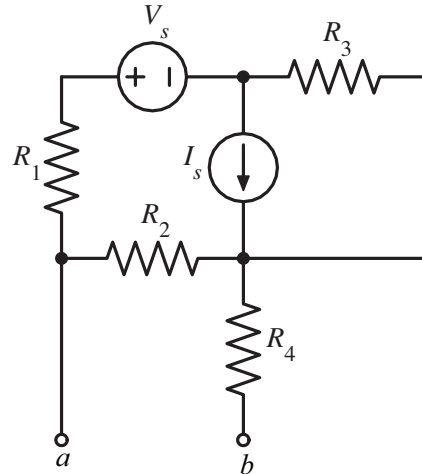2. The Thevenin equivalent of the first circuit at terminals a and b is the second circuit shown below. Find the numerical values of V_{Th} and R_{Th} .


$$V_s = 10\text{V} , I_s = 1\text{A} , R_1 = 11\Omega , R_2 = 6\Omega , R_3 = 8\Omega , R_4 = 7\Omega$$



$$V_{Th} = V_s \frac{R_2}{R_1 + R_2 + R_3} - I_s \frac{R_3}{R_1 + R_2 + R_3} R_2 = 10 \frac{6}{11+6+8} - \frac{8}{11+6+8} 6 = \frac{60}{25} - \frac{48}{25} = \frac{12}{25} = 0.48 \text{ V}$$

$$R_{Th} = R_4 + (R_1 + R_3) \parallel R_2 = 7 + \frac{17 \times 6}{23} = 11.4348 \Omega$$

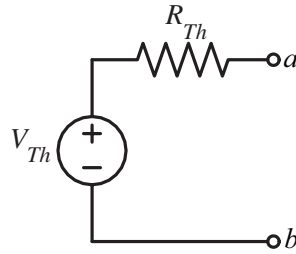
3. If $V_{Th} = 11V$ and $R_{Th} = 50\Omega$, what is the maximum amount of power that could be delivered to a resistive load R_L connected between a and b by this practical voltage source?



$$R_L = R_{Th} = 50\Omega, \quad V_L = V_{Th} / 2 = 5.5V, \quad P_L = (5.5)^2 / 50 = 0.605 \text{ W}$$

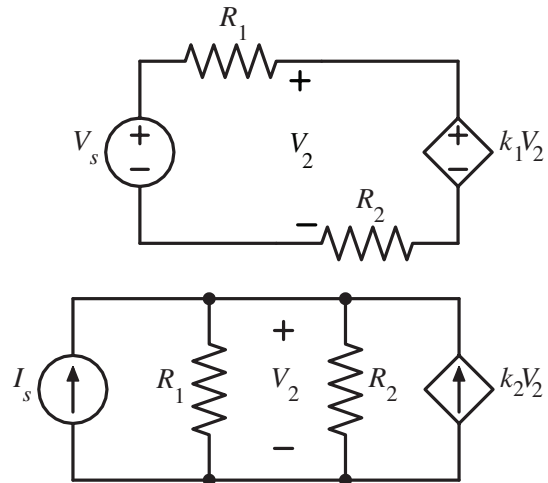4. The second circuit below was formed by source transformation on the first circuit below where V_s and R_1 form one practical voltage source and k_1V_2 and R_2 form the other practical voltage source. Find the numerical values of I_s and k_2 .


$$V_s = 38V, \quad R_1 = 17\Omega, \quad k_1 = 0.4, \quad R_2 = 13\Omega$$



$$I_s = V_s / R_1 = \frac{38}{17} = 2.2353 \text{ A}$$

$$k_2V_2 = k_1V_2 / R_2 = \frac{0.4}{13}V_2 = 0.0538V_2 \Rightarrow k_2 = 0.0308$$

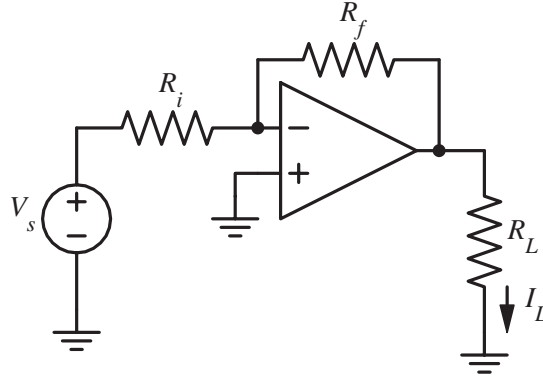
5. If $V_s = 14\text{V}$, $R_i = 10\text{k}\Omega$, $R_f = 85\text{k}\Omega$ and $R_L = 200\Omega$ find the numerical value of I_L .



$$I_L = \frac{V_s \left(-\frac{R_f}{R_i} \right)}{R_L} = \frac{14 \left(-\frac{85}{10} \right)}{200} = -0.595 \text{ A}$$

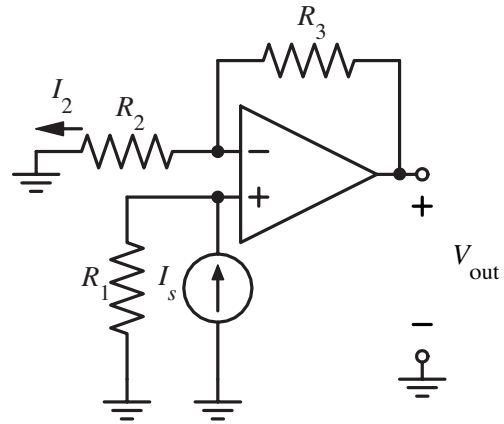6. Find the numerical values of I_2 and V_{out} .

$$I_s = 5\text{mA} , R_1 = 200\Omega , R_2 = 2\text{k}\Omega , R_3 = 11\text{k}\Omega$$




$$V_{out} = I_s R_1 \left(1 + \frac{R_3}{R_2} \right) = 0.005 \times 200 \times \left(1 + \frac{11}{2} \right) = 6.5 \text{ V}$$

$$I_2 = I_s R_1 / R_2 = 0.005 \times 200 / 2000 = 0.5\text{mA}$$

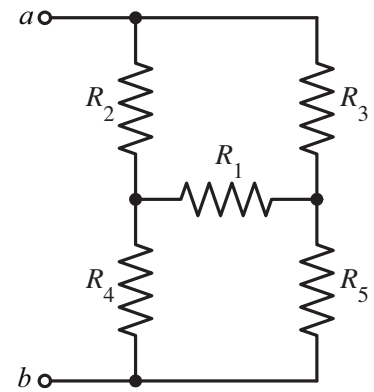7. Find the numerical resistance between terminals a and b .

$$R_1 = R_2 = R_3 = 20\Omega, R_4 = R_5 = 10\Omega$$



If we convert the top π to a T, the three elements of the T are all equal and are all

$$\frac{20 \times 20}{20 + 20 + 20} = \frac{20}{3} \Omega. \text{ Then the } ab \text{ resistance is}$$

$$R_{ab} = (10 + 20/3) \parallel (10 + 20/3) + 20/3 = 45/3 = 15\Omega$$


Solution of ECE 300 Test 2 S11

1. Find the numerical value of I_x with

(a) V_s acting alone $I_x = V_s / (R_1 + R_2) = \frac{21V}{12\Omega + 23\Omega} = 0.6A$


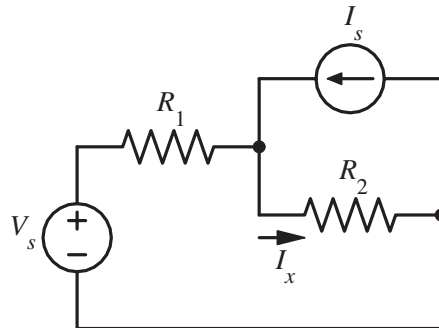
(b) I_s acting alone $I_x = \frac{R_1}{R_1 + R_2} I_s = \frac{12\Omega}{12\Omega + 23\Omega} 4A = 1.3714 A$

$$V_s = 21V, I_s = 4A, R_1 = 12\Omega, R_2 = 23\Omega$$



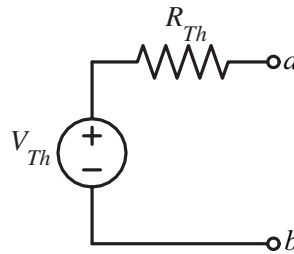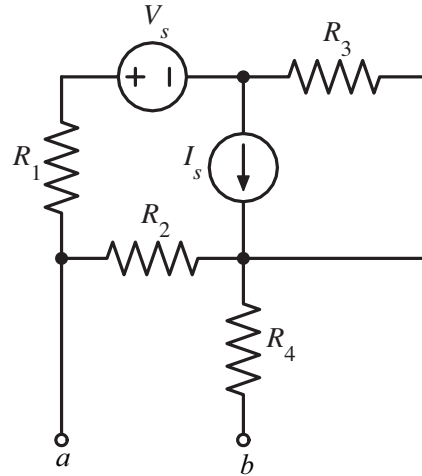2. The Thevenin equivalent of the first circuit at terminals a and b is the second circuit shown below. Find the numerical values of V_{Th} and R_{Th} .


$$V_s = 9\text{V} , I_s = 3\text{A} , R_1 = 4\Omega , R_2 = 12\Omega , R_3 = 8\Omega , R_4 = 14\Omega$$



$$V_{Th} = V_s \frac{R_2}{R_1 + R_2 + R_3} - I_s \frac{R_3}{R_1 + R_2 + R_3} R_2 = 9 \frac{12}{4 + 12 + 8} - 3 \frac{8}{4 + 12 + 8} 12 = \frac{108}{24} - \frac{288}{24} = -\frac{180}{24} = -7.5 \text{ V}$$


$$R_{Th} = R_4 + (R_1 + R_3) \parallel R_2 = 14 + \frac{12 \times 12}{24} = 20 \Omega$$

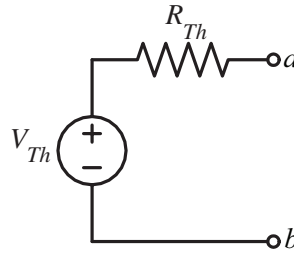3. If $V_{Th} = 35\text{V}$ and $R_{Th} = 50\Omega$, what is the maximum amount of power that could be delivered to a resistive load R_L connected between a and b by this practical voltage source?



$$R_L = R_{Th} = 50\Omega, \quad V_L = V_{Th} / 2 = 17.5\text{V}, \quad P_L = (17.5)^2 / 50 = 6.125\text{ W}$$

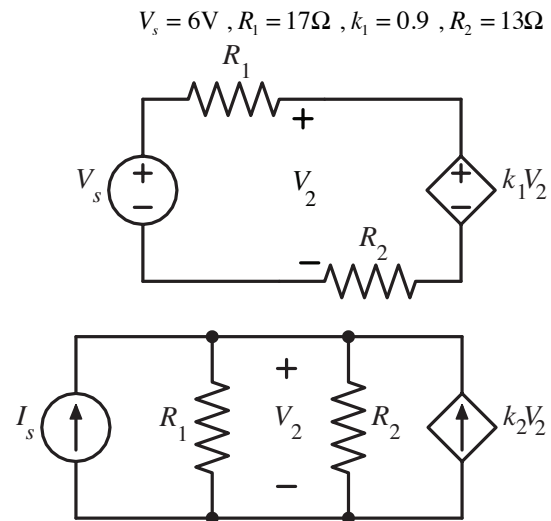
4. The second circuit below was formed by source transformation on the first circuit below where V_s and R_1 form one practical voltage source and k_1V_2 and R_2 form the other practical voltage source. Find the numerical values of I_s and k_2 .



$$I_s = V_s / R_1 = \frac{6}{17} = 0.3529\text{ A}$$

$$k_2V_2 = k_1V_2 / R_2 = \frac{0.9}{13}V_2 = 0.0392V_2 \Rightarrow k_2 = 0.0692$$

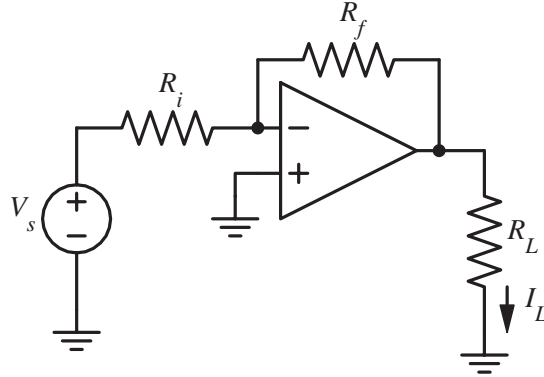
5. If $V_s = 24\text{V}$, $R_i = 10\text{k}\Omega$, $R_f = 85\text{k}\Omega$ and $R_L = 200\Omega$ find the numerical value of I_L .



$$I_L = \frac{V_s \left(-\frac{R_f}{R_i} \right)}{R_L} = \frac{24 \left(-\frac{85}{10} \right)}{200} = -1.02 \text{ A}$$

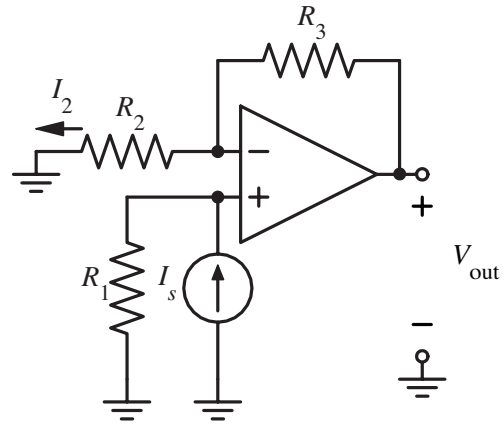6. Find the numerical values of I_2 and V_{out} .

$$I_s = 15\text{mA} , R_1 = 200\Omega , R_2 = 2\text{k}\Omega , R_3 = 11\text{k}\Omega$$




$$V_{out} = I_s R_1 \left(1 + \frac{R_3}{R_2} \right) = 0.015 \times 200 \times \left(1 + \frac{11}{2} \right) = 19.5 \text{ V}$$

$$I_2 = I_s R_1 / R_2 = 0.015 \times 200 / 2000 = 1.5\text{mA}$$

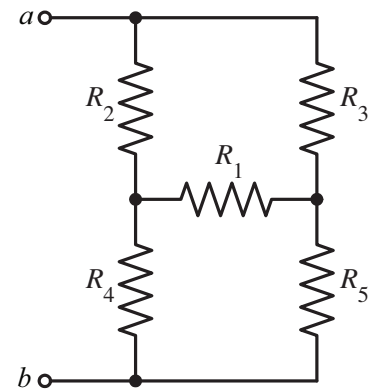7. Find the numerical resistance between terminals a and b .

$$R_1 = R_2 = R_3 = 40\Omega, R_4 = R_5 = 20\Omega$$



If we convert the top π to a T, the three elements of the T are all equal and are all

$$\frac{40 \times 40}{40 + 40 + 40} = \frac{40}{3} \Omega. \text{ Then the } ab \text{ resistance is}$$

$$R_{ab} = (20 + 40/3) \parallel (20 + 40/3) + 40/3 = 90/3 = 30\Omega$$