

Solution of EECS 300 Test 4 F08

1. In the circuit below, find the numerical value of the current I_x due to

(a) The 3A source acting alone.

The 3A current divides between the 3Ω resistor and the equivalent resistance in the other branch which is $4\Omega + 3\Omega \parallel 6\Omega$ or 6Ω . Therefore the current through the 4Ω resistor is

$$I_4 = 3A \frac{3\Omega}{3\Omega + 6\Omega} = 1A. \text{ This current returns to the current source through the bottom conductor,}$$

flowing in the direction opposite that of the arrow for I_x . Therefore I_x for 3A acting alone, = -1A.


(b) The 20V source acting alone.

The total current flowing out of the positive terminal of the 20V source is

$$I_{20} = \frac{20V}{7\Omega \parallel 3\Omega + 6\Omega} = \frac{20V}{8.1\Omega} = 2.47A$$

That current then divides between the two paths $4\Omega + 3\Omega$ and 3Ω . The fraction that flows through the $4\Omega + 3\Omega$ path is the same as I_x . That is
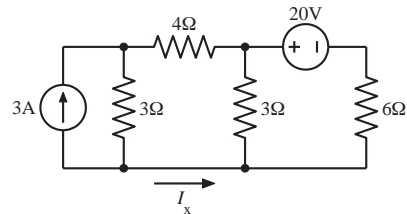
$$I_x = 2.47A \frac{3\Omega}{3\Omega + 7\Omega} = 0.741A. \text{ Therefore, for the 20V source acting alone, } I_x = 0.741A.$$



2. Find the numerical value of the Thevenin equivalent voltage V_{TH} and the Thevenin equivalent resistance R_{TH} for the circuit below.


No current flows through the dependent voltage source. Therefore I_x flows through both the 9Ω and 3Ω resistors, making them effectively in series. So $I_x = \frac{10V}{12\Omega} = 0.833A$. The voltage across the 3Ω resistor is $2.5V$. The voltage of the dependent voltage source is $3.333V$. Therefore the Thevenin equivalent voltage V_{TH} is $5.833V$.

To find the Thevenin equivalent resistance, apply a test $1V$ source at the a - b terminals with the $10V$ source set to zero.


$$3I_x + 4I_x = 1 \Rightarrow I_x = 0.143A$$

Then the voltage across the 9Ω and 3Ω resistors in parallel is $0.4286V$ and the current through the 9Ω resistor is $0.0476A$. So the current through the dependent source is $0.191A$ and the Thevenin equivalent resistance is

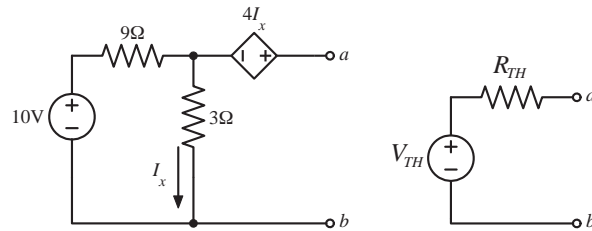
$$R_{TH} = \frac{1V}{0.191A} = 5.25\Omega.$$



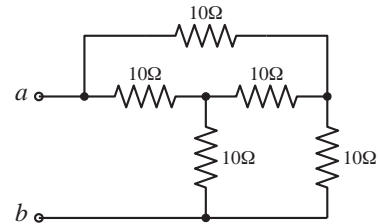3. Find the numerical value of the resistance between a and b in the circuit below.



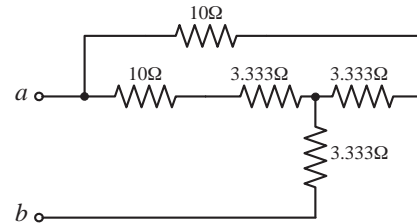Through a delta-wye conversion we can convert this circuit to



From this point on parallel and series combinations can be used to find the overall equivalent resistance.

$$R_{ab} = (10\Omega + 3.333\Omega) \parallel (10\Omega + 3.333\Omega) + 3.333\Omega = 10\Omega.$$

Solution of EECS 300 Test 4 F08

1. In the circuit below, find the numerical value of the current I_x due to

(a) The 5A source acting alone.

The 5A current divides between the 3Ω resistor and the equivalent resistance in the other branch which is $4\Omega + 3\Omega \parallel 6\Omega$ or 6Ω . Therefore the current through the 4Ω resistor is

$$I_4 = 5A \frac{3\Omega}{3\Omega + 6\Omega} = 1.667A. \text{ This current returns to the current source through the bottom}$$

conductor, flowing in the direction opposite that of the arrow for I_x . Therefore I_x for 5A acting alone, = $-1.667A$.


(b) The 10V source acting alone.

The total current flowing out of the positive terminal of the 10V source is

$$I_{20} = \frac{10V}{7\Omega \parallel 3\Omega + 6\Omega} = \frac{10V}{8.1\Omega} = 1.24A$$

That current then divides between the two paths $4\Omega + 3\Omega$ and 3Ω . The fraction that flows through the $4\Omega + 3\Omega$ path is the same as I_x . That is
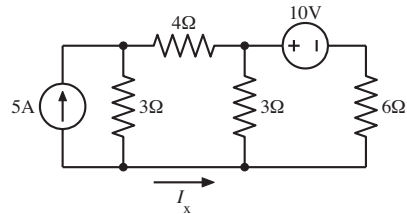
$$I_x = 1.24A \frac{3\Omega}{3\Omega + 7\Omega} = 0.371A. \text{ Therefore, for the 20V source acting alone, } I_x = 0.371A.$$



2. Find the numerical value of the Thevenin equivalent voltage V_{TH} and the Thevenin equivalent resistance R_{TH} for the circuit below.


No current flows through the dependent voltage source. Therefore I_x flows through both the 9Ω and 3Ω resistors, making them effectively in series. So $I_x = \frac{10V}{12\Omega} = 0.833A$. The voltage across the 3Ω resistor is $2.5V$. The voltage of the dependent voltage source is $1.667V$. Therefore the Thevenin equivalent voltage V_{TH} is $4.167V$.

To find the Thevenin equivalent resistance, apply a test $1V$ source at the $a-b$ terminals with the $10V$ source set to zero.


$$3I_x + 2I_x = 1 \Rightarrow I_x = 0.2A$$

Then the voltage across the 9Ω and 3Ω resistors in parallel is $0.6V$ and the current through the 9Ω resistor is $0.0667A$. So the current through the dependent source is $0.2667A$ and the Thevenin equivalent resistance is

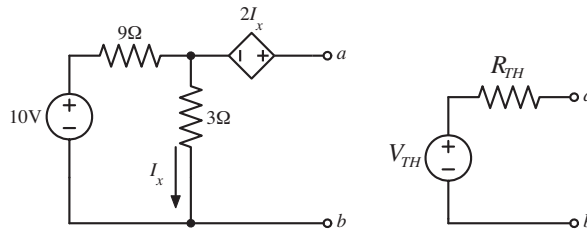
$$R_{TH} = \frac{1V}{0.2667A} = 3.75\Omega.$$



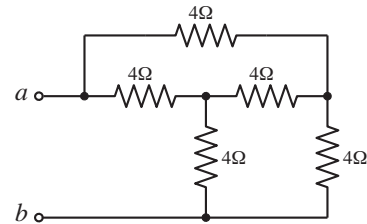3. Find the numerical value of the resistance between a and b in the circuit below.



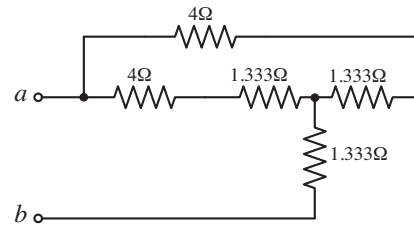Through a delta-wye conversion we can convert this circuit to



From this point on parallel and series combinations can be used to find the overall equivalent resistance.

$$R_{ab} = (4\Omega + 1.333\Omega) \parallel (4\Omega + 1.333\Omega) + 1.333\Omega = 4\Omega.$$