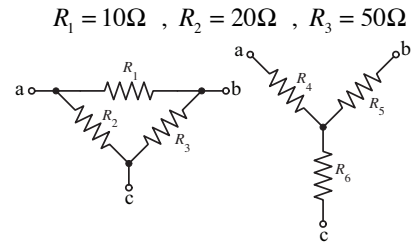


Solution of ECE 300 Test 4 S09

1. If the two networks below are equivalent at terminals a, b and c, find the numerical value of R_5 .

$$R_5 = \frac{R_1 R_3}{R_1 + R_2 + R_3} = \frac{500\Omega^2}{80\Omega} = 6.25\Omega$$




2. Find the numerical value of i_x

$$i_x = 2A$$

$$i_x = \frac{10V}{6\Omega \parallel 4\Omega} = \frac{10V}{2.4\Omega} = 4.167A$$

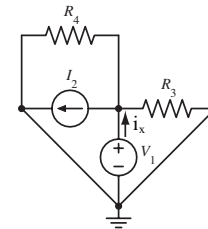
$V_1 = 10V$, $I_2 = 2A$
 $R_3 = 4\Omega$, $R_4 = 6\Omega$



3. Find the numerical values of the Thevenin equivalent voltage and resistance at terminals a and b.

V_{TH} is zero because there are no independent sources in the circuit. Apply a 1A source to the terminals flowing into a. Then $I_x = 1A$ and $0.6I_x = 0.6V$. So the voltage between a and b (a at positive polarity) is $-0.6V + 20\Omega \times 1A = 19.4V$ and therefore $R_{TH} = 19.4\Omega$.


$R_2 = 50\Omega$, $R_3 = 20\Omega$

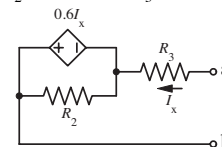

Solution of ECE 300 Test 3 S09

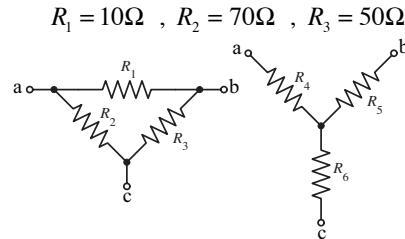1. If the two networks below are equivalent at terminals a, b and c, find the numerical value of R_5 .

$$R_5 = \frac{R_1 R_3}{R_1 + R_2 + R_3} = \frac{500\Omega^2}{130\Omega} = 3.846\Omega$$




2. Find the numerical value of i_x

(a) Due to the current source alone. $i_x = 3A$

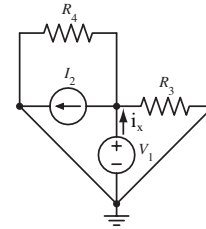(b) Due to the voltage source alone. $i_x = \frac{10V}{12\Omega \parallel 4\Omega} = \frac{10V}{3\Omega} = 3.333A$

$V_1 = 10V$, $I_2 = 3A$
 $R_3 = 4\Omega$, $R_4 = 12\Omega$



3. Find the numerical values of the Thevenin equivalent voltage and resistance at terminals a and b.

V_{TH} is zero because there are no independent sources in the circuit. Apply a 1A source to the terminals flowing into a. Then $I_x = 1A$ and $0.6I_x = 0.6V$. So the voltage between a and b (a at positive polarity) is $-0.6V + 35\Omega \times 1A = 34.4V$ and therefore $R_{TH} = 34.4\Omega$.

$R_2 = 50\Omega$, $R_3 = 35\Omega$

