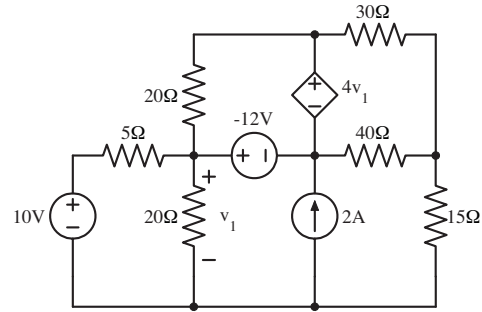


Solution of ECE 300 Test 3 F08

1. Answer the following questions about the circuit below.

- (a) How many branches are there? _____ 10
- (b) How many nodes are there? _____ 6
- (c) How many meshes are there? _____ 5
- (d) How many supernodes are there? _____ 2
- (e) How many supermeshes are there? _____ 1
- (f) In writing nodal equations for this circuit, how many equations should you write for the sum of currents leaving a node or supernode equals zero (KCL)? _____ 2
- (g) In writing mesh equations for this circuit, how many equations should you write for the sum of voltages around a mesh or supermesh equals zero (KVL)? _____ 4



2. Fill in the blanks below in the nodal and mesh equations.

$$\frac{\boxed{}}{3} + \frac{\boxed{} - v_2}{\boxed{}} = 0$$

$$\frac{\boxed{}}{5} + \frac{\boxed{}}{12} + \frac{v_2 - \boxed{}}{5} = 0$$


$$\frac{\boxed{}}{12} + \frac{v_3 - \boxed{}}{\boxed{}} = \boxed{}$$

$$\frac{\boxed{}}{6} + \frac{\boxed{}}{4} + \frac{\boxed{} - v_2}{5} + \frac{v_5}{\boxed{}} = 0$$

$$5\boxed{} + \boxed{}(i_1 - i_2) + 4\boxed{} + 6\boxed{} + \boxed{}i_1 = 0$$

$$\boxed{}i_2 + \boxed{} + 4\boxed{} + 12\boxed{} = 0$$
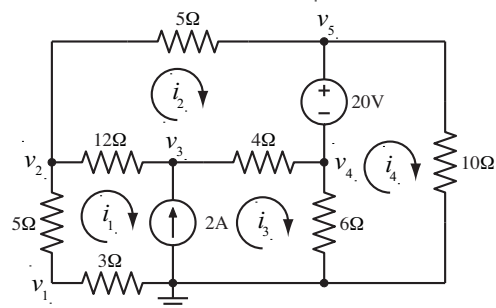
$$\boxed{}(i_4 - i_3) - 20 + 10\boxed{} = 0$$



$$\frac{V_1}{3} + \frac{V_1 - V_2}{5} = 0$$

$$\frac{V_2 - V_1}{5} + \frac{V_2 - V_3}{12} + \frac{V_2 - V_5}{5} = 0$$

$$\frac{V_3 - V_2}{12} + \frac{V_3 - V_4}{4} = 2$$

$$\frac{V_4}{6} + \frac{V_4 - V_3}{4} + \frac{V_5 - V_2}{5} + \frac{V_5}{10} = 0$$

$$5i_1 + 12(i_1 - i_2) + 4(i_3 - i_2) + 6(i_3 - i_4) + 3i_1 = 0$$


$$5i_2 + 20 + 4(i_2 - i_3) + 12(i_2 - i_1) = 0$$

$$6(i_4 - i_3) - 20 + 10i_4 = 0$$

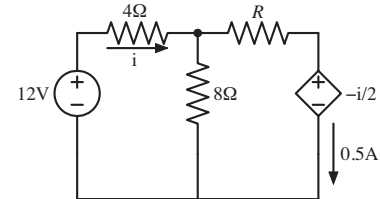3. Find the numerical value of R .

$$R = \underline{\hspace{2cm}}$$

(The numerical value of the voltage in volts across the dependent voltage source is equal to the negative of half of the numerical value of the current i in amperes.)



Assign v_1 as the node voltage at the intersection of the three resistors and the bottom node as the reference node.

$$\frac{v_1 - 12}{4} + \frac{v_1}{8} + \frac{v_1 - (-i/2)}{R} = 0$$

$$i = \frac{12 - v_1}{4} \quad 0.5 = \frac{v_1 - (-i/2)}{R}$$

$$\frac{v_1 - 12}{4} + \frac{v_1}{8} + 0.5 = 0 \Rightarrow (3/8)v_1 = 2.5 \Rightarrow v_1 = 20/3 \text{ V}$$

$$i = \frac{12 - 20/3}{4} = 4/3 \text{ A}, \quad 0.5 = \frac{20/3 - (-2/3)}{R} \Rightarrow R = \frac{20/3 - (-2/3)}{0.5} = (44/3)\Omega$$

Voltage drop across 4 ohm resistor is $16/3$ V. Current through the 8 ohm resistor is $5/6$ A. Voltage drop across R is $22/3$ V. Dependent voltage source voltage is $-2/3$ V. KVL and KCL are satisfied everywhere.

Alternate Solution:

Assign two mesh currents, i_1 in the left mesh and i_2 in the right mesh. Then immediately we know that $i_2 = 0.5$. The two mesh equations are

$$\begin{aligned} -12 + 4i_1 + 8(i_1 - i_2) &= 0 \\ 8(i_2 - i_1) + Ri_2 + (-i/2) &= 0 \end{aligned}$$

From the first mesh equation

$$-12 + 4i_1 + 8(i_1 - 0.5) = 0 \Rightarrow 12i_1 = 16 \Rightarrow i_1 = 4/3 \Rightarrow i = 4/3$$

From the second mesh equation

$$8(1/2 - 4/3) + R(1/2) + (-2/3) = 0 \Rightarrow R = 2(22/3) = (44/3)\Omega$$