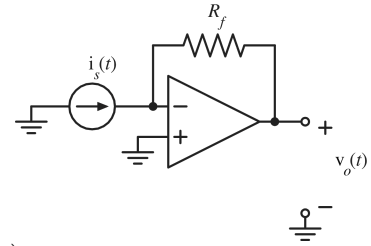


# Solution of ECE 300 Test 5 F10

1. Find the numerical value of the output voltage  $v_o(t)$  at time  $t = 0.3$  ms .

$$i_s(t) = 7 \sin(2000\pi t) \mu\text{A} , R_f = 1 \text{ M}\Omega$$




$$v_o(t) = -R_f i_s(t) = -1 \text{ M}\Omega \times 7 \sin(2000\pi t) \mu\text{A} = -7 \sin(2000\pi t) \text{ V}$$

$$v_o(0.3 \text{ ms}) = -7 \sin(2000\pi \times 0.0003) \text{ V} = -6.6574 \text{ V}$$

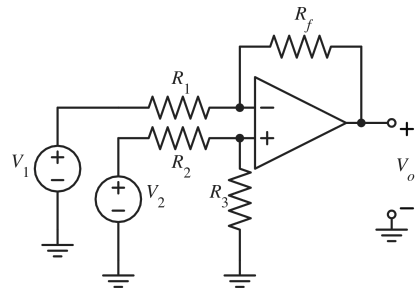2. Find the numerical value of  $V_o$  .

$$V_1 = 18\text{V} , V_2 = 7 \text{ V} , R_1 = 30 \text{ k}\Omega , R_2 = 12 \text{ k}\Omega \\ R_3 = 50 \text{ k}\Omega , R_f = 120 \text{ k}\Omega$$




$$V_o = -\frac{R_f}{R_1} V_1 + \frac{R_3}{R_2 + R_3} \frac{R_f + R_1}{R_1} V_2 = -\frac{120 \text{ k}\Omega}{30 \text{ k}\Omega} 18\text{V} + \frac{50 \text{ k}\Omega}{50 \text{ k}\Omega + 12 \text{ k}\Omega} \frac{120 \text{ k}\Omega + 30 \text{ k}\Omega}{30 \text{ k}\Omega} 7\text{V}$$

$$V_o = -72\text{V} + 0.8065 \times 5 \times 7\text{V} = -43.7742 \text{ V}$$

# Solution of ECE 300 Test 5 F10

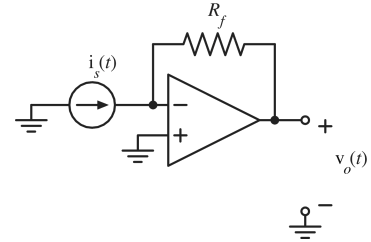1. Find the numerical value of the output voltage  $v_o(t)$  at time  $t = 0.3$  ms .

$$i_s(t) = 3 \sin(2500\pi t) \mu\text{A} \quad , \quad R_f = 1 \text{ M}\Omega$$




$$v_o(t) = -R_f i_s(t) = -1 \text{ M}\Omega \times 3 \sin(2500\pi t) \mu\text{A} = -3 \sin(2500\pi t) \text{ V}$$

$$v_o(0.3 \text{ ms}) = -3 \sin(2500\pi \times 0.0003) \text{ V} = -2.1213 \text{ V}$$

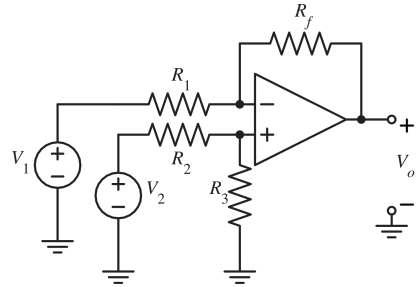2. Find the numerical value of  $V_o$  .

$$V_1 = 13 \text{ V} \quad , \quad V_2 = 11 \text{ V} \quad , \quad R_1 = 30 \text{ k}\Omega \quad , \quad R_2 = 12 \text{ k}\Omega$$

$$R_3 = 50 \text{ k}\Omega \quad , \quad R_f = 120 \text{ k}\Omega$$




$$V_o = -\frac{R_f}{R_1} V_1 + \frac{R_3}{R_2 + R_3} \frac{R_f + R_1}{R_1} V_2 = -\frac{120 \text{ k}\Omega}{30 \text{ k}\Omega} 13 \text{ V} + \frac{50 \text{ k}\Omega}{50 \text{ k}\Omega + 12 \text{ k}\Omega} \frac{120 \text{ k}\Omega + 30 \text{ k}\Omega}{30 \text{ k}\Omega} 11 \text{ V}$$

$$V_o = -52 \text{ V} + 0.8065 \times 5 \times 11 \text{ V} = -7.6452 \text{ V}$$

# Solution of ECE 300 Test 5 F10

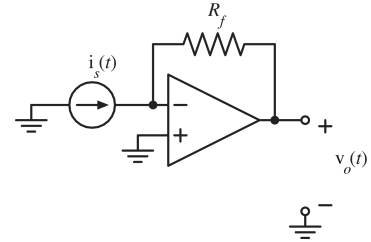1. Find the numerical value of the output voltage  $v_o(t)$  at time  $t = 0.3$  ms .

$$i_s(t) = 2 \sin(2200\pi t) \mu\text{A} , R_f = 1 \text{ M}\Omega$$




$$v_o(t) = -R_f i_s(t) = -1 \text{ M}\Omega \times 2 \sin(2200\pi t) \mu\text{A} = -2 \sin(2200\pi t) \text{ V}$$

$$v_o(0.3 \text{ ms}) = -2 \sin(2200\pi \times 0.0003) \text{ V} = -1.7526 \text{ V}$$

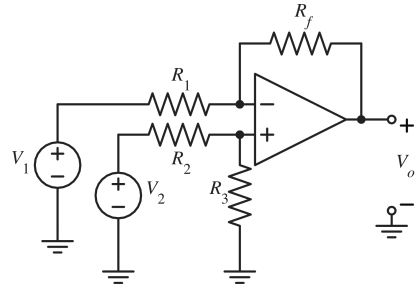2. Find the numerical value of  $V_o$  .

$$V_1 = 4 \text{ V} , V_2 = 13 \text{ V} , R_1 = 30 \text{ k}\Omega , R_2 = 12 \text{ k}\Omega$$

$$R_3 = 50 \text{ k}\Omega , R_f = 120 \text{ k}\Omega$$



$$V_o = -\frac{R_f}{R_1} V_1 + \frac{R_3}{R_2 + R_3} \frac{R_f + R_1}{R_1} V_2 = -\frac{120 \text{ k}\Omega}{30 \text{ k}\Omega} 4\text{V} + \frac{50 \text{ k}\Omega}{50 \text{ k}\Omega + 12 \text{ k}\Omega} \frac{120 \text{ k}\Omega + 30 \text{ k}\Omega}{30 \text{ k}\Omega} 13\text{V}$$

$$V_o = -16\text{V} + 0.8065 \times 5 \times 13\text{V} = 36.42 \text{ V}$$