


Solution of ECE 300 Test 5 S12

The op amp is ideal. Fill in the blanks with correct numerical voltages or currents. Please be sure to check that Ohm's law is satisfied for each resistor, KCL is satisfied at each node and KVL is satisfied around each loop.

$$I_1 = \text{_____ mA} \quad I_x = \text{_____ mA} \quad I_2 = \text{_____ mA} \quad I_L = \text{_____ mA}$$

$$I_o = \text{_____ mA} \quad V_1 = \text{_____ V} \quad V_2 = \text{_____ V} \quad V_L = \text{_____ V}$$
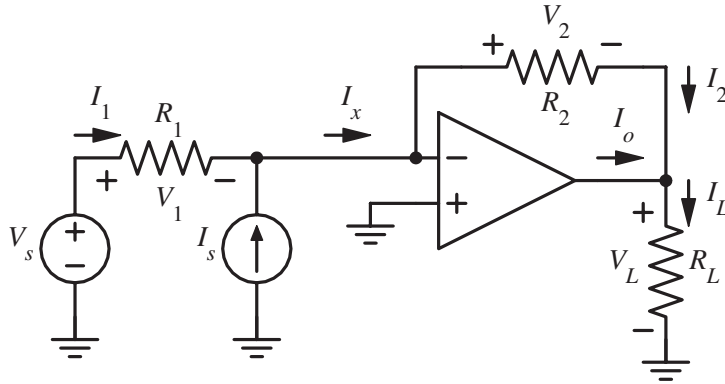
$$V_s = 8\text{V}, I_s = 60\text{mA}, R_1 = 165\Omega, R_2 = 200\Omega, R_L = 120\Omega$$



The voltage at the inverting op amp input is zero. Therefore by KVL $V_1 = V_s = 8\text{V}$ and by Ohm's law $I_1 = V_1 / R_1 = 8\text{V} / 165\Omega = 48.5\text{mA}$. By KCL, $I_x = I_1 + I_s = 48.5 + 60 = 108.5\text{mA}$. Since the input current into the op amp is zero, $I_2 = I_x = 108.5\text{mA}$, by Ohm's law $V_2 = I_2 R_2 = 108.5\text{mA} \times 200\Omega = 21.7\text{V}$ and by KVL $V_L = -V_2 = -21.7\text{V}$. Then by Ohm's law $I_L = V_L / R_L = -21.7\text{V} / 120\Omega = -180.8\text{mA}$ and by KCL,

$$I_o = I_L - I_2 = -180.8\text{mA} - 108.5\text{mA} = -289.3\text{mA}.$$


Solution of ECE 300 Test 5 S12

The op amp is ideal. Fill in the blanks with correct numerical voltages or currents. Please be sure to check that Ohm's law is satisfied for each resistor, KCL is satisfied at each node and KVL is satisfied around each loop.

$$I_1 = \underline{\hspace{2cm}} \text{ mA} \quad I_x = \underline{\hspace{2cm}} \text{ mA} \quad I_2 = \underline{\hspace{2cm}} \text{ mA} \quad I_L = \underline{\hspace{2cm}} \text{ mA}$$

$$I_o = \underline{\hspace{2cm}} \text{ mA} \quad V_1 = \underline{\hspace{2cm}} \text{ V} \quad V_2 = \underline{\hspace{2cm}} \text{ V} \quad V_L = \underline{\hspace{2cm}} \text{ V}$$
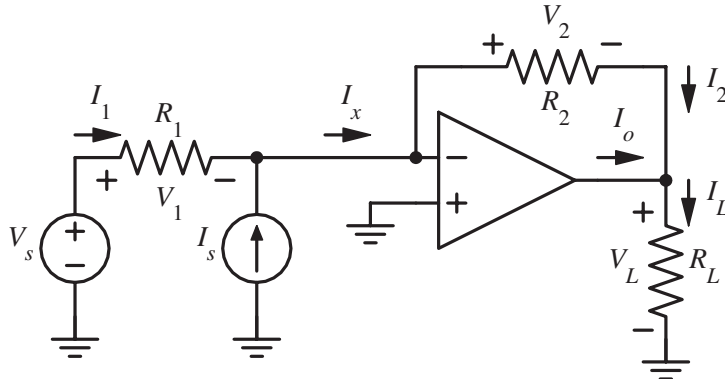
$$V_s = 4\text{V}, I_s = 60\text{mA}, R_1 = 165\Omega, R_2 = 200\Omega, R_L = 120\Omega$$



The voltage at the inverting op amp input is zero. Therefore by KVL $V_1 = V_s = 4\text{V}$ and by Ohm's law $I_1 = V_1 / R_1 = 4\text{V} / 165\Omega = 24.2\text{mA}$. By KCL, $I_x = I_1 + I_s = 24.2 + 60 = 84.2\text{mA}$. Since the input current into the op amp is zero, $I_2 = I_x = 84.2\text{mA}$, by Ohm's law $V_2 = I_2 R_2 = 84.2\text{mA} \times 200\Omega = 16.84\text{V}$ and by KVL $V_L = -V_2 = -16.84\text{V}$. Then by Ohm's law $I_L = V_L / R_L = -16.84\text{V} / 120\Omega = -140.3\text{mA}$ and by KCL,

$$I_o = I_L - I_2 = -140.3\text{mA} - 84.2\text{mA} = -224.5\text{mA}.$$


Solution of ECE 300 Test 5 S12

The op amp is ideal. Fill in the blanks with correct numerical voltages or currents. Please be sure to check that Ohm's law is satisfied for each resistor, KCL is satisfied at each node and KVL is satisfied around each loop.

$$I_1 = \underline{\hspace{2cm}} \text{ mA} \quad I_x = \underline{\hspace{2cm}} \text{ mA} \quad I_2 = \underline{\hspace{2cm}} \text{ mA} \quad I_L = \underline{\hspace{2cm}} \text{ mA}$$

$$I_o = \underline{\hspace{2cm}} \text{ mA} \quad V_1 = \underline{\hspace{2cm}} \text{ V} \quad V_2 = \underline{\hspace{2cm}} \text{ V} \quad V_L = \underline{\hspace{2cm}} \text{ V}$$
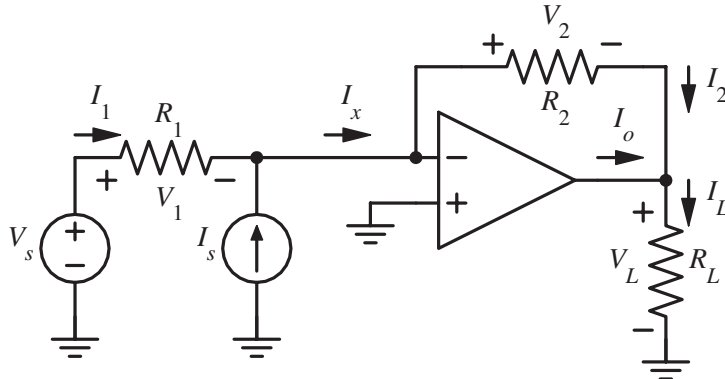
$$V_s = 12\text{V}, I_s = 60\text{mA}, R_1 = 165\Omega, R_2 = 200\Omega, R_L = 120\Omega$$



The voltage at the inverting op amp input is zero. Therefore by KVL $V_1 = V_s = 12\text{V}$ and by Ohm's law $I_1 = V_1 / R_1 = 12\text{V} / 165\Omega = 72.7\text{mA}$. By KCL, $I_x = I_1 + I_s = 72.7 + 60 = 132.7\text{mA}$. Since the input current into the op amp is zero, $I_2 = I_x = 132.7\text{mA}$, by Ohm's law $V_2 = I_2 R_2 = 132.7\text{mA} \times 200\Omega = 26.54\text{V}$ and by KVL $V_L = -V_2 = -26.54\text{V}$. Then by Ohm's law $I_L = V_L / R_L = -26.54\text{V} / 120\Omega = -221.2\text{mA}$ and by KCL,

$$I_o = I_L - I_2 = -221.2\text{mA} - 132.7\text{mA} = -353.9\text{mA}.$$