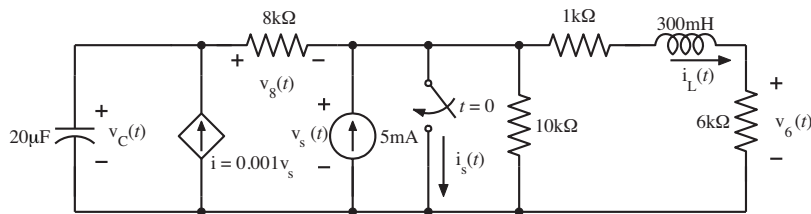


# Solution of EECS 300 Test 7 F08

1. The circuit shown below has been connected this way for a very long time and, before time  $t = 0$ , all currents and all voltages are not changing with time.

- (a) Find the numerical value of  $v_c(0^-)$ .
- (b) Find the numerical value of  $v_8(0^-)$ .
- (c) Find the numerical value of  $i_L(0^-)$ .
- (d) Find the numerical value of  $v_6(0^-)$ .
- (e) Find the numerical value of  $v_s(0^-)$ .
- (f) Find the numerical value of  $v_c(0^+)$ .
- (g) Find the numerical value of  $v_8(0^+)$ .
- (h) Find the numerical value of  $i_L(0^+)$ .
- (i) Find the numerical value of  $v_6(0^+)$ .
- (j) Find the numerical value of  $i_s(0^+)$ .



At  $t = 0^-$ ,

$$\frac{V_c - V_s}{8000} = 0.001V_s, \quad \frac{V_s}{7000} + \frac{V_s}{10000} + \frac{V_s - V_c}{8000} = 0.005. \text{ Solving for } v_s$$

$$\frac{V_s}{7000} + \frac{V_s}{10000} - 0.001V_s = 0.005$$

$$V_s(0.00014286 + 0.0001 - 0.001) = 0.005$$

$$V_s = \frac{0.005}{-0.0007572} = -6.603V$$

$$\frac{V_c + 6.603}{8000} = 0.001(-6.603) \Rightarrow V_c = -59.43V$$

$$V_8 = V_c - V_s = -59.43 - (-6.603) = -52.827V$$

$$i_L = \frac{V_s}{7000} = \frac{-6.603}{7000} = -0.943mA$$

$$V_6 = 6000i_L = -5.66V$$

At  $t = 0^+$ , the switch has closed and

$$i_L = -0.943\text{mA} \quad \text{and} \quad v_c = -59.43\text{V}$$


All the inductor current now flows through the closed switch and the 1k and 6k resistors. So  $v_6$  does not change. It is still  $-5.66\text{V}$ . The independent-current-source voltage  $v_s$  is now zero. So all the independent-current-source current flows through the closed switch. The 8k resistor and the capacitor are now in parallel so their voltages must be equal,  $-59.43\text{V}$ . The dependent-current-source current is now zero because  $v_s$  is zero. The current through the switch is the algebraic sum of the currents through the inductor, through the independent current source and through the 8k resistor. That is

$$i_s = 5\text{mA} - i_L + \frac{V_c}{8000} = 5\text{mA} - (-0.943\text{mA}) + \frac{-59.43\text{V}}{8000\Omega}$$

$$i_s = 5\text{mA} + 0.943\text{mA} - 7.43\text{mA} = -1.487\text{mA}$$

2. The circuit shown below has been connected this way for a very long time and, before time  $t = 0$ , all currents and all voltages are not changing with time. Find the numerical value of  $v(t)$  at

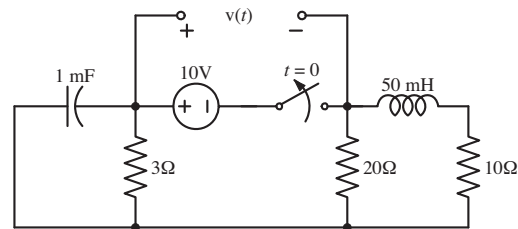- (a)  $t = -1 \text{ ms}$
- (b)  $t = 0^+$
- (c)  $t = 2 \text{ ms}$



- (a) Before  $t = 0$ ,  $v(t)$  is the voltage across the voltage source which is 10V.
- (b) At  $t = 0^+$ , the current through the inductor and the voltage across the capacitor are the same as they were at  $t = 0^-$ . At  $t = 0^-$  the inductor current is

$$\frac{10\text{V}}{3\Omega + 20\Omega \parallel 10\Omega} \times \frac{20\Omega}{20\Omega + 10\Omega} = \frac{10\text{V}}{9.667\Omega} \times \frac{2}{3} = 0.6897\text{A}$$

flowing from right to left in the diagram.

At  $t = 0^-$  the capacitor voltage is

$$\frac{10\text{V}}{3\Omega + 20\Omega \parallel 10\Omega} \times 3\Omega = 3.103\text{V}$$

positive polarity on the right side in the diagram.

At  $t = 0^+$ :

The switch has just opened so the inductor current must now flow through the  $20\Omega - 10\Omega - 50\text{mH}$  loop and the voltage across the  $20\Omega$  resistor is  $0.6897\text{A} \times 20\Omega = 13.794\text{V}$ , positive polarity on top in the diagram. The voltage across the  $3\Omega$  resistor is 3.103V positive polarity on top in the

diagram because it is in parallel with the capacitor. Therefore, summing voltages around the  $3\Omega - 20\Omega - v(t)$  loop yields  $v(0^+) = 3.103\text{V} - 13.794\text{V} = -10.691\text{V}$ .

- (c) After  $t = 0$  the voltages across the  $3\Omega$  resistor and the  $20\Omega$  resistor both decay toward zero but with different time constants. The time constant for the  $3\Omega$  resistor is  $1\text{mF} \times 3\Omega = 3\text{ms}$  and the time constant for the  $20\Omega$  resistor is  $50\text{mH} / 30\Omega = 1.667\text{ms}$ . So the  $3\Omega$  resistor voltage is

$$v_3(t) = 3.103e^{-t/0.003}\text{V} = 3.103e^{-333.33t}\text{V}$$

positive polarity on top in the diagram and the  $20\Omega$  resistor voltage is

$$v_{20}(t) = 13.794e^{-t/0.001667}\text{V} = 13.794e^{-600t}\text{V}$$


positive polarity on top in the diagram. Therefore, at  $t = 2\text{ms}$ ,

$$v(0.002) = 3.103e^{-333.33(0.002)} - 13.794e^{-600(0.002)} = 1.593\text{V} - 4.155\text{V} = -2.562\text{V}.$$

# Solution of EECS 300 Test 7 F08

1. The circuit shown below has been connected this way for a very long time and, before time  $t = 0$ , all currents and all voltages are not changing with time.

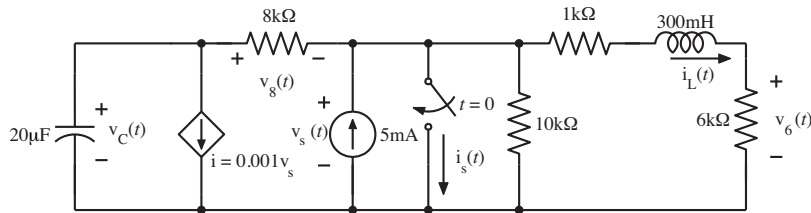- (a) Find the numerical value of  $v_c(0^-)$ .
- (b) Find the numerical value of  $v_8(0^-)$ .
- (c) Find the numerical value of  $i_L(0^-)$ .
- (d) Find the numerical value of  $v_6(0^-)$ .
- (e) Find the numerical value of  $v_s(0^-)$ .
- (f) Find the numerical value of  $v_c(0^+)$ .
- (g) Find the numerical value of  $v_8(0^+)$ .
- (h) Find the numerical value of  $i_L(0^+)$ .
- (i) Find the numerical value of  $v_6(0^+)$ .
- (j) Find the numerical value of  $i_s(0^+)$ .



At  $t = 0^-$ ,

$$\frac{V_c - V_s}{8000} + 0.001V_s = 0, \quad \frac{V_s}{7000} + \frac{V_s}{10000} + \frac{V_s - V_c}{8000} = 0.005. \text{ Solving for } V_s$$

$$\frac{V_s}{7000} + \frac{V_s}{10000} + 0.001V_s = 0.005$$

$$V_s(0.00014286 + 0.0001 + 0.001) = 0.005$$

$$V_s = \frac{0.005}{0.00124286} = 4.023\text{V}$$

$$\frac{V_c - 4.023}{8000} = -0.001(4.023) \Rightarrow V_c = -28.161\text{V}$$

$$V_8 = V_c - V_s = -28.161 - 4.023 = -32.184\text{V}$$

$$i_L = \frac{V_s}{7000} = \frac{4.023}{7000} = 0.575\text{mA}$$

$$V_6 = 6000i_L = 3.448\text{V}$$

At  $t = 0^+$ , the switch has closed and

$$i_L = 0.575\text{mA} \quad \text{and} \quad v_c = -28.161\text{V}$$


All the inductor current now flows through the closed switch and the 1k and 6k resistors. So  $v_6$  does not change. It is still 3.448V. The independent-current-source voltage  $v_s$  is now zero. So all the independent-current-source current flows through the closed switch. The 8k resistor and the capacitor are now in parallel so their voltages must be equal, -28.161V. The dependent-current-source current is now zero because  $v_s$  is zero. The current through the switch is the algebraic sum of the currents through the inductor, through the independent current source and through the 8k resistor. That is

$$i_s = 5\text{mA} - i_L + \frac{V_c}{8000} = 5\text{mA} - 0.575\text{mA} + \frac{-28.161\text{V}}{8000\Omega}$$

$$i_s = 5\text{mA} - 0.575\text{mA} - 3.52\text{mA} = 0.905\text{mA}$$

2. The circuit shown below has been connected this way for a very long time and, before time  $t = 0$ , all currents and all voltages are not changing with time. Find the numerical value of  $v(t)$  at

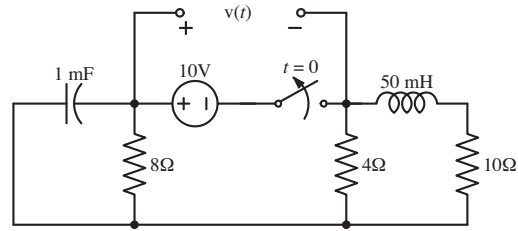- (a)  $t = -1 \text{ ms}$
- (b)  $t = 0^+$
- (c)  $t = 2 \text{ ms}$



- (a) Before  $t = 0$ ,  $v(t)$  is the voltage across the voltage source which is 10V.
- (b) At  $t = 0^+$ , the current through the inductor and the voltage across the capacitor are the same as they were at  $t = 0^-$ . At  $t = 0^-$  the inductor current is

$$\frac{10\text{V}}{8\Omega + 4\Omega \parallel 10\Omega} \times \frac{4\Omega}{4\Omega + 10\Omega} = \frac{10\text{V}}{10.857\Omega} \times \frac{4}{14} = 0.263\text{A}$$

flowing from right to left in the diagram.

At  $t = 0^-$  the capacitor voltage is

$$\frac{10\text{V}}{8\Omega + 4\Omega \parallel 10\Omega} \times 8\Omega = 7.369\text{V}$$

positive polarity on the right side in the diagram.

At  $t = 0^+$ :

The switch has just opened so the inductor current must now flow through the  $4\Omega - 10\Omega - 50\text{mH}$  loop and the voltage across the  $4\Omega$  resistor is  $0.263\text{A} \times 4\Omega = 1.052\text{V}$ , positive polarity on top in the diagram. The voltage across the  $8\Omega$  resistor is 7.369V positive polarity on top in the diagram

because it is in parallel with the capacitor. Therefore, summing voltages around the  $8\Omega - 4\Omega - v(t)$  loop yields  $v(0^+) = 7.369\text{V} - 1.052\text{V} = 6.317\text{V}$ .

- (c) After  $t = 0$  the voltages across the  $8\Omega$  resistor and the  $4\Omega$  resistor both decay toward zero but with different time constants. The time constant for the  $8\Omega$  resistor is  $1\text{mF} \times 8\Omega = 8\text{ms}$  and the time constant for the  $4\Omega$  resistor is  $50\text{mH} / 14\Omega = 3.57\text{ms}$ . So the  $8\Omega$  resistor voltage is

$$v_8(t) = 7.369e^{-t/0.008}\text{V} = 7.369e^{-125t}\text{V}$$

positive polarity on top in the diagram and the  $4\Omega$  resistor voltage is

$$v_4(t) = 1.052e^{-t/0.00357}\text{V} = 1.052e^{-280.1t}\text{V}$$

positive polarity on top in the diagram. Therefore, at  $t = 2\text{ms}$ ,

$$v(0.002) = 7.369e^{-125(0.002)} - 1.052e^{-281.1(0.002)} = 5.739 - 0.6 = 5.139\text{V}.$$