

## Solution of ECE 300 Test 7 S09

1. The switch in the circuit below has been closed a very long time. Find the numerical values of  $v_c(0^+)$ ,  $i_c(0^-)$ ,  $i_c(0^+)$ ,  $v_c(200\text{ms})$  and  $i_c(200\text{ms})$ .


Just before the switch opens the capacitor has no current through it  $[i_c(0^-) = 0]$  and  $v_c(0^-)$  is the same as the voltage across  $R_2$  which is  $100\text{ V} \frac{40\text{ k}\Omega}{40\text{ k}\Omega + 20\text{ k}\Omega} = 66.67\text{ V}$ . The capacitor voltage cannot change instantaneously so the voltage is the same at  $t = 0^+$ ,  $66.67\text{ V}$ . At  $t = 0^+$  the switch is open and the voltage across  $R_2$  is  $66.67\text{ V}$ . Therefore its current (downward) is  $1.667\text{ mA}$  and that must be the negative of the capacitor current. So  $i_c(0^+) = -1.667\text{ mA}$ . The time constant is  $\tau = 400\text{ ms}$ .

$$v_c(t) = v_c(0^+)e^{-2.5t}, t > 0 \Rightarrow v_c(200\text{ ms}) = 66.67e^{-0.5} = 40.44\text{ V}$$

$$i_c(t) = i_c(0^+)e^{-2.5t}, t > 0 \Rightarrow i_c(200\text{ ms}) = -1.67e^{-0.5} = -1.011\text{ mA}$$

$$V = 100\text{ V}, R_1 = 20\text{ k}\Omega$$
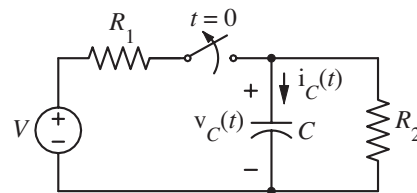
$$R_2 = 40\text{ k}\Omega, C = 10\text{ }\mu\text{F}$$




2. The switch in the circuit below has been open a very long time. Find the numerical values of  $v_c(0^+)$ ,  $i_c(0^-)$ ,  $i_c(0^+)$ ,  $i_L(0^+)$ ,  $v_L(0^-)$ ,  $v_L(0^+)$ ,  $\frac{d}{dt}(v_c(t))_{t=0^+}$  and  $\frac{d}{dt}(i_L(t))_{t=0^+}$ .

Before the switch closes all currents and voltages are constant so we know that  $i_c(0^-) = 0$  and  $v_L(0^-) = 0$ . At  $t = 0^-$  the current downward through  $R_1$  is  $3A \frac{4\Omega \parallel 6\Omega}{15\Omega + 10\Omega + 4\Omega \parallel 6\Omega} = 3A \frac{2.4\Omega}{27.4\Omega} = 0.263 A$ . So the voltage across it and  $v_c(0^-)$  are both 3.94 V. That means that  $v_c(0^+)$  is also 3.94 V because the capacitor voltage cannot change instantaneously.

Before the switch closes  $i_L(0^-)$  is  $3A \times \frac{15\Omega + 10\Omega}{15\Omega + 10\Omega + 4\Omega \parallel 6\Omega} \times \frac{6\Omega}{6\Omega + 4\Omega} = 1.642 A$ . Therefore  $i_L(0^+)$  is also 1.642 A because the current in an inductor cannot change instantaneously. At  $t = 0^+$  the switch is closed and the current-source current all flows through the switch. The capacitor is in parallel with  $R_1$  and  $R_3$  and its current is the negative of its voltage divided by  $R_1 \parallel R_3$  or -0.656 A. The inductor is now in parallel (and in series) with  $R_7$  and its voltage must be the negative of its current times  $R_7$  or -6.57 V. Using the defining equation for current and voltage for a capacitor,  $\frac{d}{dt}(v_c(t))_{t=0^+} = \frac{i_c(0^+)}{C} = \frac{-0.656 A}{5 \text{ mF}} = -131.2 \text{ V/s}$ . Using the defining equation for current and voltage for an inductor,  $\frac{d}{dt}(i_L(t))_{t=0^+} = \frac{v_L(0^+)}{L} = \frac{-6.57 \text{ V}}{2 \text{ H}} = -3.285 \text{ A/s}$ .

$$R_1 = 15 \Omega, C_2 = 5 \text{ mF}, R_3 = 10 \Omega, I_4 = 3 \text{ A}$$
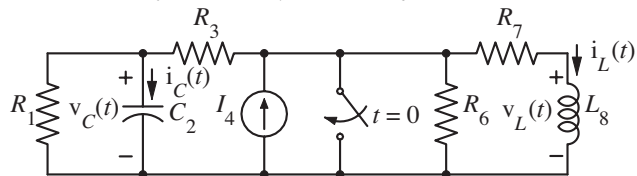
$$R_6 = 6 \Omega, R_7 = 4 \Omega, L_8 = 2 \text{ H}$$



## Solution of ECE 300 Test 7 S09

1. The switch in the circuit below has been closed a very long time. Find the numerical values of  $v_c(0^+)$ ,  $i_c(0^+)$ ,  $v_c(200\text{ms})$  and  $i_c(200\text{ms})$ .


Just before the switch opens the capacitor has no current through it [ $i_c(0^-) = 0$ ] and  $v_c(0^-)$  is the same as the voltage across  $R_2$  which is  $60\text{ V} \frac{40\text{ k}\Omega}{40\text{ k}\Omega + 20\text{ k}\Omega} = 40\text{ V}$ . The capacitor voltage cannot change instantaneously so the voltage is the same at  $t = 0^+$ ,  $40\text{ V}$ . At  $t = 0^+$  the switch is open and the voltage across  $R_2$  is  $40\text{ V}$ . Therefore its current (downward) is  $1\text{ mA}$  and that must be the negative of the capacitor current. So  $i_c(0^+) = -1\text{ mA}$ . The time constant is  $\tau = 400\text{ ms}$ .

$$v_c(t) = v_c(0^+)e^{-2.5t}, t > 0 \Rightarrow v_c(200\text{ ms}) = 40e^{-0.5} = 24.264\text{ V}$$

$$i_c(t) = i_c(0^+)e^{-2.5t}, t > 0 \Rightarrow i_c(200\text{ ms}) = -1e^{-0.5} = -0.607\text{ mA}$$

$$V = 60\text{ V}, R_1 = 20\text{ k}\Omega$$
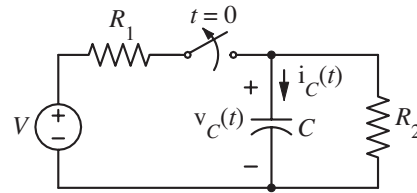
$$R_2 = 40\text{ k}\Omega, C = 10\text{ }\mu\text{F}$$




2. The switch in the circuit below has been open a very long time. Find the numerical values of  $v_c(0^+)$ ,  $i_c(0^-)$ ,  $i_c(0^+)$ ,  $i_L(0^-)$ ,  $v_L(0^-)$ ,  $v_L(0^+)$ ,  $\frac{d}{dt}(v_c(t))_{t=0^+}$  and  $\frac{d}{dt}(i_L(t))_{t=0^+}$ .

Before the switch closes all currents and voltages are constant so we know that  $i_c(0^-) = 0$  and  $v_L(0^-) = 0$ . At  $t = 0^-$  the current downward through  $R_1$  is  $5A \frac{4\Omega \parallel 6\Omega}{15\Omega + 10\Omega + 4\Omega \parallel 6\Omega} = 5A \frac{2.4\Omega}{27.4\Omega} = 0.438 A$ . So the voltage across it and  $v_c(0^-)$  are both 6.57 V. That means that  $v_c(0^+)$  is also 6.57 V because the capacitor voltage cannot change instantaneously.

Before the switch closes  $i_L(0^-)$  is  $5A \times \frac{15\Omega + 10\Omega}{15\Omega + 10\Omega + 4\Omega \parallel 6\Omega} \times \frac{6\Omega}{6\Omega + 4\Omega} = 2.74 A$ . Therefore  $i_L(0^+)$  is also 2.74 A because the current in an inductor cannot change instantaneously. At  $t = 0^+$  the switch is closed and the current-source current all flows through the switch. The capacitor is in parallel with  $R_1$  and  $R_3$  and its current is the negative of its voltage divided by  $R_1 \parallel R_3$  or -1.095 A. The inductor is now in parallel (and in series) with  $R_7$  and its voltage must be the negative of its current times  $R_7$  or -10.95 V. Using the defining equation for current and voltage for a capacitor,  $\frac{d}{dt}(v_c(t))_{t=0^+} = \frac{i_c(0^+)}{C} = \frac{-1.095 A}{5 \text{ mF}} = -219 \text{ V/s}$ . Using the defining equation for current and voltage for an inductor,  $\frac{d}{dt}(i_L(t))_{t=0^+} = \frac{v_L(0^+)}{L} = \frac{-10.95 \text{ V}}{2 \text{ H}} = -5.475 \text{ A/s}$ .

$$R_1 = 15 \Omega, C_2 = 5 \text{ mF}, R_3 = 10 \Omega, I_4 = 5 \text{ A}$$
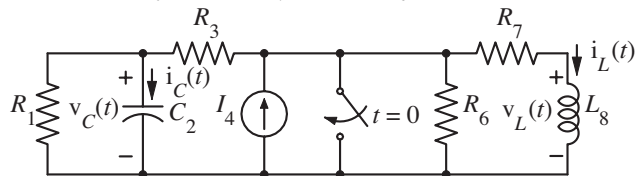
$$R_6 = 6 \Omega, R_7 = 4 \Omega, L_8 = 2 \text{ H}$$





## Solution of ECE 300 Test 7 S09

1. The switch in the circuit below has been closed a very long time. Find the numerical values of  $v_c(0^+)$ ,  $i_c(0^+)$ ,  $v_c(200\text{ms})$  and  $i_c(200\text{ms})$ .


Just before the switch opens the capacitor has no current through it [ $i_c(0^-) = 0$ ] and  $v_c(0^-)$  is the same as the voltage across  $R_2$  which is  $40\text{ V} \frac{40\text{ k}\Omega}{40\text{ k}\Omega + 20\text{ k}\Omega} = 26.67\text{ V}$ . The capacitor voltage cannot change instantaneously so the voltage is the same at  $t = 0^+$ ,  $26.67\text{ V}$ . At  $t = 0^+$  the switch is open and the voltage across  $R_2$  is  $26.67\text{ V}$ . Therefore its current (downward) is  $0.667\text{ mA}$  and that must be the negative of the capacitor current. So  $i_c(0^+) = -0.667\text{ mA}$ . The time constant is  $\tau = 400\text{ ms}$ .

$$v_c(t) = v_c(0^+)e^{-2.5t}, t > 0 \Rightarrow v_c(200\text{ ms}) = 26.67e^{-0.5} = 16.18\text{ V}$$

$$i_c(t) = i_c(0^+)e^{-2.5t}, t > 0 \Rightarrow i_c(200\text{ ms}) = -0.667e^{-0.5} = -0.4044\text{ mA}$$

$$V = 40\text{ V}, R_1 = 20\text{ k}\Omega$$
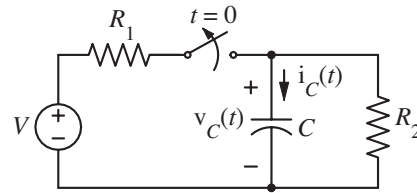
$$R_2 = 40\text{ k}\Omega, C = 10\text{ }\mu\text{F}$$



2. The switch in the circuit below has been open a very long time. Find the numerical values of  $v_c(0^+)$ ,  $i_c(0^-)$ ,  $i_c(0^+)$ ,  $i_L(0^-)$ ,  $v_L(0^-)$ ,  $v_L(0^+)$ ,  $\frac{d}{dt}(v_c(t))_{t=0^+}$  and  $\frac{d}{dt}(i_L(t))_{t=0^+}$ .

Before the switch closes all currents and voltages are constant so we know that  $i_c(0^-) = 0$  and  $v_L(0^-) = 0$ . At  $t = 0^-$  the current downward through  $R_1$  is  $2A \frac{4\Omega \parallel 6\Omega}{15\Omega + 10\Omega + 4\Omega \parallel 6\Omega} = 2A \frac{2.4\Omega}{27.4\Omega} = 0.175 A$ . So the voltage across it and  $v_c(0^-)$  are both 2.63 V.

That means that  $v_c(0^+)$  is also 2.63 V because the capacitor voltage cannot change instantaneously.

Before the switch closes  $i_L(0^-)$  is  $2A \times \frac{15\Omega + 10\Omega}{15\Omega + 10\Omega + 4\Omega \parallel 6\Omega} \times \frac{6\Omega}{6\Omega + 4\Omega} = 1.095 A$ . Therefore  $i_L(0^+)$  is

also 1.095 A because the current in an inductor cannot change instantaneously. At  $t = 0^+$  the switch is closed and the current-source current all flows through the switch. The capacitor is in parallel with  $R_1$  and  $R_3$  and its current is the negative of its voltage divided by  $R_1 \parallel R_3$  or -0.437 A. The inductor is now in parallel (and in series) with  $R_7$  and its voltage must be the negative of its current times  $R_7$  or -4.38 V.

Using the defining equation for current and voltage for a capacitor,

$$\frac{d}{dt}(v_c(t))_{t=0^+} = \frac{i_c(0^+)}{C} = \frac{-0.437 A}{5 \text{ mF}} = -87.4 \text{ V/s.}$$

Using the defining equation for current and voltage for an inductor,  $\frac{d}{dt}(i_L(t))_{t=0^+} = \frac{v_L(0^+)}{L} = \frac{-4.38 \text{ V}}{2 \text{ H}} = -2.19 \text{ A/s.}$

$$R_1 = 15 \Omega, C_2 = 5 \text{ mF}, R_3 = 10 \Omega, I_4 = 2 \text{ A}$$

$$R_6 = 6 \Omega, R_7 = 4 \Omega, L_8 = 2 \text{ H}$$

