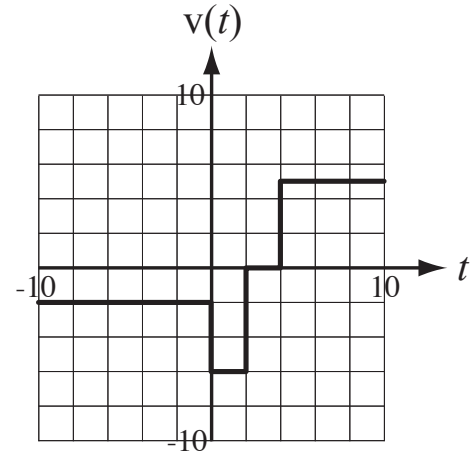


Solution of ECE 300 Test 8 F09

1. In the space provided graph this voltage versus time. Put a scale on the vertical axis so that actual voltages could be read from the graph.

$$v(t) = 4u(-t) - 6u(2-t) + 5u(t-4)$$



2. Find the numerical values of the capacitor current and voltage and the switch current at the times indicated.


$$v_c(0^-) = \text{_____ V} \quad v_c(0^+) = \text{_____ V} \quad v_c(\infty) = \text{_____ V}$$

$$i_c(0^-) = \text{_____ mA} \quad i_c(0^+) = \text{_____ mA} \quad i_c(\infty) = \text{_____ mA}$$

$$i_s(0^-) = \text{_____ mA} \quad i_s(0^+) = \text{_____ mA} \quad i_s(\infty) = \text{_____ mA}$$

What is the numerical time constant of this circuit after the switch is closed. $\tau = \text{_____ s}$
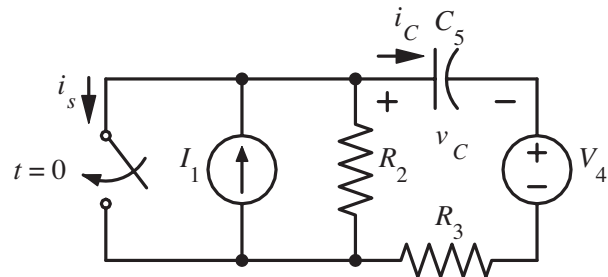
$$I_1 = 2\text{mA}, R_2 = 5\text{k}\Omega, R_3 = 10\text{k}\Omega, V_4 = 15\text{V}, C_5 = 4\mu\text{F}$$



The circuit has been in the configuration with the switch open for a very long time and all currents and voltages are constant.

For the current source only:

The current source current must all flow through resistor R_2 developing a voltage of 10V (positive on top). Then the capacitor voltage would also be 10V. The switch current is zero.

For the voltage source only:

No current flows anywhere in the circuit so the capacitor voltage must be -15V.

Overall:

The capacitor voltage is -5V and the capacitor current is zero.

At time $t = 0^+$:

The capacitor voltage remains at -5V . All the current source current now flows through the switch. The voltage across R_3 is 10V (positive on the left). Therefore the current through the capacitor, voltage source and R_3 is 1mA (counterclockwise). This current also flows through the switch along with the current from the current source for a total of 3mA .

At $t \rightarrow \infty$:

All currents and voltages are constant. The capacitor current is again zero. The only current through the switch is the current source current of 2mA . The capacitor voltage must be -15V .


$$\begin{aligned}v_c(0^-) &= -5\text{V} & v_c(0^+) &= -5\text{V} & v_c(\infty) &= -15\text{V} \\i_c(0^-) &= 0\text{mA} & i_c(0^+) &= -1\text{mA} & i_c(\infty) &= 0\text{mA} \\i_s(0^-) &= 0\text{mA} & i_s(0^+) &= 3\text{mA} & i_s(\infty) &= 2\text{mA}\end{aligned}$$

After the switch is closed the time constant is $\tau = R_3 C_3 = (10\text{k}\Omega)(4\mu\text{F}) = 40\text{ms}$.

Solution of ECE 300 Test 8 F09

1. In the space provided graph this voltage versus time. Put a scale on the vertical axis so that actual voltages could be read from the graph.

$$v(t) = 6u(-t) - 4u(2-t) + 5u(t-6)$$

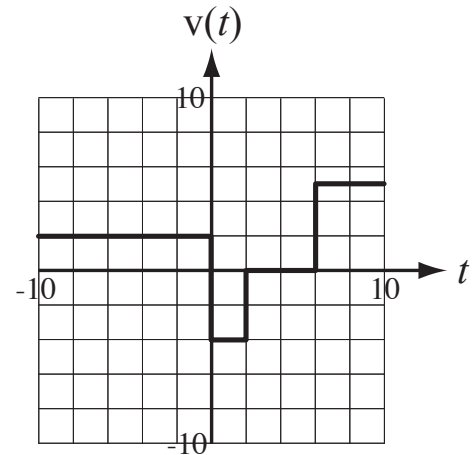

2. Find the numerical values of the capacitor current and voltage and the switch current at the times indicated.


$$v_c(0^-) = \text{_____ V} \quad v_c(0^+) = \text{_____ V} \quad v_c(\infty) = \text{_____ V}$$

$$i_c(0^-) = \text{_____ mA} \quad i_c(0^+) = \text{_____ mA} \quad i_c(\infty) = \text{_____ mA}$$

$$i_s(0^-) = \text{_____ mA} \quad i_s(0^+) = \text{_____ mA} \quad i_s(\infty) = \text{_____ mA}$$

What is the numerical time constant of this circuit after the switch is closed. $\tau = \text{_____ s}$
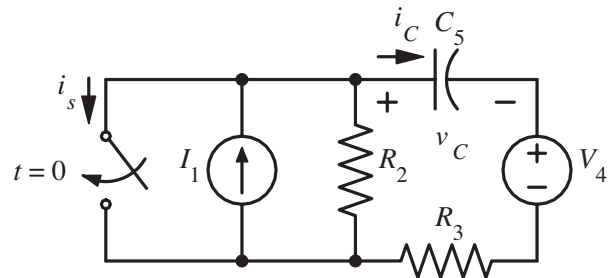
$$I_1 = 2\text{mA}, R_2 = 5\text{k}\Omega, R_3 = 5\text{k}\Omega, V_4 = 20\text{V}, C_5 = 4\mu\text{F}$$



The circuit has been in the configuration with the switch open for a very long time and all currents and voltages are constant.

For the current source only:

The current source current must all flow through resistor R_2 developing a voltage of 10V (positive on top). Then the capacitor voltage would also be 10V. The switch current is zero.

For the voltage source only:

No current flows anywhere in the circuit so the capacitor voltage must be -20V.

Overall:

The capacitor voltage is -10V and the capacitor current is zero.

At time $t = 0^+$:

The capacitor voltage remains at -10V . All the current source current now flows through the switch. The voltage across R_3 is 10V (positive on the left). Therefore the current through the capacitor, voltage source and R_3 is 2mA (counter-clockwise). This current also flows through the switch along with the current from the current source for a total of 4mA .

At $t \rightarrow \infty$:

All currents and voltages are constant. The capacitor current is again zero. The only current through the switch is the current source current of 2mA . The capacitor voltage must be -20V .


$$\begin{aligned}v_c(0^-) &= -10\text{V} & v_c(0^+) &= -10\text{V} & v_c(\infty) &= -20\text{V} \\i_c(0^-) &= 0\text{mA} & i_c(0^+) &= -2\text{mA} & i_c(\infty) &= 0\text{mA} \\i_s(0^-) &= 0\text{mA} & i_s(0^+) &= 4\text{mA} & i_s(\infty) &= 2\text{mA}\end{aligned}$$

After the switch is closed the time constant is $\tau = R_3 C_3 = (5\text{k}\Omega)(4\mu\text{F}) = 20\text{ms}$.

Solution of ECE 300 Test 8 F09

1. In the space provided graph this voltage versus time. Put a scale on the vertical axis so that actual voltages could be read from the graph.

$$v(t) = 4u(-t-2) - 6u(-t) + 2u(t-4)$$

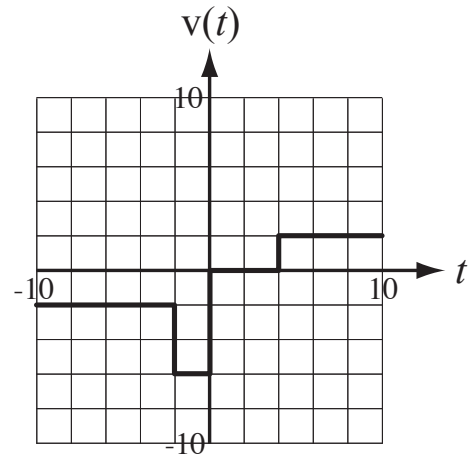

2. Find the numerical values of the capacitor current and voltage and the switch current at the times indicated.


$$v_c(0^-) = \text{_____ V} \quad v_c(0^+) = \text{_____ V} \quad v_c(\infty) = \text{_____ V}$$

$$i_c(0^-) = \text{_____ mA} \quad i_c(0^+) = \text{_____ mA} \quad i_c(\infty) = \text{_____ mA}$$

$$i_s(0^-) = \text{_____ mA} \quad i_s(0^+) = \text{_____ mA} \quad i_s(\infty) = \text{_____ mA}$$

What is the numerical time constant of this circuit after the switch is closed. $\tau = \text{_____ s}$
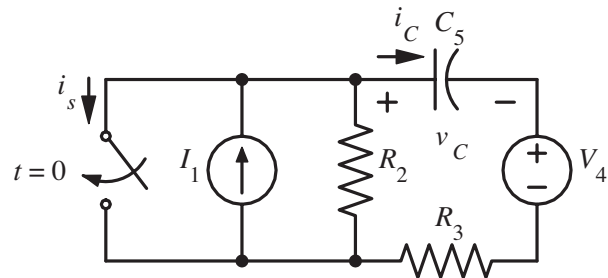
$$I_1 = 2\text{mA}, R_2 = 10\text{k}\Omega, R_3 = 5\text{k}\Omega, V_4 = 10\text{V}, C_5 = 4\mu\text{F}$$



The circuit has been in the configuration with the switch open for a very long time and all currents and voltages are constant.

For the current source only:

The current source current must all flow through resistor R_2 developing a voltage of 20V (positive on top). Then the capacitor voltage would also be 20V. The switch current is zero.

For the voltage source only:

No current flows anywhere in the circuit so the capacitor voltage must be -10V.

Overall:

The capacitor voltage is 10V and the capacitor current is zero.

At time $t = 0^+$:

The capacitor voltage remains at 10V. All the current source current now flows through the switch. The voltage across R_3 is 20V (positive on the left). Therefore the current through the capacitor, voltage source and R_3 is 4mA (counterclockwise). This current also flows through the switch along with the current from the current source for a total of 6 mA.

At $t \rightarrow \infty$:

All currents and voltages are constant. The capacitor current is again zero. The only current through the switch is the current source current of 2 mA. The capacitor voltage must be -10V.

$$\begin{aligned}v_c(0^-) &= 10\text{V} & v_c(0^+) &= 10\text{V} & v_c(\infty) &= -10\text{V} \\i_c(0^-) &= 0\text{ mA} & i_c(0^+) &= -4\text{ mA} & i_c(\infty) &= 0\text{ mA} \\i_s(0^-) &= 0\text{ mA} & i_s(0^+) &= 6\text{ mA} & i_s(\infty) &= 2\text{ mA}\end{aligned}$$

After the switch is closed the time constant is $\tau = R_3 C_3 = (5\text{k}\Omega)(4\mu\text{F}) = 20\text{ ms}$.