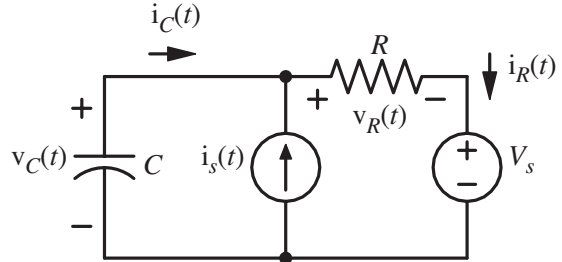


Solution of ECE 300 Test 8 F10

1. Fill in the blanks with numbers.

$$i_s(t) = 3u(t) \text{ , } V_s = 12 \text{ V , } R = 22\Omega \text{ , } C = 50\mu\text{F}$$




$$\begin{aligned} v_C(0^-) &= 12\text{V} & i_C(0^-) &= 0\text{A} & v_R(0^-) &= 0\text{V} & i_R(0^-) &= 0\text{A} \\ v_C(0^+) &= 12\text{V} & i_C(0^+) &= -3\text{A} & v_R(0^+) &= 0\text{V} & i_R(0^+) &= 0\text{A} \\ v_C(\infty) &= 78\text{V} & i_C(\infty) &= 0\text{A} & v_R(\infty) &= 66\text{V} & i_R(\infty) &= 3\text{A} \end{aligned}$$

2. Fill in the blanks with numbers.

$$v_s(t) = 10u(-t), I_s = 2A, R_1 = 15\Omega$$

$$R_2 = 7\Omega, L = 50 \text{ mH}$$

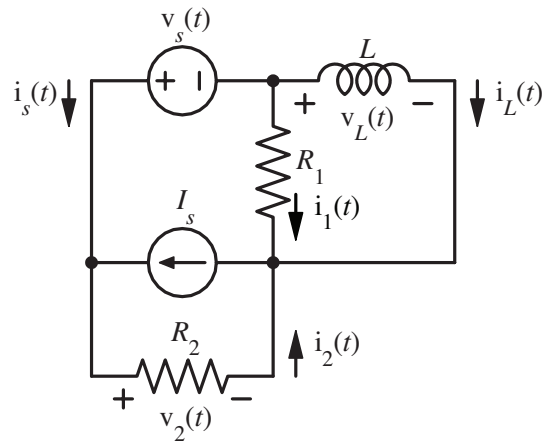

$$i_s(0^-) = -0.571A \quad i_L(0^-) = 0.571A \quad i_1(0^-) = 0A \quad i_2(0^-) = 1.429A$$

$$i_s(0^+) = -1.026A \quad i_L(0^+) = 0.571A \quad i_1(0^+) = 0.455A \quad i_2(0^+) = 0.974A$$

$$i_s(\infty) = -2A \quad i_L(\infty) = 2A \quad i_1(\infty) = 0A \quad i_2(\infty) = 0A$$

$$v_L(0^-) = 0V \quad v_2(0^-) = 10V$$


$$v_L(0^+) = 6.82V \quad v_2(0^+) = 6.82V$$

$$v_L(\infty) = 0V \quad v_2(\infty) = 0V$$

Solution of ECE 300 Test 8 F10

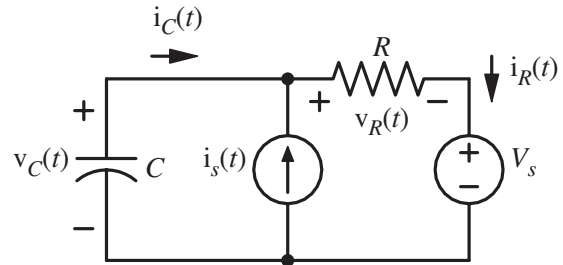1. Fill in the blanks with numbers.

$$i_s(t) = 2u(t) \text{ , } V_s = 10 \text{ V , } R = 22\Omega \text{ , } C = 50\mu\text{F}$$



$$v_C(0^-) = 10\text{V} \quad i_C(0^-) = 0\text{A} \quad v_R(0^-) = 0\text{V} \quad i_R(0^-) = 0\text{A}$$


$$v_C(0^+) = 10\text{V} \quad i_C(0^+) = -2\text{A} \quad v_R(0^+) = 0\text{V} \quad i_R(0^+) = 0\text{A}$$

$$v_C(\infty) = 54\text{V} \quad i_C(\infty) = 0\text{A} \quad v_R(\infty) = 44\text{V} \quad i_R(\infty) = 2\text{A}$$

2. Fill in the blanks with numbers.

$$v_s(t) = 5u(-t), I_s = 3A, R_1 = 15\Omega$$

$$R_2 = 7\Omega, L = 50 \text{ mH}$$

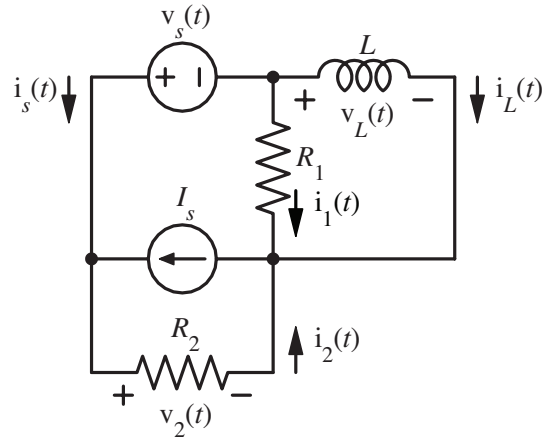

$$i_s(0^-) = -2.286A \quad i_L(0^-) = 2.286A \quad i_1(0^-) = 0A \quad i_2(0^-) = 0.714A$$

$$i_s(0^+) = -2.513A \quad i_L(0^+) = 2.286A \quad i_1(0^+) = 0.2272A \quad i_2(0^+) = 0.487A$$

$$i_s(\infty) = -3A \quad i_L(\infty) = 3A \quad i_1(\infty) = 0A \quad i_2(\infty) = 0A$$

$$v_L(0^-) = 0V \quad v_2(0^-) = 5V$$


$$v_L(0^+) = 3.408V \quad v_2(0^+) = 3.408V$$

$$v_L(\infty) = 0V \quad v_2(\infty) = 0V$$

Solution of ECE 300 Test 8 F10

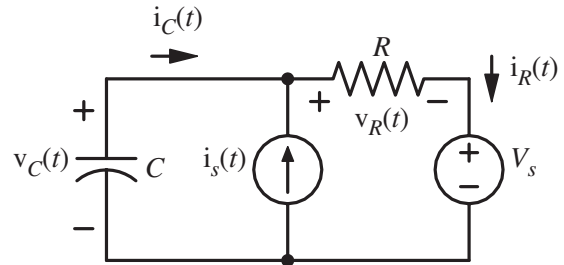1. Fill in the blanks with numbers.

$$i_s(t) = 4u(t) \text{ , } V_s = 20 \text{ V , } R = 22\Omega \text{ , } C = 50\mu\text{F}$$



$$v_C(0^-) = 20\text{V} \quad i_C(0^-) = 0\text{A} \quad v_R(0^-) = 0\text{V} \quad i_R(0^-) = 0\text{A}$$


$$v_C(0^+) = 20\text{V} \quad i_C(0^+) = -4\text{A} \quad v_R(0^+) = 0\text{V} \quad i_R(0^+) = 0\text{A}$$

$$v_C(\infty) = 108\text{V} \quad i_C(\infty) = 0\text{A} \quad v_R(\infty) = 88\text{V} \quad i_R(\infty) = 4\text{A}$$

2. Fill in the blanks with numbers.

$$v_s(t) = 15u(-t), I_s = 4A, R_1 = 15\Omega$$

$$R_2 = 7\Omega, L = 50 \text{ mH}$$

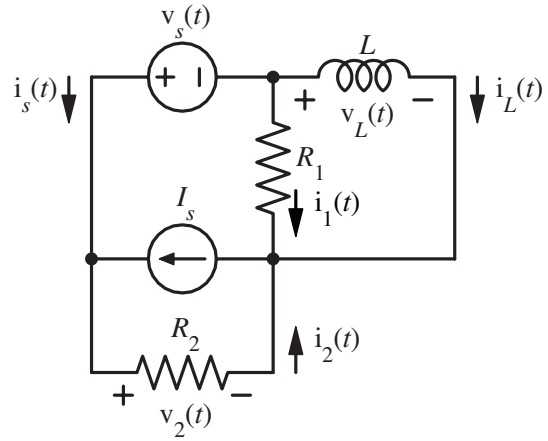

$$i_s(0^-) = -1.857A \quad i_L(0^-) = 1.857A \quad i_1(0^-) = 0A \quad i_2(0^-) = 2.143A$$

$$i_s(0^+) = -2.539A \quad i_L(0^+) = 1.857A \quad i_1(0^+) = 0.682A \quad i_2(0^+) = 1.461A$$

$$i_s(\infty) = -4A \quad i_L(\infty) = 4A \quad i_1(\infty) = 0A \quad i_2(\infty) = 0A$$

$v_L(0^-) = 0V$	$v_2(0^-) = 15V$
$v_L(0^+) = 10.228V$	$v_2(0^+) = 10.228V$
$v_L(\infty) = 0V$	$v_2(\infty) = 0V$